



# Lecture (05) Mesh Analysis

---

By:

**Dr. Ahmed ElShafee**

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

## Agenda

---

- Mesh analysis with voltage sources
- Mesh Analysis with Current Sources

# Mesh analysis with voltage sources

- Determine meshes in the circuit.
- Set the current and direction of each mesh.
- Use KVL to build system of equations (equation/mesh), use ohm's law to express voltage in terms of mesh current.
- Solve system of equations, to find the current of each mesh.
- Convert mesh current to then normal current form.

۳


Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

$$-V_1 + R_1 i_1 + R_3(i_1 - i_2) = 0$$

$$(R_1 + R_3)i_1 - R_3 i_2 = V_1$$

$$R_2 i_2 + V_2 + R_3(i_2 - i_1) = 0$$

$$-R_3 i_1 + (R_2 + R_3)i_2 = -V_2$$

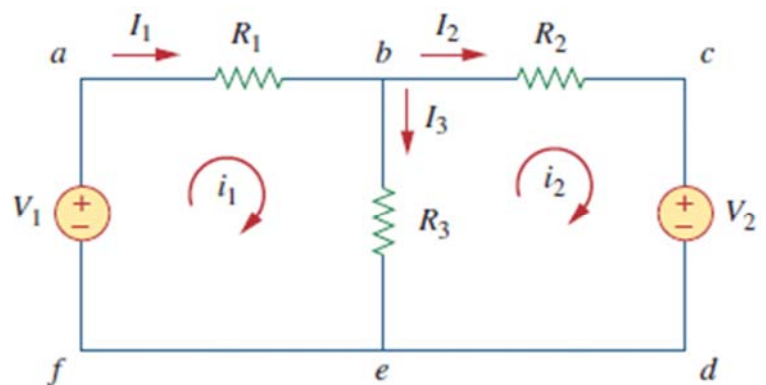


۴

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
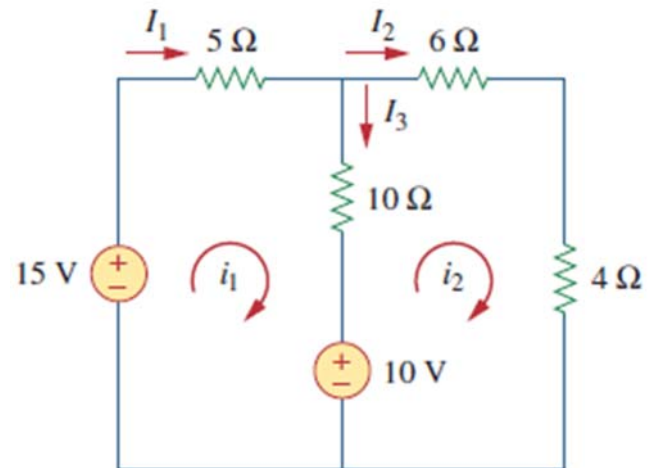
# Example 01

For the circuit in Fig. 3.18, find the branch currents  $I_1$ ,  $I_2$ , and  $I_3$  using mesh analysis.



$$i_1 = \frac{\Delta_1}{\Delta} = 1 \text{ A}, \quad i_2 = \frac{\Delta_2}{\Delta} = 1 \text{ A}$$

◦

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

## KVL@1

$$-15 + 5i_1 + (i_1 - i_2)10 + 10 = 0$$

$$-5 + 5i_1 + 10i_1 - 10i_2 = 0$$

$$15i_1 - 10i_2 = 5 \quad /5$$

$$3i_1 - 2i_2 = 1 \rightarrow 1$$


## KVL@2

$$-10 + 10(i_2 - i_1) + 6i_2 + 4i_2 = 0$$

$$10i_2 - 10i_1 + 6i_2 + 4i_2 = 10$$

$$20i_2 - 10i_1 = 10 \quad /10$$

$$-i_1 + 2i_2 = 1 \rightarrow 2$$

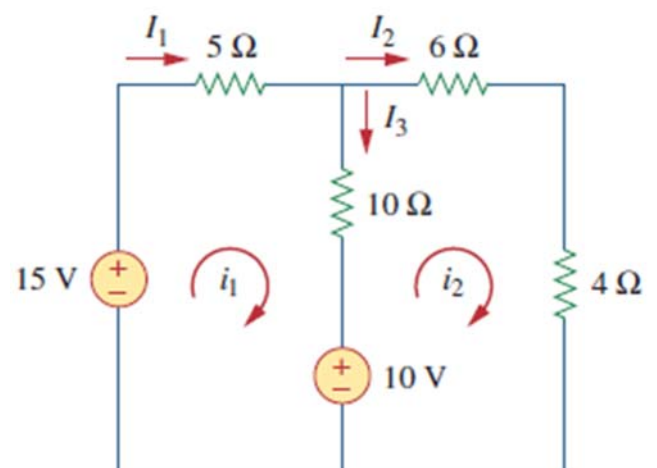

7

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

---

Add 1,2

$$2i_1 = 2$$

$$i_1 = 1 \text{ Amp}$$

Sub in 2

$$2i_2 = 2$$

$$i_2 = 1 \text{ amp}$$


Y

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
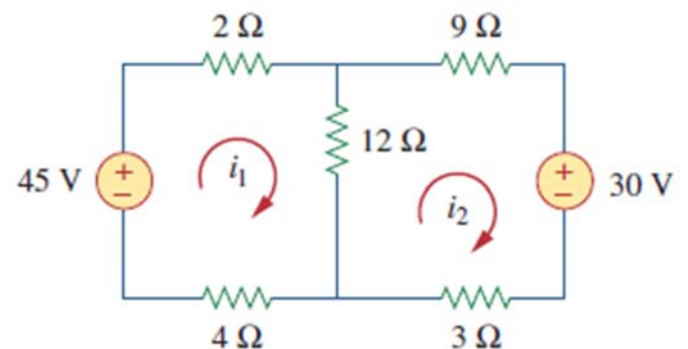
## Example 02

---

Calculate the mesh currents  $i_1$  and  $i_2$  of the circuit of Fig. 3.19.



$$i_1 = 2.5 \text{ A}, i_2 = 0 \text{ A.}$$

A

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

---

### KVL@1

$$-45 + 2i_1 + 12(i_1 - i_2) + 4i_1 = 0$$

$$2i_1 + 12i_1 - 12i_2 + 4i_1 = 45$$

$$18i_1 - 12i_2 = 45 \quad /3$$

$$6i_1 + 4i_2 = 15 \rightarrow 1$$


### KVL@2

$$12(i_2 - i_1) + 9i_2 + 3i_2 + 30 = 0$$

$$12i_2 - 12i_1 + 9i_2 + 3i_2 = -30$$

$$-12i_1 + 24i_2 = -30 \quad /6$$

$$-2i_1 + 4i_2 = -5 \rightarrow 2$$

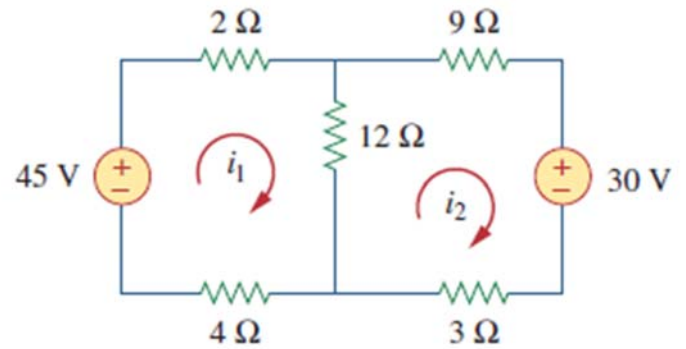

9

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

---

### Add 1,2

$$4i_1 = 10$$

$$i_1 = 2.5 \text{ Amp}$$

### Sub in 2

$$4i_2 = -5 + (2 \times 2.5) = 0$$


$$i_2 = 0 \text{ Amp}$$

10

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
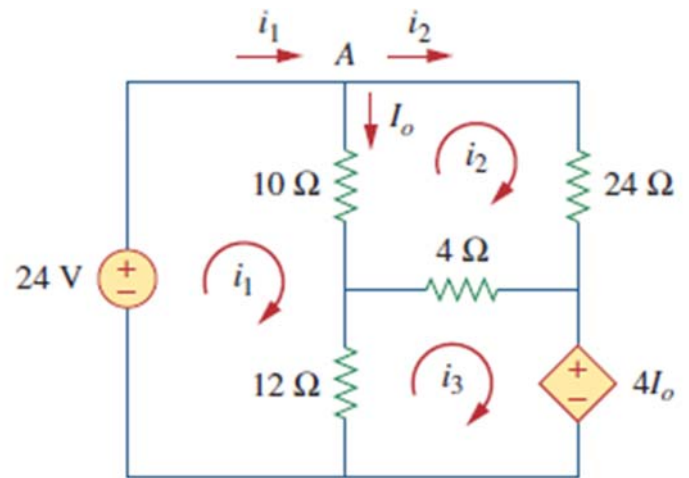
# Example 03

Use mesh analysis to find the current  $I_o$  in the circuit of Fig. 3.20.



$$\text{Thus, } I_o = i_1 - i_2 = 1.5 \text{ A.}$$

11

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

## KVL@1

$$\begin{aligned} -24 + 10(i_1 - i_2) \\ + 12(i_1 - i_3) = 0 \end{aligned}$$

$$\begin{aligned} 10i_1 - 10i_2 + 12i_1 - 12i_3 \\ = 24 \end{aligned}$$

$$22i_1 - 10i_2 - 12i_3 = 24 \quad /2$$


$$11i_1 - 5i_2 - 6i_3 = 12 \quad \rightarrow 1$$

## KVL@2

$$\begin{aligned} 10(i_2 - i_1) + 24i_2 + 4(i_2 - i_3) \\ = 0 \end{aligned}$$

$$\begin{aligned} 10i_2 - 10i_1 + 24i_2 + 4i_2 - 4i_3 \\ = 0 \end{aligned}$$

$$-10i_1 + 38i_2 - 4i_3 = 0 \quad /2$$

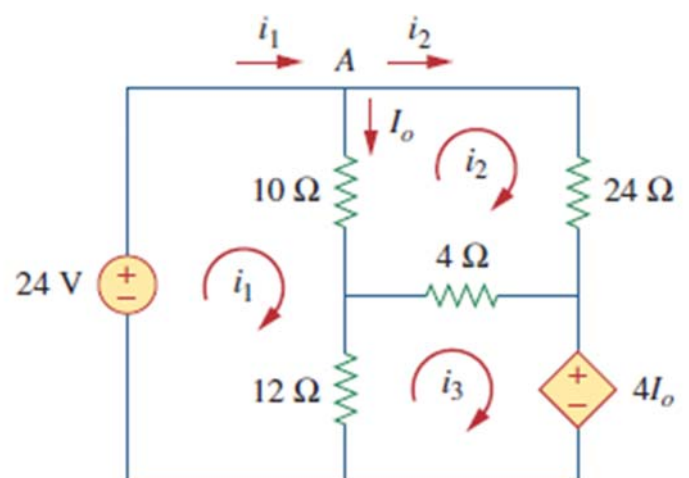

11

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

$$-5i_1 + 19i_2 - 2i_3 = 0 \rightarrow 2$$

KVL@3


$$12(i_3 - i_1) + 4(i_3 - i_2) + 4i_0 = 0$$

$$12i_3 - 12i_1 + 4i_3 - 4i_2 + 4(i_1 - i_2) = 0$$

$$12i_3 - 12i_1 + 4i_3 - 4i_2 + 4i_1 - 4i_2 = 0$$

$$-8i_1 - 8i_2 + 16i_3 = 0 \quad /8$$

$$-i_1 - i_2 + 2i_3 = 0 \rightarrow 3$$

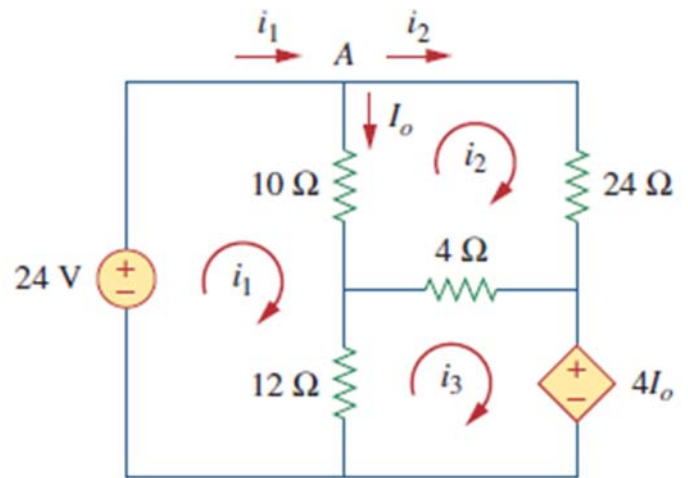

$$\begin{pmatrix} & & \\ & & \\ & & \end{pmatrix} \begin{pmatrix} \\ \\ \end{pmatrix} = \begin{pmatrix} \\ \\ \end{pmatrix}$$

Cramer

$$\begin{pmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 12 \\ 0 \\ 0 \end{pmatrix}$$

$$\Delta = 11(38 - 2) + 5(-10 - 6) - 1(10 + 114) = 396 - 80 - 124 = 192$$

$$\Delta_1 = \begin{pmatrix} 12 & -5 & -6 \\ 0 & 19 & -2 \\ 0 & -1 & 2 \end{pmatrix} = 12(38 - 2) = 432$$

$$\Delta_2 = \begin{pmatrix} 11 & 12 & -6 \\ -5 & 0 & -2 \\ -1 & 0 & 2 \end{pmatrix} = -12(-10 - 2) = 144$$

$$\Delta_3 = \begin{pmatrix} 11 & -5 & 10 \\ -5 & 19 & 0 \\ -1 & -1 & 0 \end{pmatrix} = 12(5 + 19) = 288$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{432}{192} = 2.25 \text{ Amp}$$


$$i_2 = \frac{\Delta_2}{\Delta} = \frac{144}{192} = 0.75 \text{ Amp}$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{288}{192} = 1.5 \text{ Amp}$$

$$i_0 = i_1 - i_2 = 2.25 - 0.75 = 1.5 \text{ Amp}$$
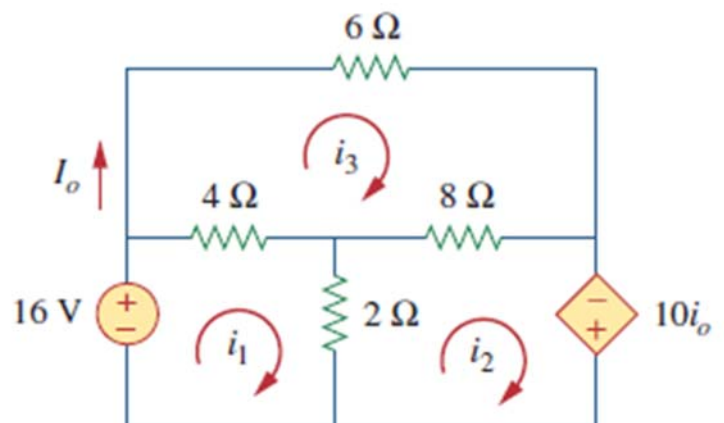
## Example 04

Using mesh analysis, find  $I_o$  in the circuit of Fig. 3.21.



**Answer: -4 A.**




### KVL@1

$$\begin{aligned} -16 + 4(i_1 - i_3) \\ + 2(i_1 - i_2) &= 0 \\ 4i_1 - 4i_3 + 2i_1 - 2i_2 &= 16 \\ 6i_1 - 2i_2 + 4i_3 &= 16 \quad /2 \\ 3i_1 - i_2 - 2i_3 &= 8 \rightarrow 1 \end{aligned}$$

### KVL@2


$$\begin{aligned} 2(i_2 - i_1) + 8(i_2 - i_3) \\ - 10i_o &= 0 \\ 2i_2 - 2i_1 + 8i_2 - 8i_3 - 10i_3 \\ &= 0 \\ -2i_1 + 10i_2 - 18i_3 &= 0 \quad /2 \end{aligned}$$

$$-i_1 + 5i_2 - 9i_3 = 0 \rightarrow 2$$

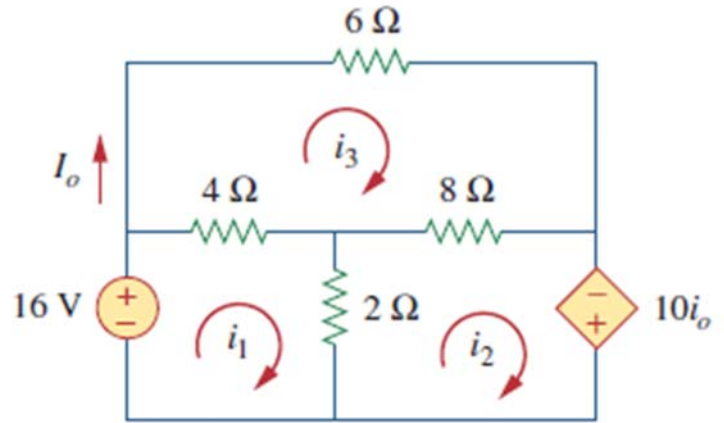
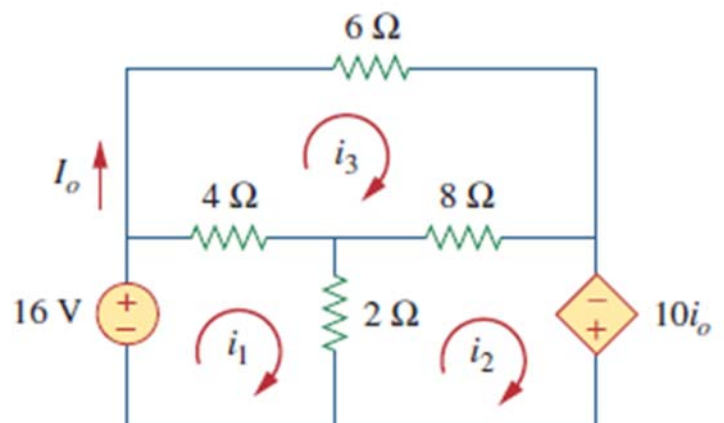
### KVL@3

$$\begin{aligned} 6i_3 + 4(i_3 - i_1) + 8(i_3 - i_2) \\ &= 0 \\ 6i_3 + 4i_3 - 4i_1 + 8i_3 - 8i_2 \\ &= 0 \\ -4i_1 - 8i_2 + 18i_3 &= 0 \quad /2 \\ -2i_1 - 4i_2 + 9i_3 &= 0 \rightarrow 3 \end{aligned}$$



---

### Cramer

$$\begin{pmatrix} 3 & -1 & -2 \\ -1 & 5 & -9 \\ -2 & -4 & 9 \end{pmatrix} \begin{pmatrix} i1 \\ i2 \\ i3 \end{pmatrix} = \begin{pmatrix} 4 \\ 0 \\ 0 \end{pmatrix}$$

$$\Delta = 3(45 - 36) + (-9 - 8) - 2(9 + 10) = 27 - 17 - 38 \\ = -27$$

$$\Delta_1 = \begin{pmatrix} 4 & -1 & -2 \\ 0 & 5 & -9 \\ 0 & -4 & 9 \end{pmatrix} = 4(45 - 36) = 36$$

$$i1 = \frac{\Delta_1}{\Delta} = -\frac{27}{36} = -0.75 \text{ Amp}$$

---

$$\Delta_2 = \begin{pmatrix} 3 & 4 & -2 \\ -1 & 0 & -9 \\ -2 & 0 & 9 \end{pmatrix} = -4(-9 - 18) = 108$$

$$i2 = \frac{108}{-27} = -4 \text{ Amp} = i0$$


$$\Delta_3 = \begin{pmatrix} 3 & -1 & 4 \\ -1 & 5 & 0 \\ -2 & -4 & 0 \end{pmatrix} = 4(4 + 10) = 56$$

$$i3 = \frac{56}{-27} = -2.07 \text{ Amp}$$


# Mesh Analysis with Current Sources

- Case 1: When a current source exists only in one mesh, mesh current = source current

$$i_2 = -5 \text{ A}$$

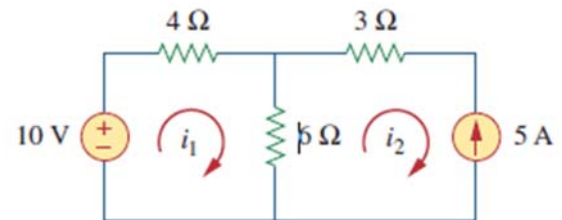

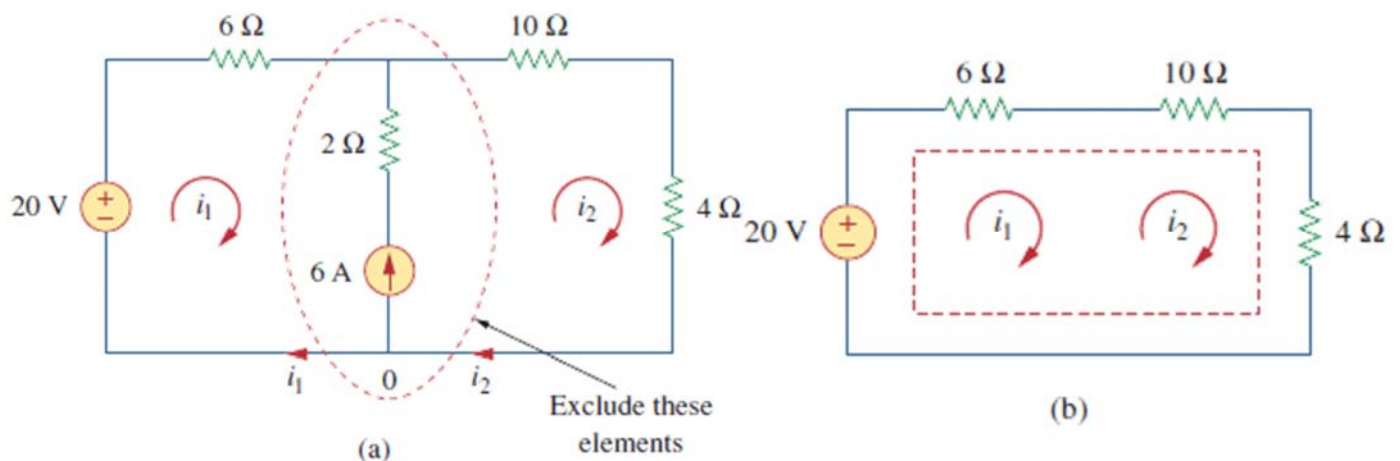
- Case 2: When a current source exists between two meshes; We create a *supermesh* by excluding the current source and any elements connected in series with it,



- Apply KCL :  $-20 + 6i_1 + 10i_2 + 4i_2 = 0$
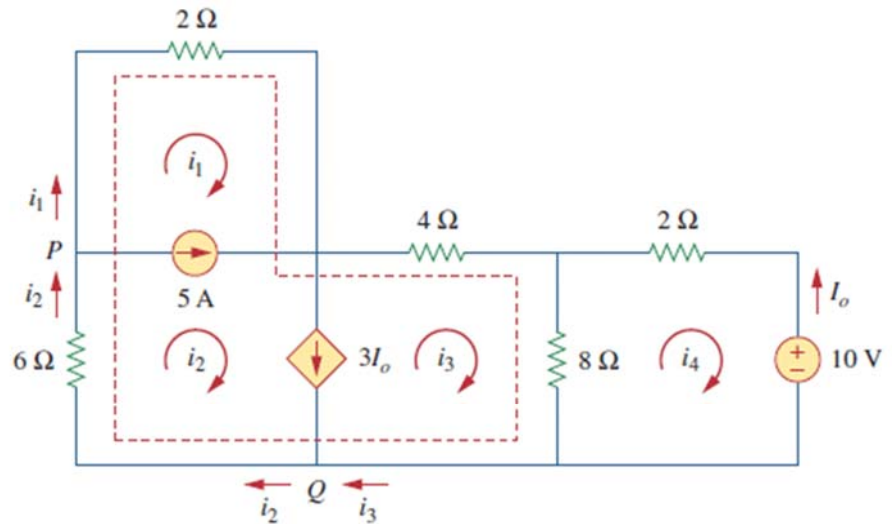
# Example 05

For the circuit in Fig. 3.24, find  $i_1$  to  $i_4$  using mesh analysis.



$$i_1 = -7.5 \text{ A}, \quad i_2 = -2.5 \text{ A}, \quad i_3 = 3.93 \text{ A}, \quad i_4 = 2.143 \text{ A}$$

۲۳

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

KVL@1,2,3 super mesh

$$2i_1 + 6i_2 + 4i_3 + 8(i_3 - i_4) = 0$$

$$2i_1 + 6i_2 + 4i_3 + 8i_3 - 8i_4 = 0$$

$$2i_1 + 6i_2 + 12i_3 - 8i_4 = 0 \quad /2$$

$$i_1 + 3i_2 + 6i_3 - 4i_4 = 0 \quad \rightarrow 1$$

KCL@ super 1,2


$$i_2 = 5 + i_1 \quad \rightarrow 2$$

KCL@ super 2,3

$$i_2 - i_3 = 3i_o$$

$$\text{But } i_o = -i_4$$
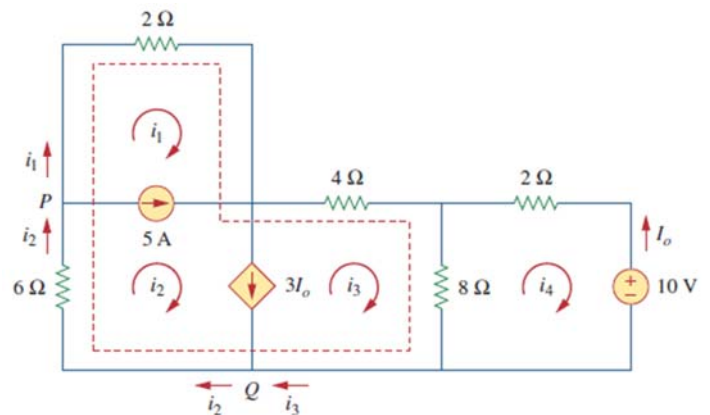
$$i_2 - i_3 + 3i_4 = 0 \quad \rightarrow 3$$



Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

### KVL@4

$$8(i_4 - i_3) + 2i_4 + 10 = 0$$

$$8i_4 - 8i_3 + 2i_4 = -10$$

$$-8i_3 + 10i_4 = -10 \quad /2$$


$$-4i_3 + 5i_4 = -5 \rightarrow 4$$

### Sub 2 in 1,3

$$i_1 + 3(i_1 + 5) + 6i_3 - 4i_4 = 0$$

$$4i_1 + 6i_3 - 4i_4 = -15 \rightarrow 5$$

$$i_1 - i_3 + 3i_4 = -5 \rightarrow 6$$

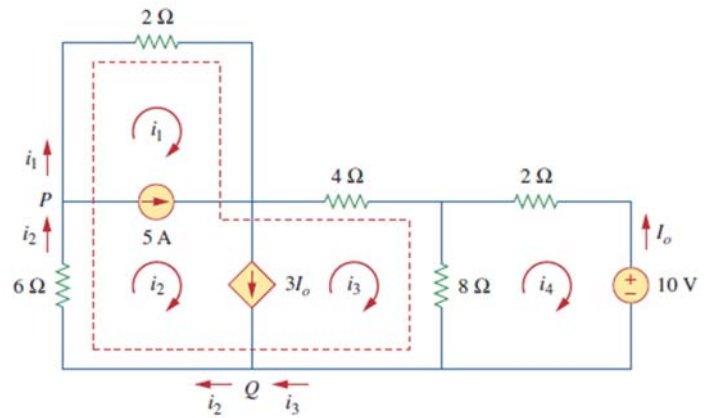

### Cramer

$$\begin{pmatrix} 4 & 6 & -4 \\ 1 & -1 & 3 \\ 0 & -4 & 5 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} -15 \\ -5 \\ -5 \end{pmatrix}$$

$$\Delta = 4(-5 + 12) - (30 - 16) = 28 - 14 = 14$$

$$\Delta_1 = \begin{pmatrix} -15 & 6 & -4 \\ -5 & -1 & 3 \\ -5 & -4 & 5 \end{pmatrix}$$

$$\begin{aligned} &= -15(-5 + 12) + 5(30 - 16) - 5(18 - 4) \\ &= -105 + 70 - 70 = -105 \end{aligned}$$

$$i_1 = \frac{\Delta_1}{\Delta} = -\frac{105}{14} = -7.5 \text{ Amp}$$

From 2

$$i_2 = 5 - 7.5 = -2.5 \text{ Amp}$$

$$\Delta 3 = \begin{pmatrix} 4 & -15 & -4 \\ 1 & -5 & 3 \\ 0 & -5 & 5 \end{pmatrix} = 4(-25 + 15) - (-75 - 20)$$

$$= -40 + 95 = 55$$

$$i_3 = \frac{\Delta 3}{\Delta} = \frac{55}{14} = 3.93 \text{ Amp}$$


$$\Delta 4 = \begin{pmatrix} 4 & 6 & -15 \\ 1 & -1 & -5 \\ 0 & -4 & -5 \end{pmatrix} = 4(5 - 20) - (-30 + 60) = 60 - 30$$

$$= 30$$

$$i_4 = \frac{\Delta 4}{\Delta} = \frac{30}{14} = 2.14 \text{ Amp}$$
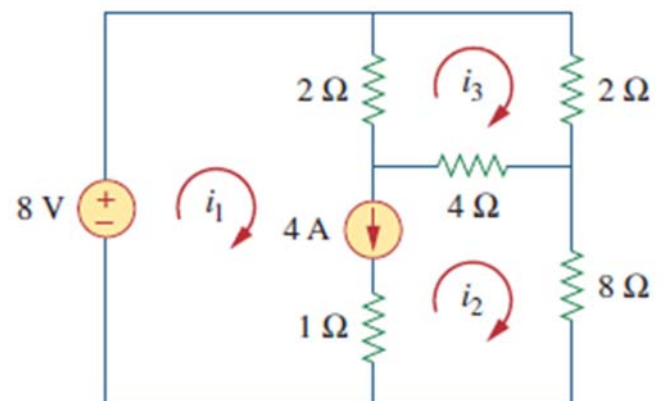
## Example 06

Use mesh analysis to determine  $i_1$ ,  $i_2$ , and  $i_3$  in Fig. 3.25.



$$i_1 = 4.632 \text{ A}, i_2 = 631.6 \text{ mA}, i_3 = 1.4736 \text{ A.}$$

### KVL@1,2 super mesh

$$-8 + 2(i_1 - i_3) + 4(i_2 - i_3) + 8i_2 = 0$$

$$2i_1 - 3i_2 + 4i_2 - 4i_3 + 8i_2 = 8$$


$$2i_1 + 12i_2 - 6i_3 = 8 \quad /2$$

$$i_1 + 6i_2 - 3i_3 = 4 \rightarrow 1$$

### KCL @ super mesh 1,2

$$i_1 - i_2 = 4$$

$$i_1 = 4 + i_2 \rightarrow 2$$

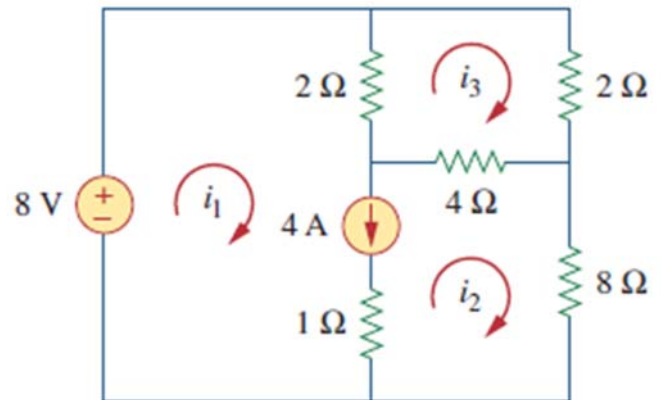

### KVL@3

$$2(i_3 - i_1) + 2i_3 + 4(i_3 - i_2) = 0$$

$$2i_3 - 2i_1 + 2i_3 + 4i_3 + 4i_3 - 4i_2 = 0$$

$$-2i_1 - 4i_2 + 8i_3 = 0 \quad /2$$

$$-i_1 - 2i_2 + 4i_3 = 0 \rightarrow 2$$


### Sub 2 in 1,2

$$4 + i_2 + 6i_2 - 3i_3 = 4$$

$$7i_2 - 3i_3 = 0 \rightarrow 4$$

$$-4 - i_2 - 2i_2 + 4i_3 = 0$$

$$-3i_2 + 4i_3 = 4 \rightarrow 3$$

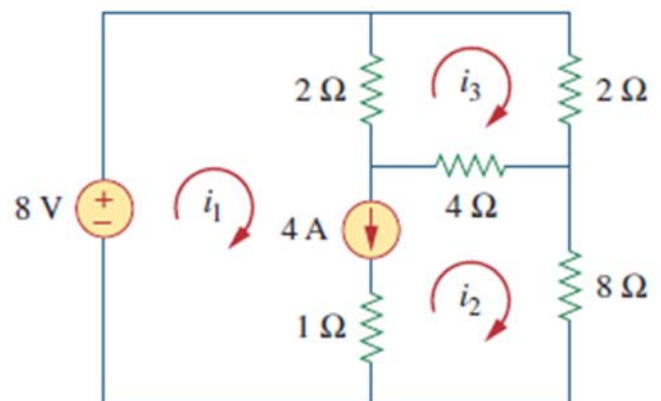

---

Mult 4 x 3 and 3 x 4

$$28i_2 - 12i_3 = 0$$

$$-9i_2 + 12i_3 = 12$$

-----  
$$19i_2 = 12$$

$$i_2 = \frac{12}{19} = 0.632 \text{ Amp}$$

Sub in 2

$$i_1 = 4 + 0.632 = 4.632 \text{ Amp}$$

Sub in 1

$$i_3 = \frac{i_1 + 6i_2 - 4}{3} = \frac{4.632 + 6(0.632) - 4}{3} = 1.47 \text{ Amp}$$



**Thanks,..**

**See you next week (ISA),...**