



# Lecture (06)

## Circuit Theorems (1)

---

By:

**Dr. Ahmed ElShafee**

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

## Agenda

---

- Linearity Property
- Super position
- Source transformation

# Linearity Property

---

- Linearity is the property of an element describing a linear relationship between cause and effect.
- The homogeneity property requires that if the input (also called the *excitation*) is multiplied by a constant, then the output (also called the *response*) is multiplied by the same constant

$$v = iR$$


- In general, a circuit is linear if it is both additive and homogeneous.

---

$$p = i^2 R = v^2 / R$$

- the relationship between power and voltage (or current) is nonlinear
- Therefore, the theorems covered in this lecture are not applicable to power

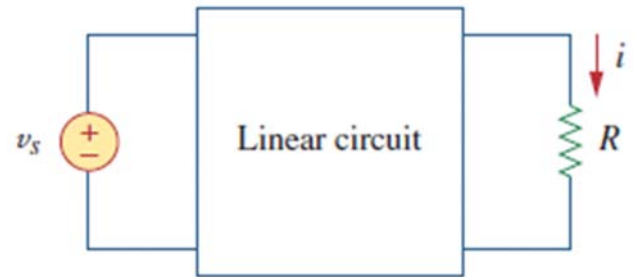
- 
- consider the linear circuit shown in Fig
  - The linear circuit has no independent sources inside it.
  - It is excited by  $V_s$  a voltage source which serves as the input.
  - The circuit is terminated by a load  $R$ .
  - We may take the current  $i$  through  $R$  as the output.



◦

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

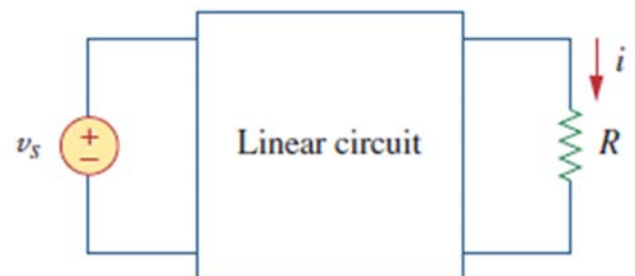- 
- If  $V_s = 10$  volt and  $I = 2$  Amp
  - So according to linearity principle
  - If  $V_s$  become 1 Volt then  $I = 0.2$  Amp




7

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
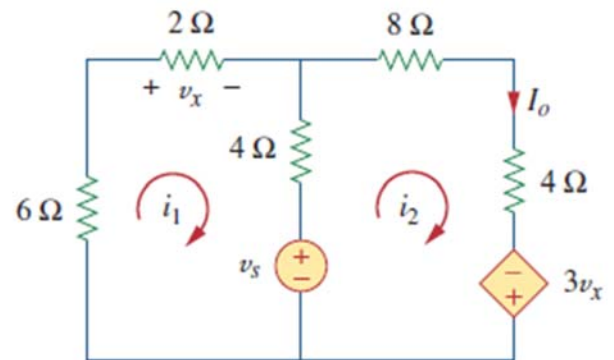
# Example 01

For the circuit in Fig. 4.2, find  $I_o$  when  $v_s = 12\text{ V}$  and  $v_s = 24\text{ V}$ .




Y

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
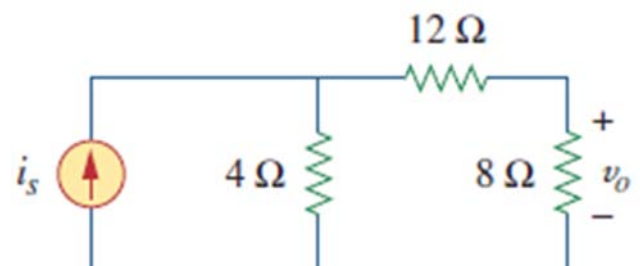
# Example 02

For the circuit in Fig. 4.3, find  $v_o$  when  $i_s = 30$  and  $i_s = 45\text{ A}$ .




**Answer:** 40 V, 60 V.

A

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
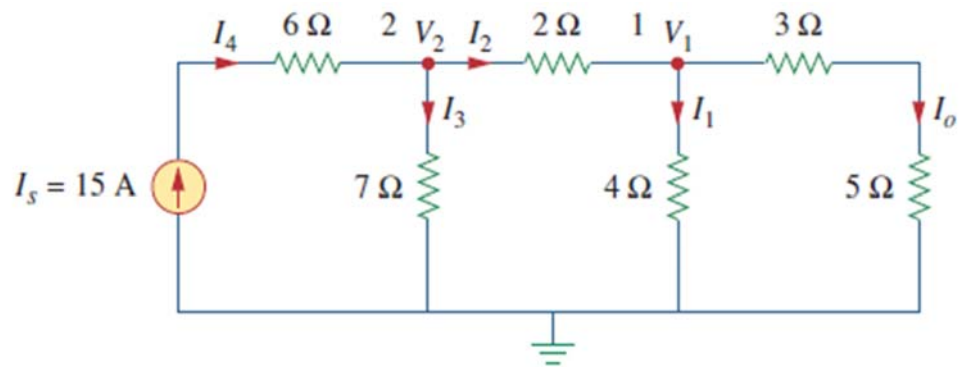
# Example 03

Assume  $I_o = 1$  A and use linearity to find the actual value of  $I_o$  in the circuit of Fig. 4.4.




$$I_o = 3 \text{ A}$$

9

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
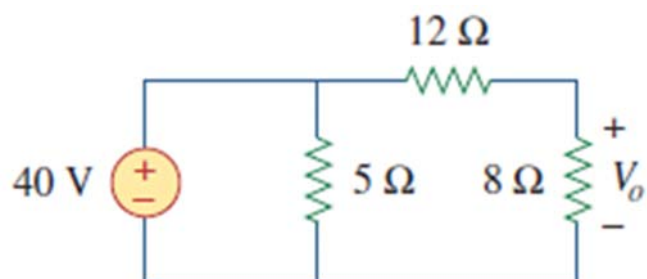
# Example 04

Assume that  $V_o = 1$  V and use linearity to calculate the actual value of  $V_o$  in the circuit of Fig. 4.5.



**Answer:** 16 V.

10

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits

# Superposition

- The superposition principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.

## Steps to Apply Superposition Principle:


- Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using the techniques covered in Chapters 2 and 3.
- Repeat step 1 for each of the other independent sources.
- Find the total contribution by adding algebraically all the contributions due to the independent sources.

11

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
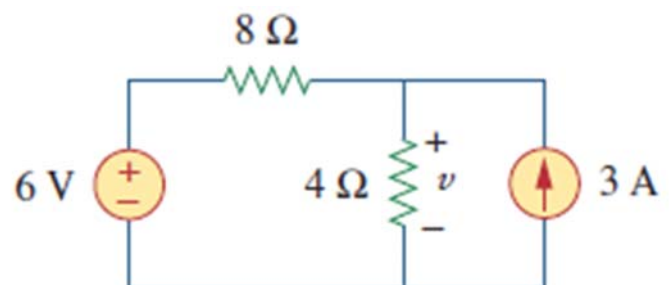
## Example 05

- Use the superposition theorem to find  $v$  in the circuit of Fig.




10 V

12

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
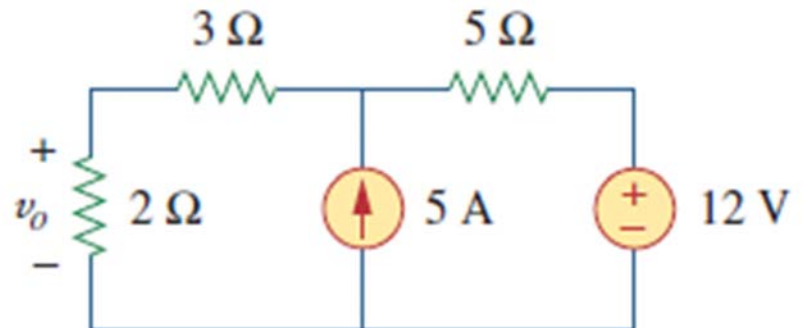
# Example 06


Using the superposition theorem, find  $v_o$  in the circuit of Fig.



**Answer:** 7.4 V.

# Example 07


Find  $i_o$  in the circuit of Fig.

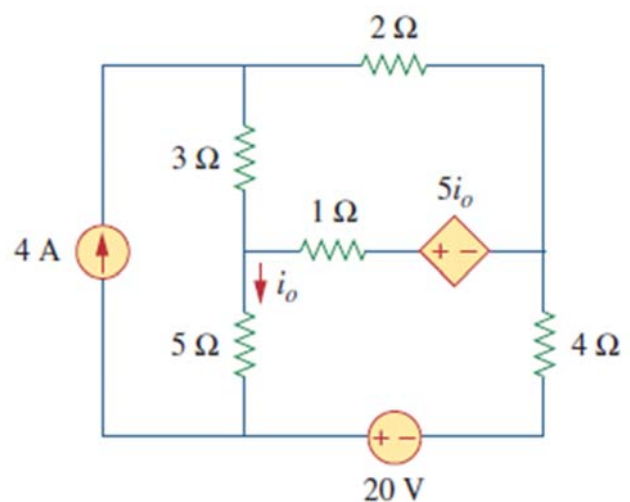

$$i_o = -\frac{8}{17} = -0.4706 \text{ A}$$
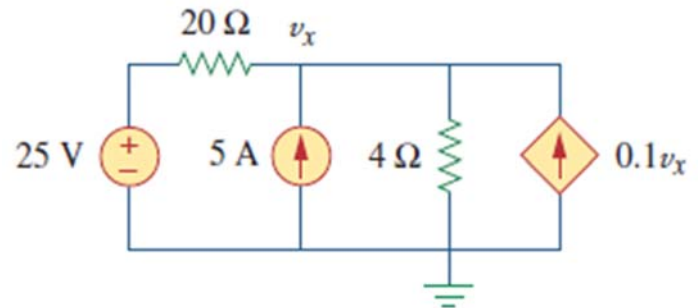
# Example 08

Use superposition to find  $v_x$  in the circuit of Fig.




$$v_x = 31.25 \text{ V.}$$

10

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits
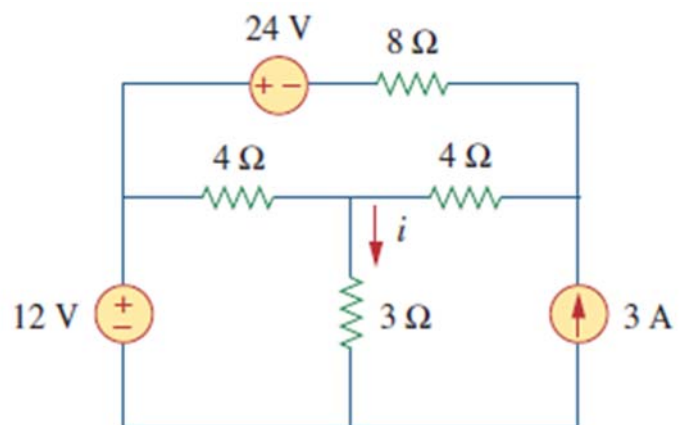
# Example 09

For the circuit in Fig. 4.12, use the superposition theorem to find  $i$ .



$$i = i_1 + i_2 + i_3 = 2 - 1 + 1 = 2 \text{ A}$$


11

Dr. Ahmed ElShafee, ACU : Fall 2015, Electric Circuits


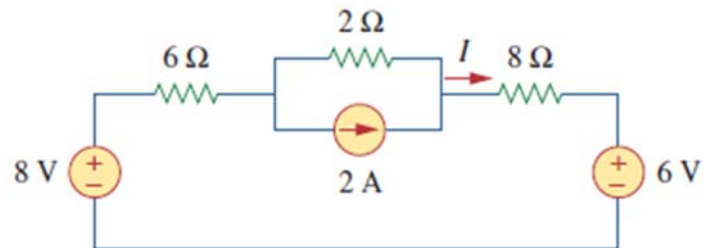
# Example 10


Find  $I$  in the circuit of Fig. 4.14 using the superposition principle.



**Answer:** 375 mA.

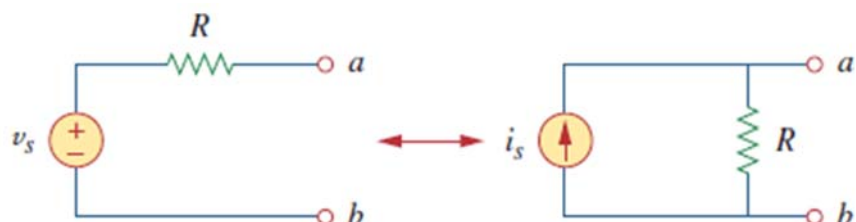
## Source Transformation

- substitute a voltage source in series with a resistor for a current source in parallel with a resistor, or vice versa, as shown in Fig.




A **source transformation** is the process of replacing a voltage source  $v_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with a resistor  $R$ , or vice versa.

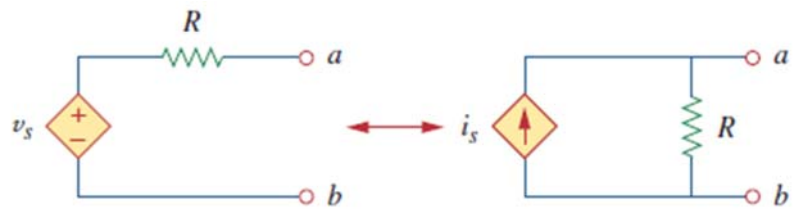- Source transformation also applies to dependent sources, provided we carefully handle the dependent variable


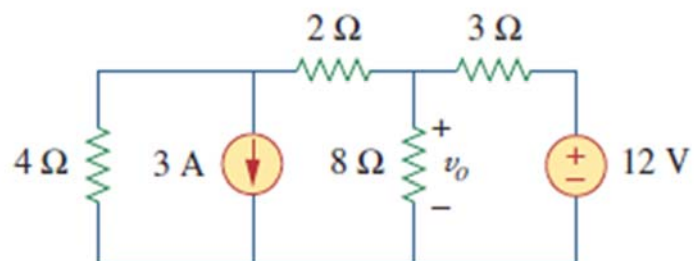
## Example 11


Use source transformation to find  $v_o$  in the circuit of Fig.



$$= 3.2 \text{ V}$$
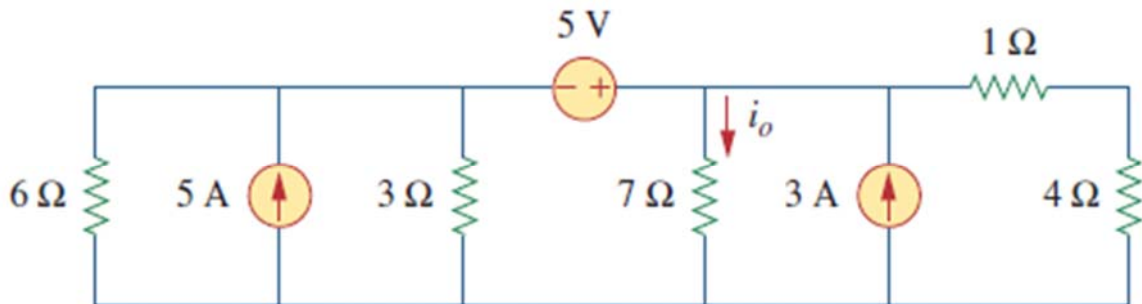
# Example 12


Find  $i_o$  in the circuit of Fig. 4.19 using source transformation.



Answer: 1.78 A.
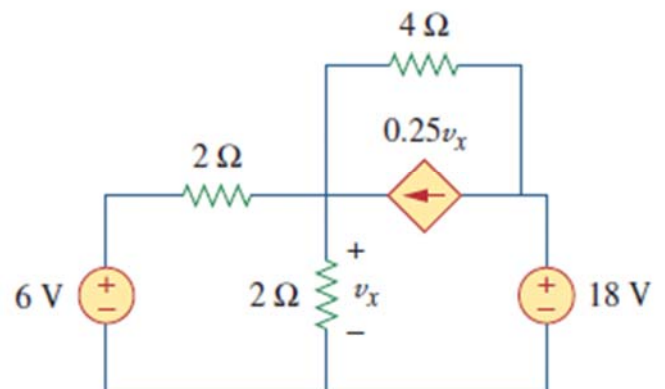
# Example 13


Find  $v_x$  in Fig. 4.20 using source transformation.



$$v_x = 3 - i = 7.5 \text{ V.}$$
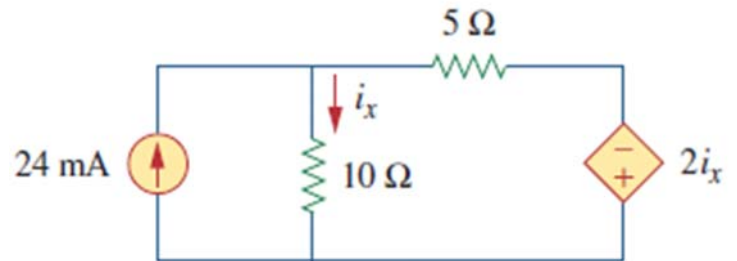
# Example 14

Use source transformation to find  $i_x$  in the circuit shown in Fig.



**Answer:** 7.059 mA.

**Thanks,..**  
**See you next week (ISA),...**