


# Circuits I – Tutorial 04

## Nodal Analysis

#	Student ID	Student Name	Grade (10)
-			

Q1

3.6 Solve for  $V_1$  in the circuit of Fig. 3.55 using nodal analysis.

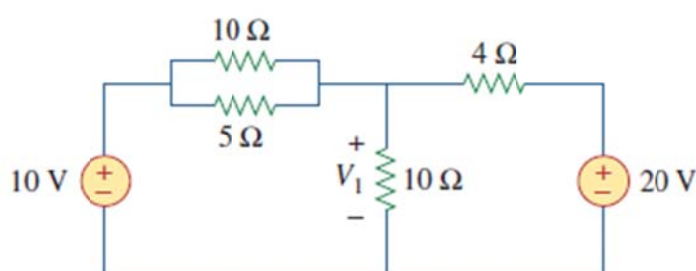

Sol 1

$$\frac{(V_1 - (-10))}{5} + \frac{(V_1 - (-10))}{10} + \frac{(V_1 - 0)}{10} + \frac{(V_1 - 20)}{10} = 0$$

Simplify and solve.


$$\left(\frac{1}{5} + \frac{1}{10} + \frac{1}{10} + \frac{1}{10}\right)V_1 = -\frac{10}{5} - \frac{10}{10} + \frac{20}{10}$$

$$(0.2 + 0.1 + 0.1 + 0.1)V_1 = 0.5V_1 = -2 - 1 + 2 = -1$$

$$V_1 = -2 \text{ V.}$$

Q2

3.13 Calculate  $v_1$  and  $v_2$  in the circuit of Fig. 3.62 using nodal analysis.

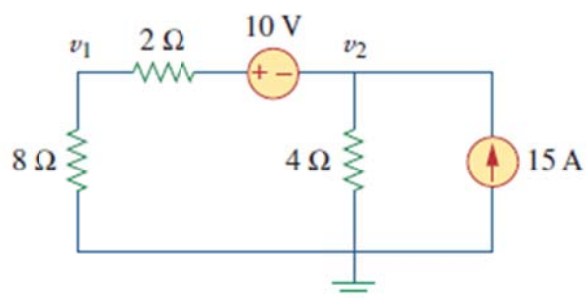

Sol 2

At node number 2,  $[(v_2 + 10) - 0]/10 + [(v_2 - 0)/4] - 15 = 0$  or  
 $(0.1 + 0.25)v_2 = 0.35v_2 = -1 + 15 = 14$  or


$$v_2 = 40 \text{ volts.}$$

Next,  $I = [(v_2 + 10) - 0]/10 = (40 + 10)/10 = 5$  amps and


$$v_1 = 8 \times 5 = 40 \text{ volts.}$$

Q3

3.15 Apply nodal analysis to find  $i_o$  and the power dissipated in each resistor in the circuit of Fig. 3.64.

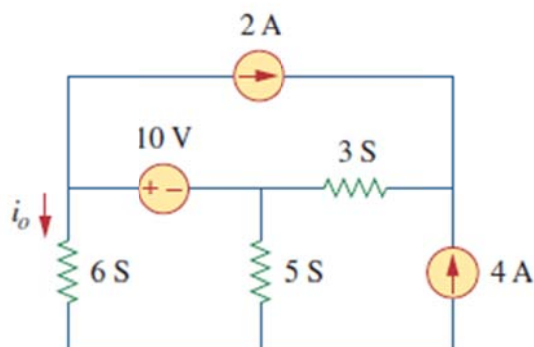

Sol 3

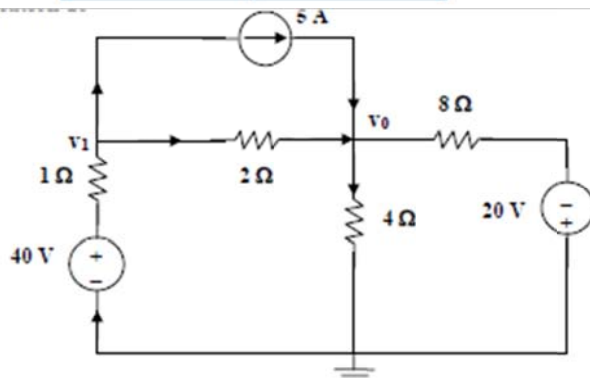

$$\text{Nodes 1 and 2 form a supernode so that } v_1 = v_2 + 10 \quad (1)$$

$$\text{At the supernode, } 2 + 6v_1 + 5v_2 = 3(v_3 - v_2) \longrightarrow 2 + 6v_1 + 8v_2 = 3v_3 \quad (2)$$

$$\text{At node 3, } 2 + 4 = 3(v_3 - v_2) \longrightarrow v_3 = v_2 + 2 \quad (3)$$

Substituting (1) and (3) into (2),

$$2 + 6v_2 + 60 + 8v_2 = 3v_2 + 6 \longrightarrow v_2 = \frac{-56}{11}$$

$$v_1 = v_2 + 10 = \frac{54}{11}$$

$$i_o = 6v_1 = 29.45 \text{ A}$$


$$P_{6S} = \frac{v_1^2}{R} = v_1^2 G = \left(\frac{54}{11}\right)^2 6 = 144.6 \text{ W}$$

$$P_{5S} = v_2^2 G = \left(\frac{-56}{11}\right)^2 5 = 129.6 \text{ W}$$

$$P_{3S} = (v_2 - v_3)^2 G = (2)^2 3 = 12 \text{ W}$$

Q4


3.20 For the circuit in Fig. 3.69, find  $v_1$ ,  $v_2$ , and  $v_3$  using nodal analysis.

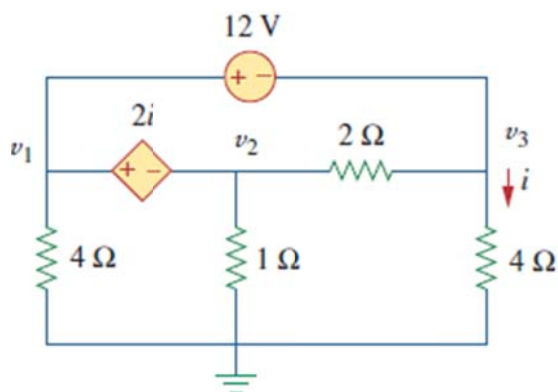

Sol 4

Nodes 1 and 2 form a supernode; so do nodes 1 and 3. Hence
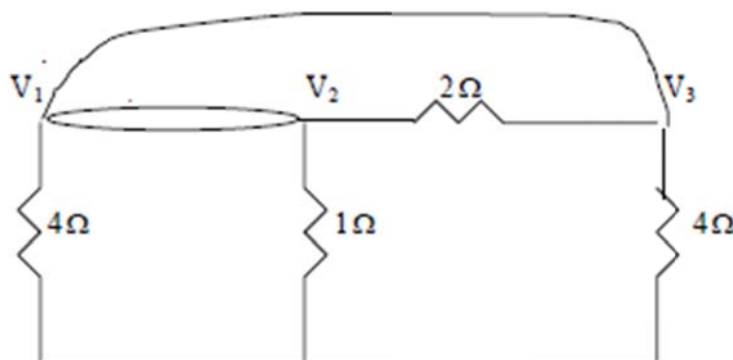
$$\frac{V_1}{4} + \frac{V_2}{1} + \frac{V_3}{4} = 0 \quad \longrightarrow \quad V_1 + 4V_2 + V_3 = 0 \quad (1)$$



Between nodes 1 and 3,

$$-V_1 + 12 + V_3 = 0 \quad \longrightarrow \quad V_3 = V_1 - 12 \quad (2)$$

Similarly, between nodes 1 and 2,

$$V_1 = V_2 + 2i \quad (3)$$

But  $i = V_3 / 4$ . Combining this with (2) and (3) gives

$$V_2 = 6 + V_1 / 2 \quad (4)$$


Solving (1), (2), and (4) leads to

$$\underline{V_1 = -3V, \quad V_2 = 4.5V, \quad V_3 = -15V}$$

Q5

3.26 Calculate the node voltages  $v_1$ ,  $v_2$ , and  $v_3$  in the circuit of Fig. 3.75.

 ML

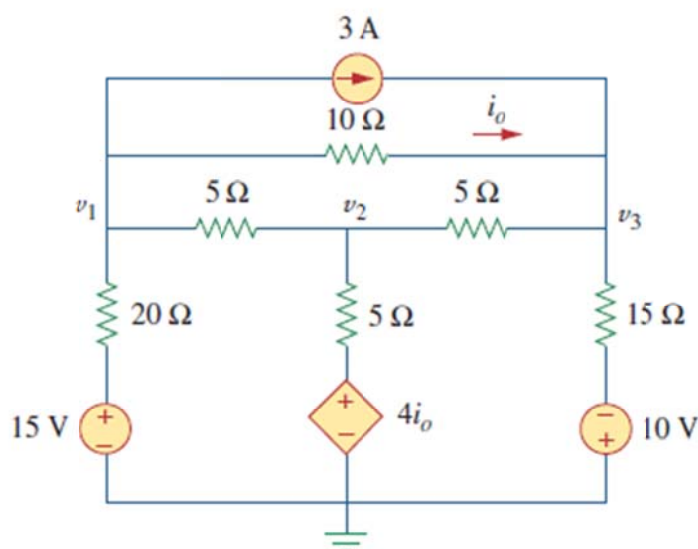

Sol 5

At node 1,

$$\frac{15 - V_1}{20} = 3 + \frac{V_1 - V_3}{10} + \frac{V_1 - V_2}{5} \quad \longrightarrow \quad -45 = 7V_1 - 4V_2 - 2V_3 \quad (1)$$

At node 2,

$$\frac{V_1 - V_2}{5} + \frac{4I_o - V_2}{5} = \frac{V_2 - V_3}{5} \quad (2)$$

But  $I_o = \frac{V_1 - V_3}{10}$ . Hence, (2) becomes

$$0 = 7V_1 - 15V_2 + 3V_3 \quad (3)$$

At node 3,

$$3 + \frac{V_1 - V_3}{10} + \frac{-10 - V_3}{15} + \frac{V_2 - V_3}{5} = 0 \quad \longrightarrow \quad 70 = -3V_1 - 6V_2 + 11V_3 \quad (4)$$

Putting (1), (3), and (4) in matrix form produces

$$\begin{pmatrix} 7 & -4 & -2 \\ 7 & -15 & 3 \\ -3 & -6 & 11 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} -45 \\ 0 \\ 70 \end{pmatrix} \quad \longrightarrow \quad AV = B$$

Using MATLAB leads to

$$V = A^{-1}B = \begin{pmatrix} -7.19 \\ -2.78 \\ 2.89 \end{pmatrix}$$

Thus,

$$V_1 = -7.19V; V_2 = -2.78V; V_3 = 2.89V.$$