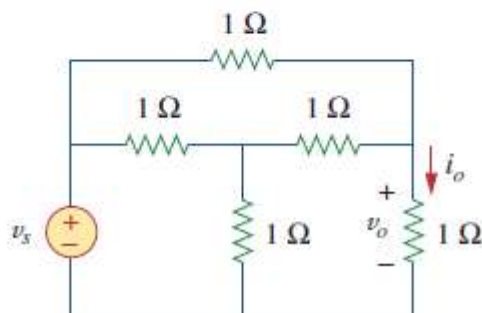


# Circuits I – Tutorial 06

## Circuit Theorems (1)


Q1

- 4.3 (a) In the circuit of Fig. 4.71, calculate  $v_o$  and  $i_o$  when  $v_s = 1$  V.  
 (b) Find  $v_o$  and  $i_o$  when  $v_s = 10$  V.  
 (c) What are  $v_o$  and  $i_o$  when each of the  $1\text{-}\Omega$  resistors is replaced by a  $10\text{-}\Omega$  resistor and  $v_s = 10$  V?



linearity

Sol 1

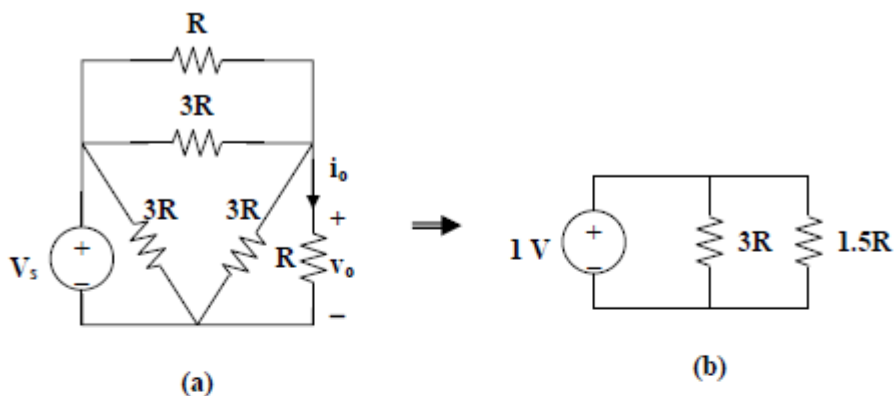

(a) We transform the Y sub-circuit to the equivalent  $\Delta$ .

$$R|3R = \frac{3R^2}{4R} = \frac{3}{4}R, \quad \frac{3}{4}R + \frac{3}{4}R = \frac{3}{2}R$$

$$v_o = \frac{v_s}{2} \text{ independent of } R$$

$$i_o = v_o/R$$


When  $v_s = 1$ V,  $v_o = 0.5$ V,  $i_o = 0.5$ A

(b) When  $v_s = 10$ V,  $v_o = 5$ V,  $i_o = 5$ A

(c) When  $v_s = 10$ V and  $R = 10\Omega$ ,  
 $v_o = 5$ V,  $i_o = 10/(10) = 500$ mA


Q2

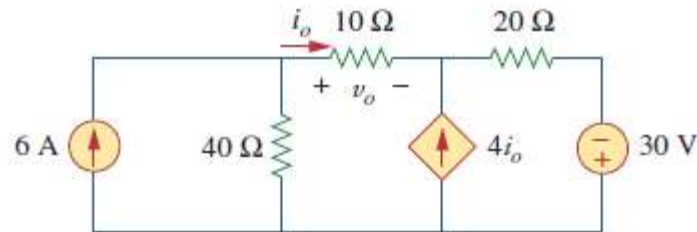4.11 Use the superposition principle to find  $i_o$  and  $v_o$  in the circuit of Fig. 4.79.



Superposition

Sol 2

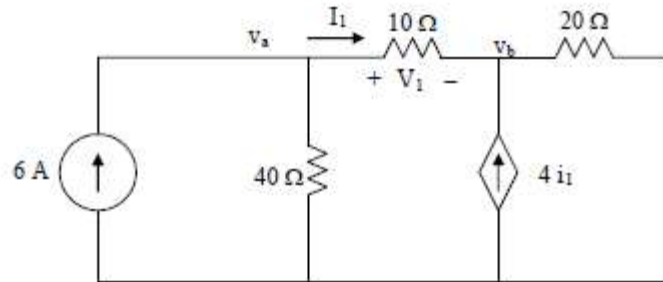

At node a,

$$6 = \frac{v_a}{40} + \frac{v_a - v_b}{10} \longrightarrow 240 = 5v_a - 4v_b \quad (1)$$

At node b,

$$-I_1 - 4I_1 + (v_b - 0)/20 = 0 \text{ or } v_b = 100I_1$$


But  $i_1 = \frac{v_a - v_b}{10}$  which leads to  $100(v_a - v_b)/10 = v_b$  or  $v_b = 0.9091v_a$  (2)

Substituting (2) into (1),

$$5v_a - 3.636v_a = 240 \text{ or } v_a = 175.95 \text{ and } v_b = 159.96$$

However,  $v_1 = v_a - v_b = 15.99 \text{ V}$ .

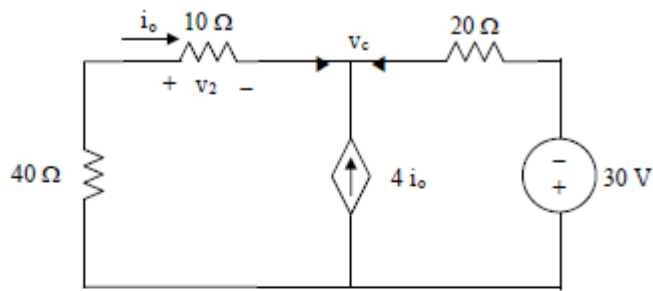To find  $v_2$ , consider the circuit below.



$$\frac{0 - v_c}{50} + 4i_o + \frac{(-30 - v_c)}{20} = 0$$

$$\text{But } i_o = \frac{(0 - v_c)}{50}$$

$$-\frac{5v_c}{50} - \frac{(30 + v_c)}{20} = 0 \longrightarrow v_c = -10 \text{ V}$$


$$i_2 = \frac{0 - v_c}{50} = \frac{0 + 10}{50} = \frac{1}{5}$$

$$v_2 = 10i_2 = 2 \text{ V}$$

$$v_o = v_1 + v_2 = 15.99 + 2 = 17.99 \text{ V and } i_o = v_o/10 = 1.799 \text{ A.}$$

Q3

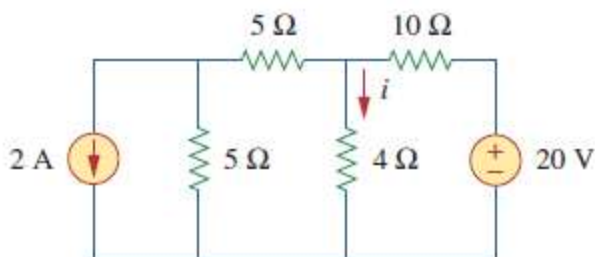
4.22 For the circuit in Fig. 4.90, use source transformation to find  $i$ .




Source transformation

Sol 3

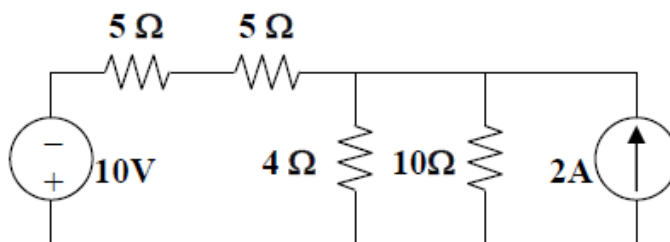We transform the two sources to get the circuit shown in Fig. (a).



(a)

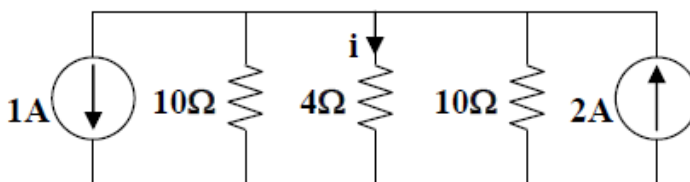

(b)

We now transform only the voltage source to obtain the circuit in Fig. (b).

$$10 \parallel 10 = 5 \text{ ohms, } i = [5 / (5 + 4)](2 - 1) = 5/9 = \mathbf{555.5 \text{ mA}}$$