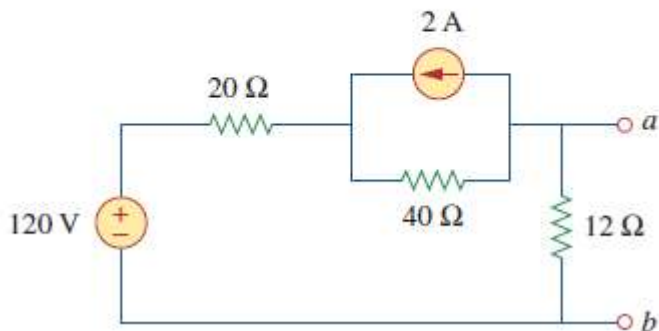


# Circuits I – Tutorial 07

## Thevenin and Norton


Q1

4.37 Find the Norton equivalent with respect to terminals  $a$ - $b$  in the circuit shown in Fig. 4.104.




Sol 1

$R_N$  is found from the circuit below.

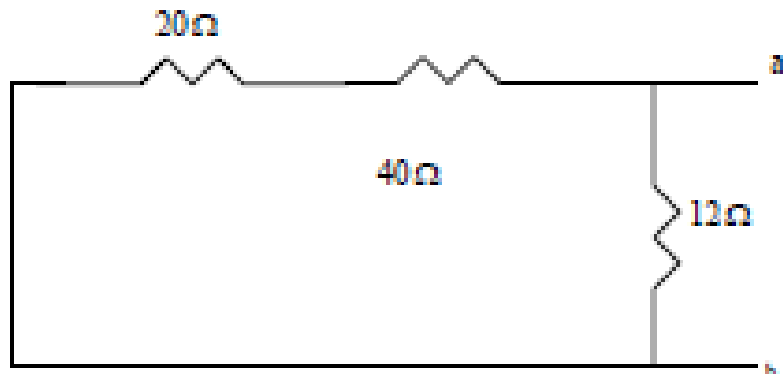


$$R_N = 12 \parallel (20 + 40) = 10 \Omega$$

$I_N$  is found from the circuit below.

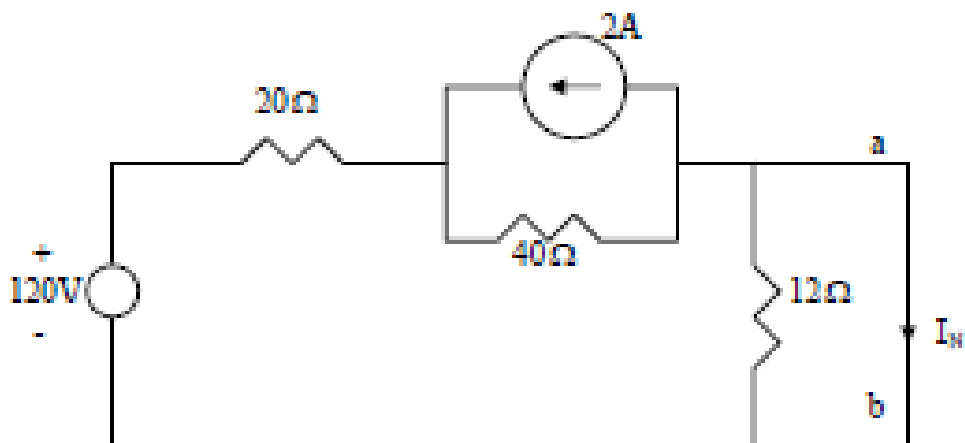

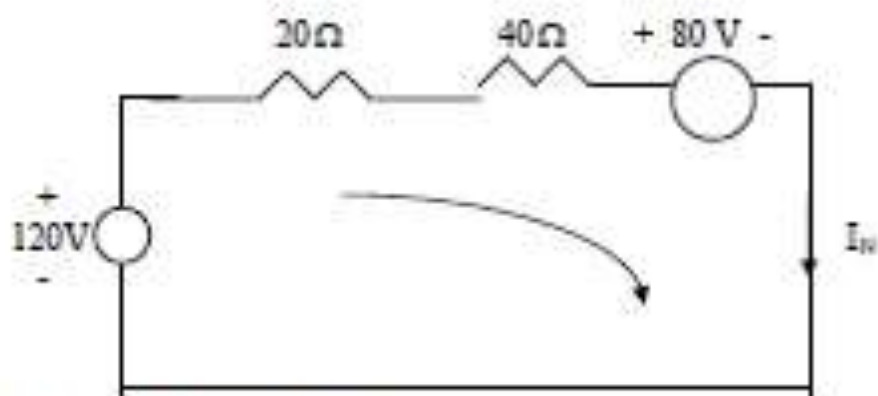Applying source transformation to the current source yields the circuit below.




Applying KVL to the loop yields

$$-120 + 80 + 60I_x = 0 \quad \longrightarrow \quad I_x = 40/60 = 666.7 \text{ mA.}$$


Q2

4.38 Apply Thevenin's theorem to find  $V_o$  in the circuit of Fig. 4.105.

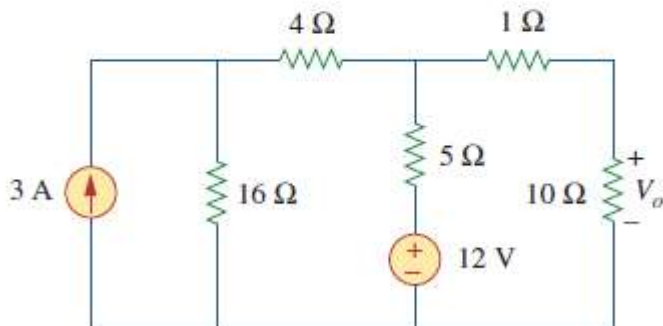


Sol 2

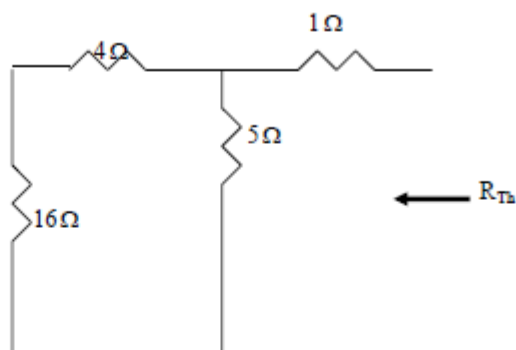We find Thevenin equivalent at the terminals of the 10-ohm resistor. For  $R_{Th}$ , consider the circuit below.



$$R_{Th} = 1 + 5 \parallel (4 + 16) = 1 + 4 = 5\Omega$$

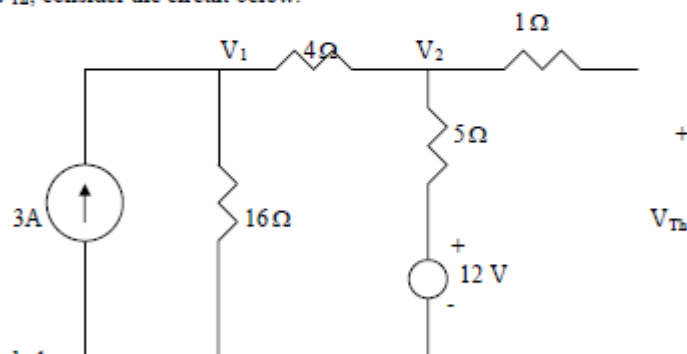For  $V_{Th}$ , consider the circuit below.



At node 1,

$$3 = \frac{V_1}{16} + \frac{V_1 - V_2}{4} \quad \longrightarrow \quad 48 = 5V_1 - 4V_2 \quad (1)$$


At node 2,

$$\frac{V_1 - V_2}{4} + \frac{12 - V_2}{5} = 0 \quad \longrightarrow \quad 48 = -5V_1 + 9V_2 \quad (2)$$

Solving (1) and (2) leads to

$$V_{Th} = V_2 = 19.2$$

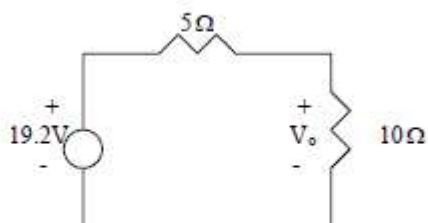Thus, the given circuit can be replaced as shown below.




Using voltage division,

$$V_o = \frac{10}{10+5}(19.2) = 12.8 \text{ V.}$$


Q3

4.53 Find the Norton equivalent at terminals  $a-b$  of the circuit in Fig. 4.119.

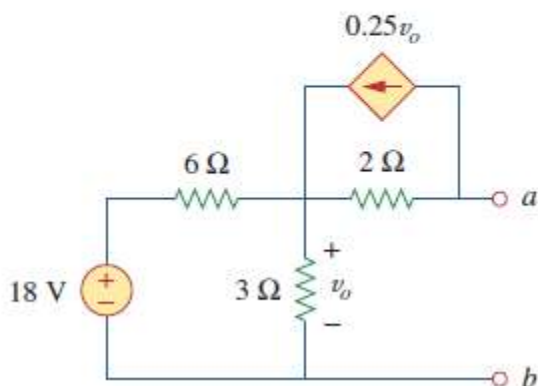


Sol 3

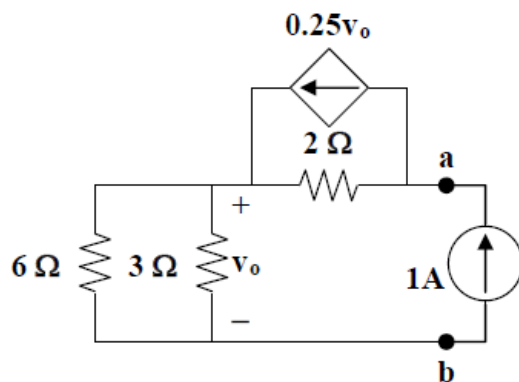To get  $R_{Th}$ , consider the circuit in Fig. (a).



(a)

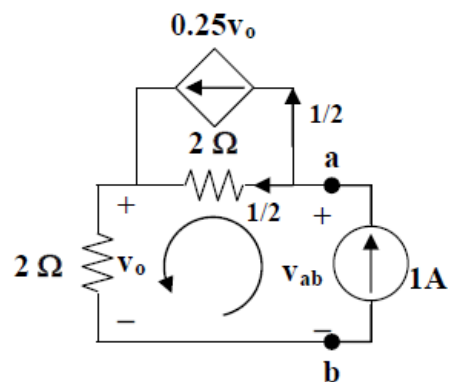

(b)


From Fig. (b),

$$v_o = 2 \times 1 = 2V, \quad -v_{ab} + 2 \times (1/2) + v_o = 0$$

$$v_{ab} = 3V$$

$$R_N = v_{ab}/1 = 3 \text{ ohms}$$

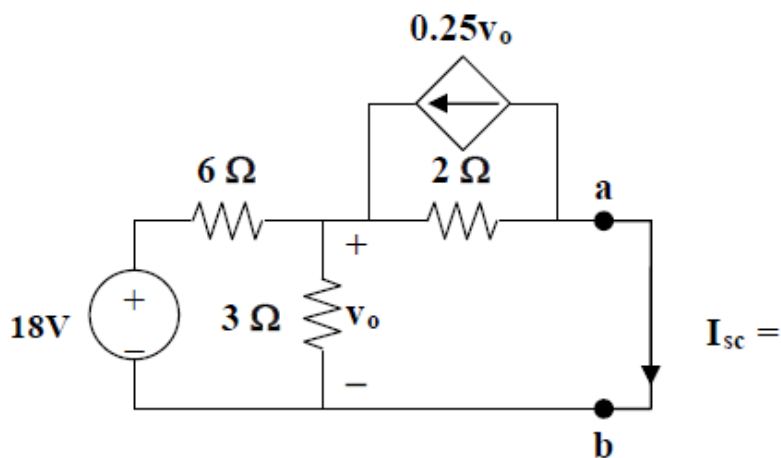To get  $I_N$ , consider the circuit in Fig. (c).



(c)


$$[(18 - v_o)/6] + 0.25v_o = (v_o/2) + (v_o/3) \text{ or } v_o = 4V$$

But,

$$(v_o/2) = 0.25v_o + I_N, \text{ which leads to } I_N = 1 \text{ A}$$

Q4


4.63 Find the Norton equivalent for the circuit in Fig. 4.129.

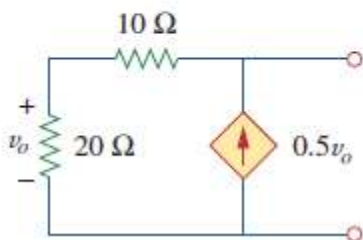

Sol 4

Because there are no independent sources,  $I_N = I_{sc} = 0 \text{ A}$

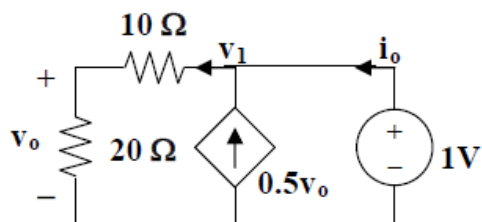$R_N$  can be found using the circuit below.



Applying KCL at node 1,  $v_1 = 1$ , and  $v_o = (20/30)v_1 = 2/3$


$$i_o = (v_1/30) - 0.5v_o = (1/30) - 0.5 \times 2/3 = 0.03333 - 0.33333 = -0.3 \text{ A.}$$

Hence,

$$R_N = 1/(-0.3) = -3.333 \text{ ohms}$$

Q5

4.66 Find the maximum power that can be delivered to the resistor  $R$  in the circuit of Fig. 4.132.

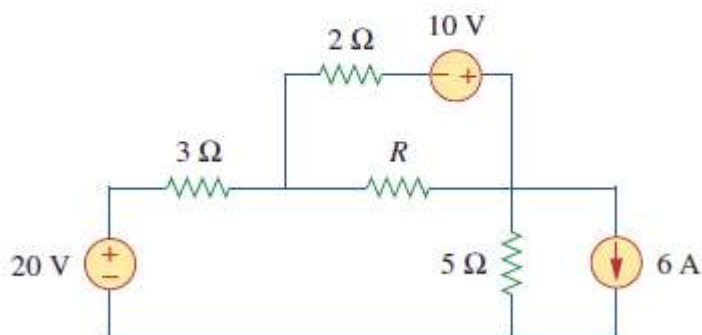






Sol 5

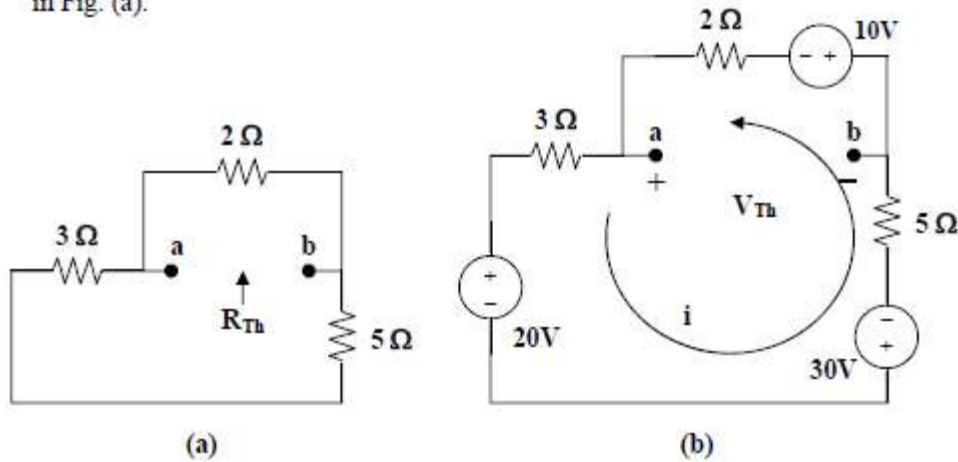We first find the Thevenin equivalent at terminals a and b. We find  $R_{Th}$  using the circuit in Fig. (a).



$$R_{Th} = 2 \parallel (3 + 5) = 2 \parallel 8 = 1.6 \text{ ohms}$$

By performing source transformation on the given circuit, we obtain the circuit in (b). We now use this to find  $V_{Th}$ .

$$10i + 30 + 20 + 10 = 0, \text{ or } i = -6$$

$$V_{Th} + 10 + 2i = 0, \text{ or } V_{Th} = 2 \text{ V}$$

$$p = V_{Th}^2 / (4R_{Th}) = (2)^2 / [4(1.6)] = 625 \text{ m watts}$$