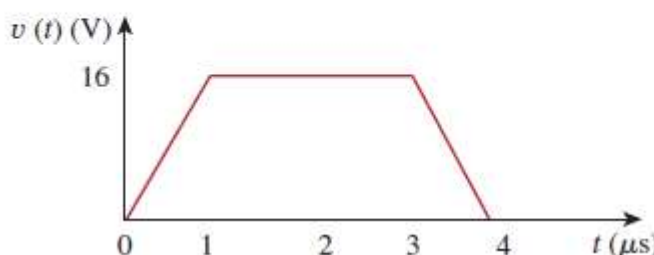


Circuits I – Tutorial 08

Capacitors and Inductors

| | |
|-------|--|
| Q1 | <p>6.1 If the voltage across a 7.5-F capacitor is $2te^{-3t}$ V, find the current and the power.</p> |
| Sol 1 | $i = C \frac{dv}{dt} = 7.5(2e^{-3t} - 6te^{-3t}) = 15(1 - 3t)e^{-3t} \text{ A}$ $p = vi = 15(1-3t)e^{-3t} \cdot 2t e^{-3t} = 30t(1 - 3t)e^{-6t} \text{ W.}$ <p>$15(1 - 3t)e^{-3t} \text{ A}, 30t(1 - 3t)e^{-6t} \text{ W}$</p> |

| | |
|----|---|
| Q2 | <p>6.10 The voltage across a 5-mF capacitor is shown in Fig. 6.47. Determine the current through the capacitor.</p>  |
|----|---|



Sol 2

$$i = C \frac{dv}{dt} = 5 \times 10^{-3} \frac{dv}{dt}$$


$$v = \begin{cases} 16t, & 0 < t < 1 \mu s \\ 16, & 1 < t < 3 \mu s \\ 64 - 16t, & 3 < t < 4 \mu s \end{cases}$$

$$\frac{dv}{dt} = \begin{cases} 16 \times 10^6, & 0 < t < 1 \mu s \\ 0, & 1 < t < 3 \mu s \\ -16 \times 10^6, & 3 < t < 4 \mu s \end{cases}$$

$$i(t) = \begin{cases} 80 \text{ kA}, & 0 < t < 1 \mu s \\ 0, & 1 < t < 3 \mu s \\ -80 \text{ kA}, & 3 < t < 4 \mu s \end{cases}$$

Q3

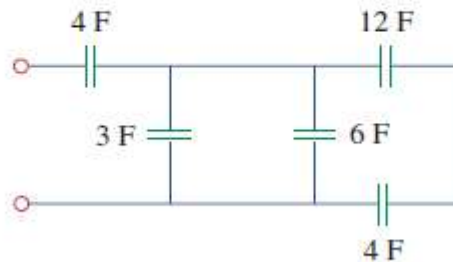6.17 Determine the equivalent capacitance for each of the circuits of Fig. 6.51.




(a)

Sol 3

(a) $4F$ in series with $12F = 4 \times 12 / (4 + 12) = 3F$
 $3F$ in parallel with $6F$ and $3F = 3 + 6 + 3 = 12F$
 $4F$ in series with $12F = 3F$
 i.e. $C_{eq} = 3F$

Q4

6.24 For the circuit in Figure 6.58, determine (a) the voltage across each capacitor and (b) the energy stored in each capacitor.

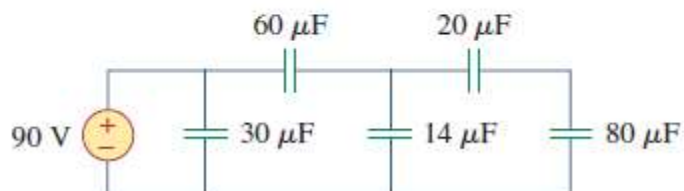

Sol 4

$20\mu\text{F}$ is series with $80\mu\text{F} = \frac{20 \times 80}{100} = 16\mu\text{F}$

$14\mu\text{F}$ is parallel with $16\mu\text{F} = 30\mu\text{F}$

(a) $V_{30\mu\text{F}} = 90\text{V}$

$V_{60\mu\text{F}} = 30\text{V}$

$V_{14\mu\text{F}} = 60\text{V}$

$V_{20\mu\text{F}} = \frac{80}{20 + 80} \times 60 = 48\text{V}$

$V_{80\mu\text{F}} = 60 - 48 = 12\text{V}$

(b) Since $w = \frac{1}{2} C V^2$

$W_{30\mu\text{F}} = \frac{1}{2} \times 30 \times 10^{-6} \times 8100 = 121.5\text{mJ}$

$W_{60\mu\text{F}} = \frac{1}{2} \times 60 \times 10^{-6} \times 900 = 27\text{mJ}$


$W_{14\mu\text{F}} = \frac{1}{2} \times 14 \times 10^{-6} \times 3600 = 25.2\text{mJ}$

$W_{20\mu\text{F}} = \frac{1}{2} \times 20 \times 10^{-6} \times (48)^2 = 23.04\text{mJ}$

$W_{80\mu\text{F}} = \frac{1}{2} \times 80 \times 10^{-6} \times 144 = 5.76\text{mJ}$

Q5

6.32 In the circuit of Fig. 6.64, let $i_s = 50e^{-2t}$ mA and $v_1(0) = 50$ V, $v_2(0) = 20$ V. Determine: (a) $v_1(t)$ and $v_2(t)$, (b) the energy in each capacitor at $t = 0.5$ s.

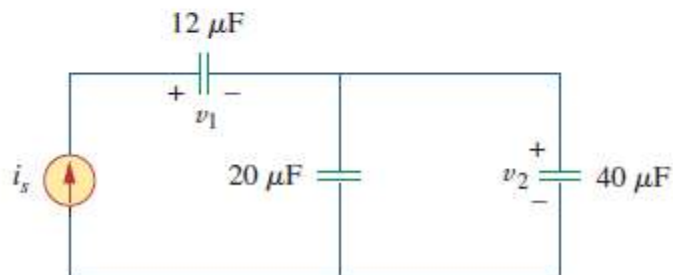

Sol 5

$$(a) C_{eq} = (12 \times 60) / 72 = 10 \mu F$$

$$v_1 = \frac{10^{-3}}{12 \times 10^{-6}} \int_0^t 50e^{-2t} dt + v_1(0) = -2083e^{-2t} \Big|_0^t + 50 = -2083e^{-2t} + 2133V$$

$$v_2 = \frac{10^{-3}}{60 \times 10^{-6}} \int_0^t 50e^{-2t} dt + v_2(0) = -416.7e^{-2t} \Big|_0^t + 20 = -416.7e^{-2t} + 436.7V$$

(b) At $t=0.5$ s,

$$v_1 = -2083e^{-1} + 2133 = 1366.7, \quad v_2 = -416.7e^{-1} + 436.7 = 283.4$$

$$w_{12\mu F} = \frac{1}{2} \times 12 \times 10^{-6} \times (1366.7)^2 = \underline{11.207 J}$$

$$w_{20\mu F} = \frac{1}{2} \times 20 \times 10^{-6} \times (283.4)^2 = \underline{803.2 mJ}$$

$$w_{40\mu F} = \frac{1}{2} \times 40 \times 10^{-6} \times (283.4)^2 = \underline{1.6063 J}$$



Q6

6.34 The current through a 10-mH inductor is $10e^{-t/2}$ A.
Find the voltage and the power at $t = 3$ s.

Sol 6

$$i = 10e^{-t/2}$$

$$v = L \frac{di}{dt} = 10 \times 10^{-3} (10) \left(\frac{1}{2} \right) e^{-t/2}$$
$$= -50e^{-t/2} \text{ mV}$$


$$v(3) = -50e^{-3/2} \text{ mV} = \mathbf{-11.157 \text{ mV}}$$

$$p = vi = -500e^{-t} \text{ mW}$$

$$p(3) = -500e^{-3} \text{ mW} = \mathbf{-24.89 \text{ mW.}}$$

Q7

6.45 If the voltage waveform in Fig. 6.68 is applied to a 10-mH inductor, find the inductor current $i(t)$. Assume $i(0) = 0$.

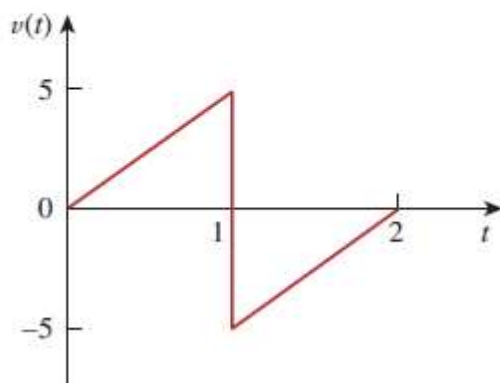

Sol 7

$$i(t) = \frac{1}{L} \int_0^t v(t) dt + i(0)$$

For $0 < t < 1$, $v = 5t$

$$\begin{aligned} i &= \frac{1}{10 \times 10^{-3}} \int_0^t 5t dt + 0 \\ &= 250t^2 \text{ A} \end{aligned}$$


For $1 < t < 2$, $v = -10 + 5t$

$$\begin{aligned} i &= \frac{1}{10 \times 10^{-3}} \int_1^t (-10 + 5t) dt + i(1) \\ &= \int_1^t (0.5t - 1) dt + 0.25 \text{ kA} \\ &= [1 - t + 0.25t^2] \text{ kA} \end{aligned}$$


$$i(t) = \begin{cases} 250t^2 \text{ A}, & 0 < t < 1 \text{ s} \\ [1 - t + 0.25t^2] \text{ kA}, & 1 < t < 2 \text{ s} \end{cases}$$

Q8

6.48 Under steady-state dc conditions, find i and v in the circuit in Fig. 6.71.

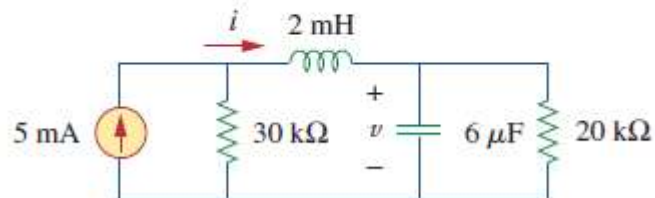

Sol 8

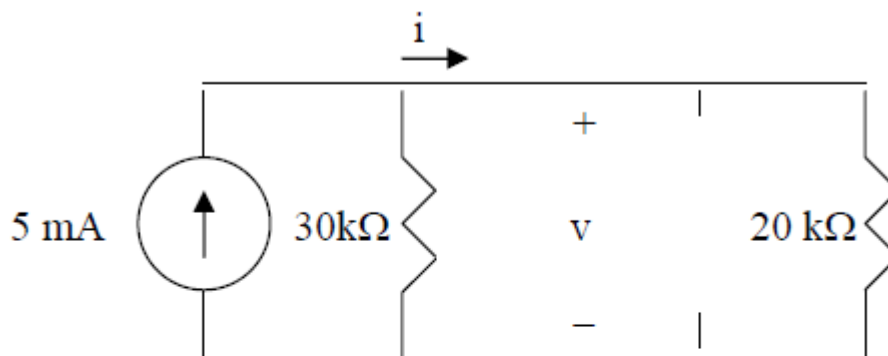


Using current division,

$$i = (30k / (30k + 20k)) (5mA) = 3 \text{ mA}$$

$$v = 20ki = 60 \text{ V}$$

Q9

6.51 Determine L_{eq} at terminals $a-b$ of the circuit in Fig. 6.73.

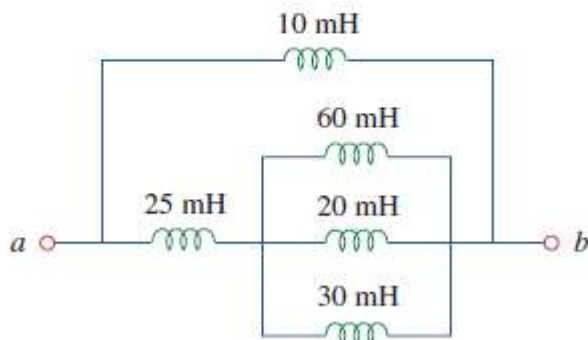

Sol 9

$$\frac{1}{L} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30} = \frac{1}{10}$$

$$L = 10 \text{ mH}$$

$$L_{eq} = 10 \parallel (25 + 10) = \frac{10 \times 35}{45}$$

$$= 7.778 \text{ mH}$$