

Electronic Circuits I – Laboratory 02 Zener diode

#	Student ID	Student Name	Grade (10)	Instructor signature
1				
2				
3				
4				
5				

Delivery Date	
---------------	--

Objective

The objective of this exercise is to examine the operation of the zener diode and to plot its characteristic curve.

Theory Overview

When forward biased, the zener diode behaves similarly to an ordinary switching diode, that is, it incurs a .7 volt drop for silicon devices. Unlike a switching diode, the zener is normally placed in reverse bias. If the circuit potential is high enough, the zener will exhibit a fixed voltage drop. This is called the zener potential or V_Z . Manufacturer's specify this voltage with respect to the zener test current, or I_{ZT} ; a point past the knee of the voltage-current curve. That is, if the zener's current is at least equal to I_{ZT} , then its voltage is approximately equal to the rated V_Z . Above this current, even very large increases in current will produce only very modest changes in voltage. Therefore, for basic circuit analysis, the zener can be replaced mathematically by a fixed voltage source equal to V_Z .

Procedure

Forward Curve

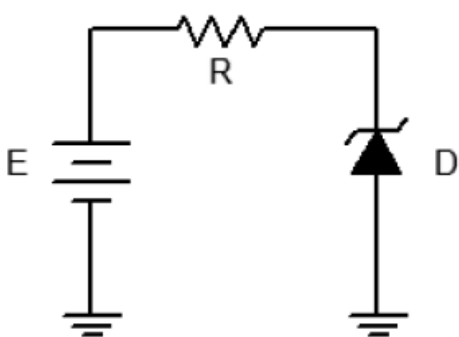


Figure 1

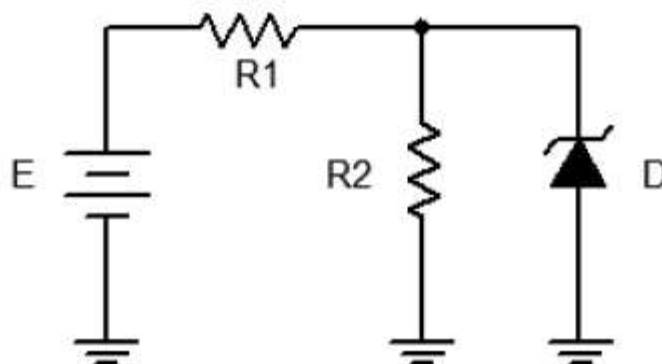


Figure 2

1. Consider the circuit of Figure 1 using $R = 2.2 \text{ k}\Omega$. For any positive value of E the zener is reverse biased. Until the zener potential is reached, the diode resistance is effectively infinite and thus no current flows. In this case the voltage across R is zero due to Ohm's Law. Consequently, all of E should appear across the zener. Once the source exceeds the zener voltage, the remainder of E (i.e. E minus the zener potential) drops across R . Thus, as E increases, the circulating current increases but the voltage across the zener remains steady.
2. Build the circuit of Figure 1 using $R = 2.2 \text{ k}\Omega$. Set E to 0 volts and measure both the diode's voltage and current and record the results in Table 2.1. Repeat this process for the remaining source voltages listed.
3. From the data collected in Table 1, plot the current versus voltage characteristic of the forward biased diode. Make sure V_D is the horizontal axis with I_D on the vertical.

Plot the curve presents V_d vs I_d

Practical Analysis

4. Consider the circuit of Figure 2 using $R_1 = 2.2 \text{ k}\Omega$ and $R_2 = 4.7 \text{ k}\Omega$. In general, to analyze circuits like this, first assume that the zener is out of the circuit and then compute the voltage across R_2 using the voltage divider rule. If the resulting voltage is less than the zener potential then the zener is inactive (high resistance) and does not affect the circuit. If, on the other hand, the resulting voltage is greater than the zener potential then the zener is active and will limit the voltage across R_2 to V_Z . Via KVL, the remainder of the voltage drops across R_1 and from this the supply current may be determined. This current will then split between R_2 and the zener. The R_2 current is found using Ohm's Law. The zener current is then found via KCL. Note that for higher and higher values of E , the voltage across (and therefore the current through) R_2 does not change. Instead, all of the "excess" current from the source passes through the zener.

5. Build the circuit of Figure 2 using $R_1 = 2.2 \text{ k}\Omega$ and $R_2 = 4.7 \text{ k}\Omega$. Set E to 2 volts. Compute the theoretical diode voltage and current, and record them in the first row of Table 2.2. Then measure the diode current and voltage and record in Table 2.2. Finally, compute and record the deviations.

6. Repeat step 5 for the remaining source voltages in Table 2.


Results and data analysis

Table 1

E (volts)	V_d	I_d
0		
1		
2		
5		
10		
15		
20		

Table 2

E (volts)	VD Theory	ID Theory	VD Exp	ID Exp	% Dev VD	% Dev ID
0						
1						
2						
5						
10						
15						
20						

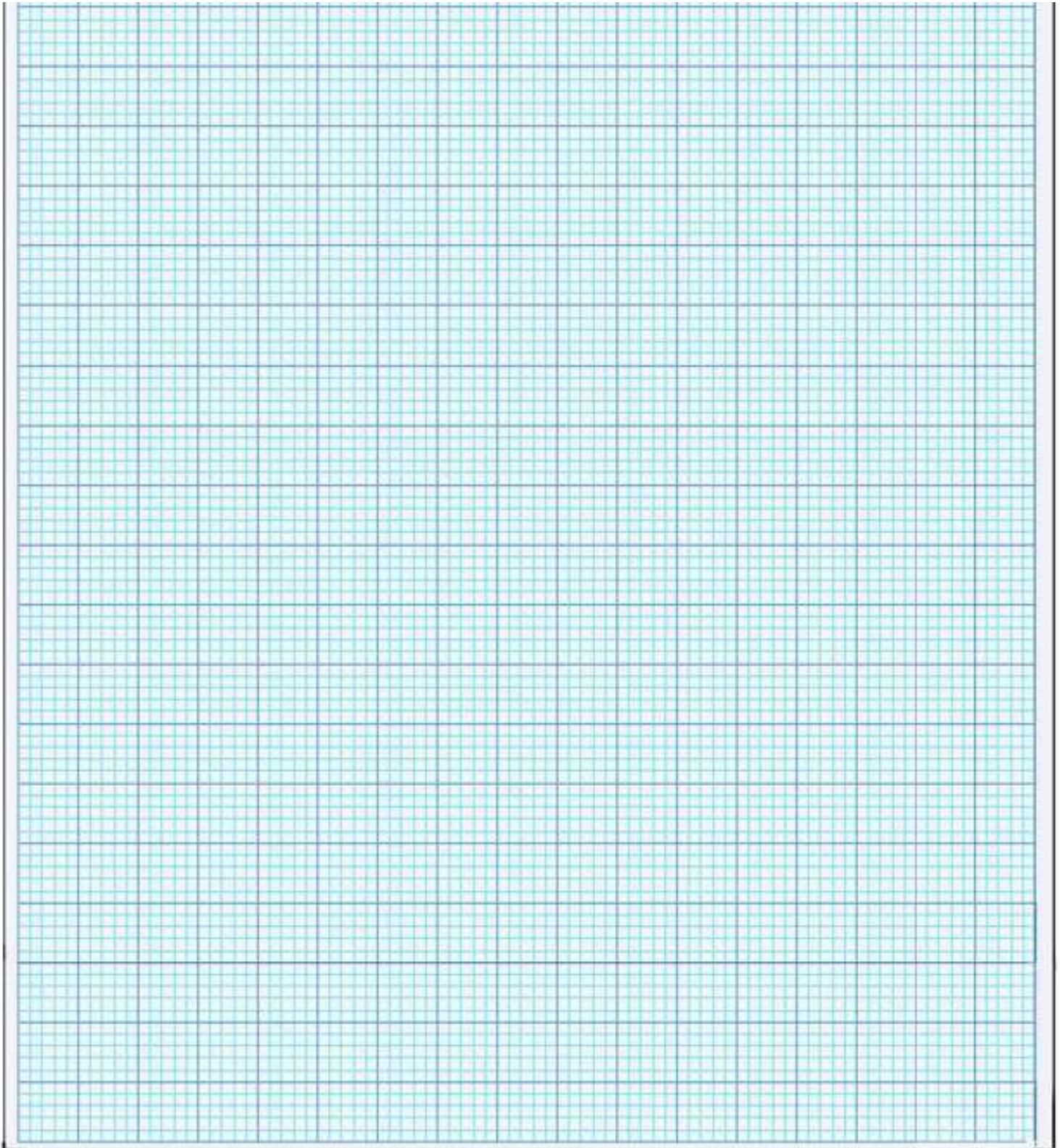

Questions and Conclusions

1. The instantaneous resistance (also known as AC resistance) of a diode may be approximated by taking the differences between adjacent current-voltage readings. That is, $r_{diode} = \Delta V_{diode} / \Delta I_{diode}$. What is the smallest effective resistance of the zener using Table 1 (show work)? ?

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

2. If the circuit of Figure 1 had been constructed with the zener reversed, how would this effect the results recorded in Table 1?

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

3. Assume that a diode with a much higher IZT rating (say, 100 mA) was used in this exercise. In general, what would the likely outcome be for the circuit of Figure 2.2?

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....