



# Lecture (04)

## Diode applications, cont.

By:

Dr. Ahmed ElShafee

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

## Agenda


- Full wave rectifier, cont.,...
- Filters
- Voltage Regulators
- Diode limiters
- Diode Clampers

۲

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

### Bridge Full-Wave Rectifier Operation


- uses four diodes connected as shown

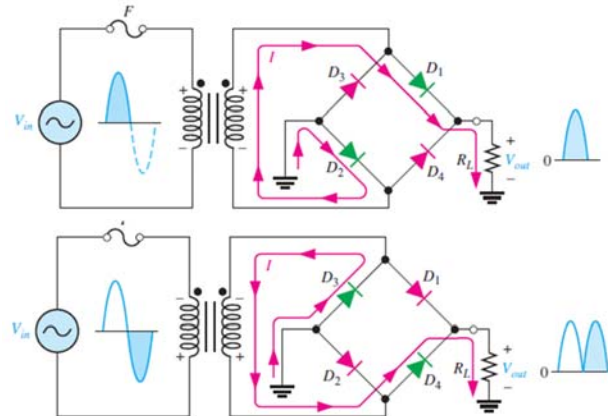

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

۳

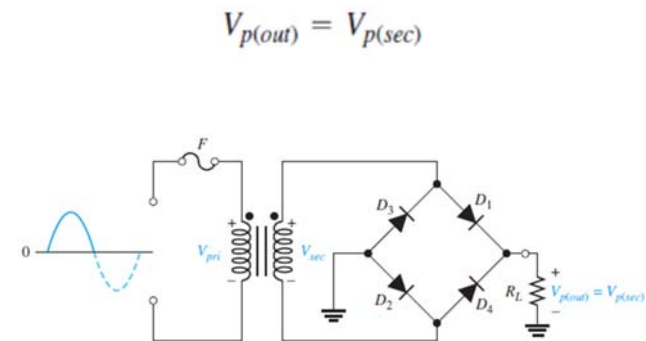- Neglecting the diode drops, the secondary voltage appears across the load resistor.




Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits


۴

- two diodes are always in series with the load resistor during both the positive and negative half-cycles. If these diode drops are taken into account, the output voltage is
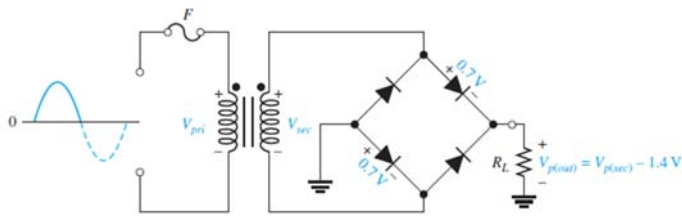
$$V_{p(out)} = V_{p(sec)} - 1.4 \text{ V}$$




- 

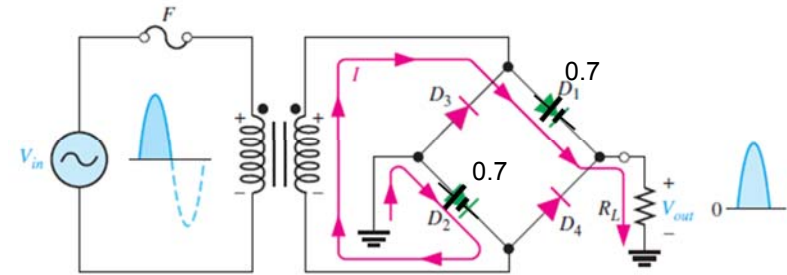


- **Peak Inverse Voltage**
- If diodes in forward bias are ideal

$$PIV = V_{p(out)}$$

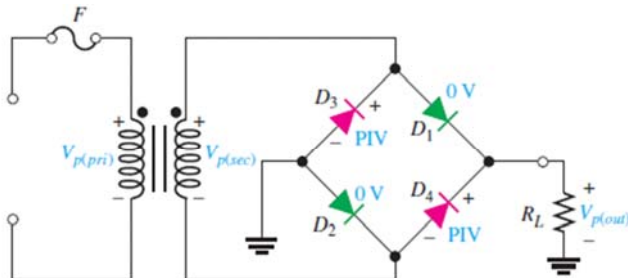



- If the diode drops of the forward-biased diodes are included

$$PIV = V_{p(out)} + 0.7 \text{ V}$$

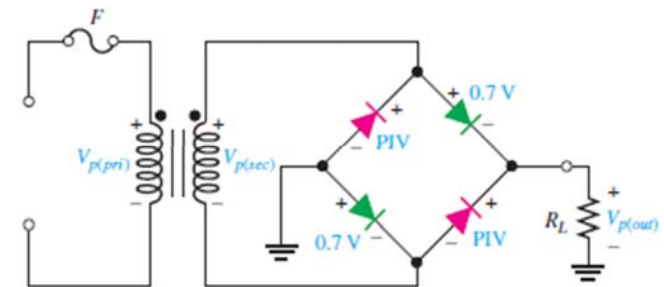
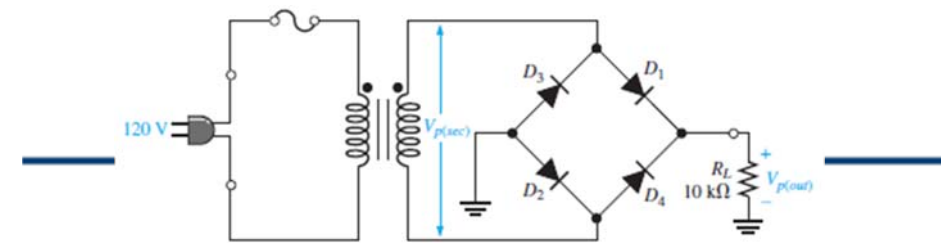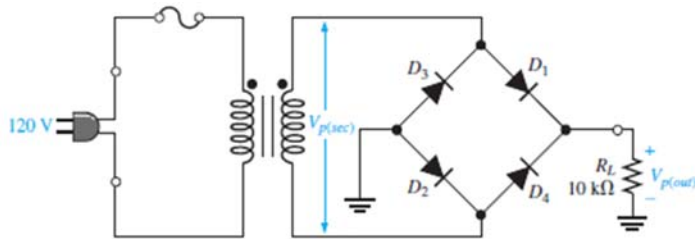
## Example 04

- Determine the peak output voltage for the bridge rectifier in Figure. Assuming the practical model, what PIV rating is required for the diodes?
- The transformer is specified to have a 17V peak secondary voltage for the standard 120 V across the primary



$$V_{p(out)} = V_{p(sec)} - 1.4 \text{ V} = 17 \text{ V} - 1.4 \text{ V} = 15.6 \text{ V}$$

$$\text{PIV} = V_{p(out)} + 0.7 \text{ V} = 15.6 \text{ V} + 0.7 \text{ V} = 16.3 \text{ V}$$

9


Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

10

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits
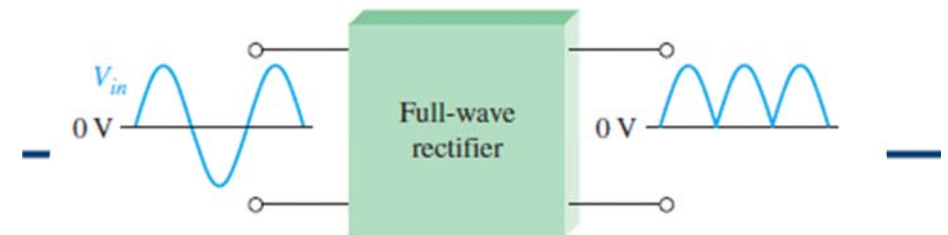
## power supply filters and regulators

- A power supply filter ideally eliminates the fluctuations in the output voltage of a halfwave or full-wave rectifier and produces a constant-level dc voltage
- Filtering is necessary because electronic circuits require a constant source of dc voltage and current to provide power and biasing for proper operation.
- Filters are implemented with capacitors,



(a) Rectifier without a filter

- The 60 Hz pulsating dc output of a half-wave rectifier or the 120 Hz pulsating output of a full-wave rectifier

11

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

12

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits




(b) Rectifier with a filter (output ripple is exaggerated)


- Figure shows filtering concept giving a nearly smooth dc output voltage from the filter.
- The small amount of fluctuation in the filter output voltage is called *ripple*.
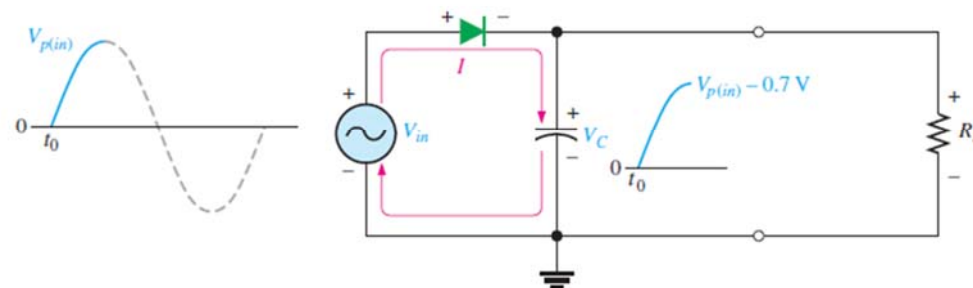
### • Capacitor-Input Filter


- During the positive first quarter-cycle of the input, the diode is forward-biased, allowing the capacitor to charge to within 0.7 V of the input peak



- When the input begins to decrease below its peak,, the capacitor retains its charge and the diode becomes reverse-biased because the cathode is more positive than the anode.
- During the remaining part of the cycle, the capacitor can discharge only through the load resistance at a rate determined by the  $RLC$  time constant, which is normally long compared to the period of the input.
- The larger the time constant, the less the capacitor will discharge.

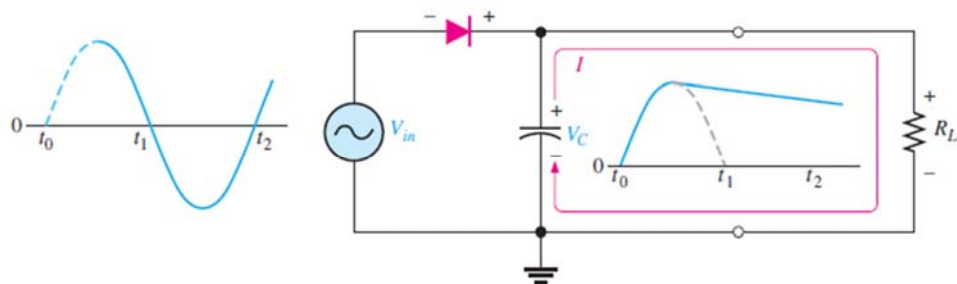


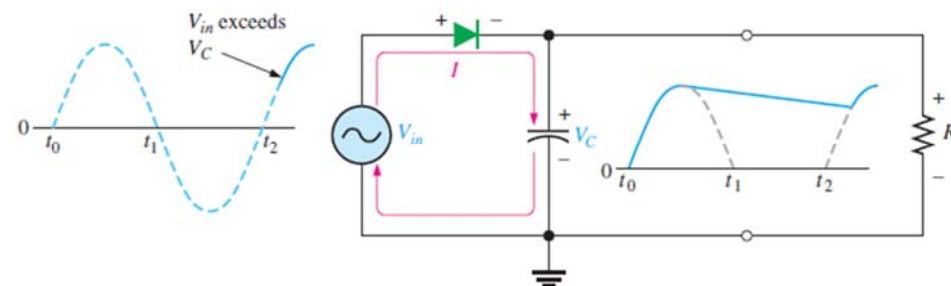- During the first quarter of the next cycle, as illustrated , the diode will again become forward-biased when the input voltage exceeds the capacitor voltage by approximately 0.7 V.




- **Ripple Voltage**

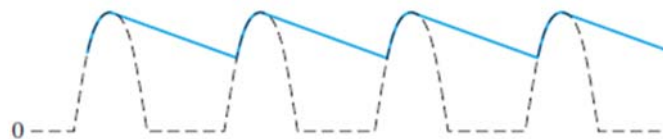- The variation in the capacitor voltage due to the charging and discharging is called the **ripple voltage**




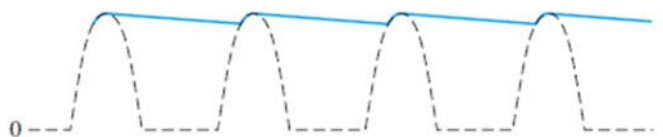(a) Larger ripple (blue) means less effective filtering.




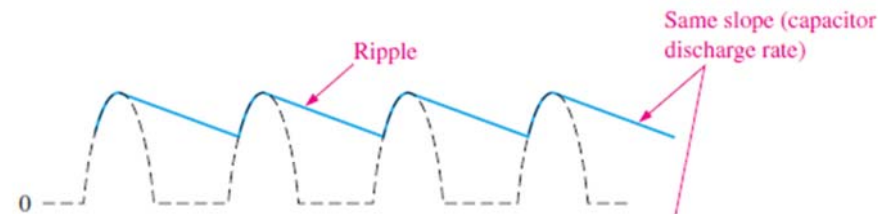(b) Smaller ripple means more effective filtering. Generally, the larger the capacitor value, the smaller the ripple for the same input and load.

- a full-wave rectifier is twice that of a half-wave rectifier, easier to filter because of the shorter time between peaks.



(a) Half-wave

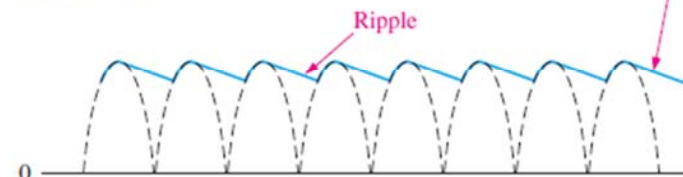


(b) Full-wave

- **Ripple Factor** The **ripple factor (r)** is an indication of the effectiveness of the filter and is defined as

$$r = \frac{V_{r(pp)}}{V_{DC}}$$

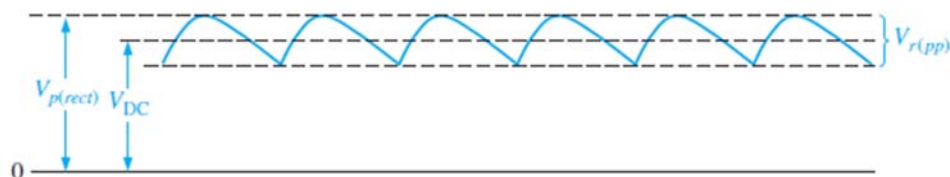- where  $V_{r(pp)}$  is the peak-to-peak ripple voltage and  $V_{DC}$  is the dc (average) value of the filter's output voltage,



- For a full-wave rectifier with a capacitor-input filter

$$V_{r(pp)} \cong \left( \frac{1}{fR_L C} \right) V_{p(rect)}$$

$$v_{dc} = v_p - \frac{v_r}{2}$$


$$v_{dc} = v_p - \frac{v_p}{2fR_L C}$$

$$v_{dc} = v_p \left( 1 - \frac{1}{2fR_L C} \right)$$

$$V_{DC} \cong \left( 1 - \frac{1}{2fR_L C} \right) V_{p(rect)}$$

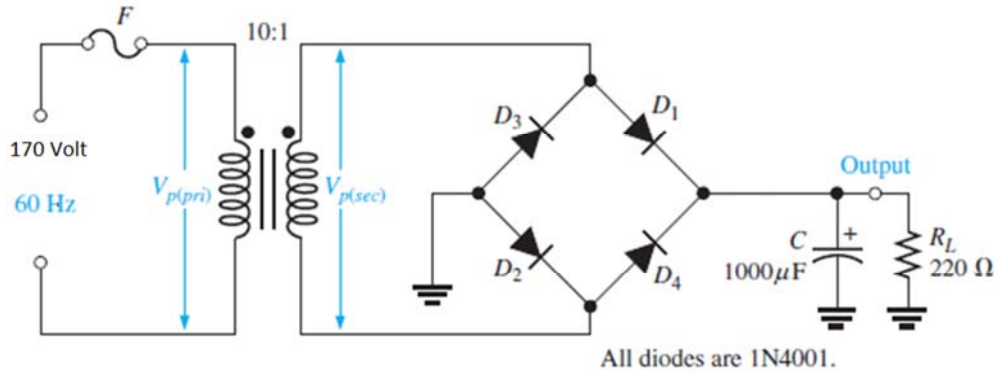
# Example 05

- Determine the ripple factor for the filtered bridge rectifier with a load as indicated in Figure



٢١

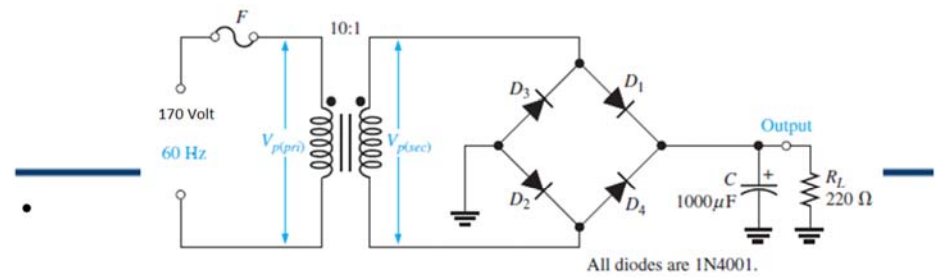Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits



$$V_{p(sec)} = nV_{p(pri)} = 0.1(170 \text{ V}) = 17.0 \text{ V}$$

$$V_{p(rect)} = V_{p(sec)} - 1.4 \text{ V} = 17.0 \text{ V} - 1.4 \text{ V} = 15.6 \text{ V}$$


$$V_{r(pp)} \cong \left( \frac{1}{fR_L C} \right) V_{p(rect)} = \left( \frac{1}{(120 \text{ Hz})(220 \Omega)(1000 \mu\text{F})} \right) 15.6 \text{ V} = 0.591 \text{ V}$$

$$V_{DC} = \left( 1 - \frac{1}{2fR_L C} \right) V_{p(rect)} = \left( 1 - \frac{1}{(240 \text{ Hz})(220 \Omega)(1000 \mu\text{F})} \right) 15.6 \text{ V} = 15.3 \text{ V}$$

$$r = \frac{V_{r(pp)}}{V_{DC}} = \frac{0.591 \text{ V}}{15.3 \text{ V}} = 0.039$$

ACU : Fall 2015, Electronic Circuits

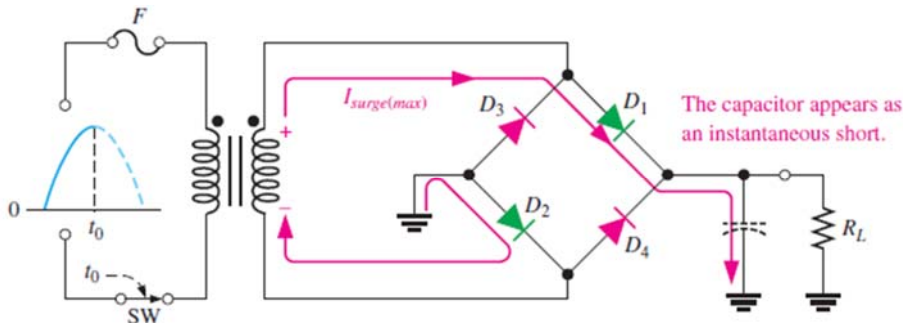- Surge Current in the Capacitor-Input Filter**
- At the instant the switch is closed, voltage is connected to the bridge and the uncharged capacitor appears as a short
- This produces an initial surge of current,  $I_{surge}$ ,



٢٢

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

- The worst-case situation occurs when the switch is closed at a peak of the secondary voltage and a maximum surge current,  $I_{surge(max)}$ ,
- A fuse is generally used because of the surge current that initially occurs when power is first turned on.
- The fuse rating is determined by power calculation.
- in an ideal transformer  $P_{in} = P_{out}$

$$I_{pri} = \frac{P_{in}}{220\text{V}}$$


- The fuse rating should be at least 20% larger than the calculated value of  $I_{pri}$ .

٢٤

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits
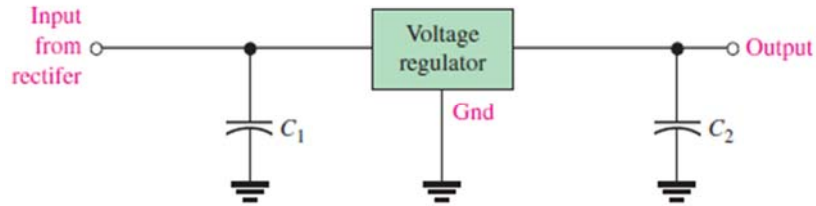
# Voltage Regulators


- Three-terminal regulators designed for fixed output voltages require only external capacitors to complete the regulation portion of the power supply



٢٥


Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

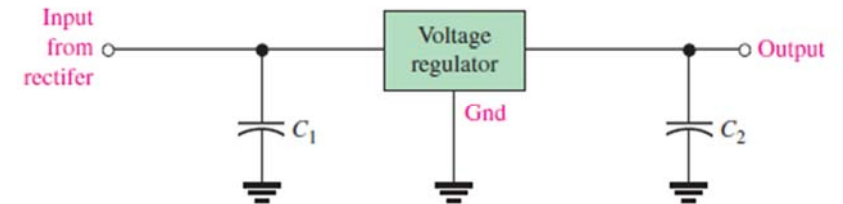- Filtering is accomplished by a large-value capacitor between the input voltage and ground.
- An output capacitor 0.1 uf to 1uf (typically ) is connected from the output to ground to improve the transient response.



٢٦

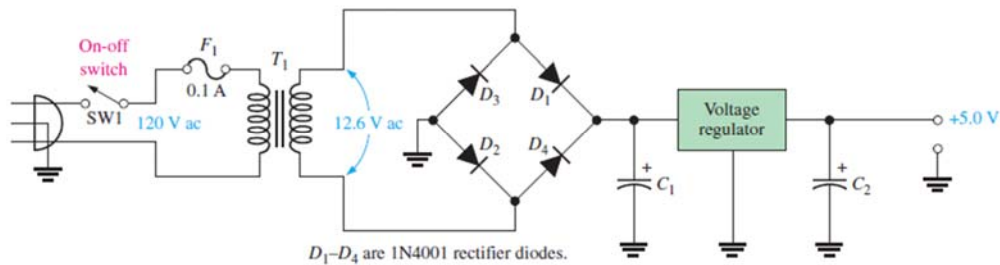Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits



٢٧

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

- **Percent Regulation**
- The regulation expressed as a percentage, It can be in terms of
  - input (line) regulation or
  - load regulation.
- **Line Regulation:** a ratio of a change in output voltage for a corresponding change in the input voltage expressed as a percentage

$$\text{Line regulation} = \left( \frac{\Delta V_{\text{OUT}}}{\Delta V_{\text{IN}}} \right) 100\%$$

٢٨

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

- **Load Regulation:** how much change occurs in the output voltage over a certain range of load current values,
- from minimum current (no load, NL) to maximum current (full load, FL).


$$\text{Load regulation} = \left( \frac{V_{NL} - V_{FL}}{V_{FL}} \right) 100\%$$

٣٩

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits
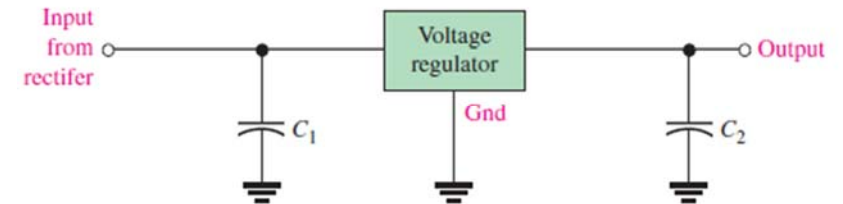
## Example 06

- A certain 7805 regulator has a measured no-load output voltage of 5.18 V and a fullload output of 5.15 V. What is the load regulation expressed as a percentage



٣٠

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

- A certain 7805 regulator has a measured no-load output voltage of 5.18 V and a fullload output of 5.15 V. What is the load regulation expressed as a percentage


$$\text{Load regulation} = \left( \frac{V_{NL} - V_{FL}}{V_{FL}} \right) 100\% = \left( \frac{5.18 \text{ V} - 5.15 \text{ V}}{5.15 \text{ V}} \right) 100\% = 0.58\%$$

٣١

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits
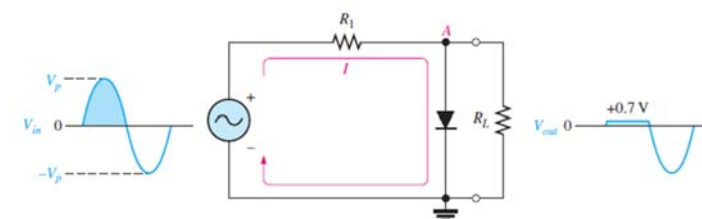
## Diode limiters

- Figure shows a diode positive **limiter** (also called **clipper**) that limits or clips the positive part of the input voltage.
- As the input voltage goes positive, the diode becomes forward biased and conducts current.
- Point A is limited to +0.7 V when the input voltage exceeds this value




٣٢

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits



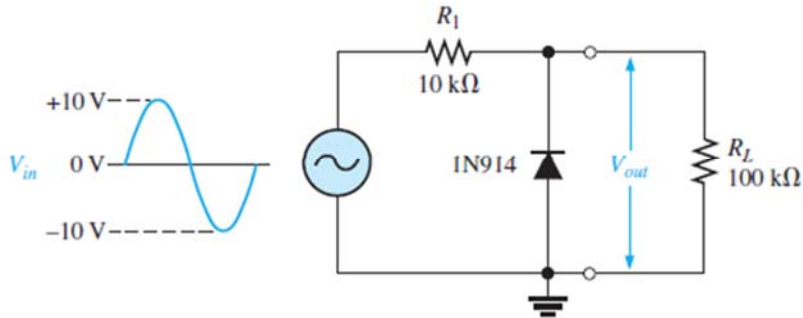
# Example

- What would you expect to see displayed on an oscilloscope connected across  $R_L$  in the limiter shown in Figure



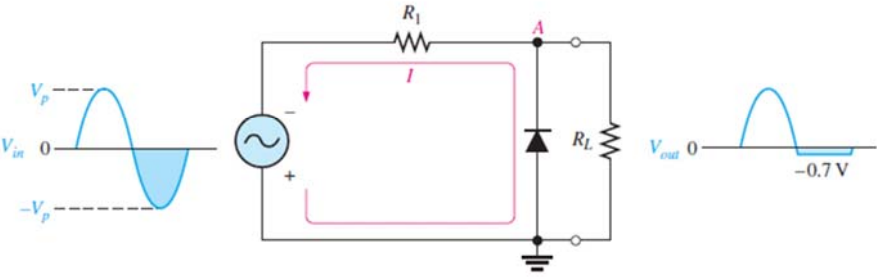
- When the input voltage goes back below 0.7 V, the diode is reverse-biased and appears as an open.




$$V_{out} = \left( \frac{R_L}{R_1 + R_L} \right) V_{in}$$


• If  $R_1$  is small compared to  $R_L$ , then  $V_{out} = V_{in}$
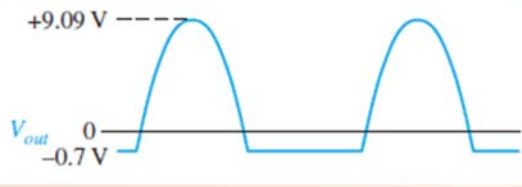
$$V_{p(out)} = \left( \frac{R_L}{R_1 + R_L} \right) V_{p(in)} = \left( \frac{100 \text{ k}\Omega}{110 \text{ k}\Omega} \right) 10 \text{ V} = 9.09 \text{ V}$$



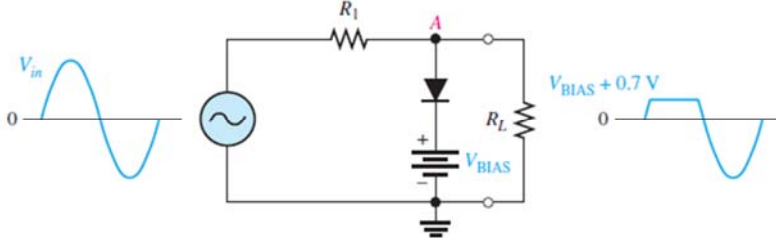- **Biased Limiters**
- The voltage at point A must equal  $V_{BIAS} + 0.7 \text{ V}$  before the diode will become forward-biased and conduct.




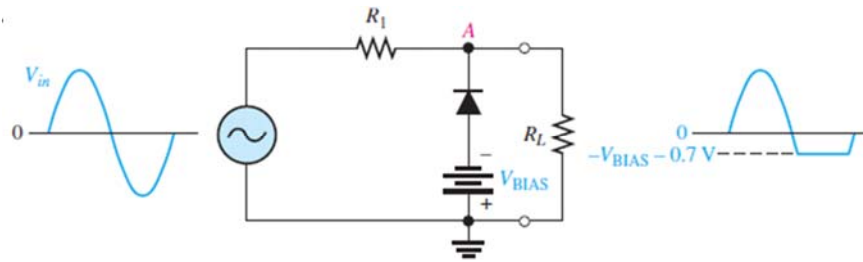

٣٧

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

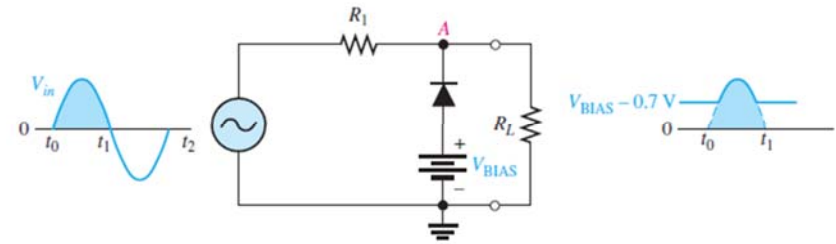
- the positive limiter can be modified to limit the output voltage to the portion of the input voltage waveform above



٣٨

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

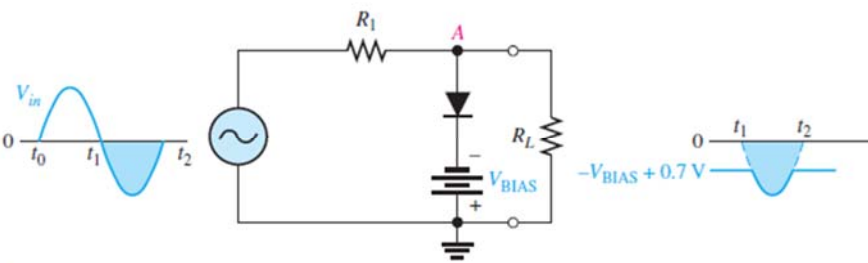- the negative limiter can be modified to limit the output voltage to the portion of the input voltage waveform




٣٩

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

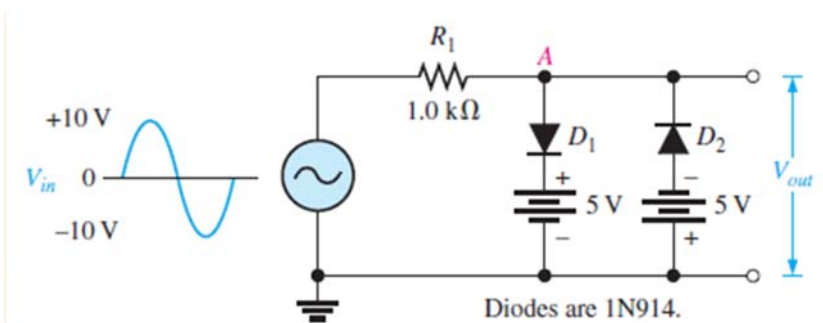
## Example

- shows a circuit combining a positive limiter with a negative limiter. Determine the output voltage waveform




٤٠

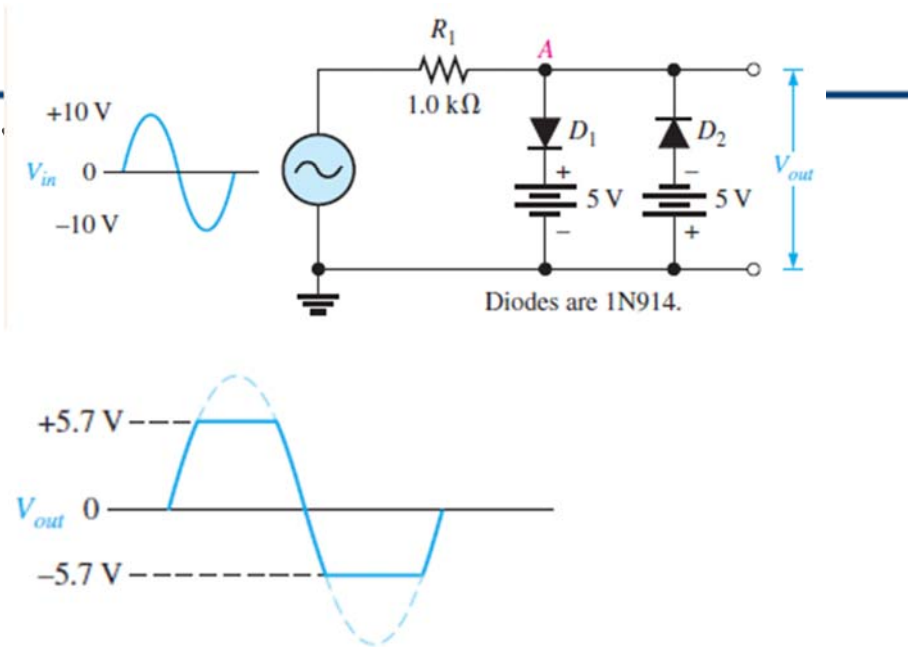Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits




: Circuits


### • Voltage-Divider Bias

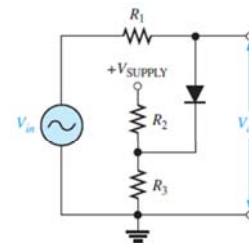

(a) Positive limiter

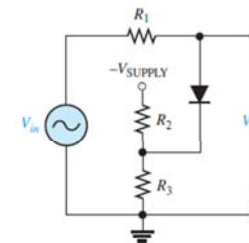

(b) Negative limiter

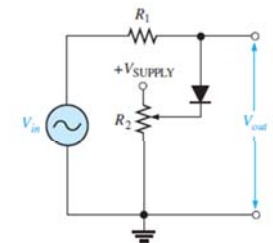

(c) Variable positive limiter


$$V_{BIAS} = \left( \frac{R_3}{R_2 + R_3} \right) V_{SUPPLY}$$

٤٢

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits
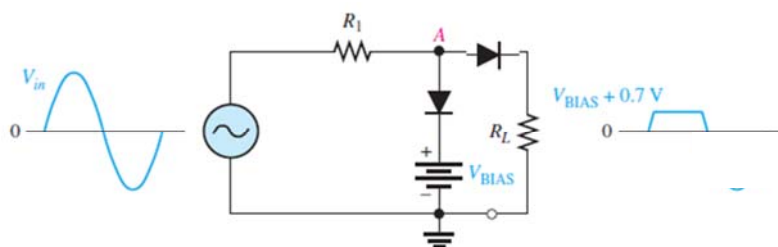
### • A Limiter Application


- almost all digital circuits should not have an input level that exceeds the power supply voltage. An input of a few volts more than this could damage the circuit.
- To prevent the input from exceeding a specific level, you may see a diode limiter across the input signal path in many digital circuits.



٤٣
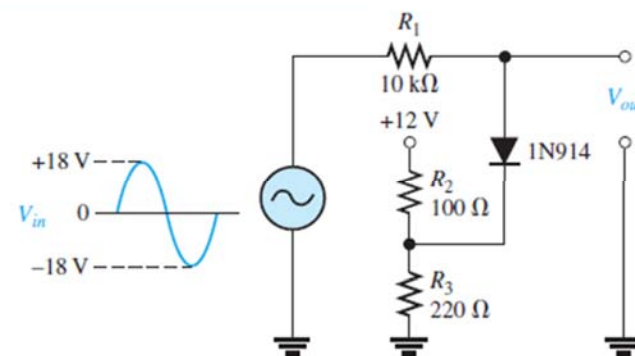
## Example

- Describe the output voltage waveform for the diode limiter in Figure




٤٤


Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

# Voltage multiplier

- Half-wave voltage doubler

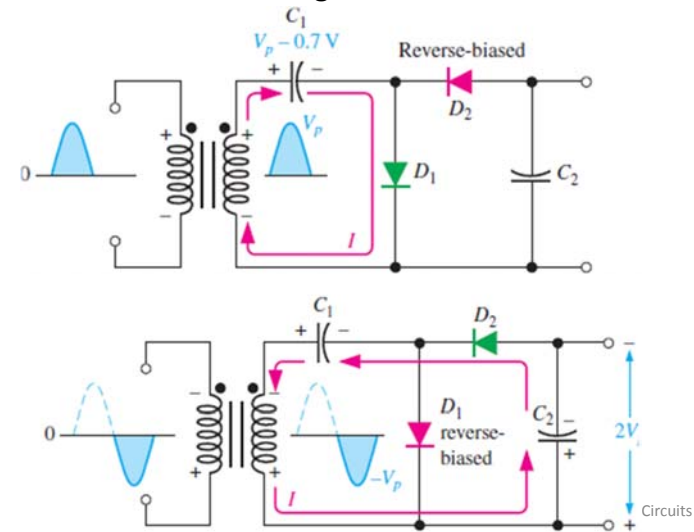

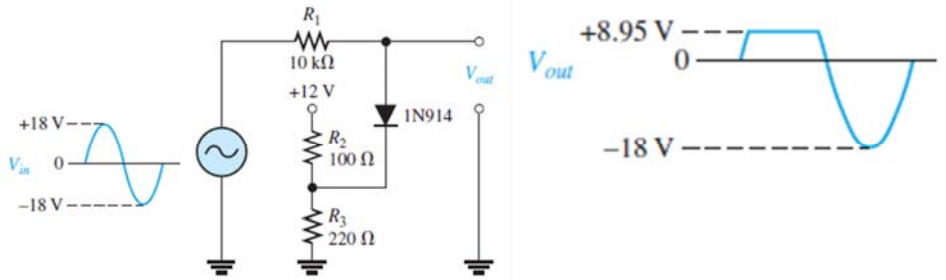
$$V_{BIAS} = \left( \frac{R_3}{R_2 + R_3} \right) V_{SUPPLY} = \left( \frac{220 \Omega}{100 \Omega + 220 \Omega} \right) 12 \text{ V} = 8.25 \text{ V}$$



٤٥

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits


- Full-Wave Voltage Doubler

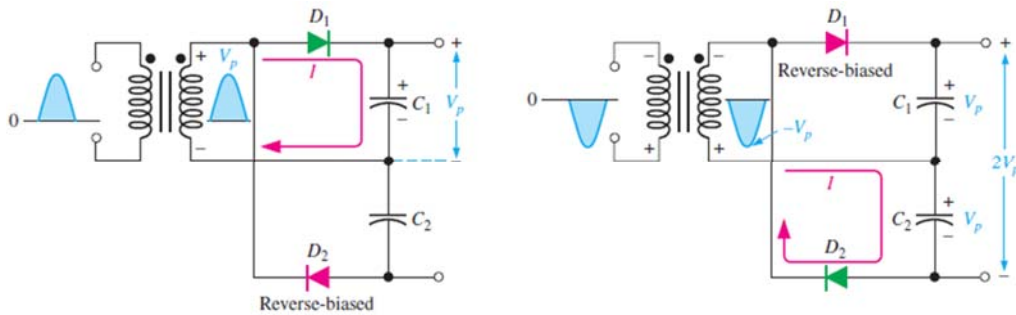

٤٧

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits


- Voltage Tripler

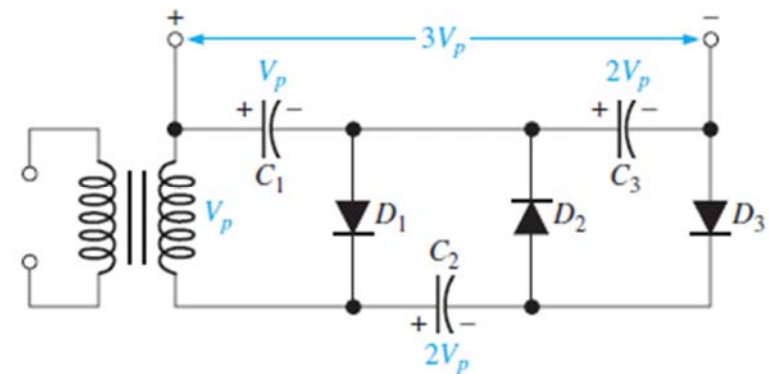

٤٨

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

- Voltage Quadrupler

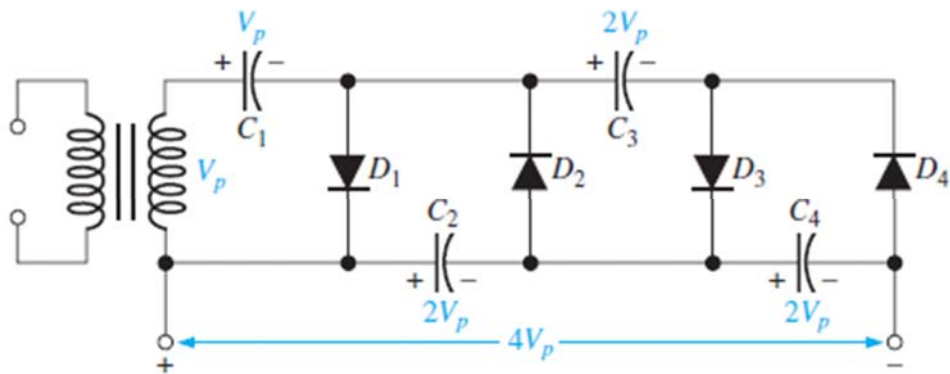

Thanks,..  
See you next week (ISA),...