



Lecture (06) Bipolar Junction Transistor



By:

Dr. Ahmed ElShafee

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

Agenda


- BJT structure
- BJT operation
- BJT characteristics

٢

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

BJT structure


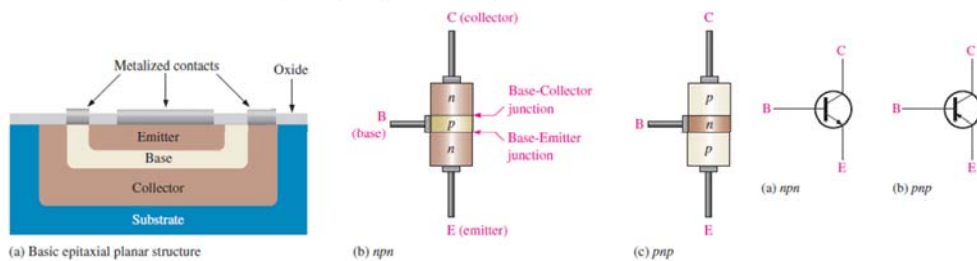
- The **BJT** is constructed with three doped semiconductor regions
- One type consists of two *n* regions separated by a *p* region (*npn*), and the other type consists of two *p* regions separated by an *n* region (*pnp*).
- The term **bipolar** refers to the use of both holes and electrons



- In order for a BJT to operate properly as an amplifier, the two *pn* junctions must be correctly biased with external dc voltages.
- In this section, we mainly use the *npn* transistor for illustration.
- The operation of the *pnp* is the same as for the *npn* except that the roles of the electrons and holes, the bias voltage polarities, and the current directions are all reversed.


٤

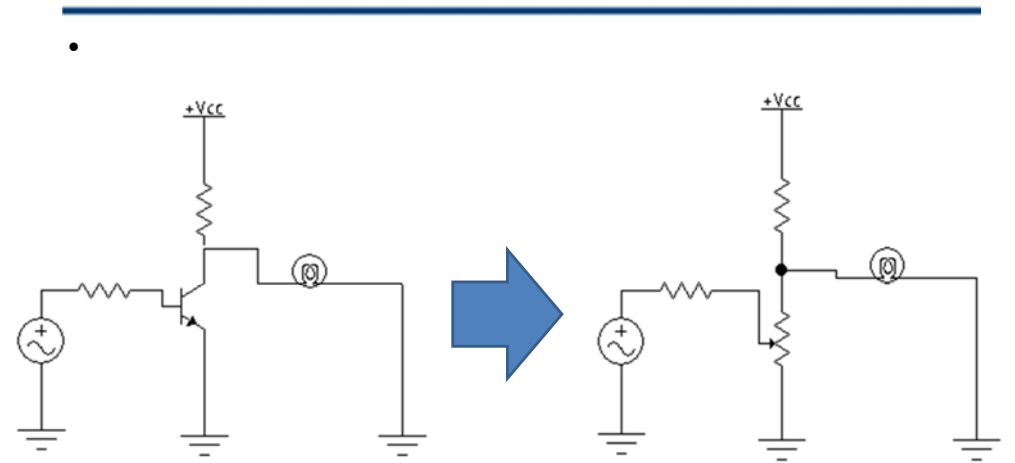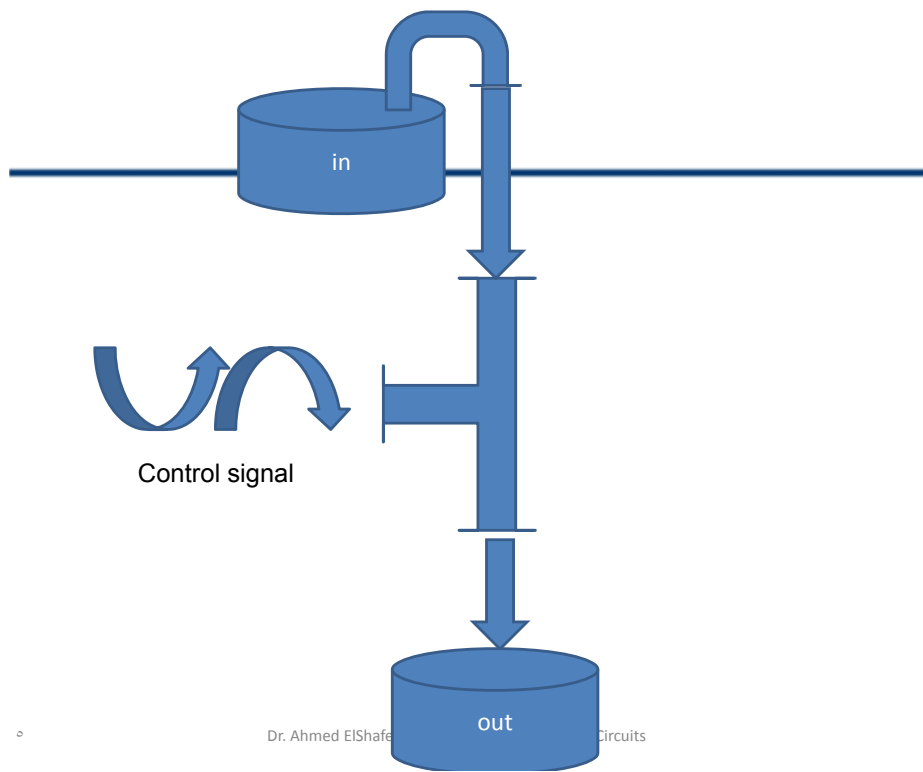Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits




Biasing

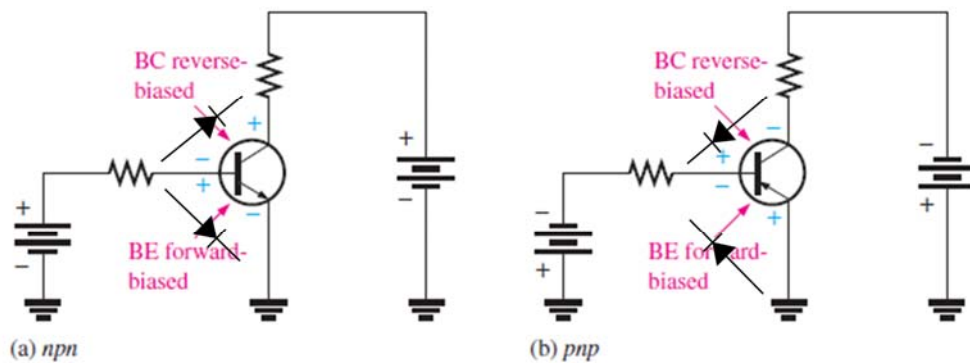base-emitter (BE) junction is forward-biased
 base-collector (BC) junction is reverse-biased
 This condition is called *forward-reverse bias*




BJT Operation

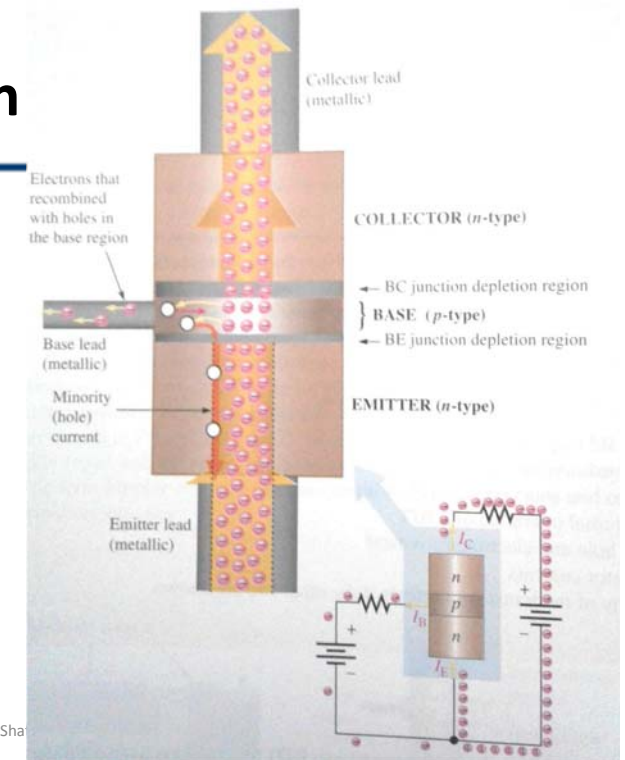- CE battery +ve terminal attract electrons from the collector N-region.
- Collector N-region compensate electrons depletion region, which become more and more wider.




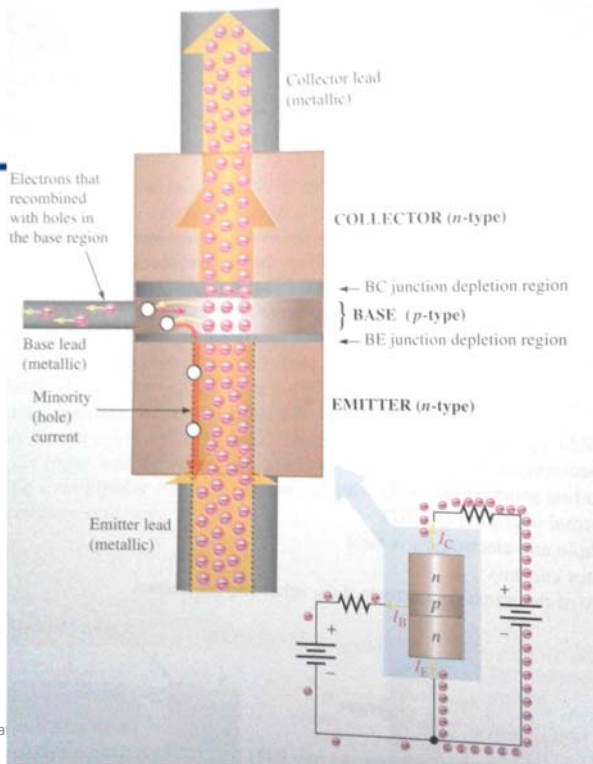- BE battery +ve terminal start attracting the small amounts of electrons (minority carrier) from base p-type region, then starts attracting electrons from depletion region, which become thinner and thinner, then electrons start to flow from Emitter N-region




Dr. Ahmed ElSha

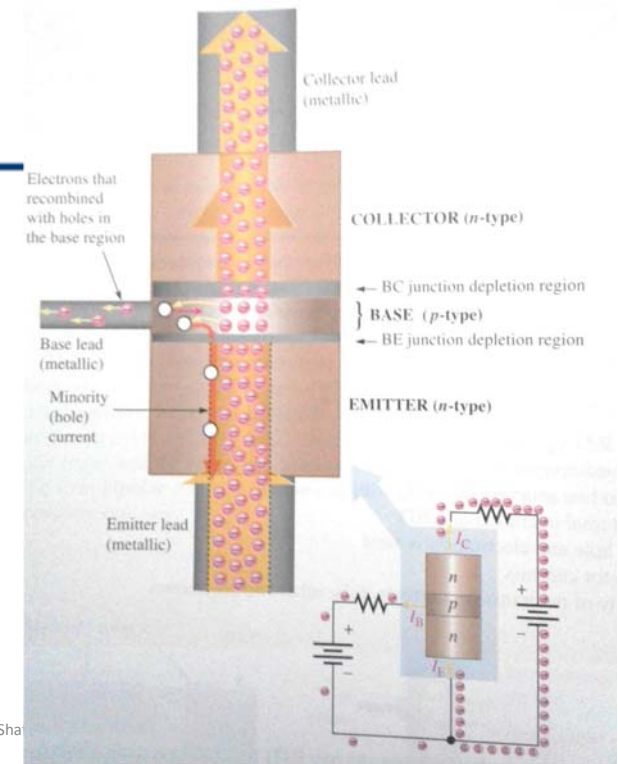- Now base p-type now how a new electrons being transferred from CE battery -ve terminal through emitter n-type.
- Electrons stream divided between
 - Directly to BE battery +ve terminal
 - CE battery +ve terminal through emitter n-type



Dr. Ahmed ElSha

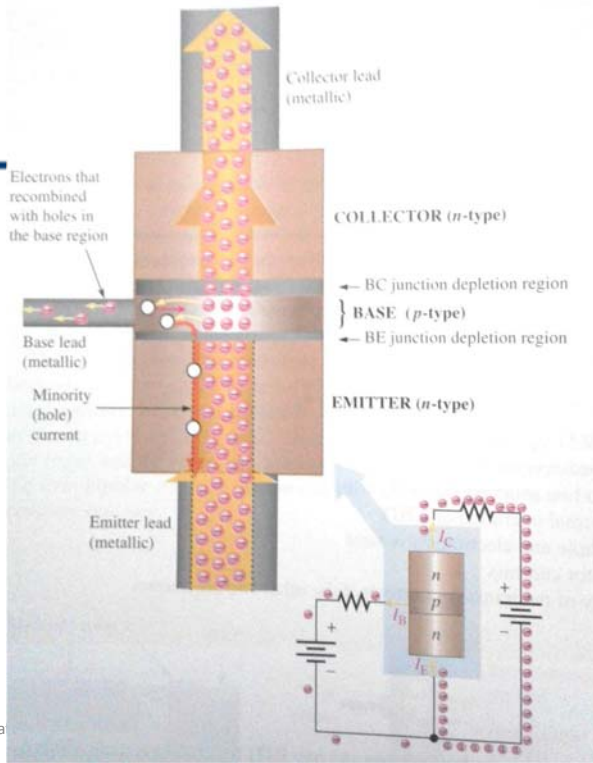
- The more +ve potential applied to base from BE battery +ve terminal, a more electrons being transferred from CE battery -ve terminal, through emitter N-region, a more electrons in turn flow to CE battery +ve terminal.



Dr. Ahmed ElSha

Transistor Currents


$$I_E = I_B + I_C$$

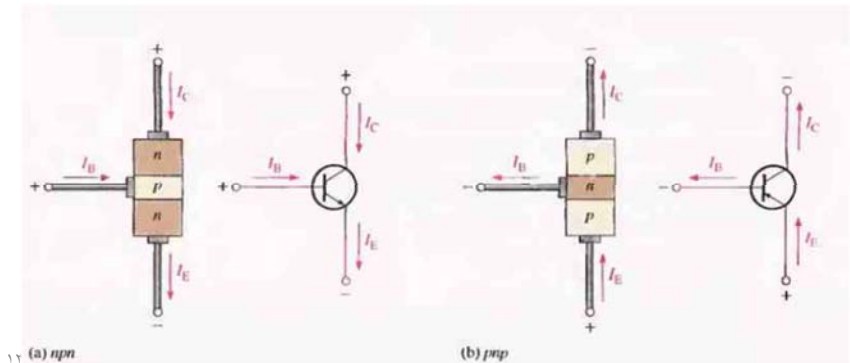


(a) npn

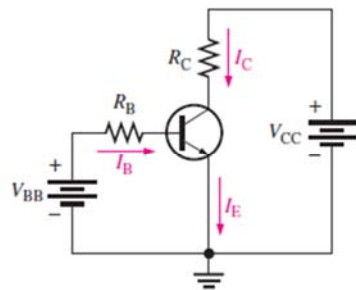(b) pnp

- V_{BB} forward-biases the base-emitter junction,
- V_{CC} reverse-biases the base-collector junction.
- In practice both V_{CC} , and V_{BB} derived from single battery with necessarily voltage divider on base terminal



(a) npn

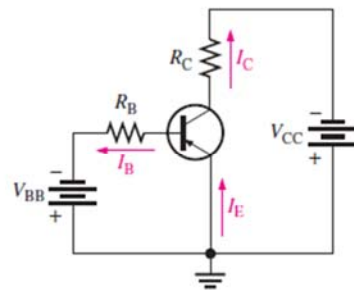

(b) pnp

- **DC Beta (β_{DC}) and DC Alpha (α_{DC})**
- DC gain called (β_{DC}) is the ratio between I_C/I_B , which called h_{FE} in data sheet, range from less than 20 to 200 or higher.

$$\beta_{DC} = \frac{I_C}{I_B}$$


$$h_{FE} = \beta_{DC}$$

- (α_{DC}) is the ratio between I_C/I_E , in range from 0.95 to 0.99 or greater

$$\alpha_{DC} = \frac{I_C}{I_E}$$

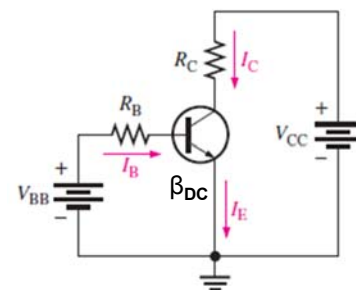Example

Determine the dc current gain β_{DC} and the emitter current I_E for a transistor where $I_B = 50 \mu A$ and $I_C = 3.65 mA$.




Example


Determine the dc current gain β_{DC} and the emitter current I_E for a transistor where $I_B = 50 \mu A$ and $I_C = 3.65 mA$.

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{3.65 \text{ mA}}{50 \mu A} = 73$$
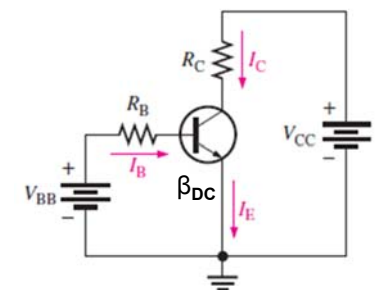
$$I_E = I_C + I_B = 3.65 \text{ mA} + 50 \mu A = 3.70 \text{ mA}$$



Transistor DC Model

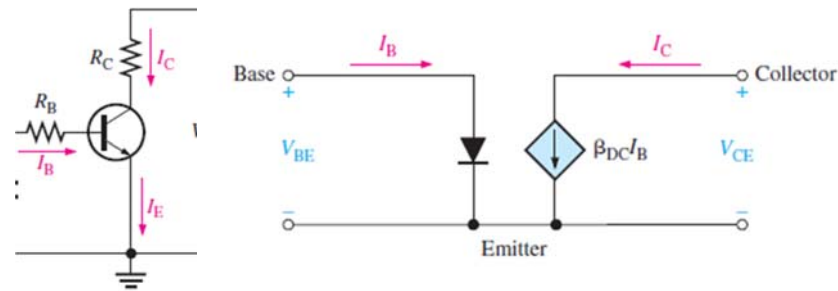

17

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

BJT Circuit Analysis


- V_{BB} , forward-biases the base-emitter junction, and the collector-bias voltage source, V_{CC} , reverse-biases the base-collector junction.

$$V_{BE} \cong 0.7 \text{ V}$$

- Kirchhoff's voltage law @1

$$V_{R_B} = V_{BB} - V_{BE}$$

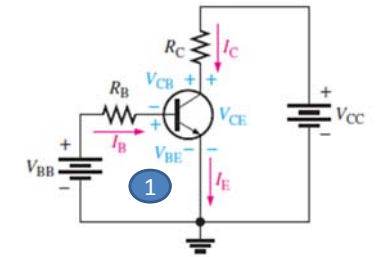I_B : dc base current
 I_E : dc emitter current
 I_C : dc collector current
 V_{BE} : dc voltage at base with respect to emitter
 V_{CB} : dc voltage at collector with respect to base
 V_{CE} : dc voltage at collector with respect to emitter



18

Dr. Ahmed ElShafee, ACU

- Ohm's law

$$V_{R_B} = I_B R_B$$

- Substitute

$$I_B R_B = V_{BB} - V_{BE}$$


- Finally

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

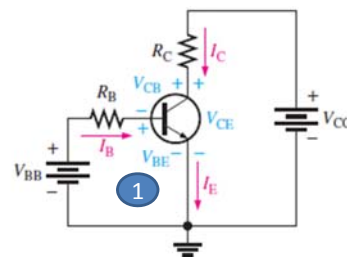I_B : dc base current
 I_E : dc emitter current
 I_C : dc collector current
 V_{BE} : dc voltage at base with respect to emitter
 V_{CB} : dc voltage at collector with respect to base
 V_{CE} : dc voltage at collector with respect to emitter



19

Dr. Ahmed ElShafee, ACU

- KVL @ 2

$$-V_{CC} + V_{R_C} + V_{CE} = 0$$

$$V_{CE} = V_{CC} - V_{R_C}$$

- Ohm's

$$V_{R_C} = I_C R_C$$


- Substitute

$$V_{CE} = V_{CC} - I_C R_C$$

- But

$$I_C = \beta_{DC} I_B$$

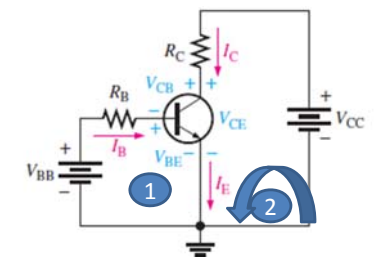I_B : dc base current
 I_E : dc emitter current
 I_C : dc collector current
 V_{BE} : dc voltage at base with respect to emitter
 V_{CB} : dc voltage at collector with respect to base
 V_{CE} : dc voltage at collector with respect to emitter




20

Dr. Ahmed ElShafee, ACU

- Consider the transistor itself

$$V_{CE} = V_{CB} + V_{BE}$$

$$V_{CB} = V_{CE} - V_{BE}$$

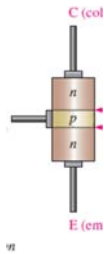


٢١

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

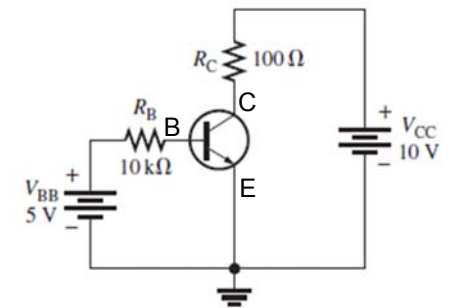Example 02

Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the circuit of Figure 4-9. The transistor has a $\beta_{DC} = 150$.



٢٢

Dr. Ahmed ElShafee, ACU : Fall 201

Example 02

Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the circuit of Figure 4-9. The transistor has a $\beta_{DC} = 150$.


Answer

$$V_{BE} \cong 0.7 \text{ V.}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 430 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (150)(430 \mu\text{A}) = 64.5 \text{ mA}$$
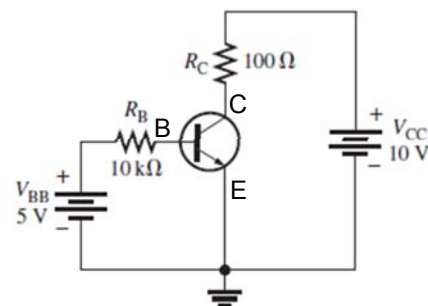
$$I_E = I_C + I_B = 64.5 \text{ mA} + 430 \mu\text{A} = 64.9 \text{ mA}$$



٢٣

Dr. Ahmed ElShafee, ACU : Fall 201


Example 02

Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the circuit of Figure 4-9. The transistor has a $\beta_{DC} = 150$.

Answer

$$V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (64.5 \text{ mA})(100 \Omega) = 10 \text{ V} - 6.45 \text{ V} = 3.55 \text{ V}$$
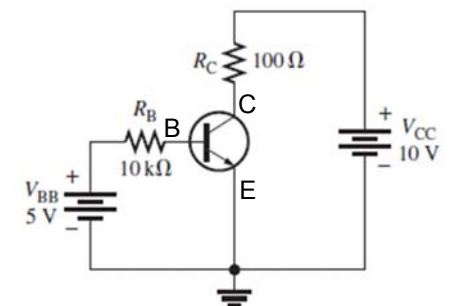
$$V_{CB} = V_{CE} - V_{BE} = 3.55 \text{ V} - 0.7 \text{ V} = 2.85 \text{ V}$$






٢٤

Dr. Ahmed ElShafee, ACU : Fall 201

BJT Characteristic

Collector Characteristic Curves

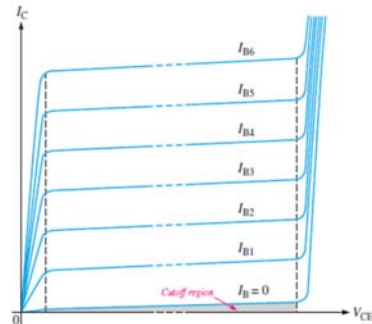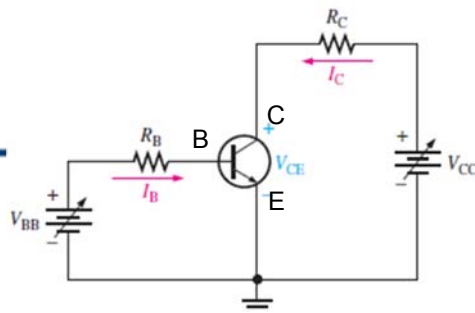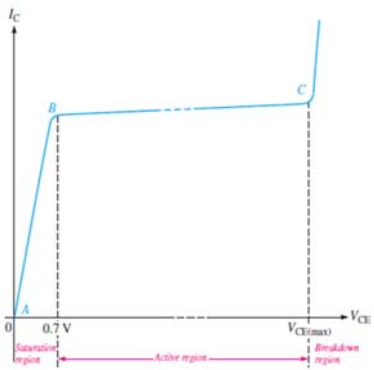


(c) Family of I_C versus V_{CE} curves for several values of I_B ($I_{B1} < I_{B2} < I_{B3}$, etc.)


Applying fixed V_{BB} , increasing V_{CC}

Saturation

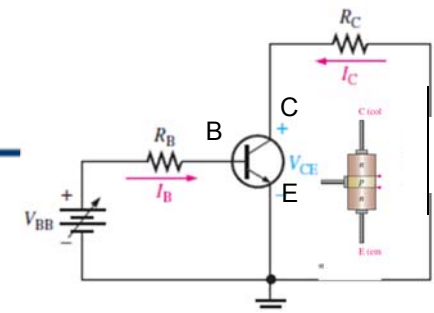- Assume that V_{BB} is set to produce a certain value of I_B and V_{CC} is zero
- both the BE junction and the BC junction are forward-biased because the base is at approximately 0.7 V while the emitter and the collector are at 0 V.
- I_C is zero.
- Saturation** is both junctions are forward-biased





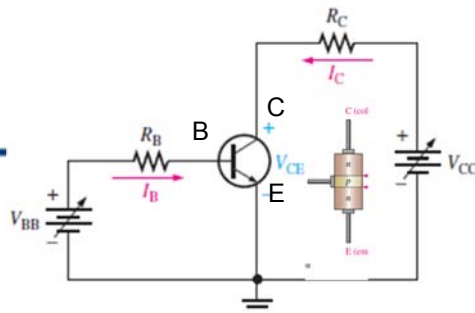- As V_{CC} is increased, V_{CE} increases as the collector current increases, because V_{CE} remains less than 0.7 V due to the forward-biased base-collector junction.





Active

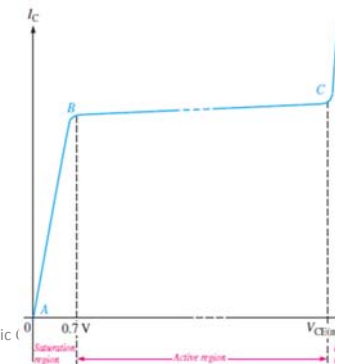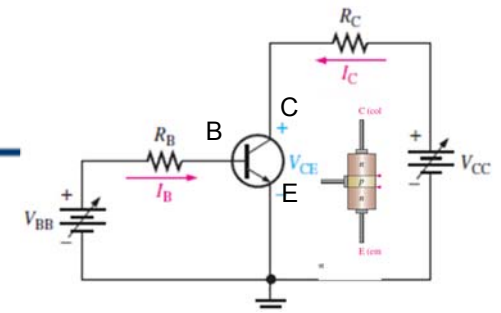- when V_{CE} exceeds 0.7 V, the base-collector junction becomes reverse-biased
- BJT become **active**, or **linear**, region
- I_C levels off and remains essentially constant for a given value of I_B as V_{CE} continues to increase



breakdown

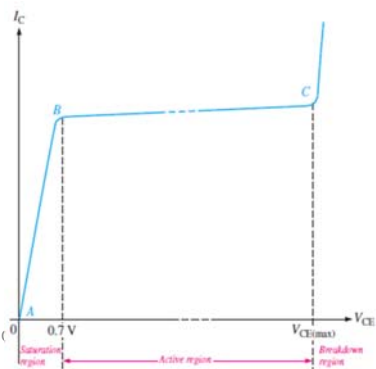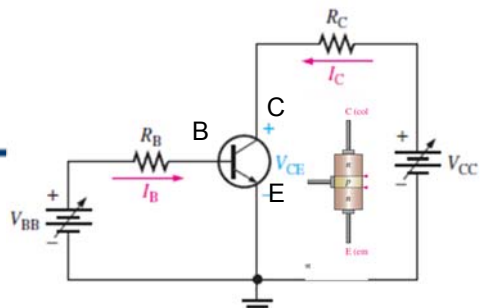
- When V_{CE} reaches a sufficiently high voltage, the reverse-biased base-collector junction goes into **breakdown**; and the collector current increases rapidly as indicated by the part of the curve to the right of point C



Dr. Ahmed Elshafee, ACU : Fall 2015, Electronic C

cutoff

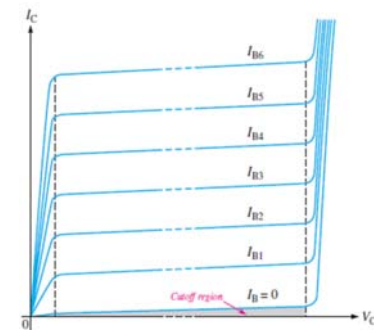- When $I_B = 0$, the transistor is in the **cutoff** region although there is a very small collector leakage current as indicated.
- Cutoff** is the nonconducting state of a transistor.




Dr. Ahmed Elshafee, ACU : Fall 2015, Electronic C

(c) Family of I_C versus V_{CE} curves for several values of I_B ($I_{B1} < I_{B2} < I_{B3}$, etc.)

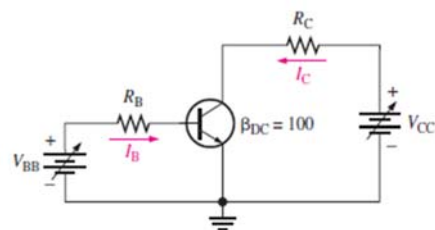
Example 03

Sketch an ideal family of collector curves for the circuit in Figure 4-11 for $I_B = 5 \mu A$ to $25 \mu A$ in $5 \mu A$ increments. Assume $\beta_{DC} = 100$ and that V_{CE} does not exceed breakdown.




$$I_C = \beta_{DC} I_B$$

I_B	I_C
$5 \mu A$	0.5 mA
$10 \mu A$	1.0 mA
$15 \mu A$	1.5 mA
$20 \mu A$	2.0 mA
$25 \mu A$	2.5 mA

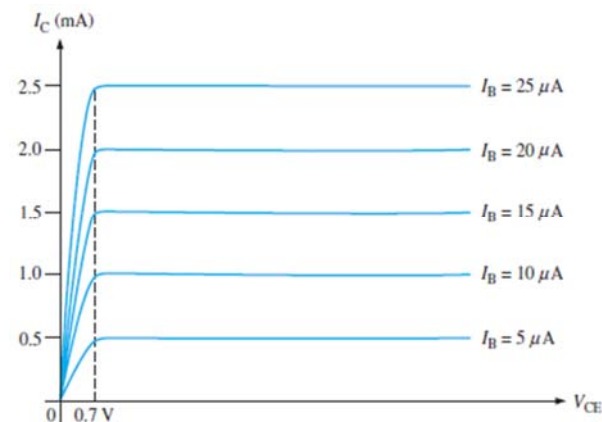


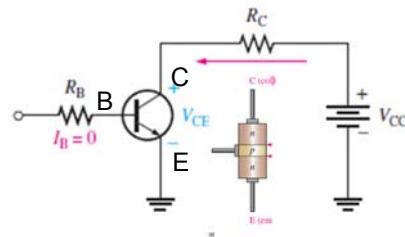Applying fixed V_{CC} , increasing V_{BB}



Cutoff

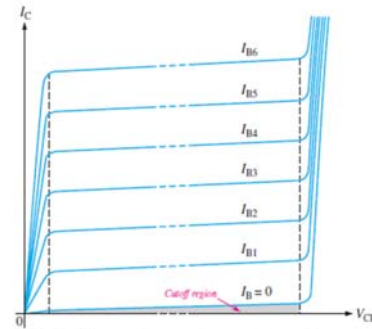- when $I_B = 0$, the transistor is in the cutoff region
- I_{CEO} is extremely small, it will usually be neglected in circuit analysis
- $V_{CE} = V_{CC}$
- CEO represents collector-to-emitter with the base open.



(c) Family of I_C versus V_{CE} curves for several values of I_B ($I_{B1} < I_{B2} < I_{B3}$, etc.)

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Ci

Applying fixed V_{CC} , increasing V_{BB}

Saturation



- When the base-emitter junction becomes forward-biased and the base current is increased, the collector current also increases

$$(I_C = \beta I_B)$$

- V_{CE} decreases as a result of more drop across the collector resistor

$$(V_{CE} = V_{CC} - I_C R_C).$$

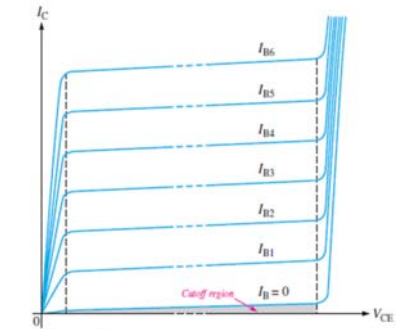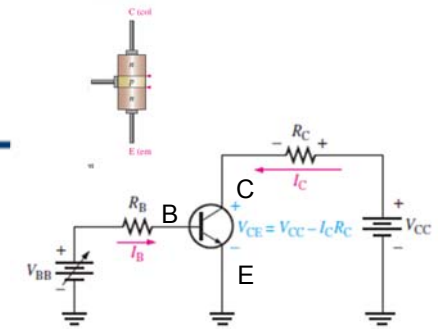- V_{CE} reaches its saturation value, $V_{CE(sat)}$,
- base-collector junction becomes forward-biased and
- At the point of saturation, the $(I_C = \beta I_B)$ is no longer valid.




(c) Family of I_C versus V_{CE} curves for several values of I_B ($I_{B1} < I_{B2} < I_{B3}$, etc.)

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Ci

DC Load Line


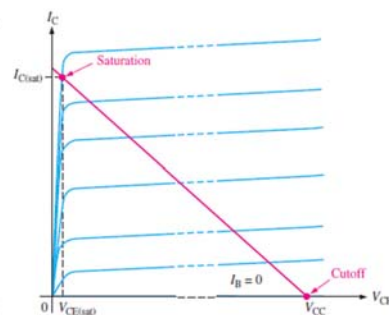
- dc load line drawn on a family of curves connecting the cutoff point and the saturation point.
- The bottom of the load line is at ideal cutoff where $I_C = 0$ and $V_{CE} = V_{CC}$.



Dr. Ahmed ElShafee, ACU : Fall 2015, Elec

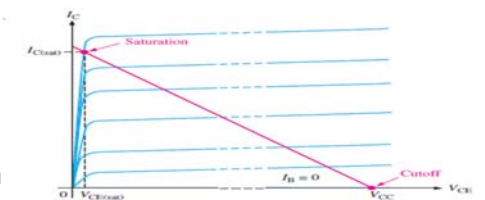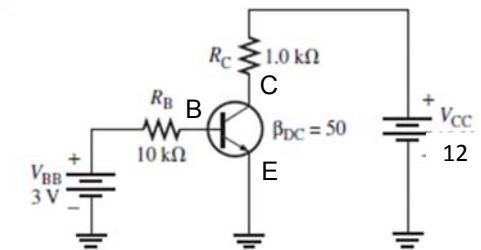Example 04

Determine whether or not the transistor in Figure 4-16 is in saturation. Assume $V_{CE(sat)} = 0.2 \text{ V}$.



Dr. Ahmed ElShafee, ACU : Fal



Example 04

Determine whether or not the transistor in Figure 4–16 is in saturation. Assume $V_{CE(sat)} = 0.2 \text{ V}$.

$$I_B = \frac{3 - 0.7}{10000} = 0.23 \text{ mA}$$

$$I_C = \beta I_B = 50 \times 0.23 = 11.5 \text{ mA}$$
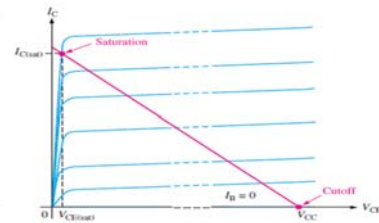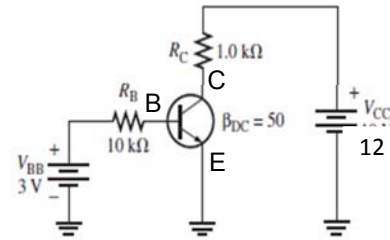
$$V_{CE} = 12 - (11.5 \times 1) = 0.5 \text{ Volt}$$




V_{CE} doesn't reach V_{CEsat} then **transistor is in active mode**,

٣٧

Dr. Ahmed ElShafee, ACU : Fall 2015, Electr

More About β_{DC}

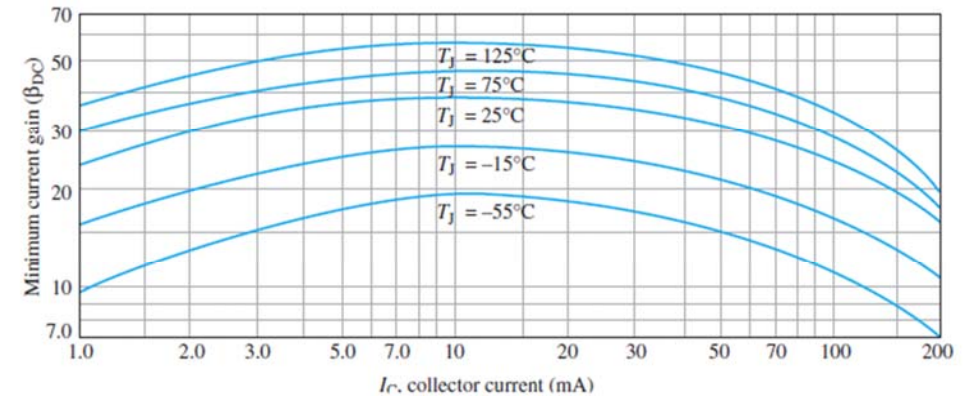- β_{DC} is not truly constant but varies with both collector current and with temperature



Thanks,..
See you next week (ISA),...