



Lecture (07) Bipolar Junction Transistor (2)

By:


Dr. Ahmed ElShafee

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

Maximum Transistor Ratings

- The product of V_{CE} and I_C must not exceed the maximum power dissipation
- Both V_{CE} and I_C cannot be maximum at the same time.
- If V_{CE} is maximum, I_C can be calculated as
$$I_C = \frac{P_{D(max)}}{V_{CE}}$$
- If I_C is maximum, V_{CE} can be calculated by
$$V_{CE} = \frac{P_{D(max)}}{I_C}$$
- Assume $P_{D(max)}$ is 500 mW, $V_{CE(max)}$ is 20 V, and $I_C(max)$ is 50 mA

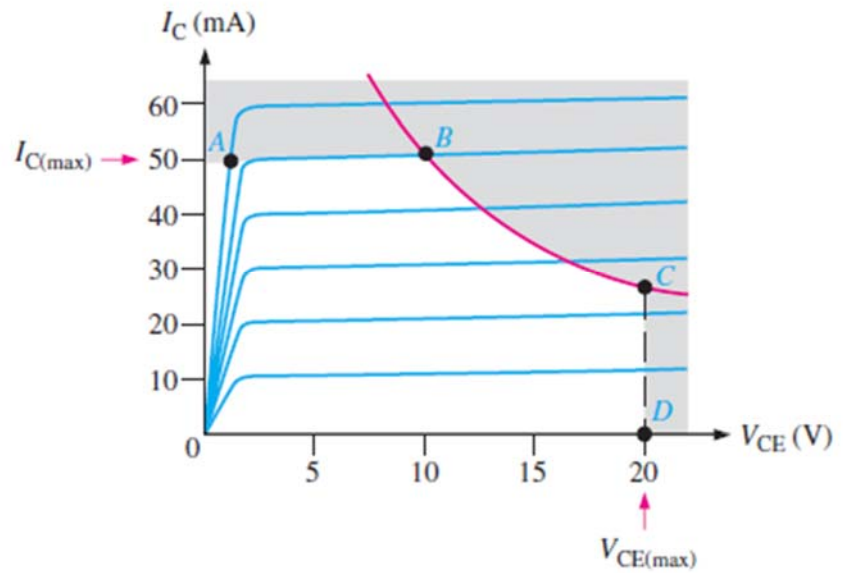- transistor cannot be operated in the shaded portion of the graph.
- $I_C(\max)$ is the limiting rating between points *A* and *B*, $P_D(\max)$ is the limiting rating between points *B* and *C*, and $V_{CE}(\max)$ is the limiting rating between points *C* and *D*.



$P_{D(\max)}$	V_{CE}	I_C
500 mW	5 V	100 mA
500 mW	10 V	50 mA
500 mW	15 V	33 mA
500 mW	20 V	25 mA

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

Example 01

A certain transistor is to be operated with $V_{CE} = 6$ V. If its maximum power rating is 250 mW, what is the most collector current that it can handle?

Example 01

A certain transistor is to be operated with $V_{CE} = 6 \text{ V}$. If its maximum power rating is 250 mW, what is the most collector current that it can handle?


$$I_C = \frac{P_{D(\max)}}{V_{CE}} = \frac{250 \text{ mW}}{6 \text{ V}} = 41.7 \text{ mA}$$

o

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

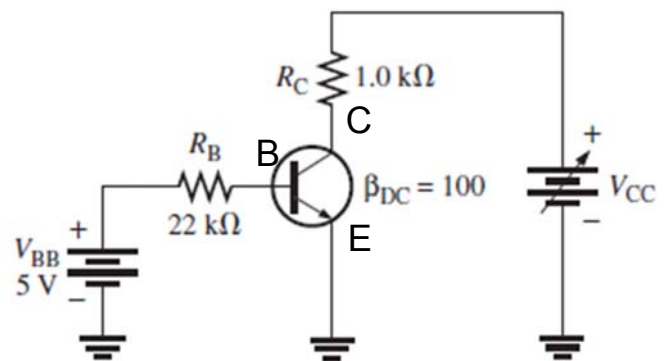Example 02

The transistor in Figure 4–19 has the following maximum ratings: $P_{D(\max)} = 800 \text{ mW}$, $V_{CE(\max)} = 15 \text{ V}$, and $I_{C(\max)} = 100 \text{ mA}$. Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating. Which rating would be exceeded first?



7

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

Example 02


The transistor in Figure 4–19 has the following maximum ratings: $P_{D(\max)} = 800 \text{ mW}$, $V_{CE(\max)} = 15 \text{ V}$, and $I_{C(\max)} = 100 \text{ mA}$. Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating. Which rating would be exceeded first?

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{22 \text{ k}\Omega} = 195 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (100)(195 \mu\text{A}) = 19.5 \text{ mA}$$

I_C is much less than $I_{C(\max)}$ and ideally will not change with V_{CC} . It is determined only by I_B and β_{DC} .
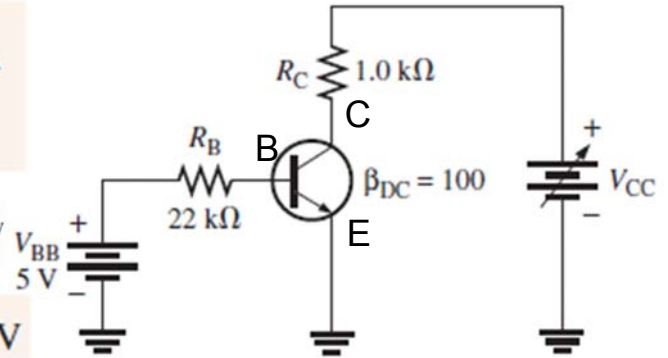
$$V_{R_C} = I_C R_C = (19.5 \text{ mA})(1.0 \text{ k}\Omega) = 19.5 \text{ V}$$



- V_{CC} max occurs when V_{CE} max, calculated using KVL


$$V_{CC(\max)} = V_{CE(\max)} + V_{R_C} = 15 \text{ V} + 19.5 \text{ V} = 34.5 \text{ V}$$

Example 02

The transistor in Figure 4–19 has the following maximum ratings: $P_{D(\max)} = 800 \text{ mW}$, $V_{CE(\max)} = 15 \text{ V}$, and $I_{C(\max)} = 100 \text{ mA}$. Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating. Which rating would be exceeded first?

- Now calculating PD @ $V_{CE(\max)}$
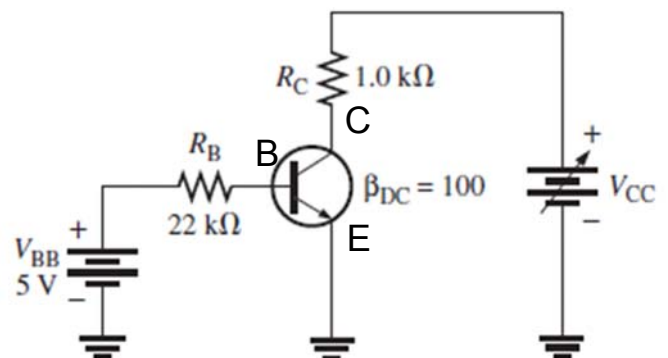
$$P_D = V_{CE(\max)} I_C = (15 \text{ V})(19.5 \text{ mA}) = 293 \text{ mW}$$



Since $P_{D(\max)}$ is 800 mW, it is *not* exceeded when $V_{CC} = 34.5 \text{ V}$. So, $V_{CE(\max)} = 15 \text{ V}$ is the limiting rating in this case.

Derating $P_{D(max)}$

- $P_{D(max)}$ is usually specified at 25°C. For higher temperatures, $P_{D(max)}$ is less.
- example, a derating factor of 2 mW/°C indicates that the maximum power dissipation is reduced 2 mW for each degree Celsius increase in temperature.

Example 03

A certain transistor has a $P_{D(max)}$ of 1 W at 25°C. The derating factor is 5 mW/°C. What is the $P_{D(max)}$ at a temperature of 70°C?

Example 03

A certain transistor has a $P_{D(max)}$ of 1 W at 25°C. The derating factor is 5 mW/°C. What is the $P_{D(max)}$ at a temperature of 70°C?

The change (reduction) in $P_{D(max)}$ is

$$\Delta P_{D(max)} = (5 \text{ mW/}^\circ\text{C})(70^\circ\text{C} - 25^\circ\text{C}) = (5 \text{ mW/}^\circ\text{C})(45^\circ\text{C}) = 225 \text{ mW}$$

Therefore, the $P_{D(max)}$ at 70°C is


$$1 \text{ W} - 225 \text{ mW} = 775 \text{ mW}$$

11


Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

BJT Datasheet

- 2N3904
npn transistor




2N3904




TO-92

MMBT3904

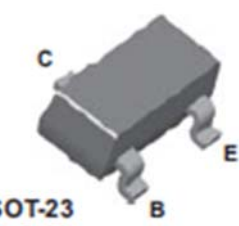

SOT-23
Mark: 1A

PZT3904

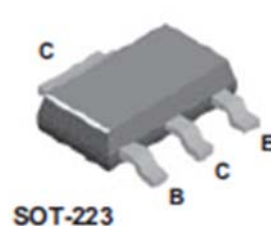

SOT-223

NPN General Purpose Amplifier

This device is designed as a general purpose amplifier and switch. The useful dynamic range extends to 100 mA as a switch and to 100 MHz as an amplifier.

Absolute Maximum Ratings* T_a = 25°C unless otherwise noted

Symbol	Parameter	Value	Units
V _{CEO}	Collector-Emitter Voltage	40	V
V _{CBO}	Collector-Base Voltage	60	V
V _{EB0}	Emitter-Base Voltage	6.0	V
I _C	Collector Current - Continuous	200	mA
T _J , T _{stg}	Operating and Storage Junction Temperature Range	-55 to +150	°C

12

Thermal Characteristics

$T_A = 25^\circ\text{C}$ unless otherwise noted

Symbol	Characteristic	Max			Units
		2N3904	*MMBT3904	**PZT3904	
P_D	Total Device Dissipation Derate above 25°C	625 5.0	350 2.8	1,000 8.0	mW mW/ $^\circ\text{C}$
$R_{\theta JC}$	Thermal Resistance, Junction to Case	22.2			$^\circ\text{C}/\text{W}$
$R_{\theta JA}$	Thermal Resistance, Junction to Ambient	200	357	125	$^\circ\text{C}/\text{W}$

*Device mounted on FR-4 PCB 1.6" X 1.6" X 0.06"

**Device mounted on FR-4 PCB 36 mm X 18 mm X 1.5 mm; mounting pad for the collector lead min. 6 cm^2 .

۱۳

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

Electrical Characteristics

$T_A = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Test Conditions	Min	Max	Units
OFF CHARACTERISTICS					
$V_{(BR)CEO}$	Collector-Emitter Breakdown Voltage	$I_C = 1.0 \text{ mA}, I_E = 0$	40		V
$V_{(BR)CBO}$	Collector-Base Breakdown Voltage	$I_C = 10 \mu\text{A}, I_E = 0$	60		V
$V_{(BR)EBO}$	Emitter-Base Breakdown Voltage	$I_E = 10 \mu\text{A}, I_C = 0$	6.0		V
I_{BL}	Base Cutoff Current	$V_{CE} = 30 \text{ V}, V_{EB} = 3 \text{ V}$		50	nA
I_{CEX}	Collector Cutoff Current	$V_{CE} = 30 \text{ V}, V_{EB} = 3 \text{ V}$		50	nA
ON CHARACTERISTICS*					
h_{FE}	DC Current Gain	$I_C = 0.1 \text{ mA}, V_{CE} = 1.0 \text{ V}$ $I_C = 1.0 \text{ mA}, V_{CE} = 1.0 \text{ V}$ $I_C = 10 \text{ mA}, V_{CE} = 1.0 \text{ V}$ $I_C = 50 \text{ mA}, V_{CE} = 1.0 \text{ V}$ $I_C = 100 \text{ mA}, V_{CE} = 1.0 \text{ V}$	40 100 60 30	300	
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C = 10 \text{ mA}, I_B = 1.0 \text{ mA}$ $I_C = 50 \text{ mA}, I_B = 5.0 \text{ mA}$		0.2 0.5	V V
$V_{BE(sat)}$	Base-Emitter Saturation Voltage	$I_C = 10 \text{ mA}, I_B = 1.0 \text{ mA}$ $I_C = 50 \text{ mA}, I_B = 5.0 \text{ mA}$	0.65	0.85 0.95	V V
SMALL SIGNAL CHARACTERISTICS					
f_T	Current Gain - Bandwidth Product	$I_C = 10 \text{ mA}, V_{CE} = 20 \text{ V},$ $f = 100 \text{ MHz}$	300		MHz
C_{obo}	Output Capacitance	$V_{CB} = 5.0 \text{ V}, I_E = 0,$ $f = 1.0 \text{ MHz}$		4.0	pF
C_{ibo}	Input Capacitance	$V_{EB} = 0.5 \text{ V}, I_C = 0,$ $f = 1.0 \text{ MHz}$		8.0	pF
NF	Noise Figure	$I_C = 100 \mu\text{A}, V_{CE} = 5.0 \text{ V},$ $R_S = 1.0 \text{ k}\Omega, f = 10 \text{ Hz to } 15.7 \text{ kHz}$		5.0	dB

۱۴

SWITCHING CHARACTERISTICS

t_d	Delay Time	$V_{CC} = 3.0\text{ V}, V_{CE} = 0.5\text{ V},$	35	ns
t_r	Rise Time	$I_C = 10\text{ mA}, I_{B1} = 1.0\text{ mA}$	35	ns
t_s	Storage Time	$V_{CC} = 3.0\text{ V}, I_C = 10\text{ mA}$	200	ns
t_f	Fall Time	$I_{B1} = I_{B2} = 1.0\text{ mA}$	50	ns


* Pulse Test: Pulse Width $\leq 300\mu\text{s}$, Duty Cycle $\leq 2.0\%$

10

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

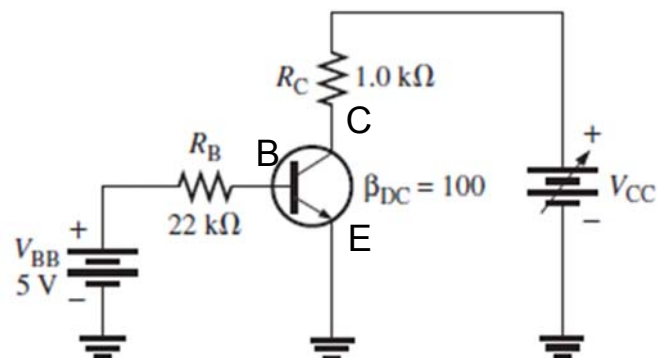Example 04

A 2N3904 transistor is used in the circuit of Figure 4–19 (Example 4–6). Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating. Which rating would be exceeded first? Refer to the datasheet in Figure 4–20.



11

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

Example 04

A 2N3904 transistor is used in the circuit of Figure 4–19 (Example 4–6). Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating. Which rating would be exceeded first? Refer to the datasheet in Figure 4–20.

$$P_{D(\max)} = P_D = 625 \text{ mW}$$

$$V_{CE(\max)} = V_{CE0} = 40 \text{ V}$$

$$I_{C(\max)} = I_C = 200 \text{ mA}$$


$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{22 \text{ k}\Omega} = 195 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (100)(195 \mu\text{A}) = 19.5 \text{ mA}$$

$$V_{R_C} = I_C R_C = (19.5 \text{ mA})(1.0 \text{ k}\Omega) = 19.5 \text{ V}$$

$$V_{CC(\max)} = V_{CE(\max)} + V_{R_C} = 40 \text{ V} + 19.5 \text{ V} = 59.5 \text{ V}$$
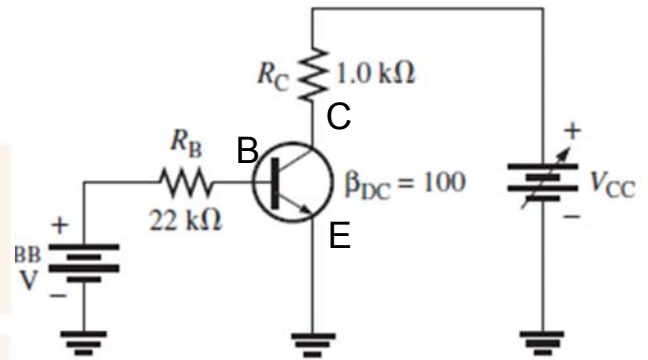
$$P_D = V_{CE(\max)} I_C = (40 \text{ V})(19.5 \text{ mA}) = 780 \text{ mW}$$




Power dissipation exceeds the maximum of 625 mW specified on the datasheet.

THE BJT AS AN AMPLIFIER

- **Amplification** is the process of linearly increasing the amplitude of an electrical signal and is one of the major properties of a transistor.
- a BJT exhibits current gain (β) When a BJT is biased in the active (or linear) region,

DC quantities	AC quantities
VBE	Vbe
VCE	Vce
IC	Vb
IB	Vc
IE	r'e
VB	
VC	

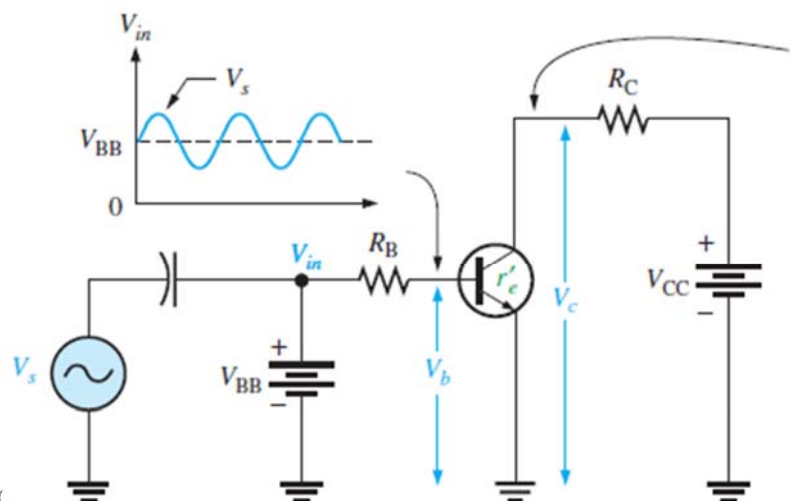- An ac voltage, V_s , is superimposed
- on the dc bias voltage V_{BB} by capacitive coupling as shown. The dc bias voltage V_{CC}
- is connected to the collector through the collector resistor, R_C .



- The ac input voltage produces an ac base current, which results in a much larger ac collector current.
- The ac collector current produces an ac voltage across R_C , thus producing an amplified, but inverted,

internal ac emitter resistance r'_e is designated in and appears in series with R_B .

The ac base voltage is


$$V_b = I_e r'_e$$

The ac collector voltage, V_c , equals the ac voltage drop across R_C

$$V_c = I_c R_C$$

Since the $I_c \cong I_e$, ac collector voltage is

$$V_c \cong I_e R_C$$

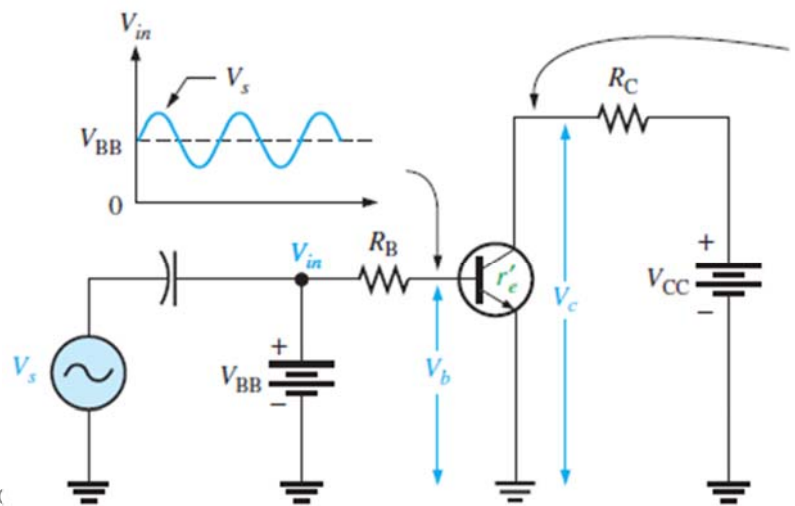

٢١

imed ElShafee, A/


- But remember that V_b

$$V_b = V_s - I_b R_B$$

- the ac voltage gain, A_v , of the transistor

$$A_v = \frac{V_c}{V_b} \cong \frac{I_e R_C}{I_e r'_e}$$


$$A_v \cong \frac{R_C}{r'_e}$$

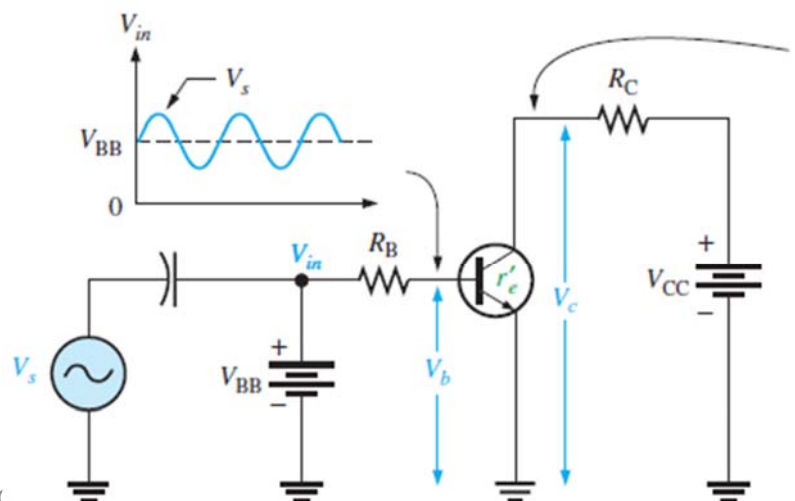

٢٢


Dr. Ahmed ElShafee, A/

$$\frac{VRc}{Vr'e} = \frac{Ic \times RC}{Ie \times r'e} = \frac{Rc}{r'e}$$

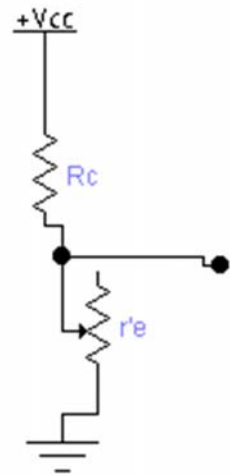

Example 05

Determine the voltage gain and the ac output voltage in Figure 4–22 if $r'_e = 50 \Omega$.

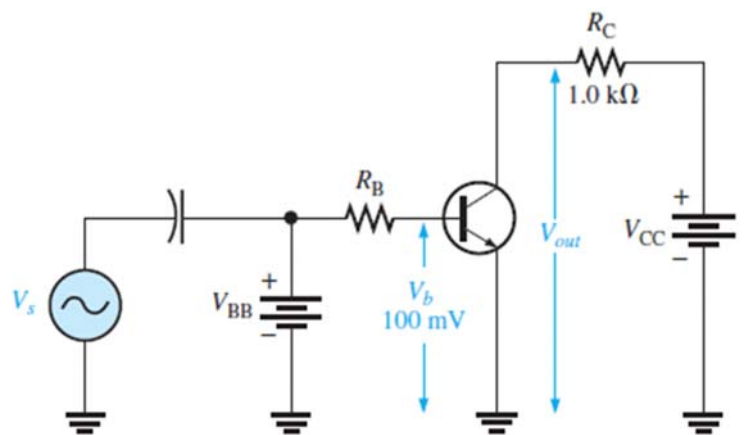

Example 05


Determine the voltage gain and the ac output voltage in Figure 4–22 if $r'_e = 50 \Omega$.

The voltage gain is

$$A_v \cong \frac{R_C}{r'_e} = \frac{1.0 \text{ k}\Omega}{50 \Omega} = 20$$

Therefore, the ac output voltage is
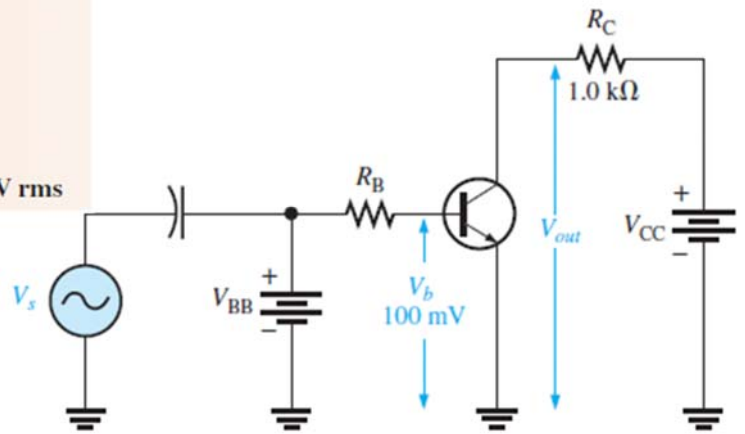
$$V_{out} = A_v V_b = (20)(100 \text{ mV}) = 2 \text{ V rms}$$



Thanks,..
See you next week (ISA),...