



# Lecture (07) Bipolar Junction Transistor (2)

By:

Dr. Ahmed ElShafee



Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

## Maximum Transistor Ratings

- The product of  $V_{CE}$  and  $I_C$  must not exceed the maximum power dissipation
- Both  $V_{CE}$  and  $I_C$  cannot be maximum at the same time.
- If  $V_{CE}$  is maximum,  $I_C$  can be calculated as

$$I_C = \frac{P_{D(max)}}{V_{CE}}$$

- If  $I_C$  is maximum,  $V_{CE}$  can be calculated by


$$V_{CE} = \frac{P_{D(max)}}{I_C}$$

- Assume  $P_{D(max)}$  is 500 mW,  $V_{CE(max)}$  is 20 V, and  $I_C(max)$  is 50 mA

۳

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

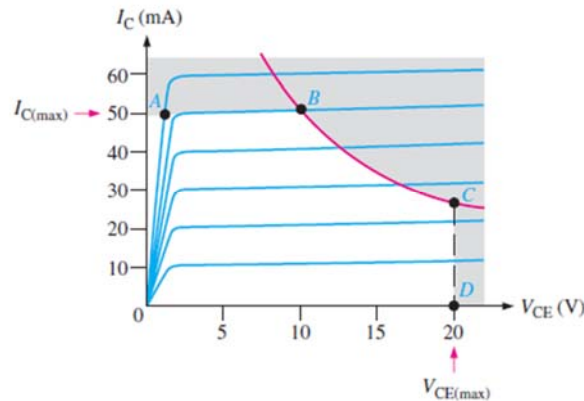- transistor cannot be operated in the shaded portion of the graph.
- $I_C(max)$  is the limiting rating between points A and B,  $P_{D(max)}$  is the limiting rating between points B and C, and  $V_{CE(max)}$  is the limiting rating between points C and D.



$P_{D(max)}$	$V_{CE}$	$I_C$
500 mW	5 V	100 mA
500 mW	10 V	50 mA
500 mW	15 V	33 mA
500 mW	20 V	25 mA

## Example 01

A certain transistor is to be operated with  $V_{CE} = 6$  V. If its maximum power rating is 250 mW, what is the most collector current that it can handle?

۴

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits


## Example 01

A certain transistor is to be operated with  $V_{CE} = 6\text{ V}$ . If its maximum power rating is 250 mW, what is the most collector current that it can handle?

$$I_C = \frac{P_{D(\max)}}{V_{CE}} = \frac{250\text{ mW}}{6\text{ V}} = 41.7\text{ mA}$$
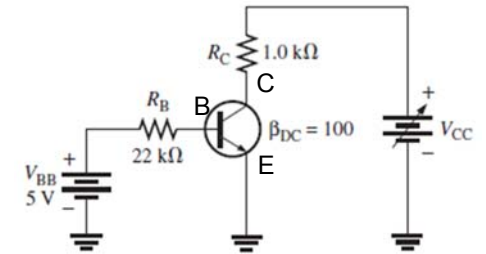
## Example 02

The transistor in Figure 4–19 has the following maximum ratings:  $P_{D(\max)} = 800\text{ mW}$ ,  $V_{CE(\max)} = 15\text{ V}$ , and  $I_{C(\max)} = 100\text{ mA}$ . Determine the maximum value to which  $V_{CC}$  can be adjusted without exceeding a rating. Which rating would be exceeded first?



## Example 02


The transistor in Figure 4–19 has the following maximum ratings:  $P_{D(\max)} = 800\text{ mW}$ ,  $V_{CE(\max)} = 15\text{ V}$ , and  $I_{C(\max)} = 100\text{ mA}$ . Determine the maximum value to which  $V_{CC}$  can be adjusted without exceeding a rating. Which rating would be exceeded first?

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5\text{ V} - 0.7\text{ V}}{22\text{ k}\Omega} = 195\text{ }\mu\text{A}$$

$$I_C = \beta_{DC} I_B = (100)(195\text{ }\mu\text{A}) = 19.5\text{ mA}$$

$I_C$  is much less than  $I_{C(\max)}$  and ideally will not change with  $V_{CC}$ . It is determined only by  $I_B$  and  $\beta_{DC}$ .
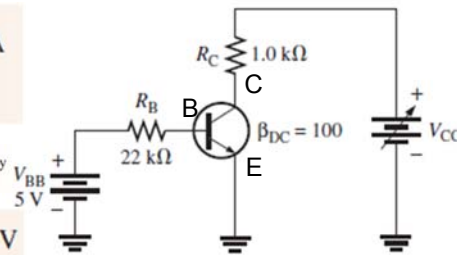
$$V_{R_C} = I_C R_C = (19.5\text{ mA})(1.0\text{ k}\Omega) = 19.5\text{ V}$$



- $V_{CC}$  max occurs when  $V_{CE}$  max, calculated using KVL


$$V_{CC(\max)} = V_{CE(\max)} + V_{R_C} = 15\text{ V} + 19.5\text{ V} = 34.5\text{ V}$$

## Example 02

The transistor in Figure 4–19 has the following maximum ratings:  $P_{D(\max)} = 800\text{ mW}$ ,  $V_{CE(\max)} = 15\text{ V}$ , and  $I_{C(\max)} = 100\text{ mA}$ . Determine the maximum value to which  $V_{CC}$  can be adjusted without exceeding a rating. Which rating would be exceeded first?

- Now calculating PD @  $V_{CE(\max)}$
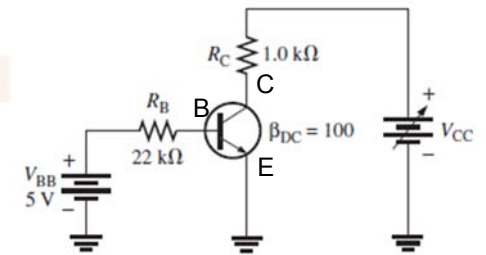
$$P_D = V_{CE(\max)} I_C = (15\text{ V})(19.5\text{ mA}) = 293\text{ mW}$$



Since  $P_{D(\max)}$  is 800 mW, it is *not* exceeded when  $V_{CC} = 34.5\text{ V}$ . So,  $V_{CE(\max)} = 15\text{ V}$  is the limiting rating in this case.

# Example 03

A certain transistor has a  $P_{D(max)}$  of 1 W at 25°C. The derating factor is 5 mW/°C. What is the  $P_{D(max)}$  at a temperature of 70°C?

## Derating $P_{D(max)}$

- $P_{D(max)}$  is usually specified at 25°C. For higher temperatures,  $P_{D(max)}$  is less.
- example, a derating factor of 2 mW/°C indicates that the maximum power dissipation is reduced 2 mW for each degree Celsius increase in temperature.

# Example 03

A certain transistor has a  $P_{D(max)}$  of 1 W at 25°C. The derating factor is 5 mW/°C. What is the  $P_{D(max)}$  at a temperature of 70°C?

The change (reduction) in  $P_{D(max)}$  is

$$\Delta P_{D(max)} = (5 \text{ mW/}^\circ\text{C})(70^\circ\text{C} - 25^\circ\text{C}) = (5 \text{ mW/}^\circ\text{C})(45^\circ\text{C}) = 225 \text{ mW}$$

Therefore, the  $P_{D(max)}$  at 70°C is

$$1 \text{ W} - 225 \text{ mW} = 775 \text{ mW}$$

## BJT Datasheet

- 2N3904 npn transistor

**2N3904**

TO-92

**MMBT3904**

SOT-23  
Mark: 1A

**PZT3904**

SOT-223

**NPN General Purpose Amplifier**

This device is designed as a general purpose amplifier and switch. The useful dynamic range extends to 100 mA as a switch and to 100 MHz as an amplifier.

**Absolute Maximum Ratings\***  $T_A = 25^\circ\text{C}$  unless otherwise noted

Symbol	Parameter	Value	Units
$V_{CE0}$	Collector-Emitter Voltage	40	V
$V_{CB0}$	Collector-Base Voltage	60	V
$V_{EB0}$	Emitter-Base Voltage	6.0	V
$I_C$	Collector Current - Continuous	200	mA
$T_A, T_{stg}$	Operating and Storage Junction Temperature Range	-55 to +150	°C


Thermal Characteristics <small>T<sub>A</sub> = 25°C unless otherwise noted</small>					
Symbol	Characteristic	Max			Units
		2N3904	*MMBT3904	**PZT3904	
P <sub>D</sub>	Total Device Dissipation Derate above 25°C	625 5.0	350 2.8	1,000 8.0	mW mW/°C
R <sub>θJC</sub>	Thermal Resistance, Junction to Case	23.2			°C/W
R <sub>θJA</sub>	Thermal Resistance, Junction to Ambient	200	357	125	°C/W

\* Device mounted on FR-4 PCB 1.6" X 1.6" X 0.06"  
\*\* Device mounted on FR-4 PCB 36 mm X 18 mm X 1.5 mm, mounting pad for the collector lead min. 6 cm<sup>2</sup>.

Electrical Characteristics <small>T<sub>A</sub> = 25°C unless otherwise noted</small>					
Symbol	Parameter	Test Conditions	Min	Max	Units
<b>OFF CHARACTERISTICS</b>					
V <sub>(BR)CEO</sub>	Collector-Emitter Breakdown Voltage	I <sub>C</sub> = 1.0 mA, I <sub>B</sub> = 0	40		V
V <sub>(BR)CBO</sub>	Collector-Base Breakdown Voltage	I <sub>C</sub> = 10 μA, I <sub>E</sub> = 0	60		V
V <sub>(BR)EBO</sub>	Emitter-Base Breakdown Voltage	I <sub>E</sub> = 10 μA, I <sub>C</sub> = 0	6.0		V
I <sub>BL</sub>	Base Cutoff Current	V <sub>CE</sub> = 30 V, V <sub>EB</sub> = 3V		50	nA
I <sub>CEX</sub>	Collector Cutoff Current	V <sub>CE</sub> = 30 V, V <sub>EB</sub> = 3V		50	nA
<b>ON CHARACTERISTICS*</b>					
h <sub>FE</sub>	DC Current Gain	I <sub>C</sub> = 0.1 mA, V <sub>CE</sub> = 1.0 V I <sub>C</sub> = 1.0 mA, V <sub>CE</sub> = 1.0 V I <sub>C</sub> = 10 mA, V <sub>CE</sub> = 1.0 V I <sub>C</sub> = 50 mA, V <sub>CE</sub> = 1.0 V I <sub>C</sub> = 100 mA, V <sub>CE</sub> = 1.0 V	40 100 80 30	300	
V <sub>CE(sat)</sub>	Collector-Emitter Saturation Voltage	I <sub>C</sub> = 10 mA, I <sub>B</sub> = 1.0 mA I <sub>C</sub> = 50 mA, I <sub>B</sub> = 5.0 mA		0.2 0.15	V
V <sub>BE(sat)</sub>	Base-Emitter Saturation Voltage	I <sub>C</sub> = 10 mA, I <sub>B</sub> = 1.0 mA I <sub>C</sub> = 50 mA, I <sub>B</sub> = 5.0 mA	0.65	0.95 0.95	V
<b>SMALL SIGNAL CHARACTERISTICS</b>					
f <sub>T</sub>	Current Gain - Bandwidth Product	I <sub>C</sub> = 10 mA, V <sub>CE</sub> = 20 V, f = 100 MHz	300		MHz
C <sub>obo</sub>	Output Capacitance	V <sub>CB</sub> = 5.0 V, I <sub>E</sub> = 0, f = 1.0 MHz		4.0	pF
C <sub>ibo</sub>	Input Capacitance	V <sub>EB</sub> = 0.5 V, I <sub>C</sub> = 0, f = 1.0 MHz		8.0	pF
NF	Noise Figure	I <sub>C</sub> = 100 μA, V <sub>CE</sub> = 5.0 V, R <sub>S</sub> = 1.0 kΩ, f = 10 Hz to 15.7 kHz		5.0	dB
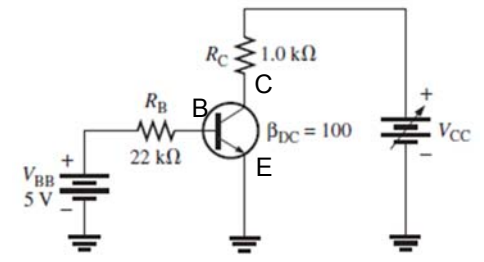
## Example 04

A 2N3904 transistor is used in the circuit of Figure 4-19 (Example 4-6). Determine the maximum value to which V<sub>CC</sub> can be adjusted without exceeding a rating. Which rating would be exceeded first? Refer to the datasheet in Figure 4-20.



## Example 04

A 2N3904 transistor is used in the circuit of Figure 4–19 (Example 4–6). Determine the maximum value to which  $V_{CC}$  can be adjusted without exceeding a rating. Which rating would be exceeded first? Refer to the datasheet in Figure 4–20.

$$P_{D(\max)} = P_D = 625 \text{ mW}$$

$$V_{CE(\max)} = V_{CEO} = 40 \text{ V}$$

$$I_{C(\max)} = I_C = 200 \text{ mA}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{22 \text{ k}\Omega} = 195 \mu\text{A}$$


$$I_C = \beta_{DC} I_B = (100)(195 \mu\text{A}) = 19.5 \text{ mA}$$

$$V_{R_C} = I_C R_C = (19.5 \text{ mA})(1.0 \text{ k}\Omega) = 19.5 \text{ V}$$

$$V_{CC(\max)} = V_{CE(\max)} + V_{R_C} = 40 \text{ V} + 19.5 \text{ V} = 59.5 \text{ V}$$

$$P_D = V_{CE(\max)} I_C = (40 \text{ V})(19.5 \text{ mA}) = 780 \text{ mW}$$

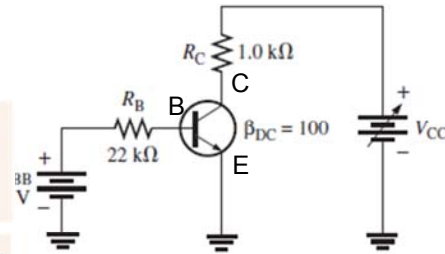**Power dissipation** exceeds the maximum of 625 mW specified on the datasheet.



## THE BJT AS AN AMPLIFIER


- **Amplification** is the process of linearly increasing the amplitude of an electrical signal and is one of the major properties of a transistor.
- a BJT exhibits current gain ( $\beta$ ) When a BJT is biased in the active (or linear) region,

18

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

DC quantities	AC quantities
$V_{BE}$	$V_{be}$
$V_{CE}$	$V_{ce}$
$I_C$	$I_b$
$I_B$	$I_c$
$I_E$	$r'_e$
$V_B$	
$V_C$	

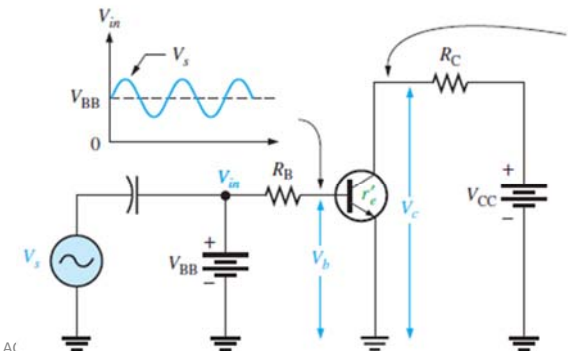- An ac voltage,  $V_s$ , is superimposed
- on the dc bias voltage  $V_{BB}$  by capacitive coupling as shown. The dc bias voltage  $V_{CC}$
- is connected to the collector through the collector resistor,  $R_C$ .



19

Dr. Ahmed ElShafee, ACU

- The ac input voltage produces an ac base current, which results in a much larger ac collector current.
- The ac collector current produces an ac voltage across  $R_C$ , thus producing an amplified, but inverted,

internal ac emitter resistance  $r'_e$  is designated in and appears in series with  $R_B$ .

The ac base voltage is


$$V_b = I_e r'_e$$

The ac collector voltage,  $V_c$ , equals the ac voltage drop across  $R_C$

$$V_c = I_c R_C$$

Since the  $I_c \cong I_e$ , ac collector voltage is

$$V_c \cong I_e R_C$$

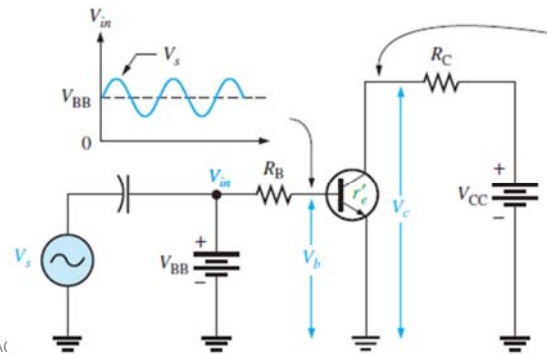

٢١

Dr. Ahmed ElShafee, AC


- But remember that  $V_b$

$$V_b = V_s - I_b R_B$$

- the ac voltage gain,  $A_v$ , of the transistor

$$A_v = \frac{V_c}{V_b} \cong \frac{I_e R_C}{I_e r'_e}$$

$$A_v \cong \frac{R_C}{r'_e}$$

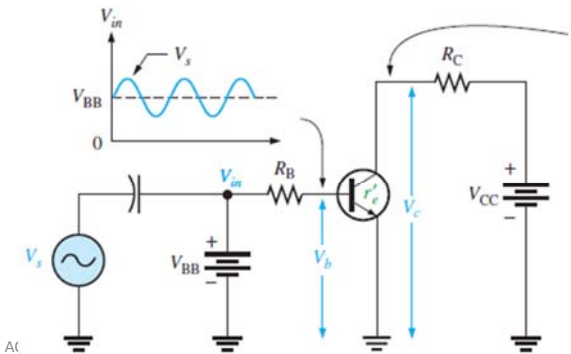


٢٢

Dr. Ahmed ElShafee, AC
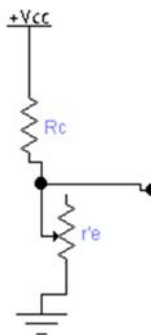
## Example 05


Determine the voltage gain and the ac output voltage in Figure 4-22 if  $r'_e = 50 \Omega$ .

$$\frac{V_c}{V_b} = \frac{I_c \times R_C}{I_e \times r'_e} = \frac{R_C}{r'_e}$$



٢٣

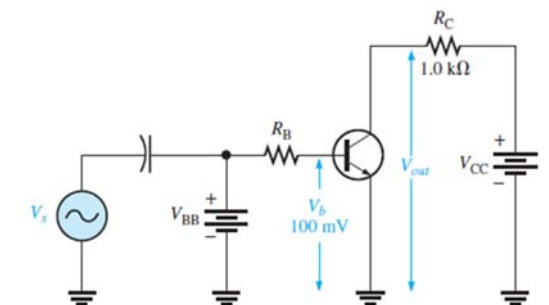Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits



٢٤

Dr. Ahmed ElShafee, ACU : Fall 2015, Electronic Circuits

## Example 05


Determine the voltage gain and the ac output voltage in Figure 4–22 if  $r'_e = 50 \Omega$ .

The voltage gain is

$$A_v \cong \frac{R_C}{r'_e} = \frac{1.0 \text{ k}\Omega}{50 \Omega} = 20$$

Therefore, the ac output voltage is
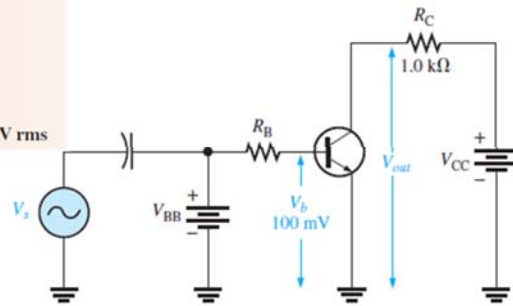
$$V_{out} = A_v V_b = (20)(100 \text{ mV}) = 2 \text{ V rms}$$



Thanks,..  
See you next week (ISA),...