

Electronic Circuits – Assignment

03

Diode Applications I

#	Student ID	Student Name	Grade (10)
-			

Delivery Date	
---------------	--


١. يتم تسليم التمرين محلولا في خلال أسبوع من تاريخ التمرين، و يتم حذف درجتين من التمرين عن كل أسبوع تأخير
٢. يتم التسليم لمعيد المقرر مباشرة
٣. تتم أجابه التمرين في نفس ورق الأسئلة

T & False questions

#	Question	Answer
1	The two regions of a diode are the anode and the collector.	F
2	A diode conducts current when forward-biased.	T
3	Two types of current in a diode are electron and hole.	T
4	The output frequency of a half-wave rectifier is twice the input frequency.	F
5	PIV stands for positive inverse voltage.	F
6	The output frequency of a full-wave rectifier is twice the input frequency.	T


MCQ

#	Question	
1	When a diode is forward-biased and the bias voltage is increased, the voltage across the diode (assuming the practical model) will (a) increase (b) decrease (c) not change	c
2	When a diode is reverse-biased and the bias voltage is increased, the reverse current (assuming the complete model) will (a) increase (b) decrease (c) not change	a
3	If the forward current in a diode is increased, the diode voltage (assuming the practical model) will (a) increase (b) decrease (c) not change	c
4	If the barrier potential of a diode is exceeded, the forward current will (a) increase (b) decrease (c) not change	a
5	If the turns ratio of the transformer in Figure 2-28 is decreased, the forward current through the diode will	b

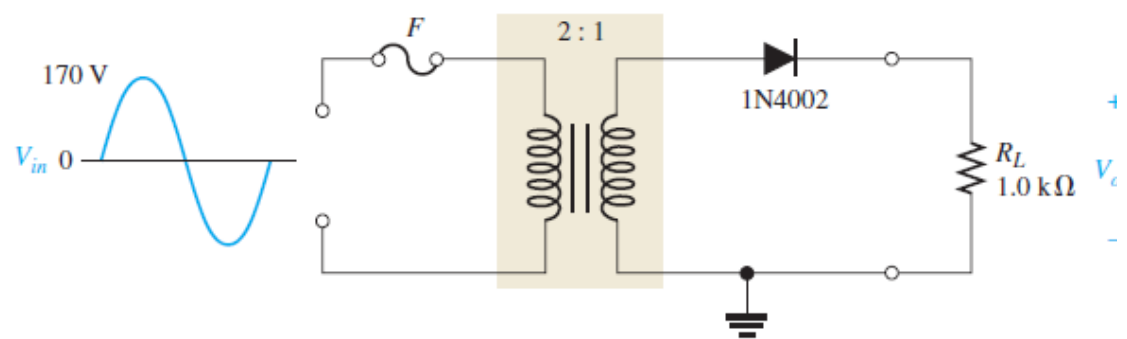

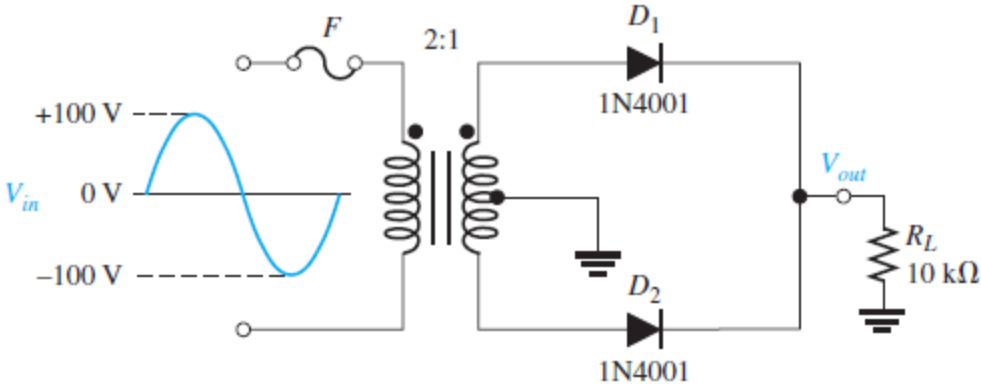(a) increase **(b)** decrease **(c)** not change



6	<p>If the PIV rating of the diodes in Figure 2–36 is increased, the current through R_L will</p>  <p>(a) increase (b) decrease (c) not change</p>	c
7	<p>To forward-bias a diode,</p> <p>(a) an external voltage is applied that is positive at the anode and negative at the cathode</p> <p>(b) an external voltage is applied that is negative at the anode and positive at the cathode</p> <p>(c) an external voltage is applied that is positive at the p region and negative at the n region</p> <p>(d) answers (a) and (c)</p>	d
8	<p>Although current is blocked in reverse bias,</p> <p>(a) there is some current due to majority carriers</p> <p>(b) there is a very small current due to minority carriers</p> <p>(c) there is an avalanche current</p>	b
9	<p>When forward-biased, a diode</p> <p>(a) blocks current (b) conducts current</p> <p>(c) has a high resistance (d) drops a large voltage</p>	b
10	<p>The dynamic resistance can be important when a diode is</p> <p>(a) reverse-biased (b) forward-biased</p> <p>(c) in reverse breakdown (d) unbiased</p>	b
1	<p>Ideally, a diode can be represented by a</p> <p>(a) voltage source (b) resistance (c) switch (d) all of these</p>	c
1	<p>In the complete diode model,</p> <p>(a) the barrier potential is taken into account</p> <p>(b) the forward dynamic resistance is taken into account</p> <p>(c) the reverse resistance is taken into account</p> <p>(d) all of these</p>	d
13	<p>When a 60 Hz sinusoidal voltage is applied to the input of a half-wave rectifier, the output frequency is</p> <p>(a) 120 Hz (b) 30 Hz (c) 60 Hz (d) 0 Hz</p>	c



14	For the circuit in Question 15, the diode must be able to withstand a reverse voltage of (a) 10 V (b) 5 V (c) 20 V (d) 3.18 V	a
15	When a 60 Hz sinusoidal voltage is applied to the input of a full-wave rectifier, the output frequency is (a) 120 Hz (b) 60 Hz (c) 240 Hz (d) 0 Hz	a
16	When the peak output voltage is 100 V, the PIV for each diode in a center-tapped full-wave rectifier is (neglecting the diode drop) (a) 100 V (b) 200 V (c) 141 V (d) 50 V	b