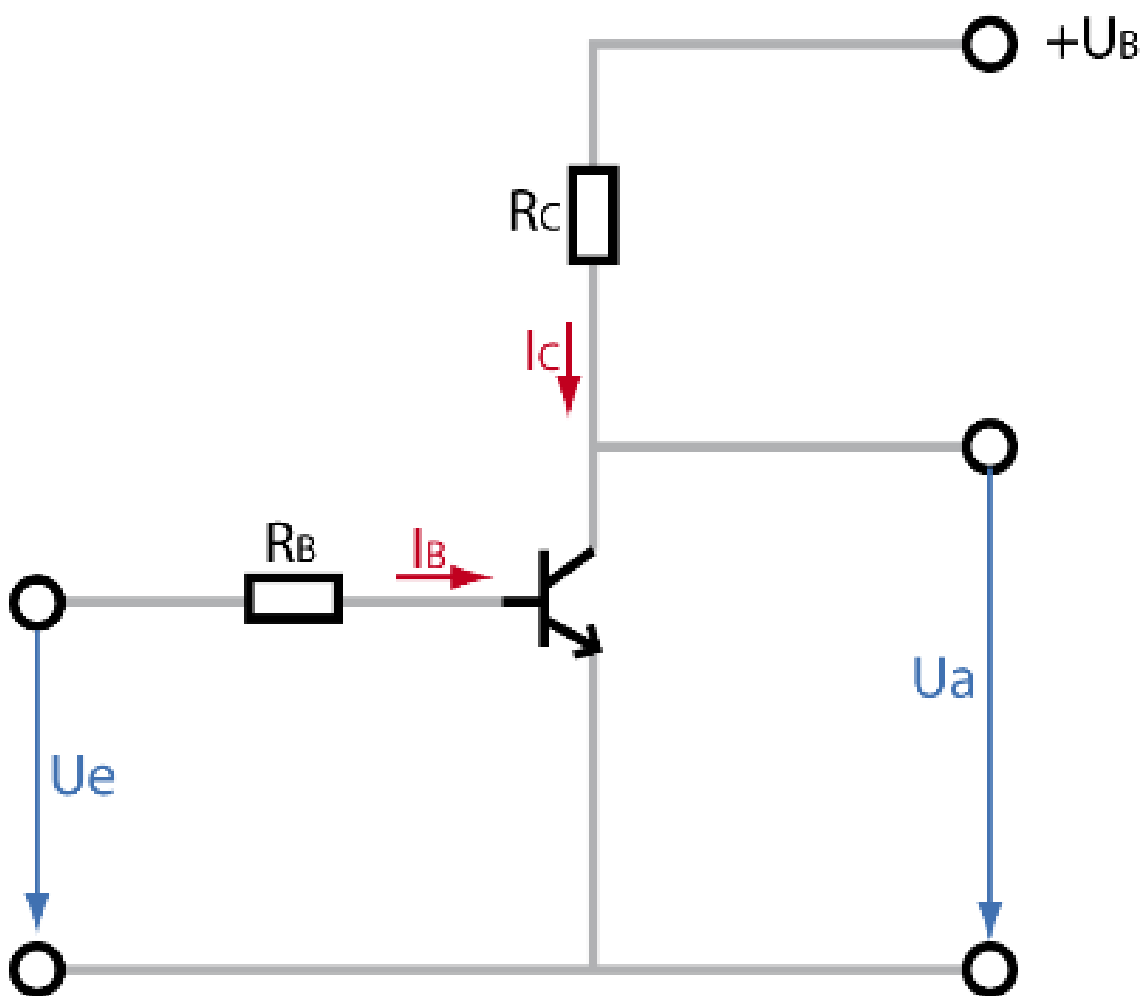


Electronic Circuits I – Laboratory 06 Transistors as Amplifier

#	Student ID	Student Name	Grade (10)	Instructor signature
1				
2				
3				
4				
5				

Delivery Date	
---------------	--

One of the main applications for transistors is transistor switching stages. They are used for contactless, fast switching of small and medium loads. When used in this manner, the transistor is simply shifted between two states. Switching between these two states happens within a few microseconds.



Transistor switched off

In this state, the input base current $I_B = 0$ A. In this case, the transistor is switched off and no collector current is able to flow. Because there is no voltage drop across the resistor R_C , the output voltage V_{out} corresponds to the supply voltage V_B .


Transistor switched on

In this state, a base current is fed to the transistor via R_B by applying an input voltage. This causes a collector current to flow, which must be sufficiently large that most of the supply voltage V_B drops across the collector resistor R_C . The output voltage V_{out} therefore sinks almost to 0 V. The voltage does not fall all the way to 0 V due to the fact that the resistance between the collector and the emitter of the transistor is not exactly 0 Ω . This residual voltage is also called the saturation voltage V_{CEsat} .

In order to ensure that this saturation level is achieved, a base current is supplied, which is not just the amount required for a collector current, but several times that current. As a consequence, the base is overdriven. This multiple is also referred to as the overdrive factor and, in practice, commonly has a value of between 2 and 10.

Part 1: AC response

Circuit diagram

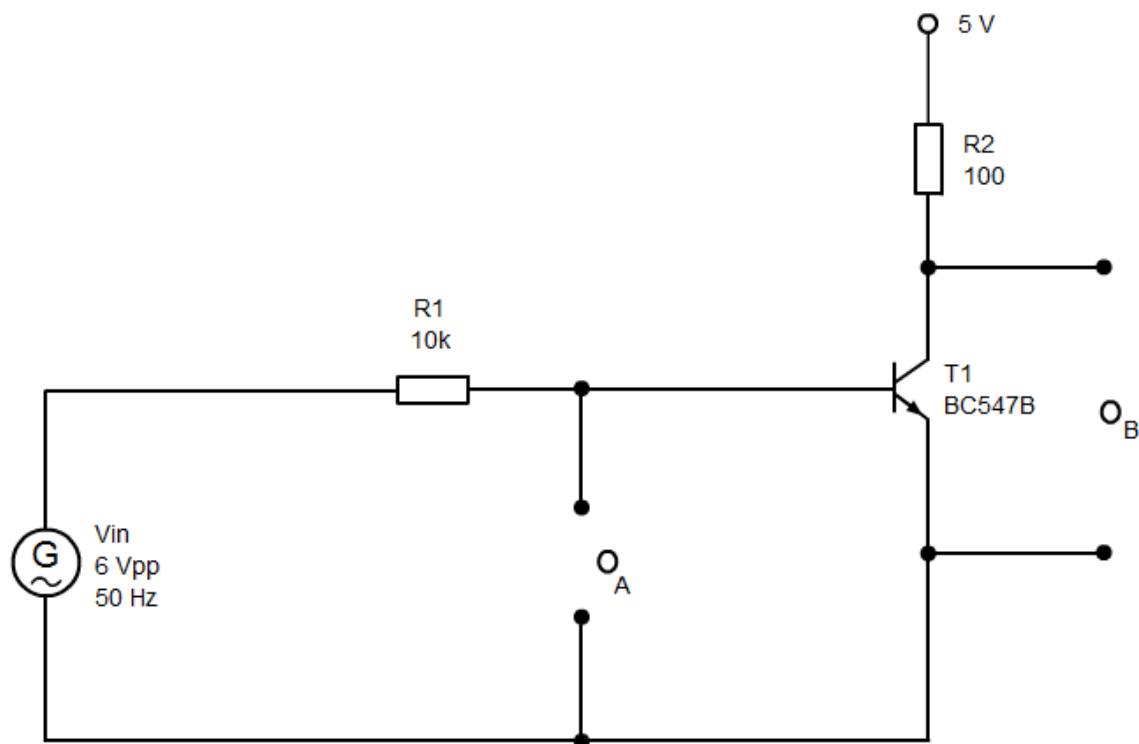



This experiment is based on the following circuit




Equipment

The following equipment is needed for this experiment and should be configured as shown:

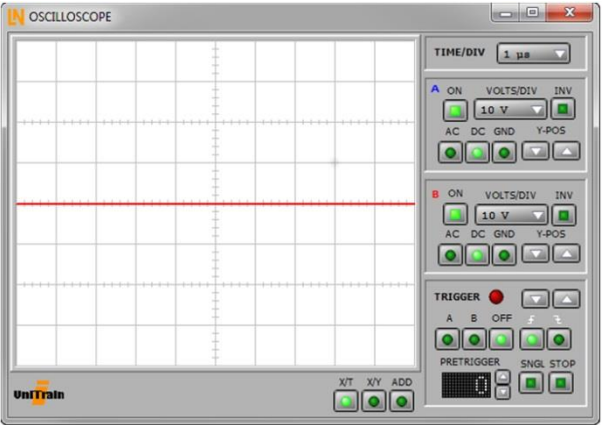Equipment	Settings		
		Channel A	
	Sensitivity	1 V/div	2 V/div
	Coupling	DC	DC
	Polarity	Normal	Normal
	Y position	0	0
	Time base	5ms/div	
	Mode	X/T	
	Trigger channel	-	
	Trigger edge	-	

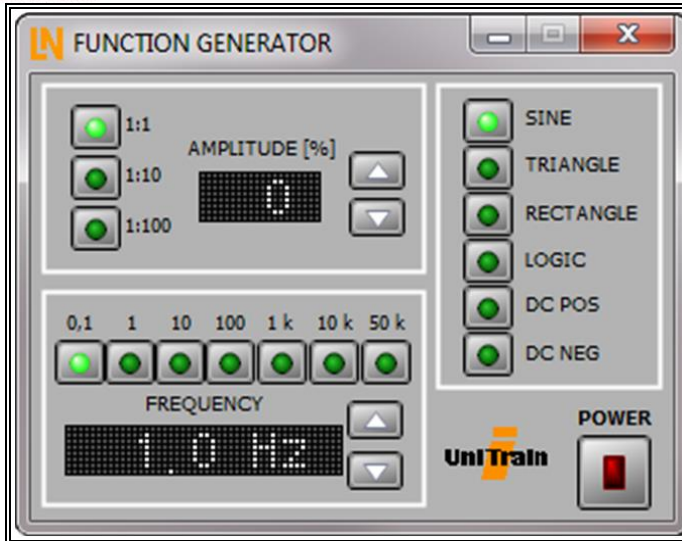


Waveform	Sine
Amplitude	6 Vpp (30%, 1:1)
Frequency factor	10
Frequency	50 Hz

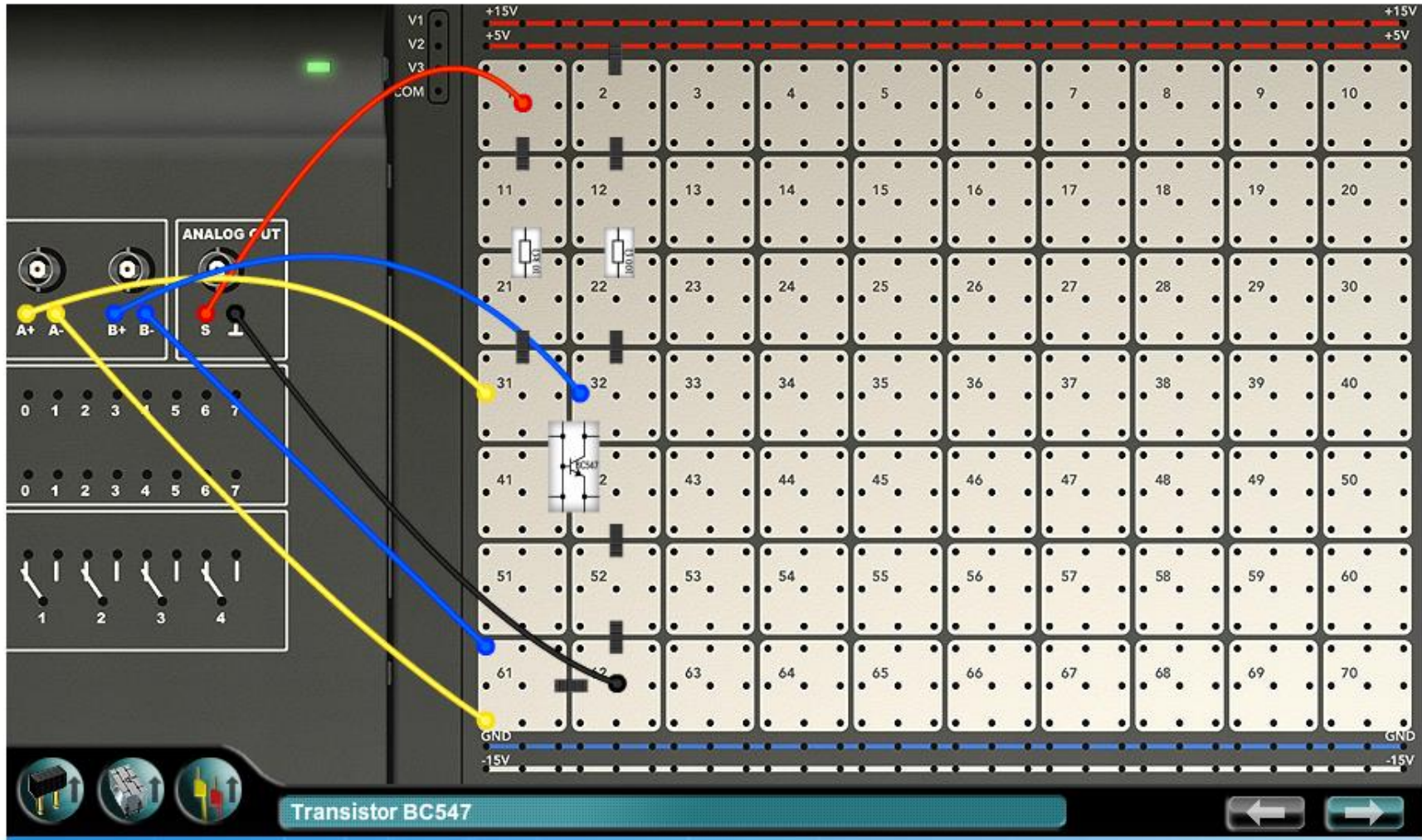

Experiment procedure and exercises

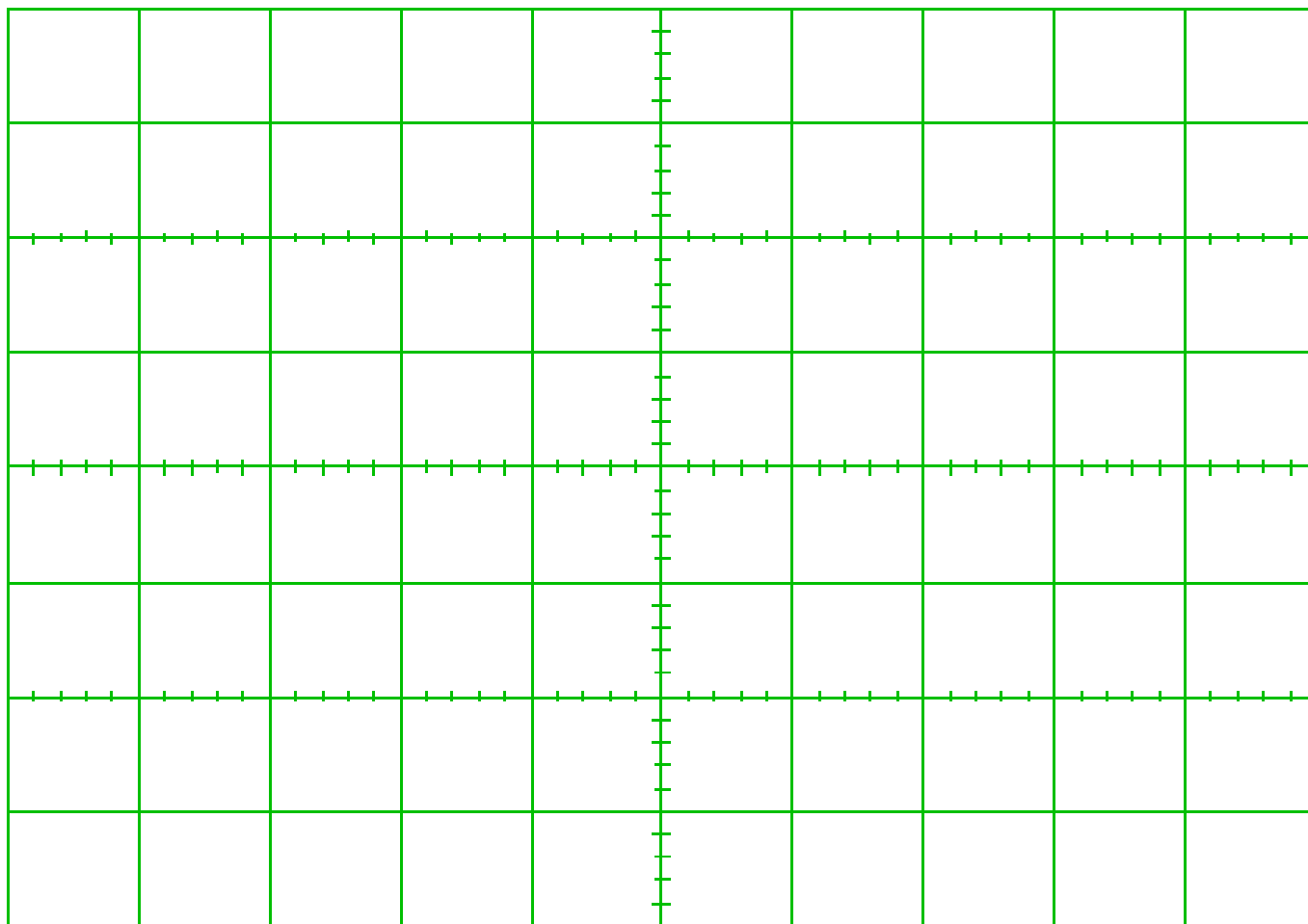Configure the oscilloscope and function generator with the values given above. Record the voltages V_{BE} and V_{CE} and copy the oscilloscope trace into the space below






Faculty of Engineering

Which of the following statements are correct?	
<input type="checkbox"/>	The transistor does not conduct when the input voltage is negative.
<input type="checkbox"/>	The transistor does not conduct when no control voltage is present.
<input type="checkbox"/>	The transistor conducts more current as the control voltage increases.
<input type="checkbox"/>	The transistor consists of four semiconductor layers.

<input type="checkbox"/>	What kind of transistor is this?
<input type="checkbox"/>	A bipolar PNP transistor
<input type="checkbox"/>	A bipolar NPN transistor

Part 2: Current gain calculation


Circuit diagram

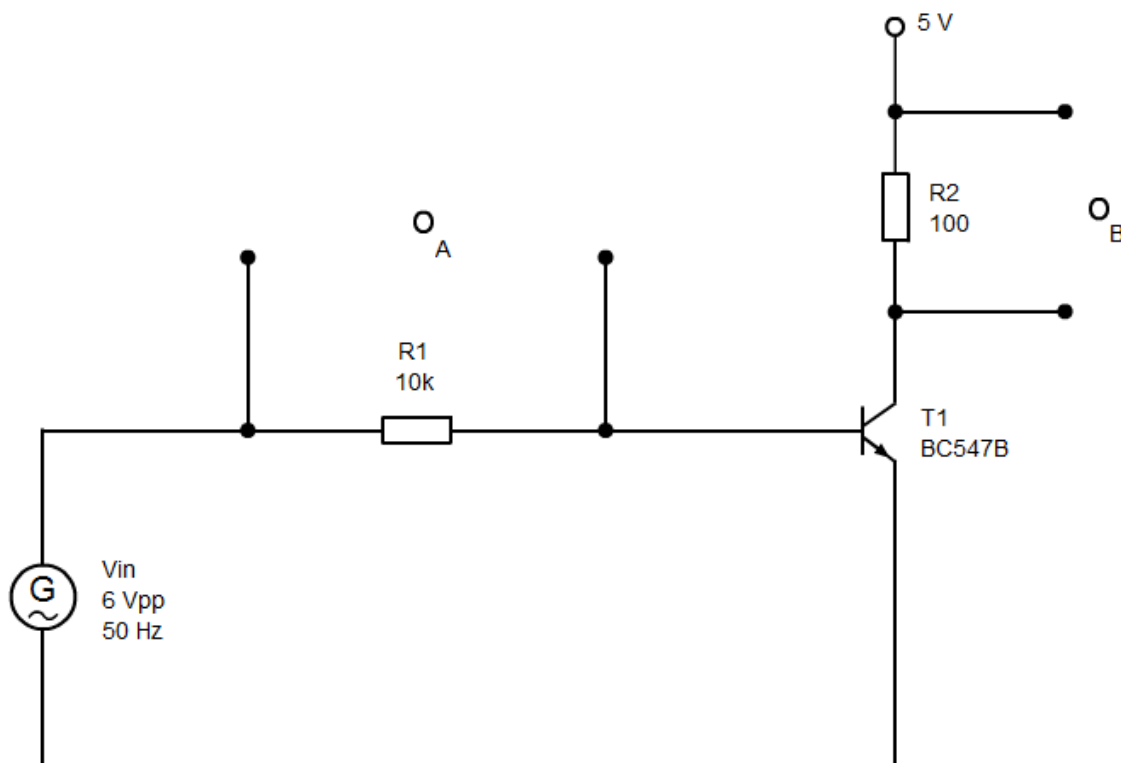





Equipment

The following equipment is needed for this experiment and should be configured as shown:

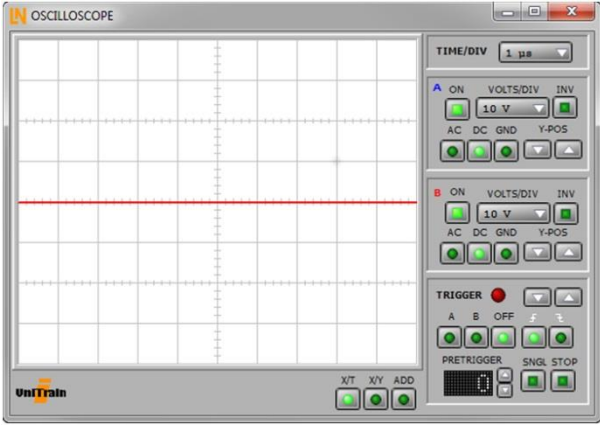Equipment	Settings		
		Channel A	
	Sensitivity	2 V/div	2 V/div
	Coupling	DC	DC
	Polarity	Normal	Normal
	Y position	0	0
	Time base	2ms/div	
	Mode	X/Y	
	Trigger channel	-	
	Trigger edge	-	

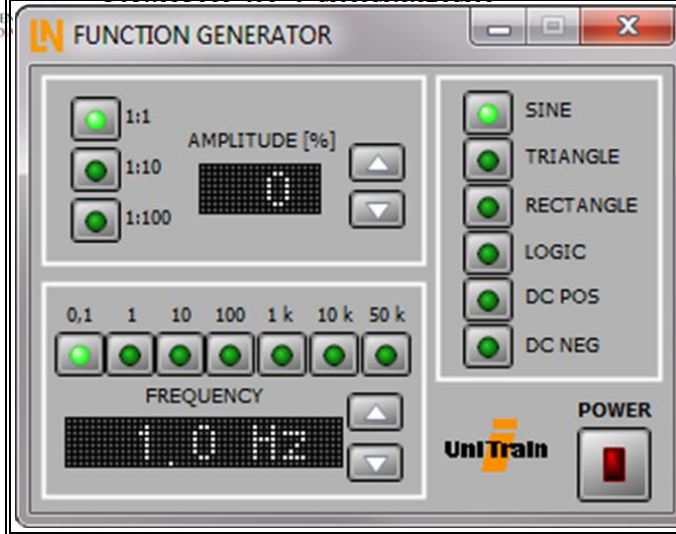

Waveform	Sine
Amplitude	6 Vpp (30%, 1:1)
Frequency factor	10
Frequency	50 Hz

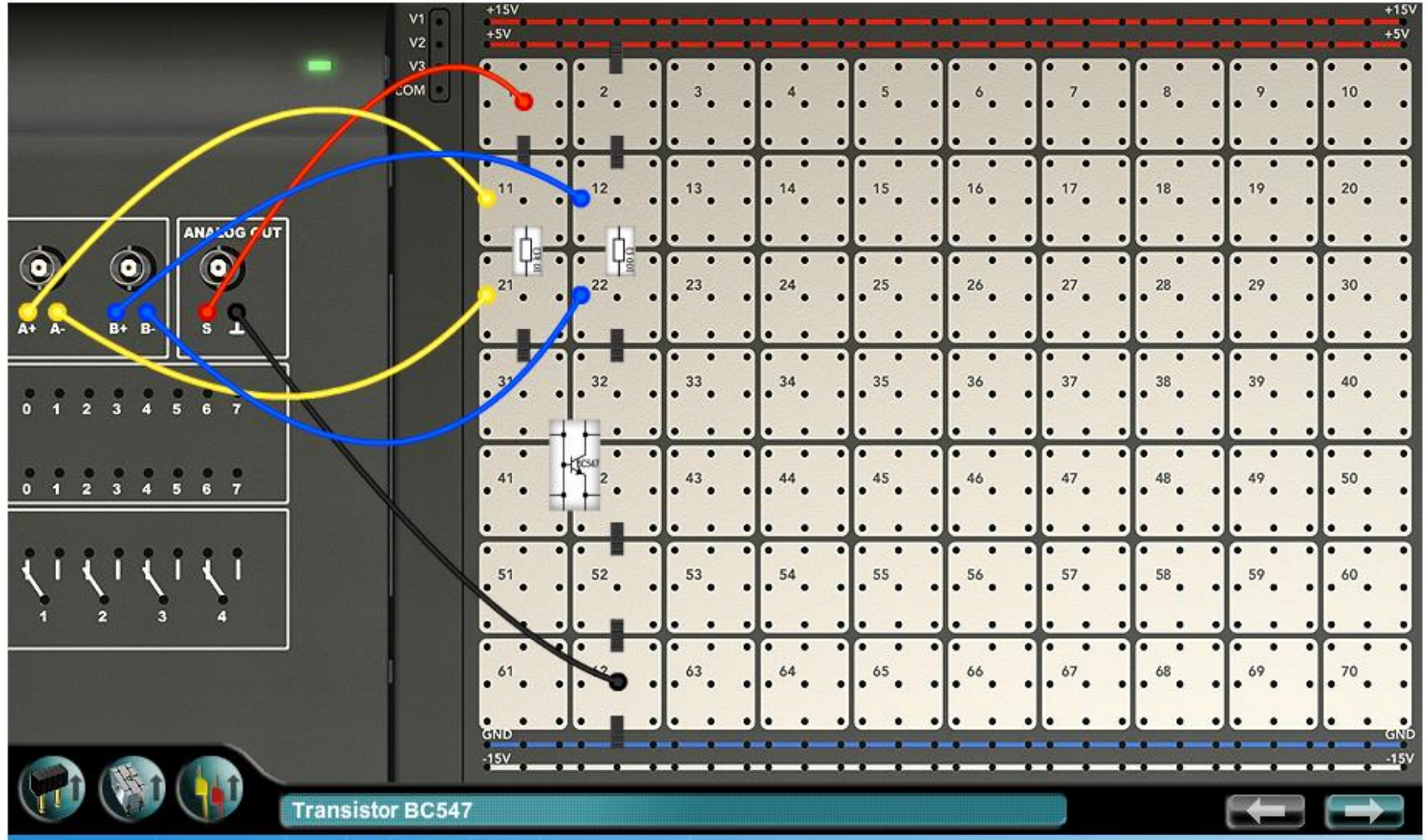

Experiment procedure and exercises

Record the currents I_B and I_C and copy the oscilloscope trace into the space below.

Now calculate the current gain of the transistor. This is given by the ratio of the collector current to the base current.

$$\text{Gain} = \frac{I_{CE}}{I_{BE}}$$

Calculate the current gain.	
$I_{BE} =$ mA	
$I_{CE} =$ mA	
Gain	

Now replace resistor R2 with one of 330 ohms. Calculate the current gain once again.	
$I_{BE} =$ mA	
$I_{CE} =$ mA	
Gain	

