



Lecture (06) Bipolar Junction Transistor

By:

Dr. Ahmed ElShafee


Dr. Ahmed ElShafee, ACU : Fall 2016, Electronic Circuits I

Agenda



- BJT structure
- BJT operation

BJT structure

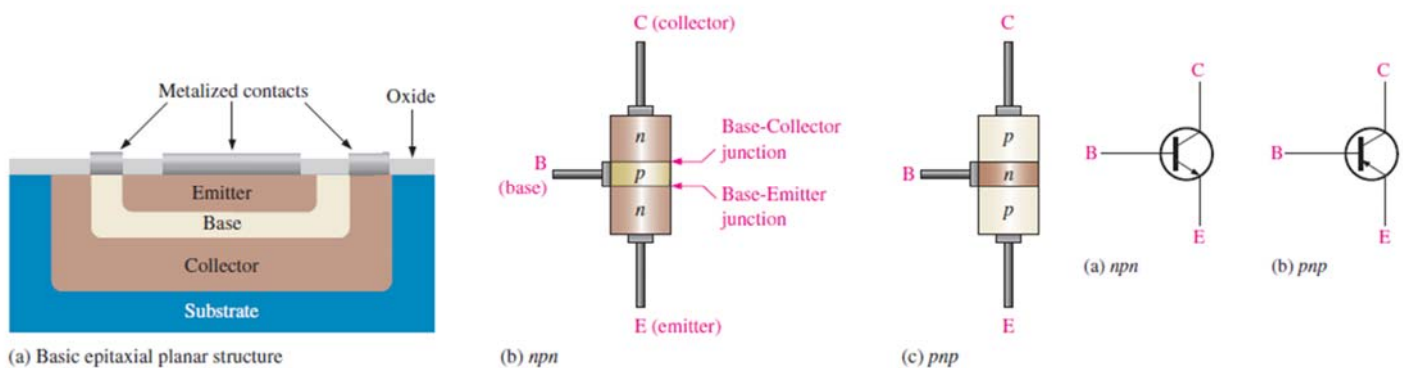- The **BJT** is constructed with three doped semiconductor regions
- One type consists of two n regions separated by a p region (npn), and the other type consists of two p regions separated by an n region (pnp).
- The term **bipolar** refers to the use of both holes and electrons



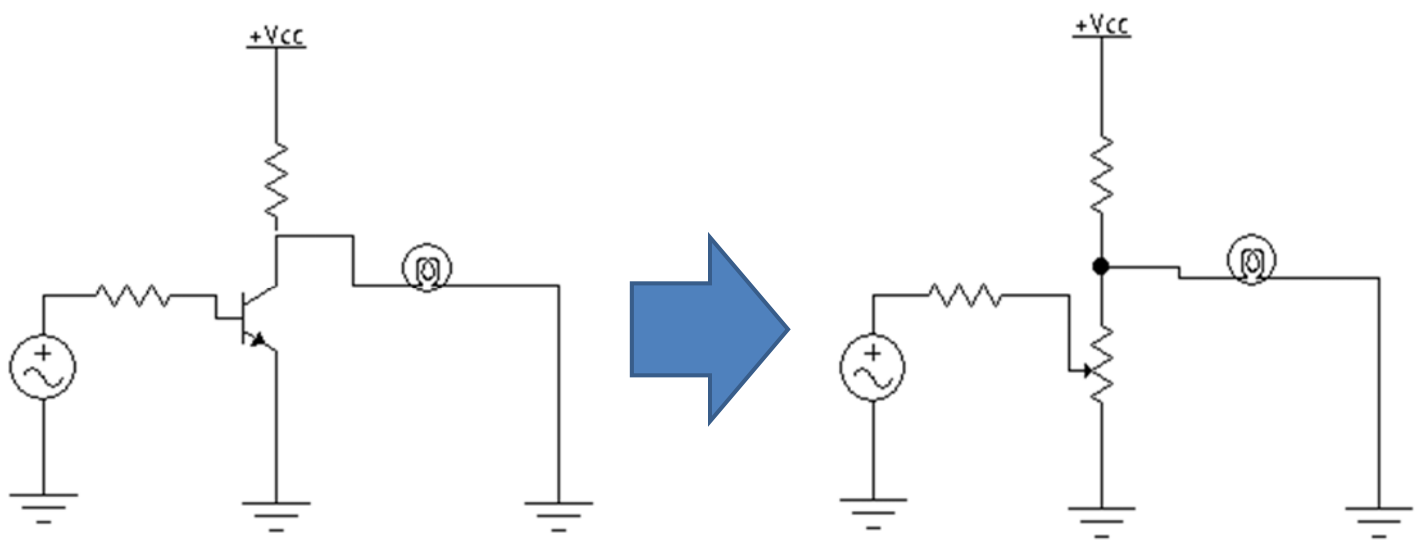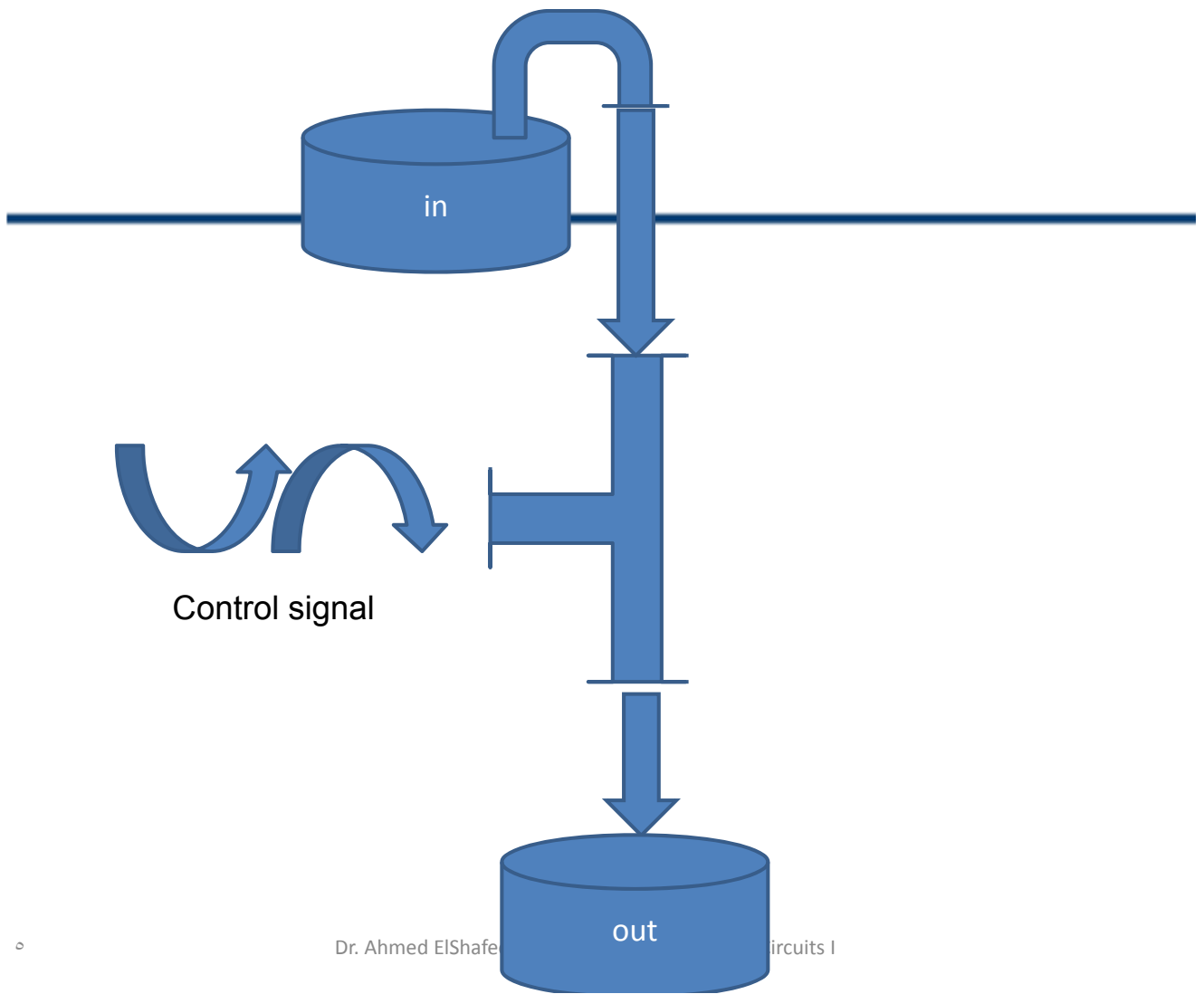- In order for a BJT to operate properly as an amplifier, the two pn junctions must be correctly biased with external dc voltages.
- In this section, we mainly use the npn transistor for illustration.
- The operation of the pnp is the same as for the npn except that the roles of the electrons and holes, the bias voltage polarities, and the current directions are all reversed.




Biasing

base-emitter (BE) junction is forward-biased


base-collector (BC) junction is reverse-biased

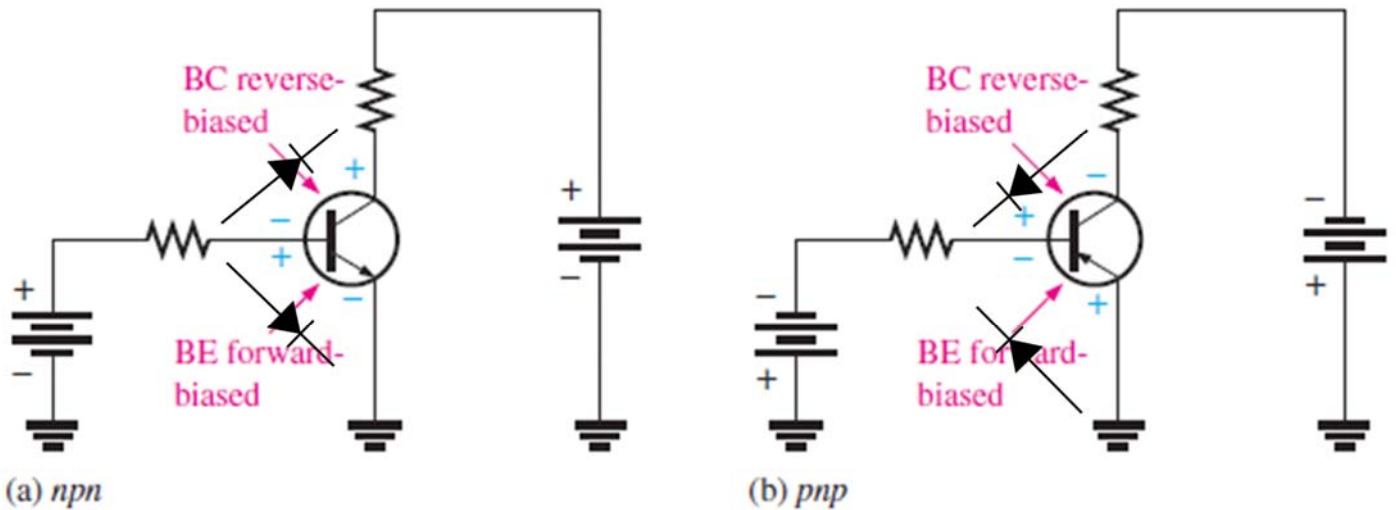This condition is called *forward-reverse bias*




BJT Operation

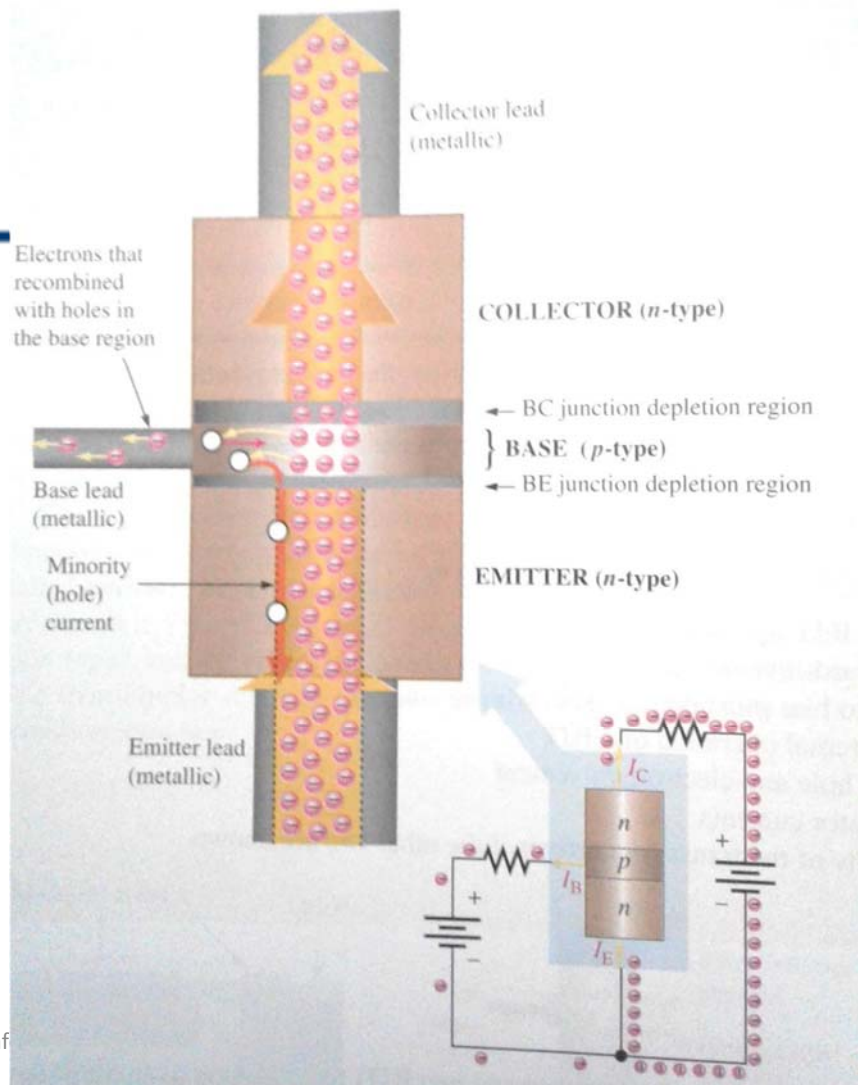- CE battery +ve terminal attract electrons from the collector N-region.
- Collector N-region compensate electrons depletion region, which become more and more wider.




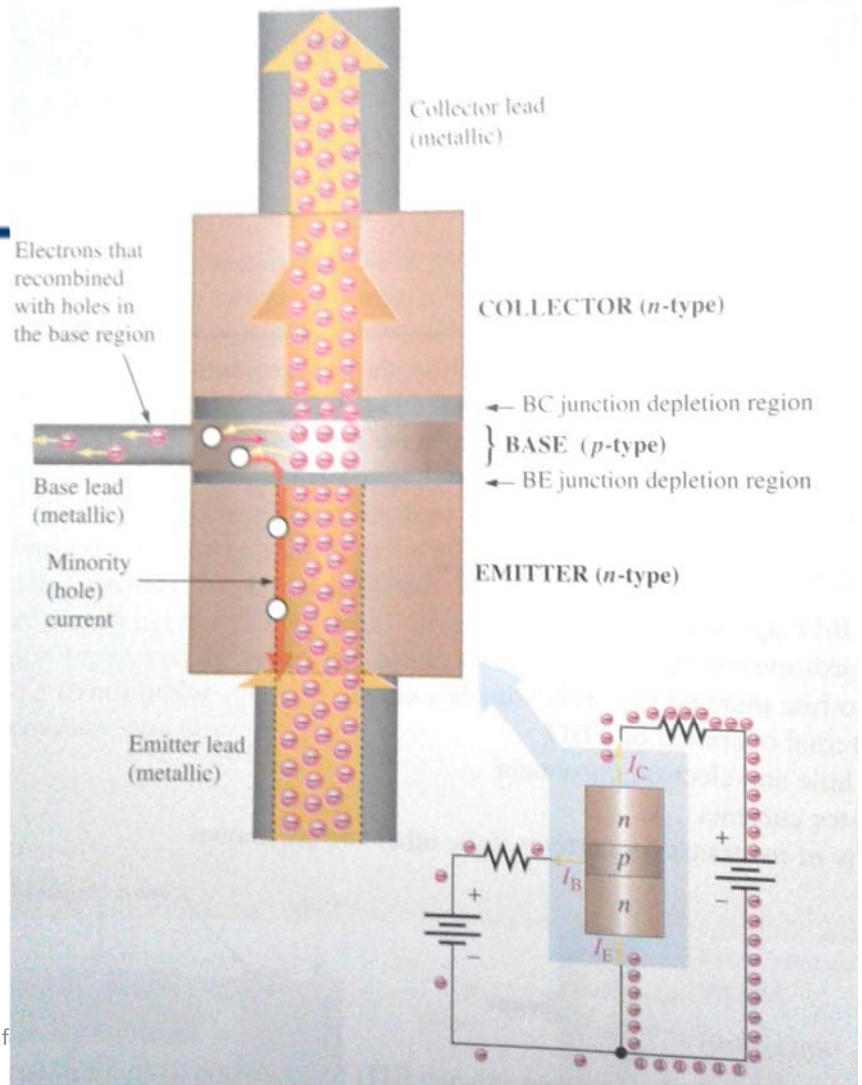- BE battery +ve terminal start attracting the small amounts of electrons (minority carrier) from base p-type region, then starts attracting electrons from depletion region, which become thinner and thinner, then electrons start to flow from Emitter N-region




Dr. Ahmed ElShaf

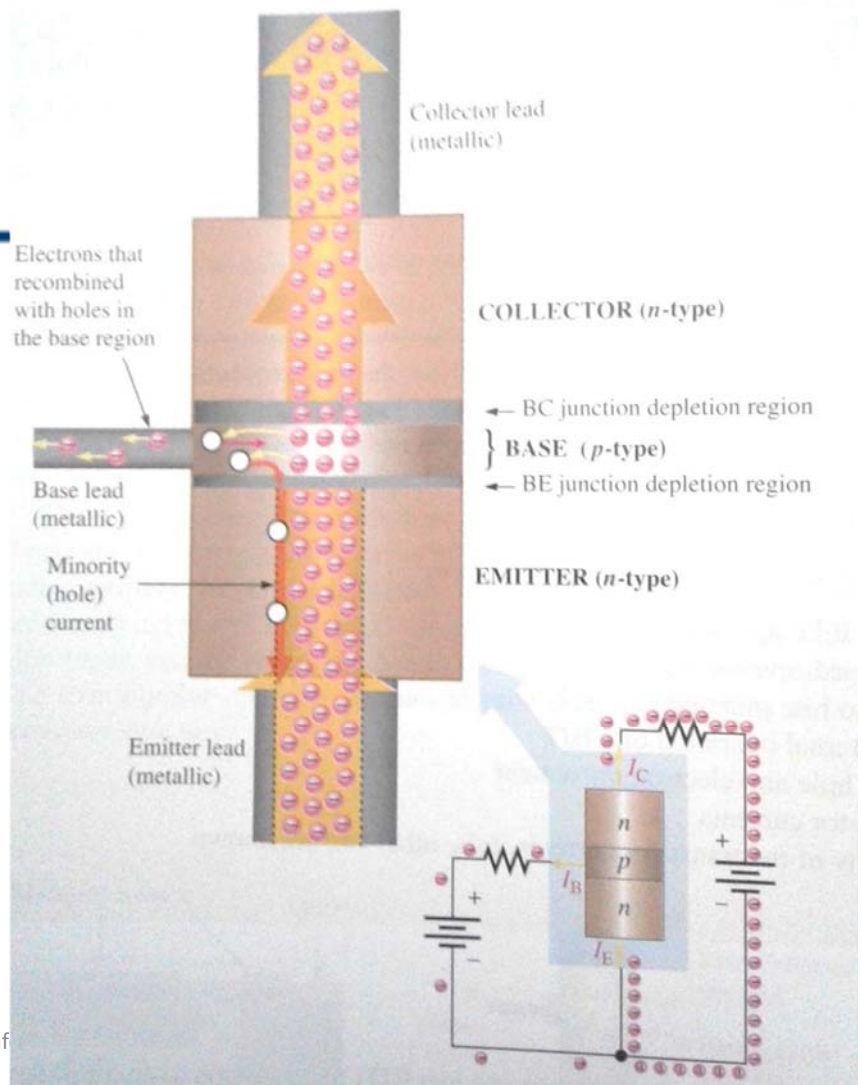- Now base p-type now how a new electrons being transferred from CE battery -ve terminal through emitter n-type.
- Electrons stream divided between
 - Directly to BE battery +ve terminal
 - CE battery +ve terminal through emitter n-type



Dr. Ahmed ElShaf

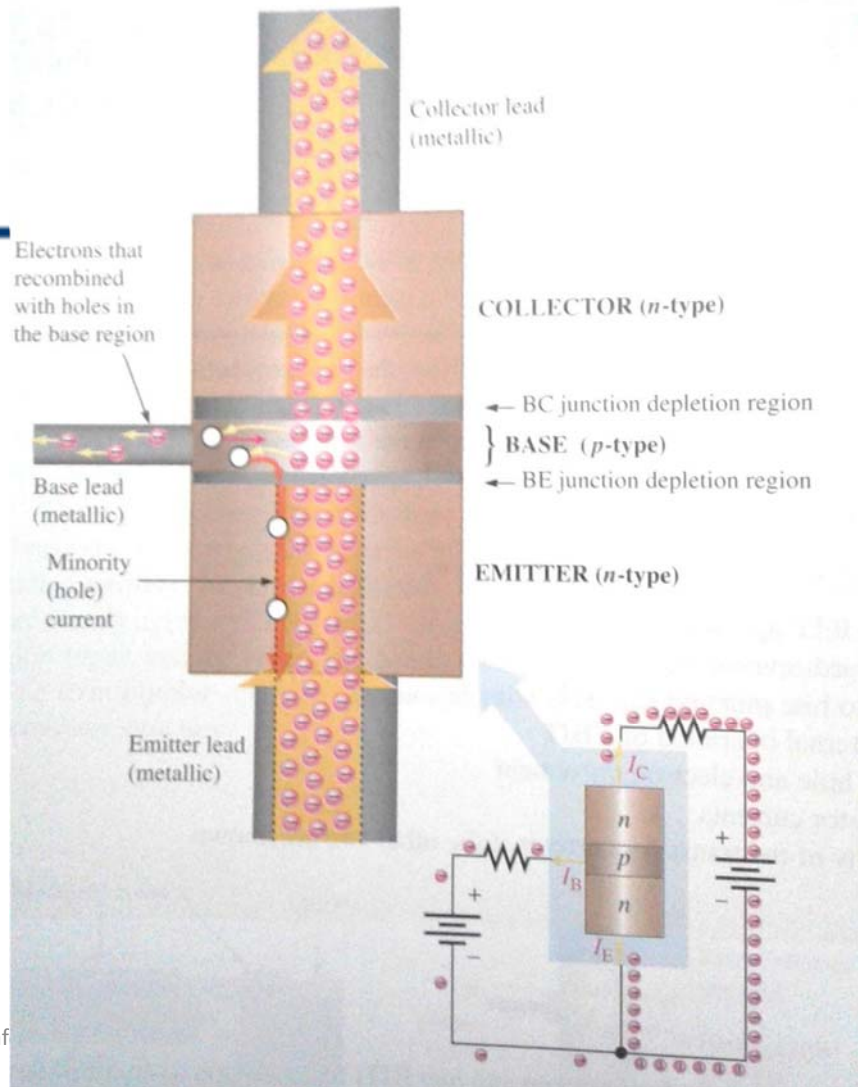- The more +ve potential applied to base from BE battery +ve terminal, a more electrons being transferred from CE battery -ve terminal, through emitter N-region, a more electrons in turn flow to CE battery +ve terminal.




11

Dr. Ahmed ElShaf

Transistor Currents


$$I_E = I_B + I_C$$

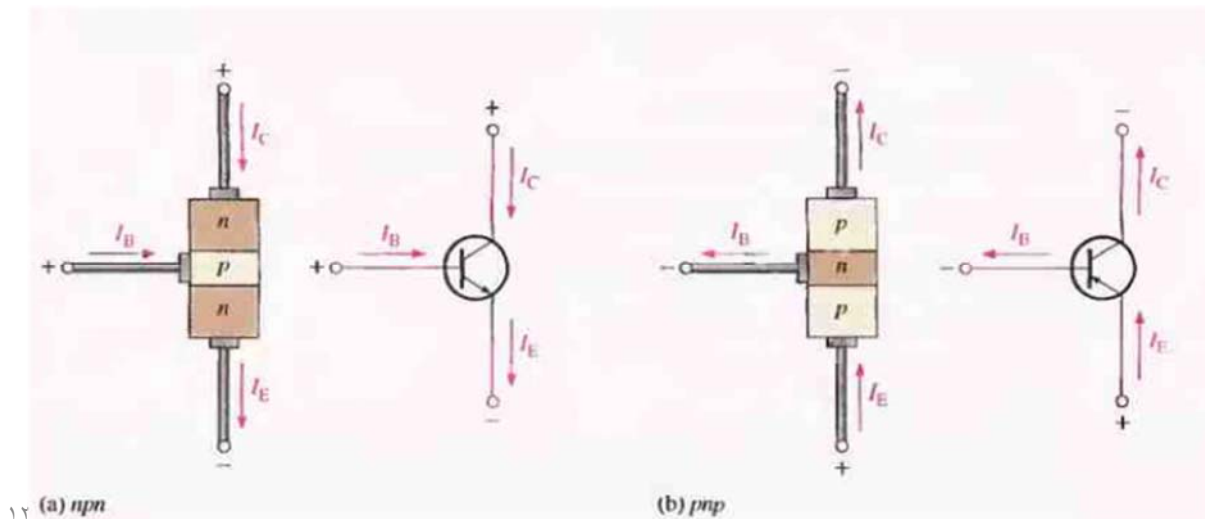


12 (a) npn

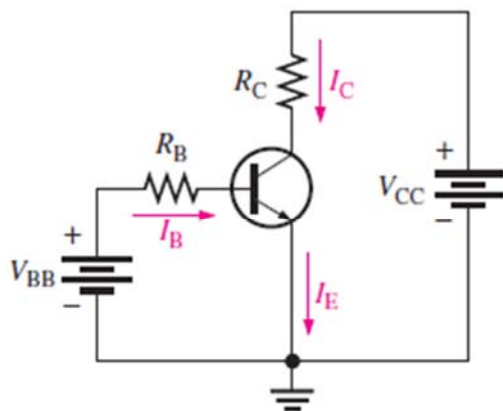(b) pnp

- V_{BB} forward-biases the base-emitter junction,
- V_{CC} reverse-biases the base-collector junction.
- In practice both V_{CC} , and V_{BB} derived from single battery with necessarily voltage divider on base terminal



١٣ (a) npn

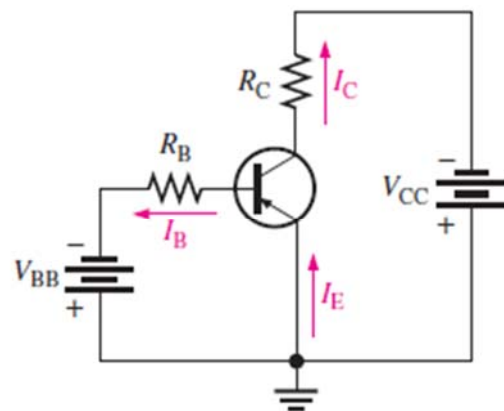

(b) pnp

- **DC Beta (β_{DC}) and DC Alpha (α_{DC})**
- DC gain called (β_{DC}) is the ratio between I_C/I_B , which called h_{FE} in data sheet, range from less than 20 to 200 or higher.

$$\beta_{DC} = \frac{I_C}{I_B}$$


$$h_{FE} = \beta_{DC}$$

- (α_{DC}) is the ratio between I_C/I_E , in range from 0.95 to 0.99 or greater

$$\alpha_{DC} = \frac{I_C}{I_E}$$

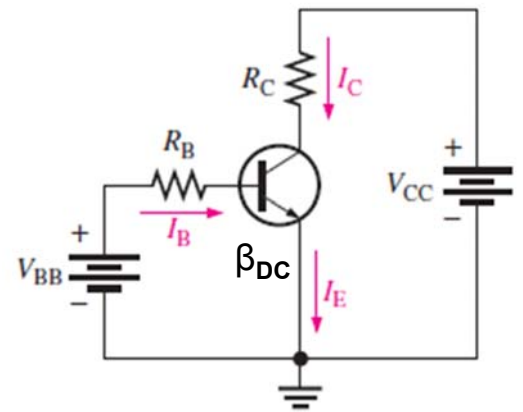Example

Determine the dc current gain β_{DC} and the emitter current I_E for a transistor where $I_B = 50 \mu\text{A}$ and $I_C = 3.65 \text{ mA}$.



10


Dr. Ahmed ElShafee, ACU : Fall 2016, Electronic Circuits I

Example

Determine the dc current gain β_{DC} and the emitter current I_E for a transistor where $I_B = 50 \mu\text{A}$ and $I_C = 3.65 \text{ mA}$.

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{3.65 \text{ mA}}{50 \mu\text{A}} = 73$$

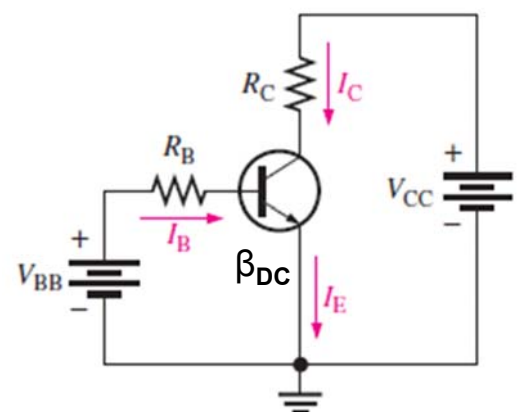
$$I_E = I_C + I_B = 3.65 \text{ mA} + 50 \mu\text{A} = 3.70 \text{ mA}$$



11

Dr. Ahmed ElShafee, ACU : Fall 2016, Electronic Circuits I

Transistor DC Model

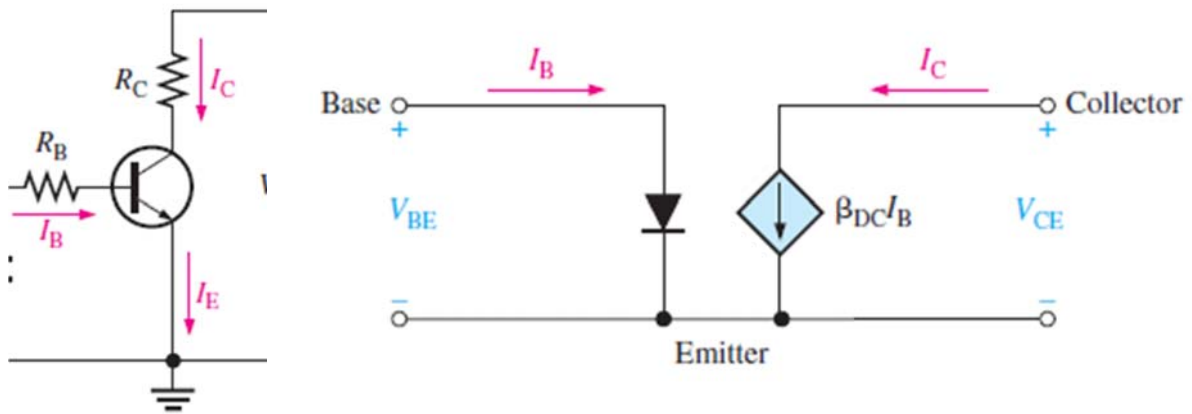

17

Dr. Ahmed ElShafee, ACU : Fall 2016, Electronic Circuits I

BJT Circuit Analysis

- V_{BB} , forward-biases the base-emitter junction, and the collector-bias voltage source, V_{CC} , reverse-biases the base-collector junction.

$$V_{BE} \cong 0.7 \text{ V}$$

- Kirchhoff's voltage law @1

$$V_{R_B} = V_{BB} - V_{BE}$$

I_B : dc base current


I_E : dc emitter current

I_C : dc collector current

V_{BE} : dc voltage at base with respect to emitter

V_{CB} : dc voltage at collector with respect to base

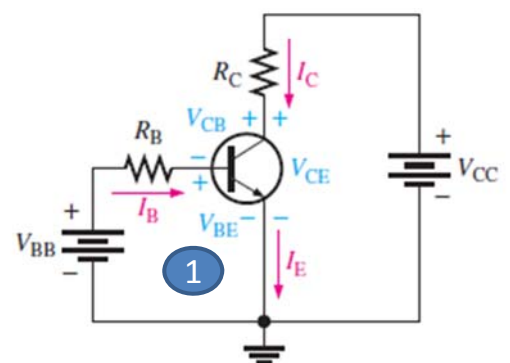V_{CE} : dc voltage at collector with respect to emitter



18

Dr. Ahmed ElShafee, ACU

- Ohm's law

$$V_{R_B} = I_B R_B$$

- Substitute

$$I_B R_B = V_{BB} - V_{BE}$$

- Finally

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

I_B : dc base current


I_E : dc emitter current

I_C : dc collector current

V_{BE} : dc voltage at base with respect to emitter

V_{CB} : dc voltage at collector with respect to base

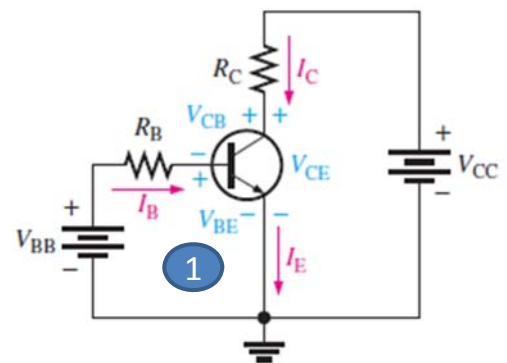V_{CE} : dc voltage at collector with respect to emitter



- KVL @ 2

$$-V_{CC} + V_{R_C} + V_{CE} = 0$$

$$V_{CE} = V_{CC} - V_{R_C}$$

- Ohm's

$$V_{R_C} = I_C R_C$$

- Substitute

$$V_{CE} = V_{CC} - I_C R_C$$

- But

$$I_C = \beta_{DC} I_B$$

I_B : dc base current


I_E : dc emitter current

I_C : dc collector current

V_{BE} : dc voltage at base with respect to emitter

V_{CB} : dc voltage at collector with respect to base

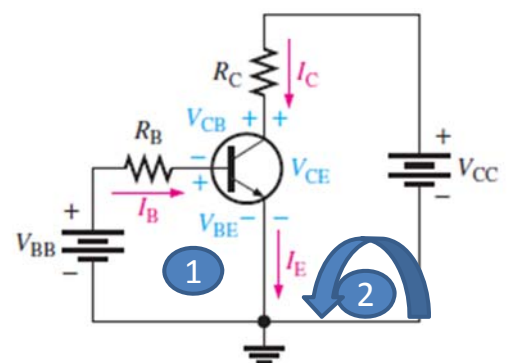
V_{CE} : dc voltage at collector with respect to emitter



- Consider the transistor itself


$$V_{CE} = V_{CB} + V_{BE}$$

$$V_{CB} = V_{CE} - V_{BE}$$

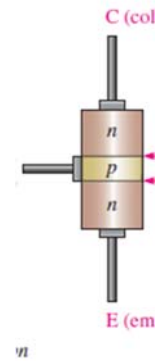

Example 02

Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the circuit of Figure 4–9. The transistor has a $\beta_{DC} = 150$.

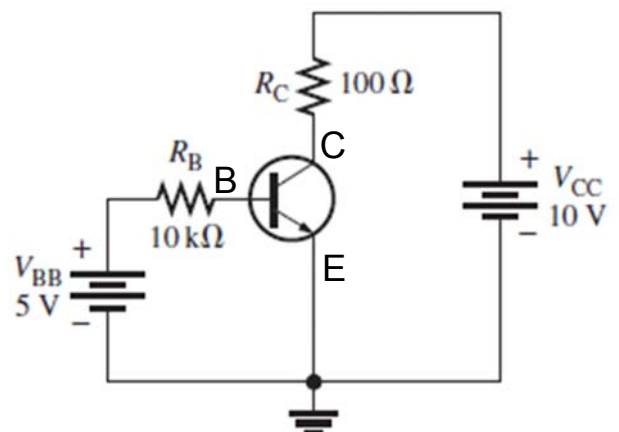

Example 02

Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the circuit of Figure 4–9. The transistor has a $\beta_{DC} = 150$.


Answer

$$V_{BE} \cong 0.7 \text{ V.}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 430 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (150)(430 \mu\text{A}) = 64.5 \text{ mA}$$
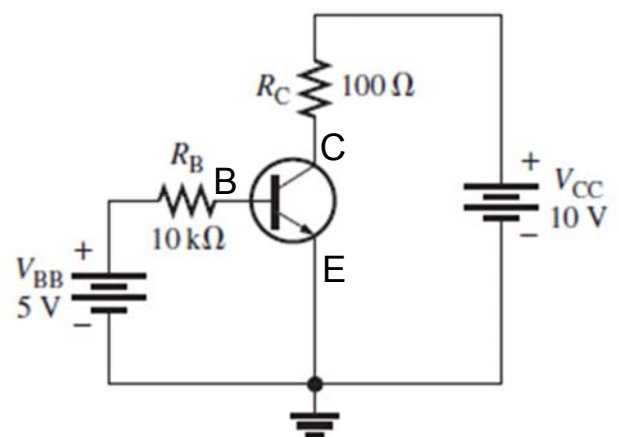
$$I_E = I_C + I_B = 64.5 \text{ mA} + 430 \mu\text{A} = 64.9 \text{ mA}$$



٢٣

Dr. Ahmed ElShafee, ACU : Fall 2016


Example 02

Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the circuit of Figure 4–9. The transistor has a $\beta_{DC} = 150$.

Answer

$$V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (64.5 \text{ mA})(100 \Omega) = 10 \text{ V} - 6.45 \text{ V} = 3.55 \text{ V}$$
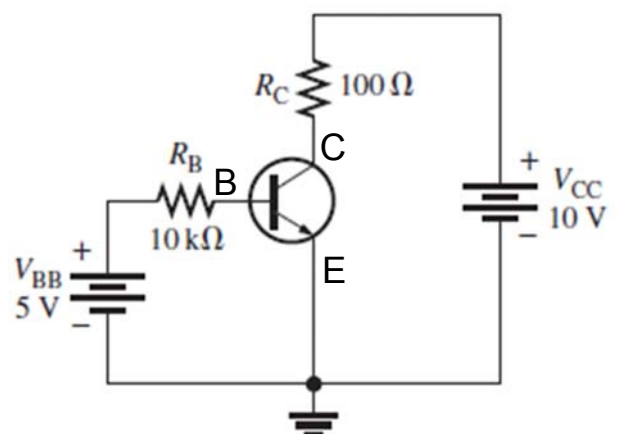
$$V_{CB} = V_{CE} - V_{BE} = 3.55 \text{ V} - 0.7 \text{ V} = 2.85 \text{ V}$$



٢٤

Dr. Ahmed ElShafee, ACU : Fall 2016



Thanks,..
See you next week (ISA),...

Dr. Ahmed ElShafee, ACU : Fall 2016, Electronic Circuits I