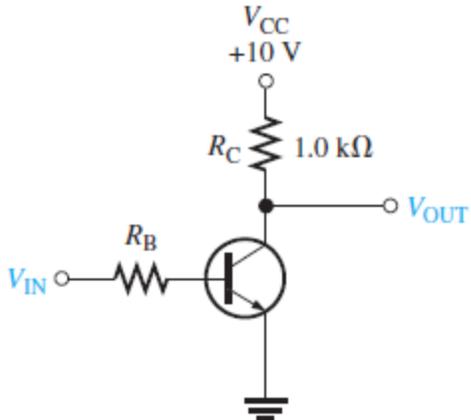
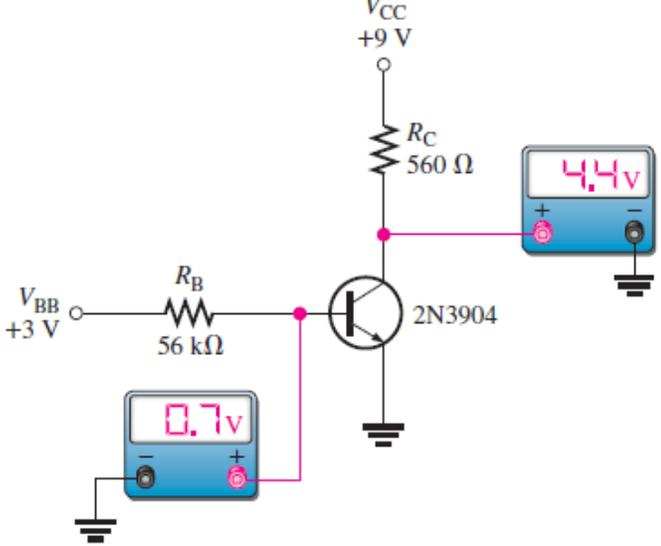


# Electronic Circuits - Tutorial 08


## BJT transistor 2

#	Question	
1	cutoff and saturation are the two normal states of a linear transistor amplifier.	F
2	When a transistor is saturated, the collector current is maximum.	T
3	Voltage gain of a transistor amplifier depends on the collector resistor and the internal acresistance.	T
4	A transistor in cutoff acts as an open switch.	T


MCQ

#	Question	
1	 <p>If the transistor in Figure is saturated and the base current is increased, the collector current will  <b>(a) increase (b) decrease (c) not change</b></p>	c
2	 <p>If the transistor in Figure is open from collector to emitter, the voltage across <math>R_C</math> will  <b>(a) increase (b) decrease (c) not change</b></p>	b

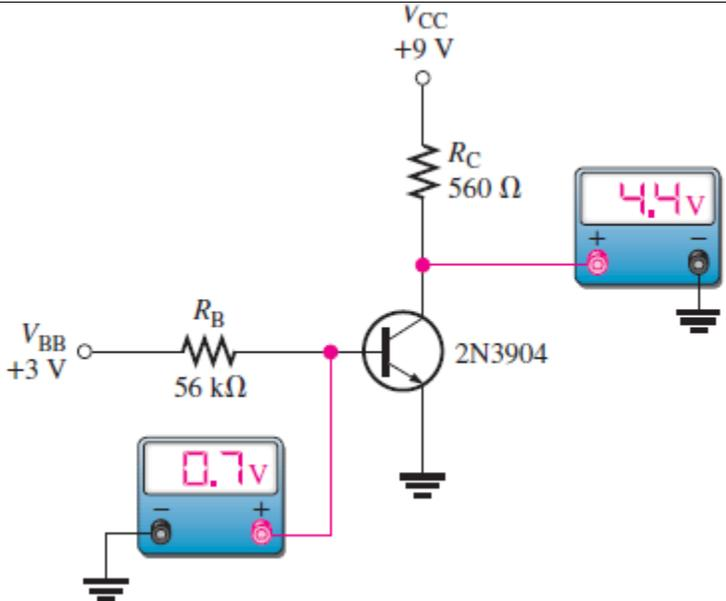

3	 <p>If the base resistor in Figure is open, the transistor collector voltage will  <b>(a) increase (b) decrease (c) not change</b></p>	a
4	<p>In a given transistor amplifier, <math>R_C = 2.2 \text{ k}\Omega</math> and <math>r'_e = 20 \Omega</math>, the voltage gain is  <b>(a) 2.2 (b) 110 (c) 20 (d) 44</b></p>	b
5	<p>In cutoff, <math>V_{CE}</math> is  <b>(a) 0 V (b) minimum (c) maximum</b></p>	f
6	<p>To saturate a BJT,  <b>(a) <math>I_B = I_{C(sat)}</math> (b) <math>I_B &gt; I_{C(sat)}/\beta_{DC}</math></b>  <b>(c) <math>V_{CC}</math> must be at least 10 V (d) the emitter must be grounded</b></p>	b
7	<p>In a phototransistor, base current is  <b>(a) set by a bias voltage (b) directly proportional to light intensity</b>  <b>(c) inversely proportional to light intensity (d) not a factor</b></p>	b
8	<p>An optocoupler usually consists of  <b>(a) two LEDs (b) an LED and a photodiode</b>  <b>(c) an LED and a phototransistor (d) both (b) and (c)</b></p>	d
9	<p>A DMM measuring on open transistor junction shows  <b>(a) 0 V (b) 0.7 V (c) OL (d) <math>V_{CC}</math></b></p>	c


10

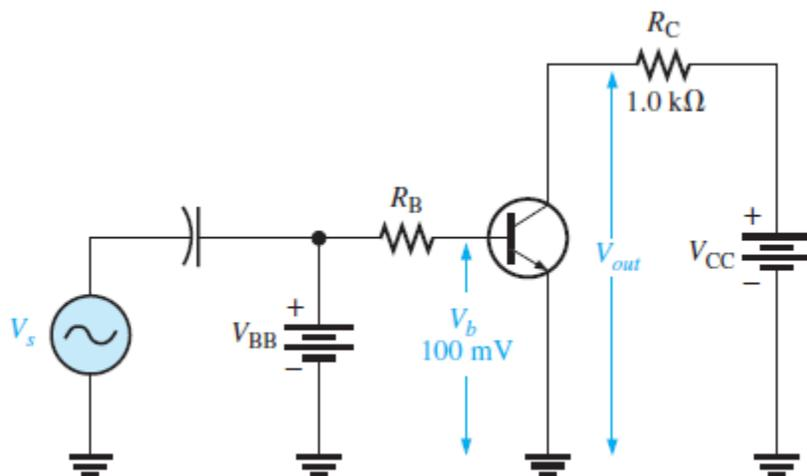

If the amplitude of  $V_{in}$  in Figure is decreased, the ac output voltage amplitude will  
(a) increase (b) decrease (c) not change



b

11

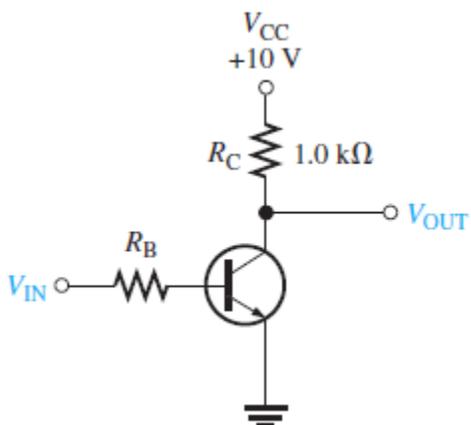

$R_C$  in Figure is reduced in value, the value of  $I_{C(sat)}$  will  
(a) increase (b) decrease (c) not change

a

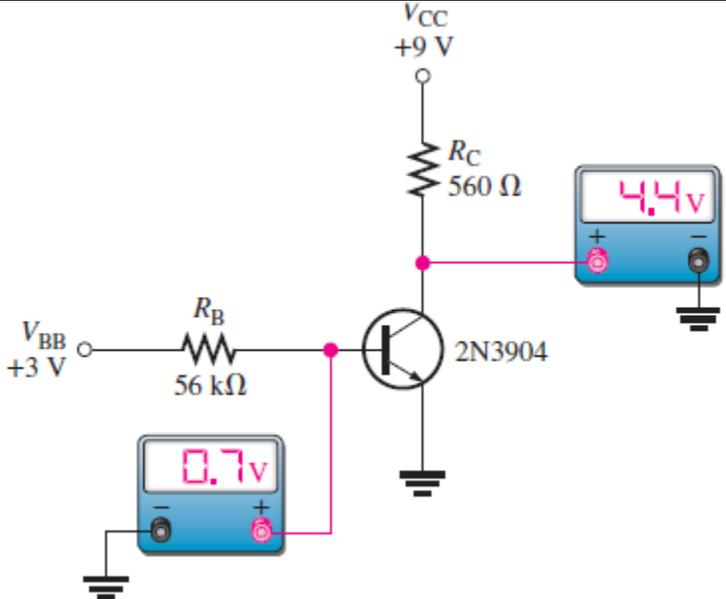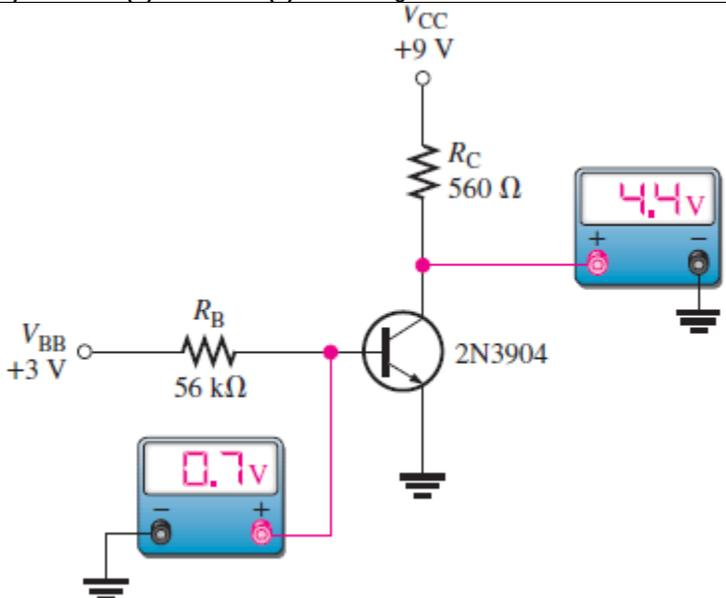12	 <p>If the transistor in Figure is open from collector to emitter, the collector voltage will (a) increase (b) decrease (c) not change</p>	a
13	 <p>If the emitter in Figure becomes disconnected from ground, the collector voltage will (a) increase (b) decrease (c) not change</p>	a
14	When operated in cutoff and saturation, the transistor acts like a (a) linear amplifier (b) switch (c) variable capacitor (d) variable resistor	b
15	In saturation, $V_{CE}$ is (a) 0.7 V (b) equal to $V_{CC}$ (c) minimum (d) maximum	c
16	Once in saturation, a further increase in base current will (a) cause the collector current to increase (b) not affect the collector current (c) cause the collector current to decrease (d) turn the transistor off	b
17	The relationship between the collector current and a light-generated base current is (a) $I_C = \beta_{DC} I_\lambda$ (b) $I_C = \alpha_{DC} I_\lambda$ (c) $I_C = \lambda I_\lambda$ (d) $I_C = \beta_{DC}^2 I_\lambda$	a



كلية الهندسة



جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY


*Faculty of Engineering*

18	In a transistor amplifier, if the base-emitter junction is open, the collector voltage is (a) $V_{CC}$ (b) 0 V (c) floating (d) 0.2 V	a
----	--	---




Problems:

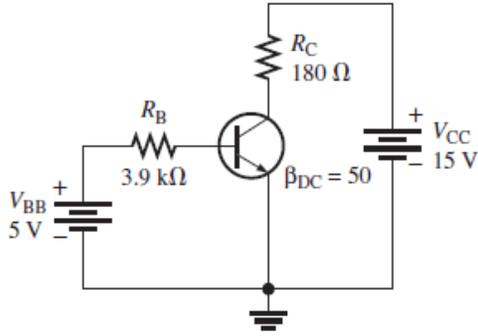Q1 Find  $V_{CE}$ ,  $V_{BE}$ , and  $V_{CB}$  in both circuits of Figure 4–55.



(a)

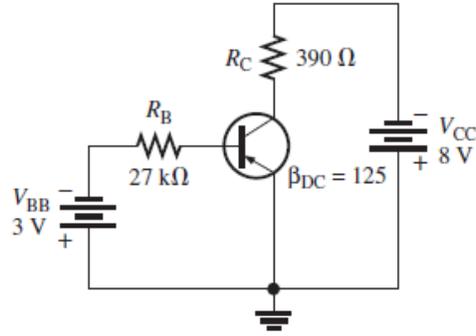

(b)

Sol  
1

..... (a)  $V_{BE} = 0.7 \text{ V}, V_{CE} = 5.10 \text{ V}, V_{CB} = 4.40 \text{ V}$  .....

..... (b)  $V_{BE} = -0.7 \text{ V}, V_{CE} = -3.83 \text{ V}, V_{CB} = -3.13 \text{ V}$  .....

































