



كلية الهندسة

Faculty of Engineering



جامعة الأهرام الكندية
AHRAM CANADIAN UNIVERSITY



Electronic Circuits II – Tutorial



01

T & F

1	The linear region of a transistor's operation lies between saturation and cutoff.	T
2	Voltage-divider bias is rarely used.	F
3	Input resistance at the base of the transistor can affect voltage-divider bias.	T
4	Stiff voltage-divider bias is essentially independent of base loading.	T


MCQ
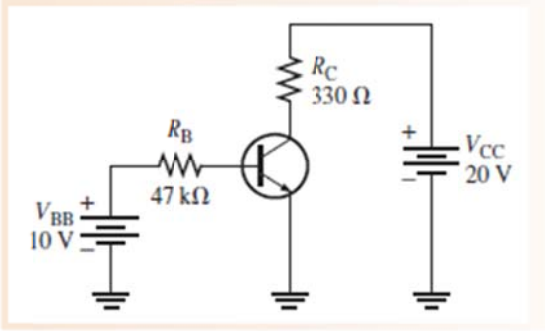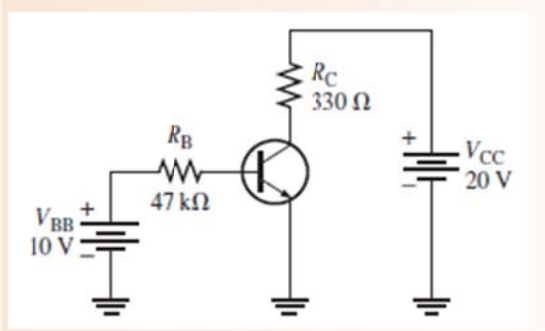
#	Question	
1	<p>If V_{BB} in Figure is increased, the Q-point value of collector current will</p>  <p>(a) increase (b) decrease (c) not change</p>	a
2	<p>If V_{BB} in Figure is increased, the Q-point value of V_{CE} will</p>  <p>(a) increase (b) decrease (c) not change</p>	b

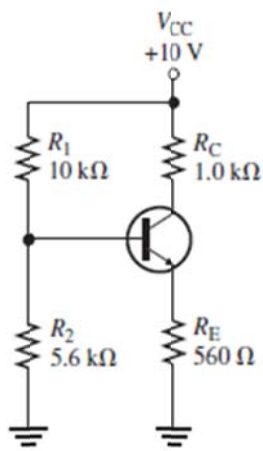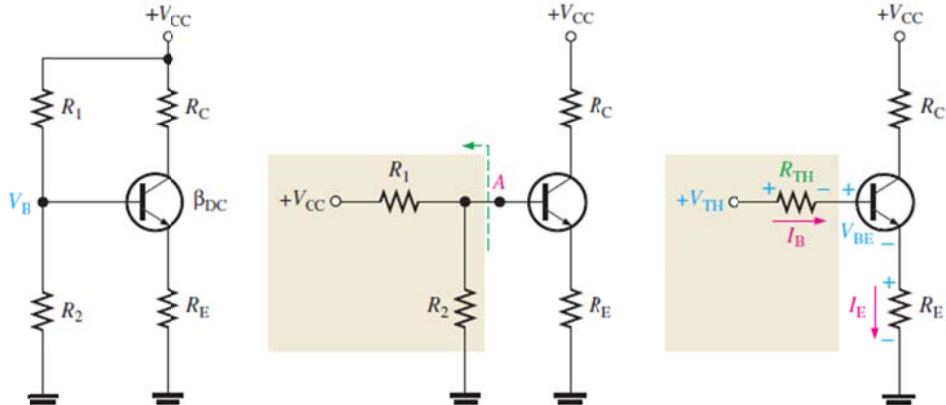3	<p>If the value of R_2 in Figure is reduced, the base voltage will</p>  <p>(a) increase (b) decrease (c) not change</p>	b
4	<p>The maximum value of collector current in a biased transistor is</p> <p>(a) $\beta_{DC} I_B$ (b) $I_{C(sat)}$ (c) greater than I_E (d) $I_E - I_B$</p>	b
5	<p>If a sinusoidal voltage is applied to the base of a biased <i>nnpn</i> transistor and the resulting sinusoidal collector voltage is clipped near zero volts, the transistor is</p> <p>(a) being driven into saturation (b) being driven into cutoff (c) operating nonlinearly (d) answers (a) and (c) (e) answers (b) and (c)</p>	d
6	 <p>In a voltage-divider biased transistor circuit such as in Figure . $R_{IN(BASE)}$ can generally be neglected in calculations when</p> <p>(a) $R_{IN(BASE)} > R_2$ (b) $R_2 > 10R_{IN(BASE)}$ (c) $R_{IN(BASE)} > 10R_2$ (d) $R_1 \ll R_2$</p>	c


7	<p>Voltage-divider bias</p> <p>(a) cannot be independent of β_{DC} (b) can be essentially independent of β_{DC}</p> <p>(c) is not widely used (d) requires fewer components than all the other methods</p>	b
---	--	---

Problems

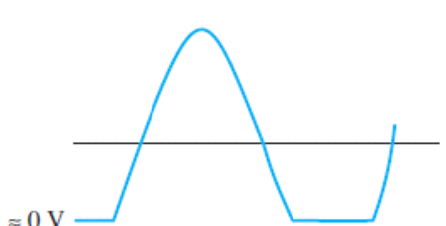Q1	<p>The output (collector voltage) of a biased transistor amplifier is shown in Figure . Is the transistor biased too close to cutoff or too close to saturation?</p> <div style="text-align: center;">  </div>
Sol 1	<p>.....</p> <div style="border: 1px solid black; height: 40px; width: 500px; margin: 0 auto;"></div> <p>.....</p>

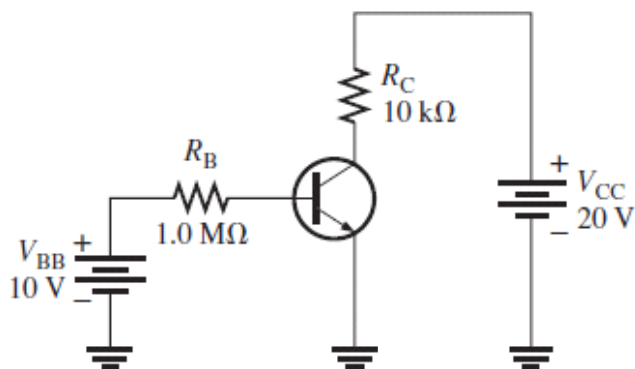Q
2

Determine the intercept points of the dc load line on the vertical and horizontal axes of collector-characteristic curves for the circuit in Figure




So
12

.....
 $V_{CE} = 20 \text{ V}; I_{C(\text{sat})} = 2 \text{ mA}$

Q4

► FIGURE

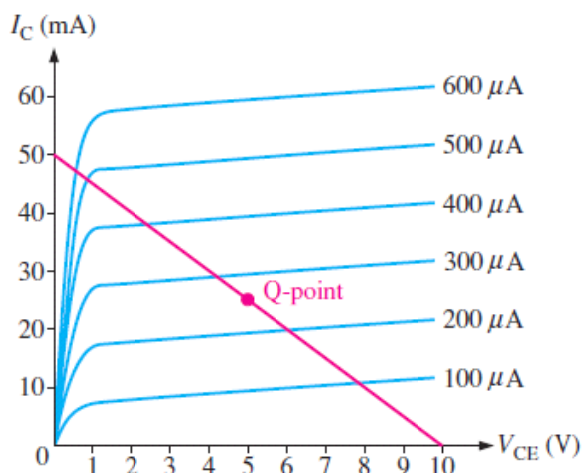


From the collector characteristic curves and the dc load line in Figure , determine the following:

- (a) Collector saturation current
- (b) V_{CE} at cutoff
- (c) Q-point values of I_B , I_C , and V_{CE}

Sol
4

-
- ... (a) $I_{C(sat)} = 50$ mA
- ... (b) $V_{CE(CUTOFF)} = 10$ V
- ... (c) $I_B = 250 \mu A; I_C = 25$ mA; $V_{CE} = 5$ V
-
-
-

Q5

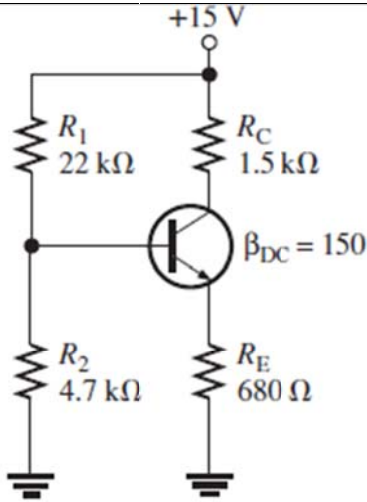

What is the minimum value of β_{DC} in Figure that makes $R_{IN(BASE)} \cong 10R_2$?

Sol
5

.....

.....

.....


.....

.....

.....


.....

Q6

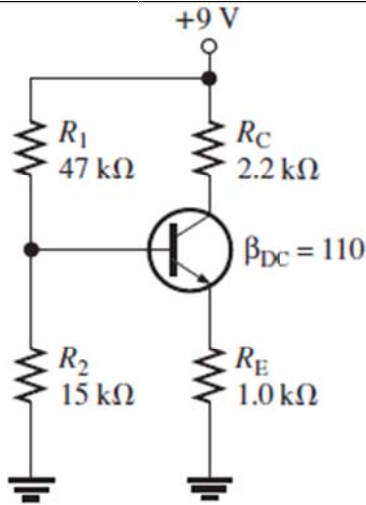


Show the connections required to replace the transistor in Figure ' ' with a *pn*p device.

Sol
6

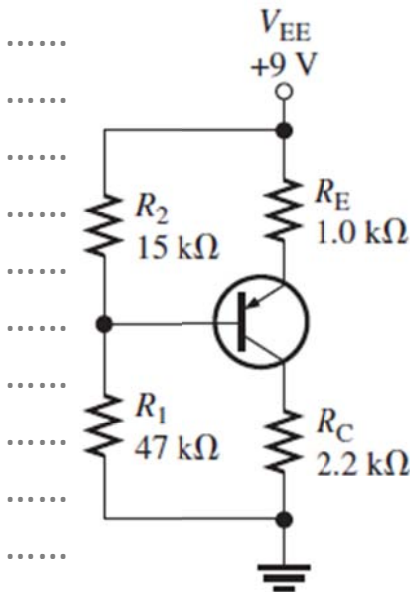

Q7

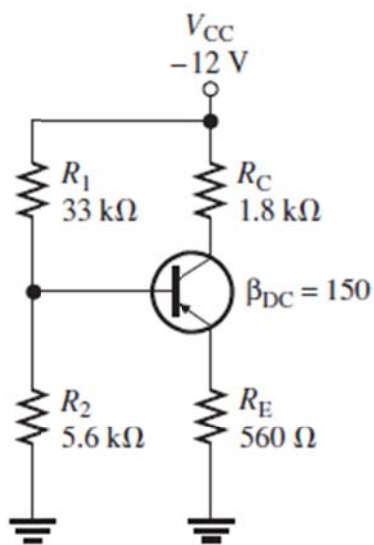

Determine the following in Figure :

- (a) Q-point values
- (b) The minimum power rating of the transistor

Sol
7

.....

.....

.....

.....

.....

.....

.....