



FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY

جامعة الاهرام الكندية  
كلية الهندسة

Faculty of Engineering




# Electronic Circuits II -

## Tutorial 06

# BJT Amplifiers 1

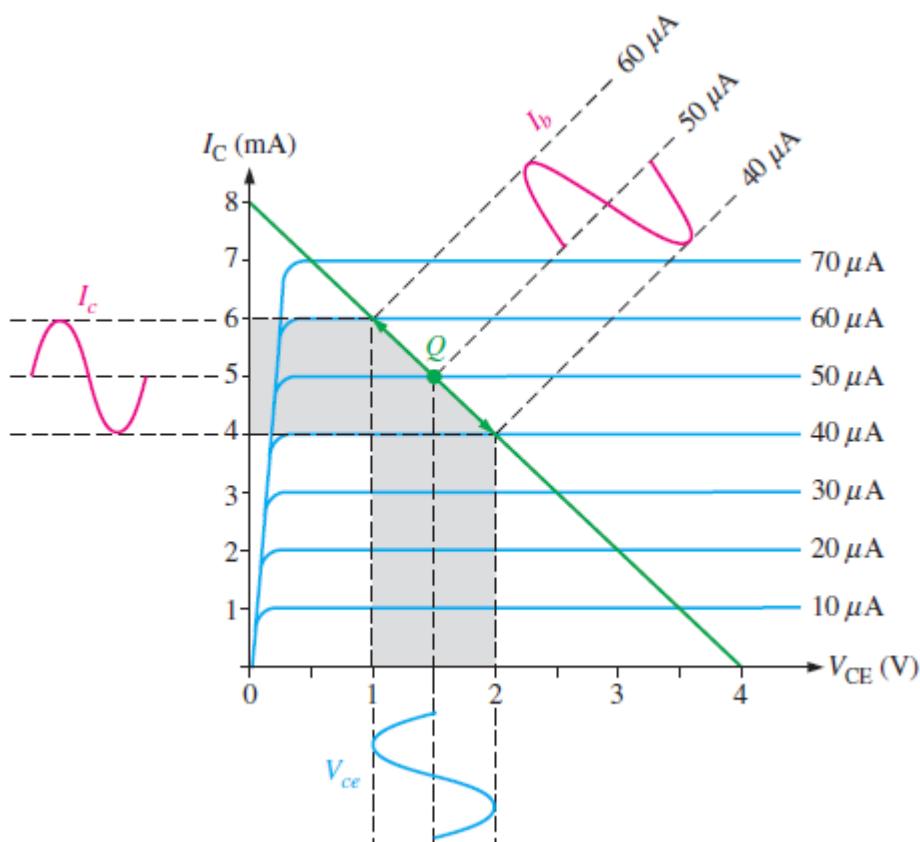Q1

What is the lowest value of dc collector current to which a transistor having the characteristic curves in Figure 1 can be biased and still retain linear operation with a peak-to-peak base current swing of  $20 \mu\text{A}$ ?



Sol  
1

Less than 2 mA and greater than 1 mA



---

## *Faculty of Engineering*



---

## *Faculty of Engineering*



---

## *Faculty of Engineering*



## Faculty of Engineering



FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY

جامعة الاهرام الكندية  
كلية الهندسة



## Faculty of Engineering

Q6

At the dc bias point of a certain transistor circuit,  $I_B = 15 \mu\text{A}$  and  $I_C = 2 \text{ mA}$ . Also, a variation in  $I_B$  of  $3 \mu\text{A}$  about the Q-point produces a variation in  $I_C$  of  $0.35 \text{ mA}$  about the Q-point. Determine  $\beta_{DC}$  and  $\beta_{ac}$ .

Sol  
6

$$DC = 133.33$$

$$AC=116.67$$