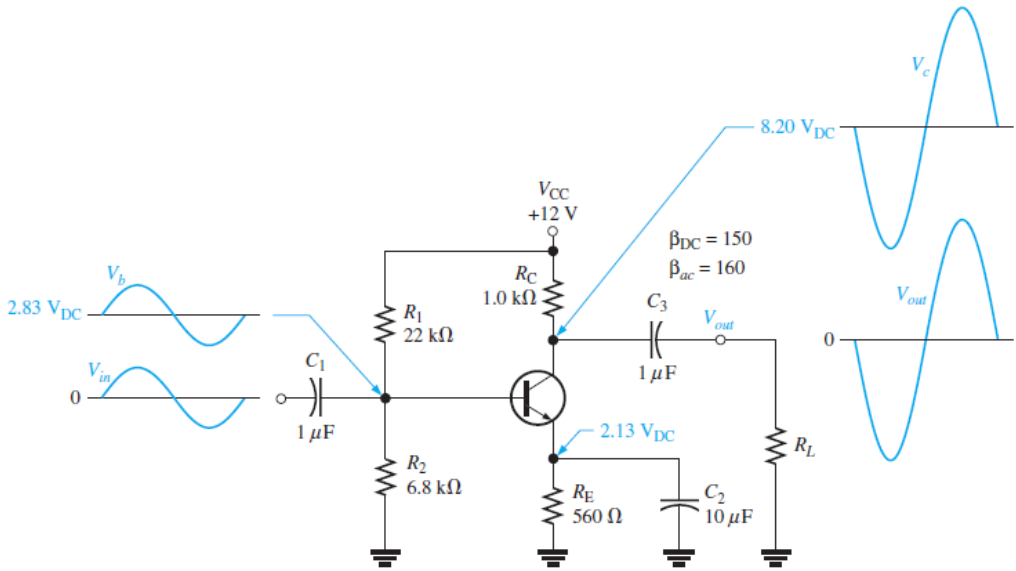


# Electronic Circuits II - Tutorial 07

## BJT Amplifiers 2

#		
1	In an amplifier, a coupling capacitor should appear ideally as a short to the signal.	T
2	r parameters include	T
3	h parameters are never specified on a datasheet.	F
4	The r parameter is the same as the h parameter hfe.	T
5	A bypass capacitor in a CE amplifier decreases the voltage gain.	F
6	If RC in a CE amplifier is increased, the voltage gain is reduced.	F
7	The load is the amount of current drawn from the output of an amplifier.	T
8	In a CE amplifier, the gain can be stabilized by using a swamping resistor.	T
9	An emitter-follower is a CC amplifier.	T
10	A CC amplifier has high voltage gain.	F
11	A Darlington pair consists essentially of two CC amplifiers.	T
12	A CB amplifier has high current gain.	F
13	The overall voltage gain of a multistage amplifier is the product of the gains of each stage.	T
14	A differential amplifier amplifies the difference of two input signals.	T
15	CMRR is the common-mode resistance ratio.	F

MCQ

#	Question	Answer
1	 <p>If the transistor in Figure is exchanged for one with higher betas, Vout will</p>	a



	(a) increase (b) decrease (c) not change	
2	<p>If C2 is removed from the circuit in Figure, Vout will (a) increase (b) decrease (c) not change</p> <p>2.83 V<sub>DC</sub> <math>V_b</math> 0 <math>V_{in}</math> 1 <math>\mu\text{F}</math> <math>C_1</math> 22 k<math>\Omega</math> <math>R_1</math> 6.8 k<math>\Omega</math> <math>R_2</math> +12 V <math>V_{CC}</math> 1.0 k<math>\Omega</math> <math>R_C</math> 150 <math>\beta_{DC}</math> 160 <math>\beta_{ac}</math> 1 <math>\mu\text{F}</math> <math>C_3</math> <math>V_{out}</math> 10 <math>\mu\text{F}</math> <math>C_2</math> 560 <math>\Omega</math> <math>R_E</math> 2.13 V<sub>DC</sub> <math>R_L</math> 8.20 V<sub>DC</sub> <math>V_c</math> 0</p>	b
3	<p>If the value of RC in Figure is increased, Vout will (a) increase (b) decrease (c) not change</p> <p>2.83 V<sub>DC</sub> <math>V_b</math> 0 <math>V_{in}</math> 1 <math>\mu\text{F}</math> <math>C_1</math> 22 k<math>\Omega</math> <math>R_1</math> 6.8 k<math>\Omega</math> <math>R_2</math> +12 V <math>V_{CC}</math> 1.0 k<math>\Omega</math> <math>R_C</math> 150 <math>\beta_{DC}</math> 160 <math>\beta_{ac}</math> 1 <math>\mu\text{F}</math> <math>C_3</math> <math>V_{out}</math> 10 <math>\mu\text{F}</math> <math>C_2</math> 560 <math>\Omega</math> <math>R_E</math> 2.13 V<sub>DC</sub> <math>R_L</math> 8.20 V<sub>DC</sub> <math>V_c</math> 0</p>	a



4	<p>If the amplitude of <math>V_{in}</math> in Figure is decreased, <math>V_{out}</math> will (a) increase (b) decrease (c) not change</p>	b
5	<p>If <math>C_2</math> in Figure is shorted, the average value of the output voltage will (a) increase (b) decrease (c) not change</p>	a



6	<p>If the value of <math>R_E</math> in Figure is increased, the voltage gain will (a) increase (b) decrease (c) not change</p>	c
7	<p>If the value of <math>C_1</math> in Figure is increased, <math>V_{out}</math> will (a) increase (b) decrease (c) not change</p>	c



8	<p>If the value of <math>R_C</math> in Figure is increased, the current gain will (a) increase (b) decrease (c) not change</p>	c
9	<p><math>\beta_{DC} = \beta_{ac} = 150</math> for <math>Q_1</math> and <math>Q_2</math></p> <p>If <math>C_2</math> and <math>C_4</math> in Figure are increased in value, <math>V_{out}</math> will (a) increase (b) decrease (c) not change</p>	c



10	<p style="text-align: center;"><math>\beta_{DC} = \beta_{ac} = 150</math> for <math>Q_1</math> and <math>Q_2</math></p> <p>If the value of <math>R_4</math> in Figure is reduced, the overall voltage gain will (a) increase (b) decrease (c) not change</p>	C
11	<p>1. A small-signal amplifier (a) uses only a small portion of its load line (b) always has an output signal in the mV range (c) goes into saturation once on each input cycle (d) is always a common-emitter amplifier</p>	a
12	<p>The parameter <math>h_{fe}</math> corresponds to (a) <math>\beta_{DC}</math> (b) <math>\beta_{ac}</math> (c) <math>r'_e</math> (d) <math>r'_c</math></p>	b
13	<p>If the dc emitter current in a certain transistor amplifier is 3 mA, the approximate value of <math>r'_e</math> is (a) 3 kΩ (b) 3 Ω (c) 8.33 Ω (d) 0.33 kΩ</p>	c
14	<p>A certain common-emitter amplifier has a voltage gain of 100. If the emitter bypass capacitor is removed, (a) the circuit will become unstable (b) the voltage gain will decrease (c) the voltage gain will increase (d) the Q-point will shift</p>	b
15	<p>For a common-emitter amplifier, <math>R_C = 1.0</math> kΩ, <math>R_E = 390</math> Ω, <math>r'_e = 15</math> Ω, and <math>\beta_{ac} = 75</math>. Assuming that <math>R_E</math> is completely bypassed at the operating frequency, the voltage gain is (a) 66.7 (b) 2.56 (c) 2.47 (d) 75</p>	a
16	<p>For a common-emitter amplifier, <math>R_C = 1.0</math> kΩ, <math>R_E = 390</math> Ω, <math>r'_e = 15</math> Ω, and <math>\beta_{ac} = 75</math>. , if the frequency is reduced to the point where <math>X_{C(bypass)} = R_E</math>, the voltage gain - - (a) remains the same (b) is less (c) is greater</p>	b
17	<p>In a common-emitter amplifier with voltage-divider bias, <math>R_{in(base)} = 68</math> kΩ, <math>R_1 = 33</math> kΩ, and <math>R_2 = 15</math> kΩ. The total ac input resistance is (a) 68 kΩ (b) 8.95 kΩ (c) 22.2 kΩ (d) 12.3 kΩ</p>	b
18	<p>A CE amplifier is driving a 10 kΩ load. If <math>R_C = 2.2</math> kΩ and <math>r'_e = 10</math> Ω, the voltage gain is approximately (a) 220 (b) 1000 (c) 10 (d) 180</p>	d



19	For a common-collector amplifier, $R_E = 100 \Omega$ , $r'_e = 10 \Omega$ , and $\beta_{ac} = 150$ . The ac input resistance at the base is (a) $1500 \Omega$ (b) $15 \text{ k}\Omega$ (c) $110 \Omega$ (d) $16.5 \text{ k}\Omega$	d
20	For a common-collector amplifier, $R_E = 100 \Omega$ , $r'_e = 10 \Omega$ , and $\beta_{ac} = 150$ . If a $10 \text{ mV}$ signal is applied to the base of the emitter-follower circuit, the output signal is approximately (a) $100 \text{ mV}$ (b) $150 \text{ mV}$ (c) $1.5 \text{ V}$ (d) $10 \text{ mV}$	d
21	In a certain emitter-follower circuit, the current gain is 50. The power gain is approximately (a) $50A_v$ (b) 50      (c) 1      (d) answers (a) and (b)	d
22	In a Darlington pair configuration, each transistor has an ac beta of 125. If $R_E$ is $560 \Omega$ , the input resistance is (a) $560 \Omega$ (b) $70 \text{ k}\Omega$ (c) $8.75 \text{ M}\Omega$ (d) $140 \text{ k}\Omega$	c
23	The input resistance of a common-base amplifier is (a) very low      (b) very high (c) the same as a CE      (d) the same as a CC	a
24	Each stage of a four-stage amplifier has a voltage gain of 15. The overall voltage gain is (a) 60      (b) 15      (c) 50,625      (d) 3078	c
25	The overall gain found in Question 14 can be expressed in decibels as (a) 94.1 dB      (b) 47.0 dB      (c) 35.6 dB      (d) 69.8 dB	a
26	A differential amplifier (a) is used in op-amps      (b) has one input and one output (c) has two outputs      (d) answers (a) and (c)	d
27	When a differential amplifier is operated single-ended, (a) the output is grounded (b) one input is grounded and a signal is applied to the other (c) both inputs are connected together (d) the output is not inverted	b
28	In the double-ended differential mode, (a) opposite polarity signals are applied to the inputs (b) the gain is 1 (c) the outputs are different amplitudes (d) only one supply voltage is used	a





FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY

كلية الهندسة

Faculty of Engineering




جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

29	In the common mode, (a) both inputs are grounded (b) the outputs are connected together (c) an identical signal appears on both inputs (d) the output signals are in-phase	c
----	--	---






Q2

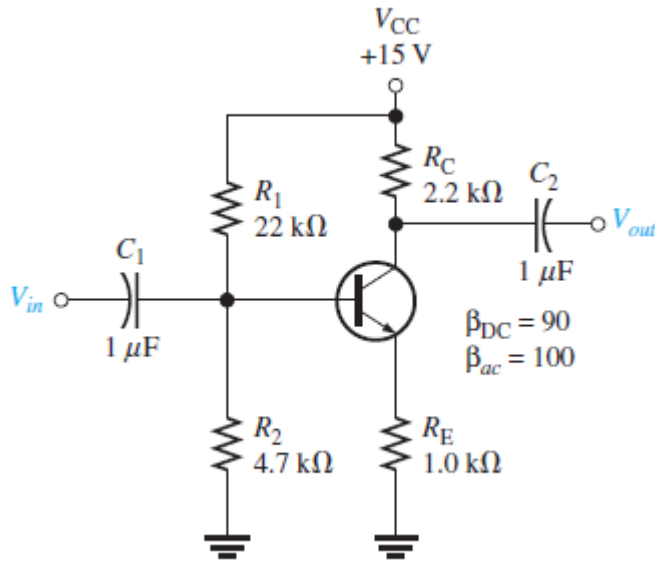


Draw the dc equivalent circuit and the ac equivalent circuit for the unloaded amplifier in Figure

Sol  
2

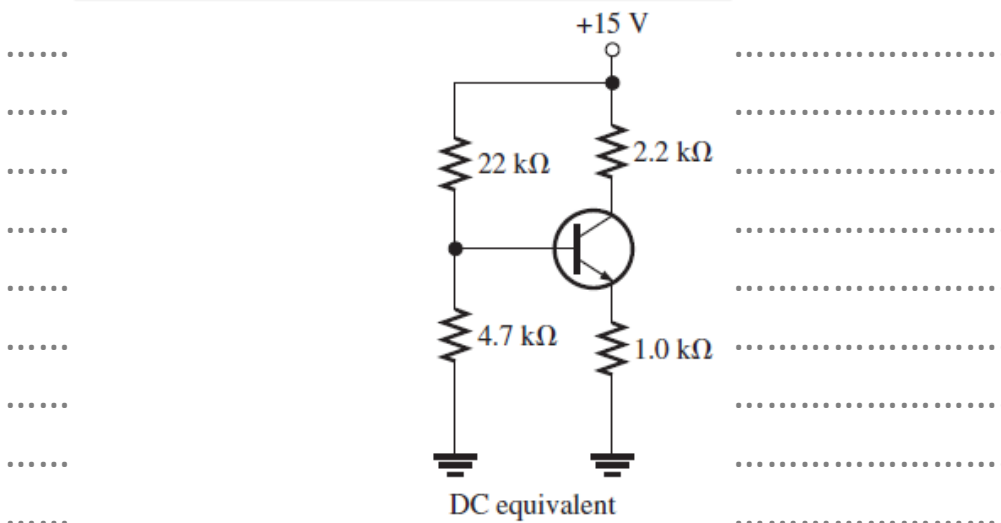

DC equivalent

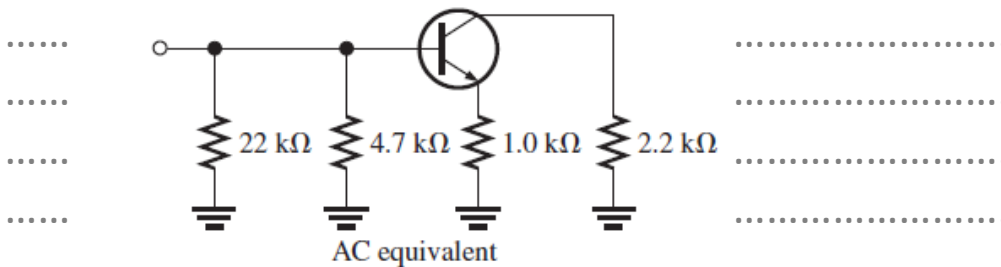

AC equivalent







كلية الهندسة

Faculty of Engineering

FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY




جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a vertical margin on the left and horizontal dotted lines for writing.



Q4

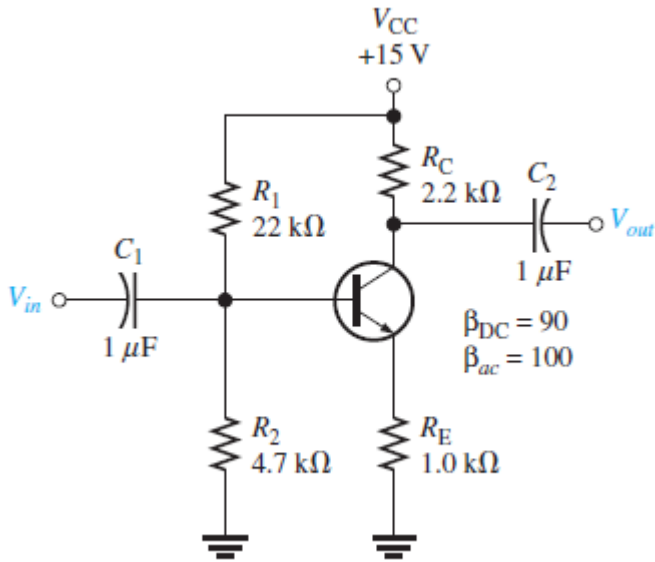


Calculate the quiescent power dissipation in Figure

Sol  
4

..... 37.5 mW .....



Q5

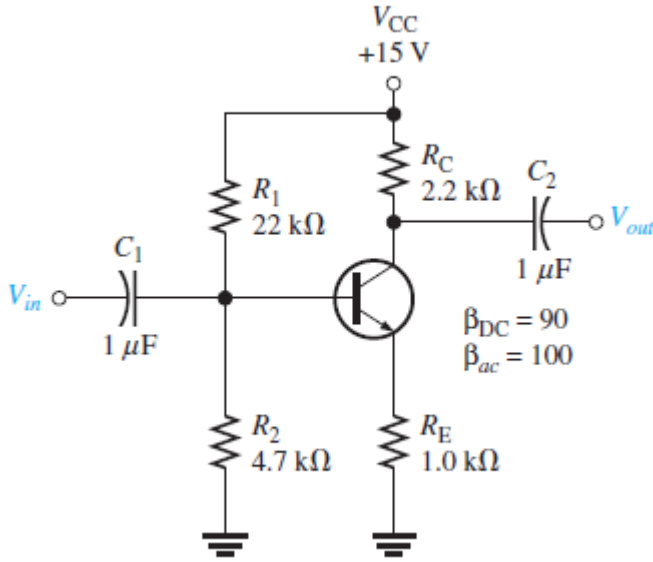

Determine the following dc values for the amplifier in Figure

- (a)  $V_B$       (b)  $V_E$       (c)  $I_E$       (d)  $I_C$       (e)  $V_C$

Sol  
5

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....





كلية الهندسة

Faculty of Engineering

FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY




جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a dotted line pattern, intended for student answers or notes.



Q6

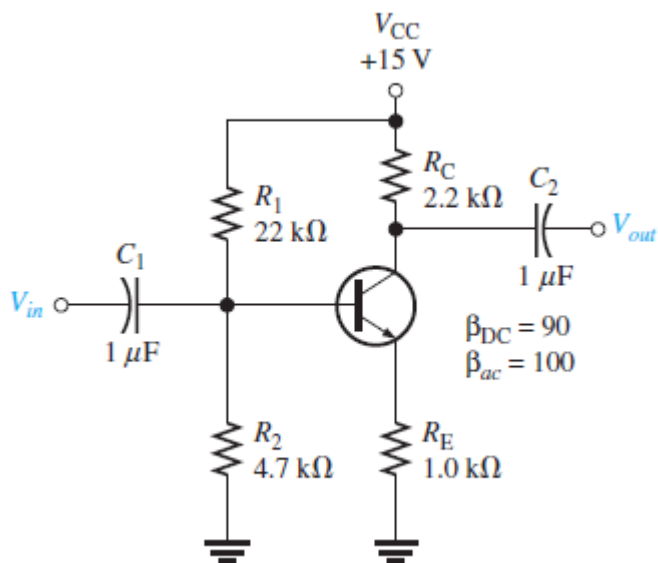

Connect a bypass capacitor across  $R_E$  in Figure , and repeat

- (a)  $R_{in(base)}$       (b)  $R_{in(tot)}$       (c)  $A_v$

Sol  
6

... (a) 1.29 kΩ      (b) 968 Ω      (c) 171 .....



كلية الهندسة

Faculty of Engineering

FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY




جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a vertical margin on the left and horizontal dotted lines for writing.



Q7

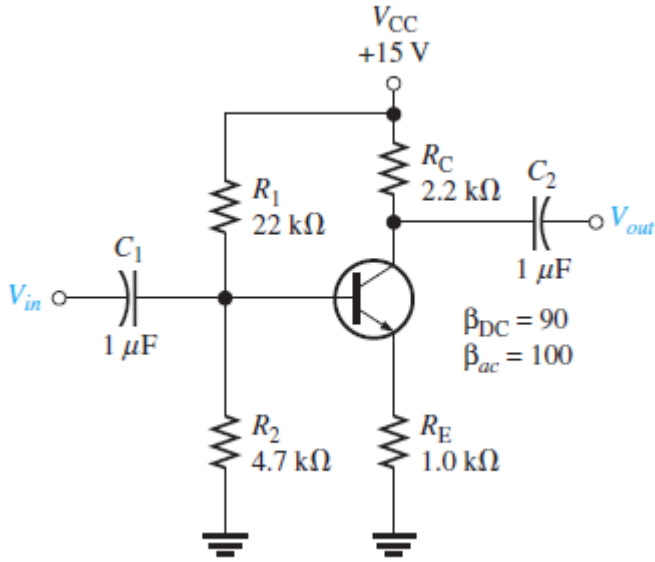

Connect a  $10\text{ k}\Omega$  load resistor to the output in Figure  
 Connect a bypass capacitor across  $R_E$  in Figure , and repeat

- (a)  $R_{in(base)}$       (b)  $R_{in(tot)}$       (c)  $A_v$

Sol  
7

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....



كلية الهندسة

Faculty of Engineering

FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY



جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a vertical margin on the left and horizontal dotted lines for writing.





FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY

كلية الهندسة

Faculty of Engineering



جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a dotted horizontal line pattern, intended for writing or drawing.







كلية الهندسة

Faculty of Engineering

FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY



جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a vertical margin on the left and horizontal dotted lines for writing.













كلية الهندسة

Faculty of Engineering

FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY



جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a vertical margin on the left and horizontal dotted lines for writing.







كلية الهندسة

Faculty of Engineering

FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY




جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a vertical margin on the left and horizontal dotted lines for writing.




Q  
14

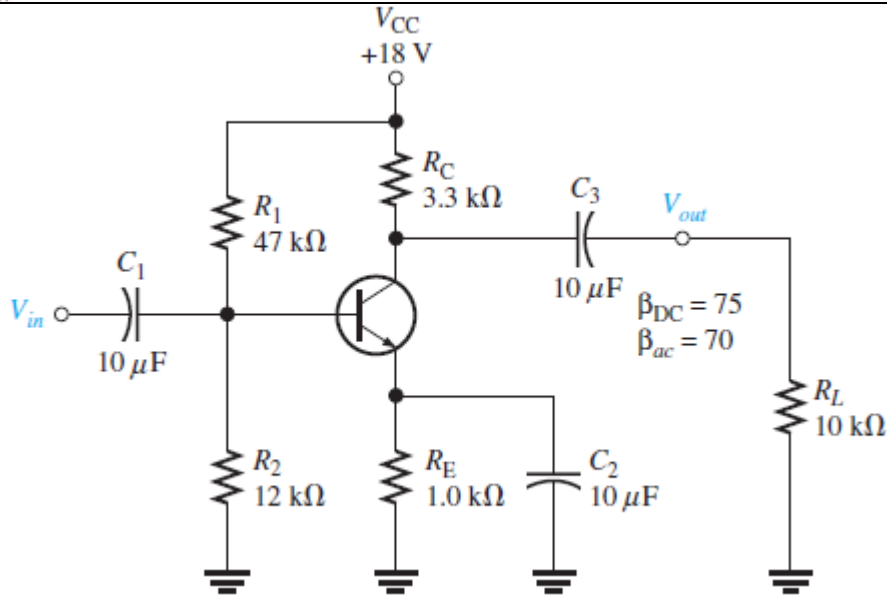

Modify the schematic to show how you would “swamp out” the temperature effects of  $r'_e$  in Figure by making  $R_e$  at least ten times larger than  $r'_e$ . Keep the same total  $R_E$ . How does this affect the voltage gain?

Sol  
14

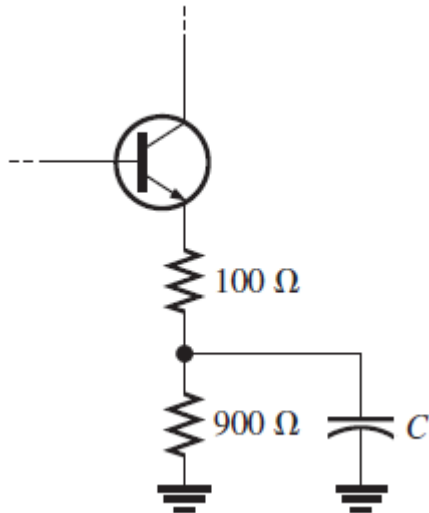



كلية الهندسة

Faculty of Engineering

FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY



جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a vertical margin on the left and horizontal dotted lines for writing.