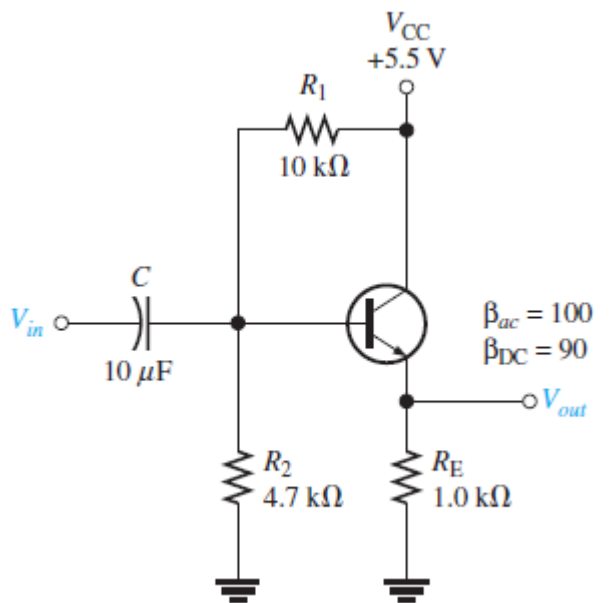



Electronic Circuits II - Tutorial 08

BJT Amplifier 3

Problems

<p>Q1</p>	<p>Determine the <i>exact</i> voltage gain for the unloaded emitter-follower in Figure</p> 
<p>Sol 1</p>	<p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p>

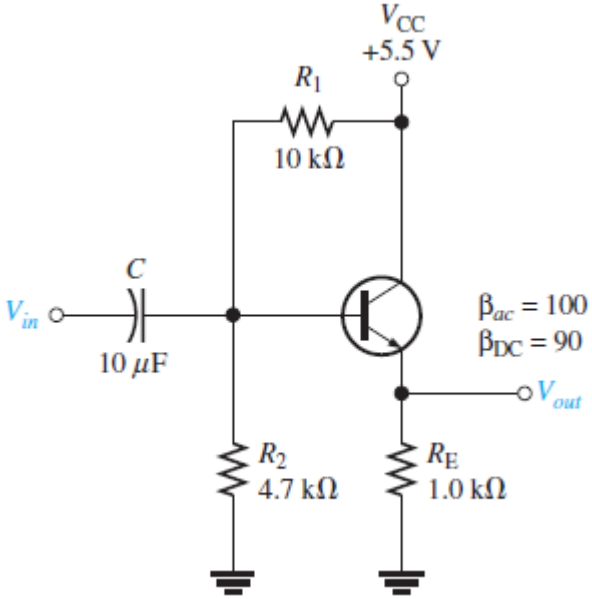Q2 What is the total input resistance in Figure ? What is the dc output voltage?



V_{in}
 C
 $10 \mu\text{F}$
 R_1
 $10 \text{ k}\Omega$
 V_{CC}
 $+5.5 \text{ V}$
 R_2
 $4.7 \text{ k}\Omega$
 $\beta_{ac} = 100$
 $\beta_{DC} = 90$
 R_E
 $1.0 \text{ k}\Omega$
 V_{out}

Sol
2

.....
 $R_{in(tot)} = 3.1 \text{ k}\Omega; V_{OUT} = 1.06 \text{ V}$


.....



Faculty of Engineering

FACULTY OF ENGINEERING
AHRAM CANADIAN UNIVERSITY

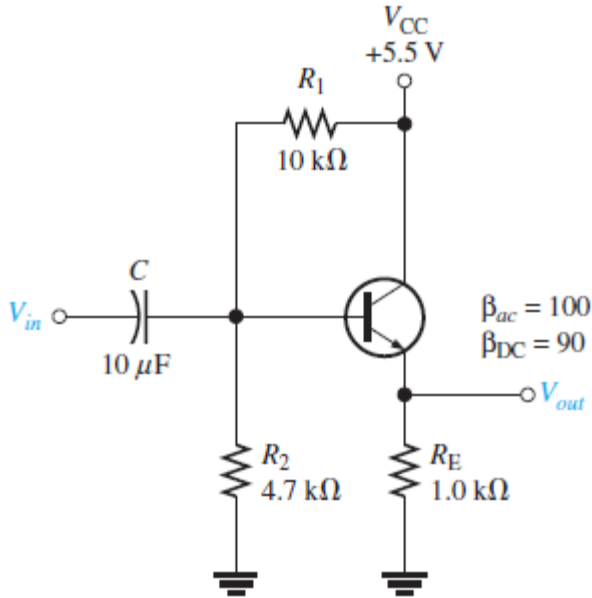Q3 A load resistance is capacitive coupled to the emitter in Figure . In terms of signal operation, the load appears in parallel with R_E and reduces the effective emitter resistance.
How does this affect the voltage gain?



Sol
3

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

.....

.....

.....

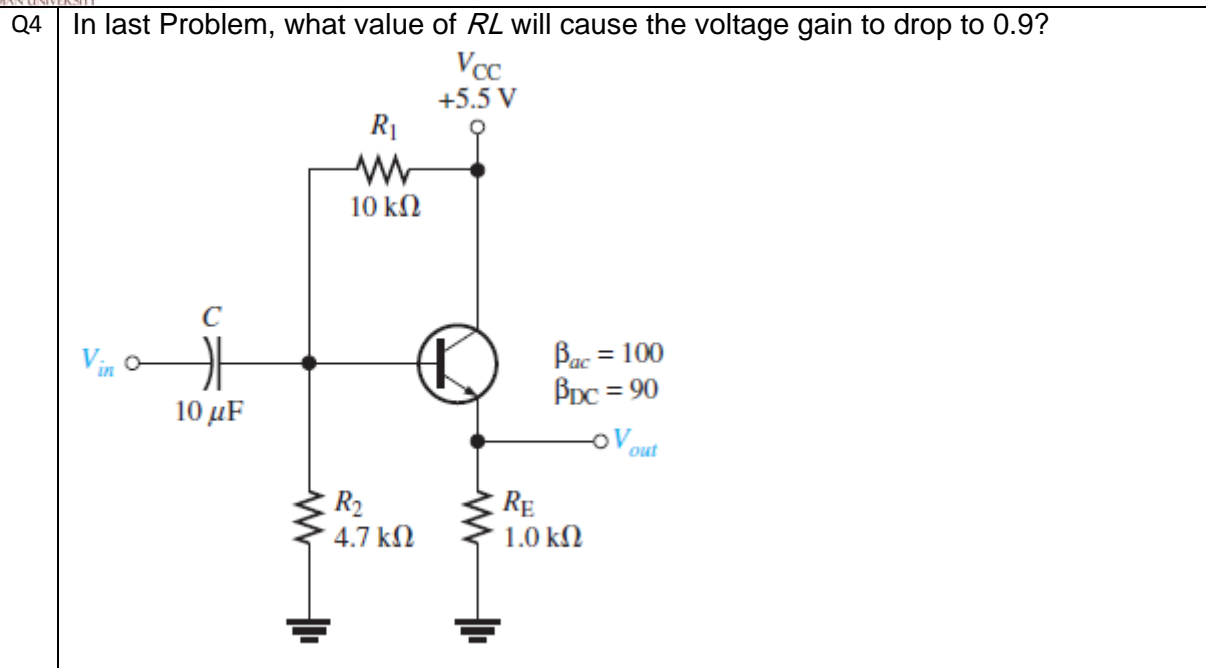

Sol
4
.....
..... 270 Ω
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....




Faculty of Engineering

Q5

For the circuit in Figure 1, determine the following:

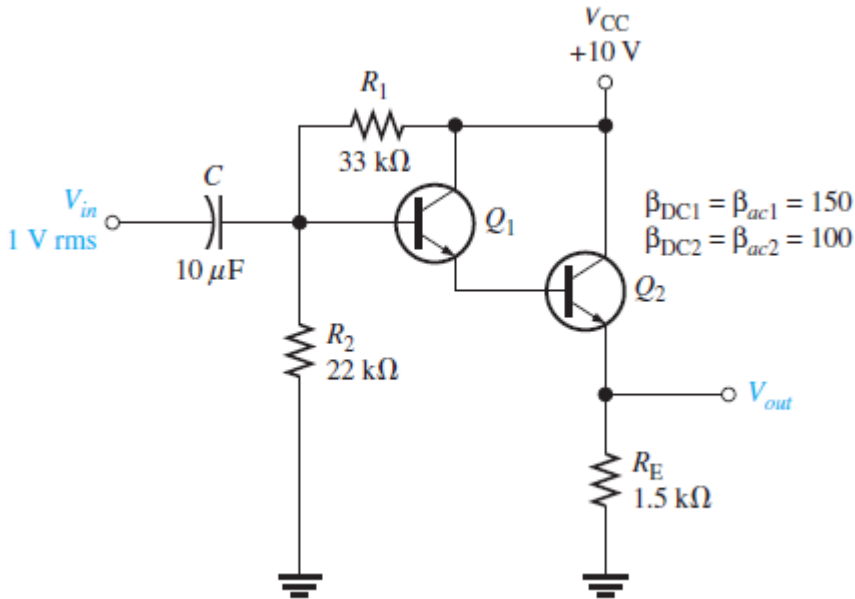- (a) Q_1 and Q_2 dc terminal voltages
- (b) overall β_{ac}
- (c) r'_e for each transistor
- (d) total input resistance



Sol
5

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

.....

.....

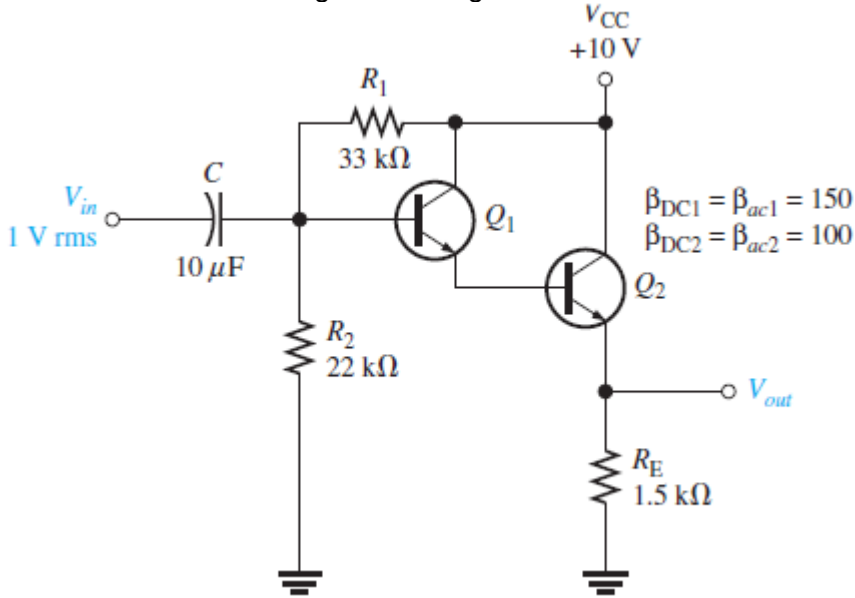Q6 Find the overall current gain A_i in Figure



Sol
6

.....
..... **8.8**
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....



Faculty of Engineering

Q9

Match the following generalized characteristics with the appropriate amplifier configuration.

- (a) Unity current gain, high voltage gain, very low input resistance
- (b) High current gain, high voltage gain, low input resistance
- (c) High current gain, unity voltage gain, high input resistance

Sol
9

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....



Q10 Each of two cascaded amplifier stages has an $A_v = 20$. What is the overall gain?


Sol
10

... 400



Faculty of Engineering

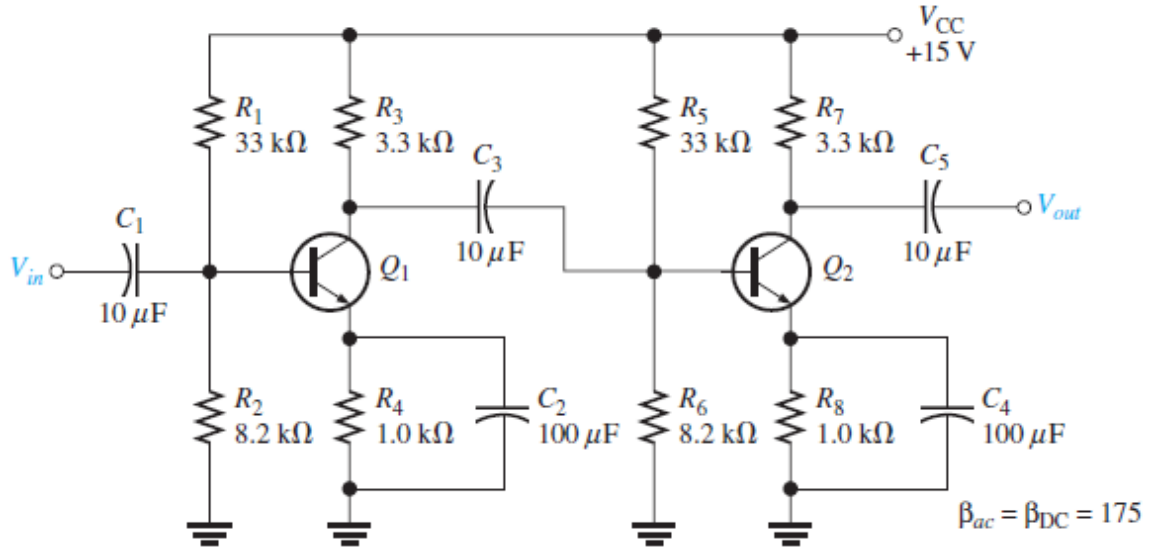Q12 For the two-stage, capacitively coupled amplifier in Figure , find the following values:
(a) voltage gain of each stage
(b) overall voltage gain
(c) Express the gains found in (a) and (b) in dB.



Sol
12

.....
 ... **(a)** $A_{v1} = 93.6, A_{v2} = 303$..
 ... **(b)** $A'_v = 28,361$..
 ... **(c)** $A_{v1(\text{dB})} = 39.4 \text{ dB}, A_{v2(\text{dB})} = 49.6 \text{ dB}, A'_{v(\text{dB})} = 89.1 \text{ dB}$..




Faculty of Engineering

Q1
3

If the multistage amplifier in Figure is driven by a $75 \Omega, 50 \mu\text{V}$ source and the second stage is loaded with an $R_L = 18 \text{ k}\Omega$, determine

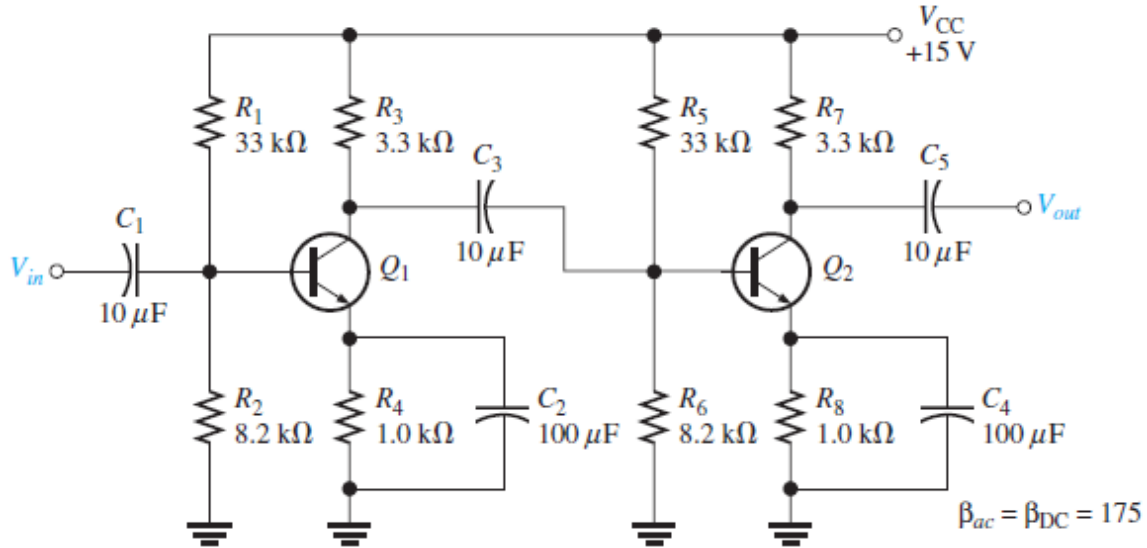- (a) voltage gain of each stage
- (b) overall voltage gain
- (c) Express the gains found in (a) and (b) in dB.



Sol
13

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

.....

Q14

Figure shows a direct-coupled (that is, with no coupling capacitors between stages) two-stage amplifier. The dc bias of the first stage sets the dc bias of the second. Determine all dc voltages for both stages and the overall ac voltage gain.

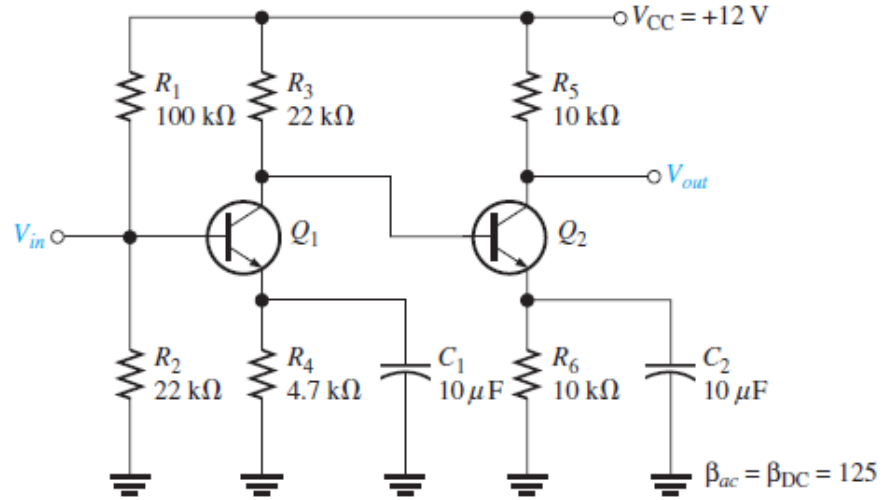

Sol
14

.....
 ... $V_{B1} = 2.16 \text{ V}$, $V_{E1} = 1.46 \text{ V}$, $V_{C1} \cong 5.16 \text{ V}$, $V_{B2} = 5.16 \text{ V}$, ..
 ... $V_{E2} = 4.46 \text{ V}$, $V_{C2} \cong 7.54 \text{ V}$, $A_{v1} = 66$, $A_{v2} = 179$, ..
 ... $A'_v = 11,814$..


Faculty of Engineering

Q16	Express the following voltage gains in dB as standard voltage gains: (a) 3 dB (b) 6 dB (c) 10 dB (d) 20 dB (e) 40 dB
Sol 16 (a) 1.41 (b) 2.00 (c) 3.16 (d) 10.0 (e) 100

Faculty of Engineering

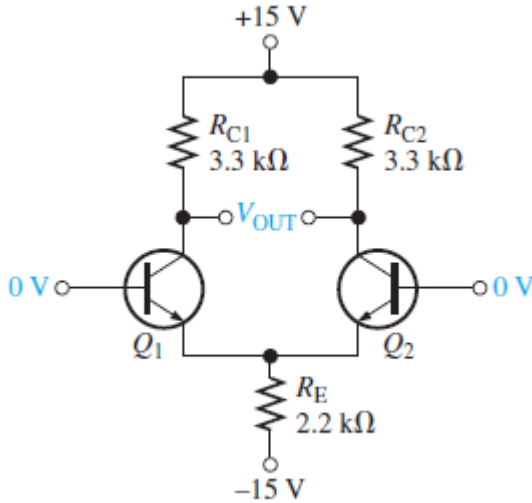Q17

The dc base voltages in Figure are zero. Using your knowledge of transistor analysis, determine the dc differential output voltage. Assume that Q_1 has an $\alpha = 0.980$ and Q_2 has an $\alpha = 0.975$.



Sol
17

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

.....



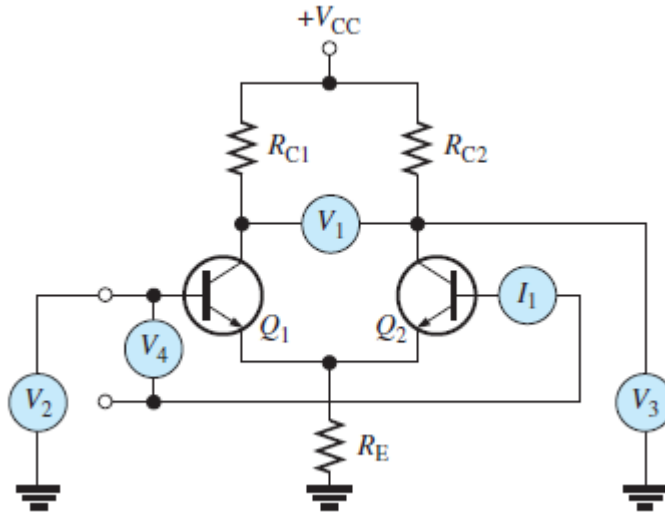Q18 Identify the quantity being measured by each meter in Figure




Sol
18

- ... V_1 : differential output voltage
- ... V_2 : noninverting input voltage
- ... V_3 : single-ended output voltage
- ... V_4 : differential input voltage
- ... I_1 : bias current




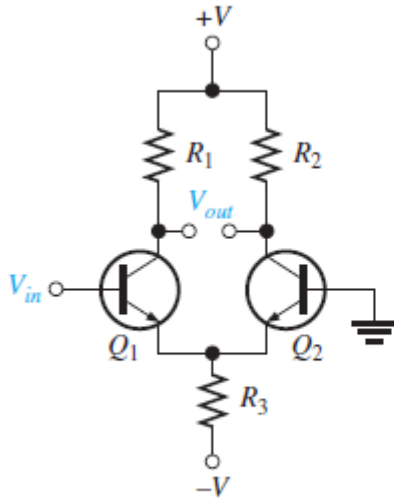Q20


Identify the type of input and output configuration for each basic differential amplifier in Figure




(a)

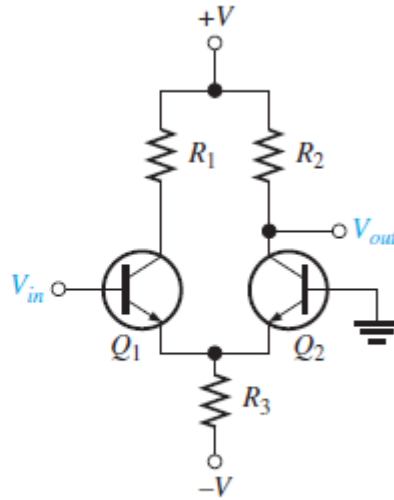

(b)

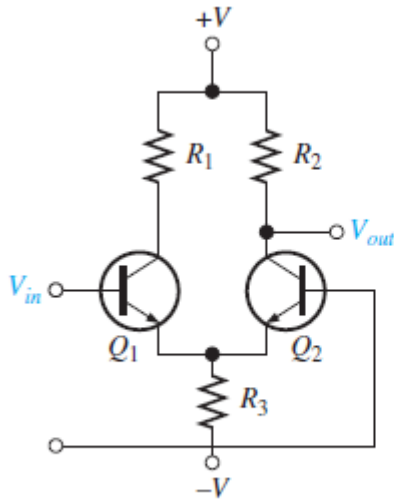

(c)

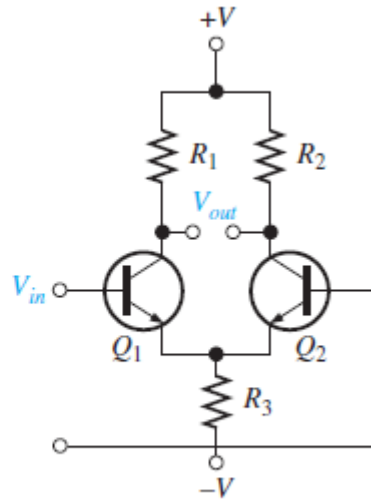

(d)

Sol
20

-
- ... (a) Single-ended differential input; differential output
 - ... (b) Single-ended differential input; single-ended output
 - ... (c) Double-ended differential input; single-ended output
 - ... (d) Double-ended differential input; differential output
-