

# Electronic Circuits – Assignment

## 03


# Diode Applications II

#	Student ID	Student Name	Grade (10)
-			

Delivery Date	
---------------	--

1. يتم تسليم التمرين محلولا في خلال أسبوع من تاريخ التمرين، و يتم حذف درجتين من التمرين عن كل أسبوع تأخير
2. يتم التسليم لمعيد المقرر مباشرة
3. تتم أجابه التمرين في نفس ورق الأسئلة

T & False questions
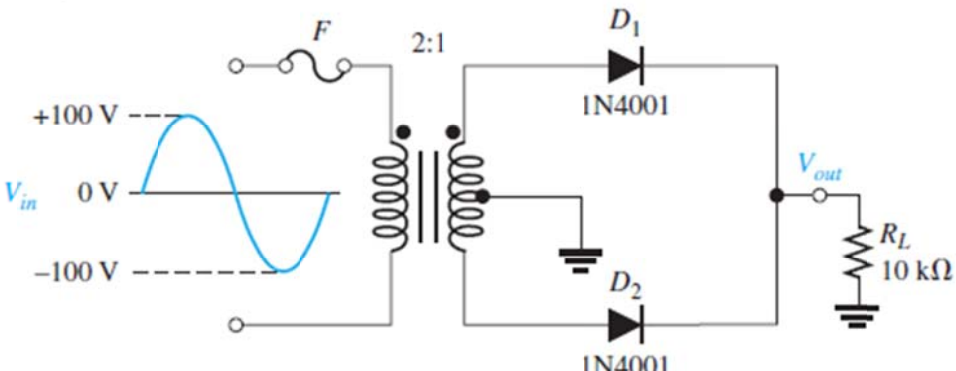
#	Question	Answer
1	The output frequency of a full-wave rectifier is twice the input frequency.	
2	<p>If the PIV rating of the diodes in Figure 2–36 is increased, the current through <math>R_L</math> will</p>  <p>(a) increase (b) decrease (c) not change</p>	
3	<p>To forward-bias a diode,</p> <p>(a) an external voltage is applied that is positive at the anode and negative at the cathode</p> <p>(b) an external voltage is applied that is negative at the anode and positive at the cathode</p> <p>(c) an external voltage is applied that is positive at the <math>p</math> region and negative at the <math>n</math> region</p> <p>(d) answers (a) and (c)</p>	
4	<p>Although current is blocked in reverse bias,</p> <p>(a) there is some current due to majority carriers</p> <p>(b) there is a very small current due to minority carriers</p> <p>(c) there is an avalanche current</p>	
5	<p>When forward-biased, a diode</p> <p>(a) blocks current (b) conducts current</p> <p>(c) has a high resistance (d) drops a large voltage</p>	
6	<p>The dynamic resistance can be important when a diode is</p> <p>(a) reverse-biased (b) forward-biased</p> <p>(c) in reverse breakdown (d) unbiased</p>	
7	<p>Ideally, a diode can be represented by a</p> <p>(a) voltage source (b) resistance (c) switch (d) all of these</p>	
8	<p>In the complete diode model,</p> <p>(a) the barrier potential is taken into account</p> <p>(b) the forward dynamic resistance is taken into account</p> <p>(c) the reverse resistance is taken into account</p> <p>(d) all of these</p>	

9	When a 60 Hz sinusoidal voltage is applied to the input of a half-wave rectifier, the output frequency is <b>(a) 120 Hz (b) 30 Hz (c) 60 Hz (d) 0 Hz</b>	
10	For the circuit in Question 15, the diode must be able to withstand a reverse voltage of <b>(a) 10 V (b) 5 V (c) 20 V (d) 3.18 V</b>	
11	When a 60 Hz sinusoidal voltage is applied to the input of a full-wave rectifier, the output frequency is <b>(a) 120 Hz (b) 60 Hz (c) 240 Hz (d) 0 Hz</b>	
12	When the peak output voltage is 100 V, the PIV for each diode in a center-tapped full-wave rectifier is (neglecting the diode drop) <b>(a) 100 V (b) 200 V (c) 141 V (d) 50 V</b>	












Q4

Consider the circuit in Figure.

- (a) What type of circuit is this?
- (b) What is the total peak secondary voltage?
- (c) Find the peak voltage across each half of the secondary.
- (d) Sketch the voltage waveform across  $R_L$ .
- (e) What is the peak current through each diode?
- (f) What is the PIV for each diode?

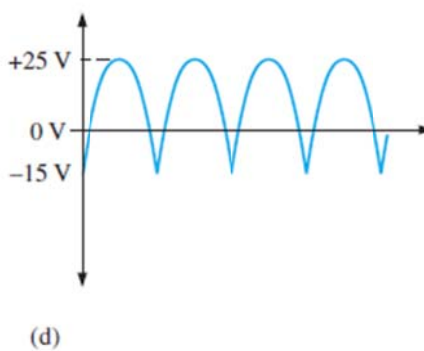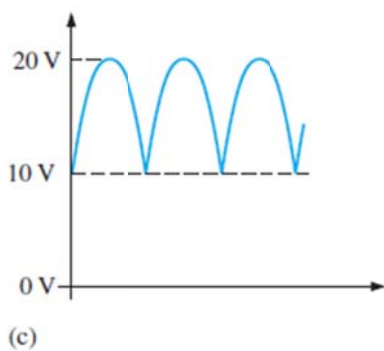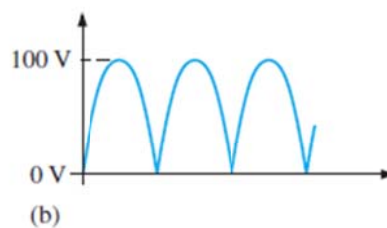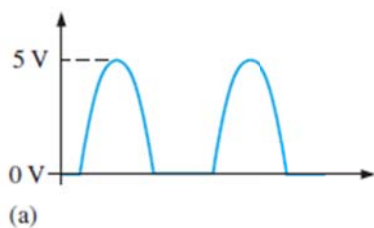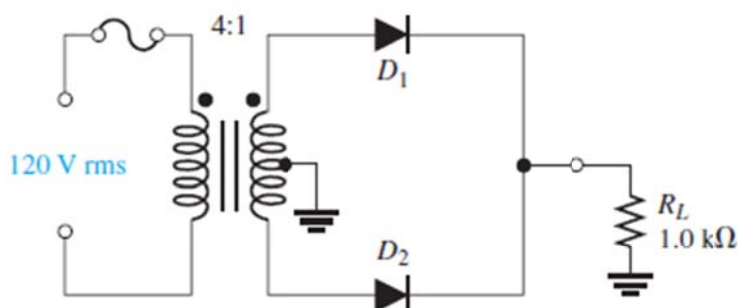

Sol 4

.....

.....

.....

.....

.....





