

# Electronic Circuits – Assignment

## 05

# Special Purpose Diodes

#	Student ID	Student Name	Grade (10)
-			



Delivery Date

1. يتم تسليم التمرين محلولا في خلال أسبوع من تاريخ التمرين، و يتم حذف درجتين من التمرين عن كل أسبوع تأخير
2. يتم التسليم لمعيد المقرر مباشرة
3. تتم أجابه التمرين في نفس ورق الأسئلة


T & F

#	Question	
1	The zener diode normally operates in reverse breakdown.	
2	There is no current when a zener is in reverse breakdown.	
3	The varactor diode is used as a variable capacitor.	
4	The LED is based on the process of electroluminescence.	
5	OLED stands for operational light-emitting diode.	
6	The reverse current of a photodiode increases as the incident light increases.	

MCQ

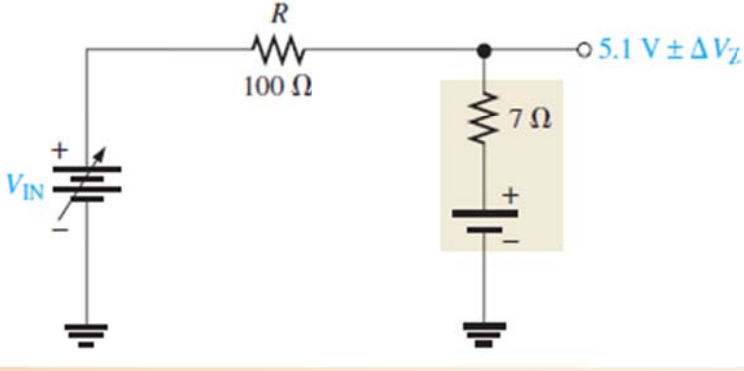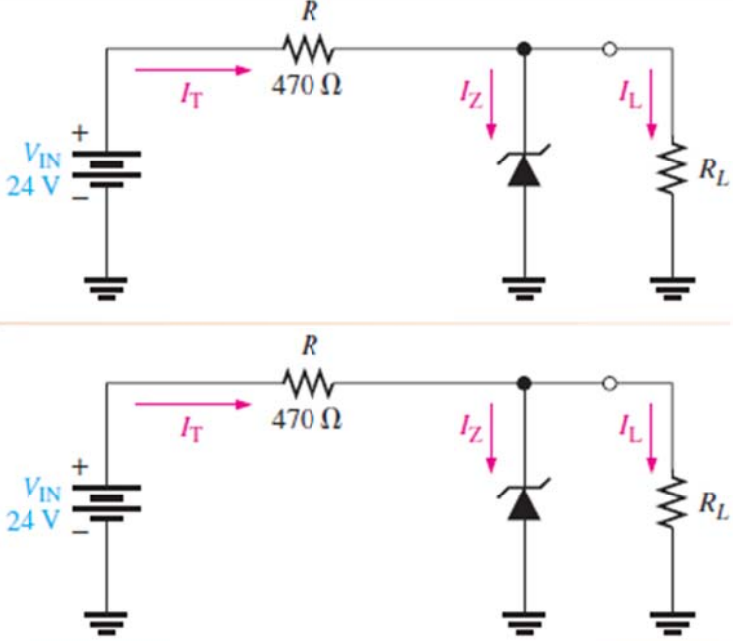
#	Question
1	 <p>If the input voltage in Figure is increased from 5 V to 10 V, ideally the output voltage will  <b>(a) increase (b) decrease (c) not change</b></p>
2	 <p>If <math>R_L</math> in Figure is removed, the current through the zener diode will  <b>(a) increase (b) decrease (c) not change</b></p>

3

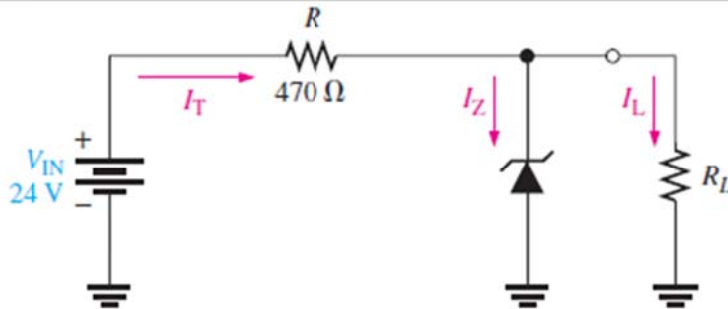

If  $R$  in Figure is increased, the current to the load resistor will  
(a) increase (b) decrease (c) not change


4

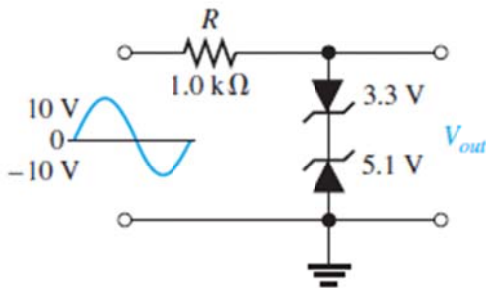


(a)

If the input voltage amplitude in Figure is reduced, the amplitude of the output voltage will  
(a) increase (b) decrease (c) not change

5

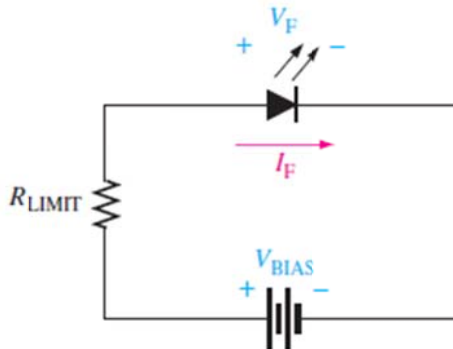

(a) Forward-biased operation

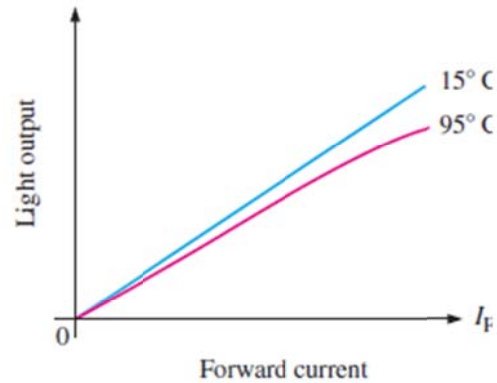

(b) General light output versus forward current for two temperatures


If the bias voltage in Figure 3-30 is reversed, the light output of the LED will

(a) increase (b) decrease (c) not change

6	A varactor diode exhibits (a) a variable capacitance that depends on reverse voltage (b) a variable resistance that depends on reverse voltage (c) a variable capacitance that depends on forward current (d) a constant capacitance over a range of reverse voltages	
7	Compared to a visible red LED, an infrared LED (a) produces light with shorter wavelengths (b) produces light of all wavelengths (c) produces only one color of light (d) produces light with longer wavelengths	
8	An OLED differs from a conventional LED in that it (a) requires no bias voltage (b) has layers of organic material in the place of a <i>pn</i> junction (c) can be implemented using an inkjet printing process (d) both (b) and (c)	
9	The internal resistance of a photodiode (a) increases with light intensity when reverse-biased (b) decreases with light intensity when reverse-biased (c) increases with light intensity when forward-biased (d) decreases with light intensity when forward-biased	
10	A diode that has a negative resistance characteristic is the (a) Schottky diode (b) tunnel diode (c) laser diode (d) hot-carrier diode	

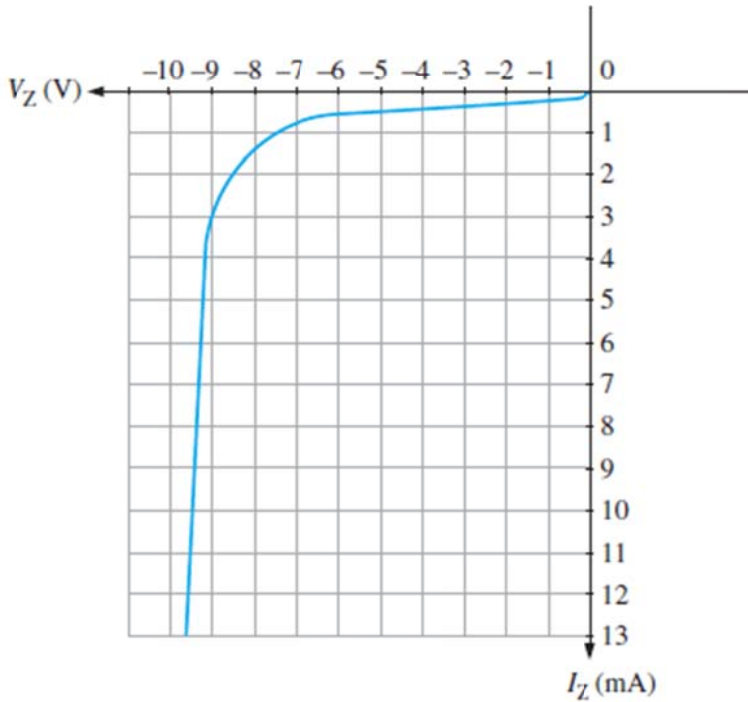Problems:

1 From the characteristic curve in Figure 3-67, what is the approximate minimum zener current ( $I_{ZK}$ ) and the approximate zener voltage at  $I_{ZK}$ ?



.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....








3

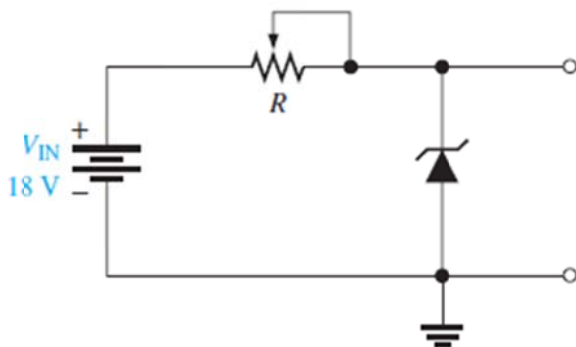To what value must  $R$  be adjusted in Figure 3–69 to make  $I_Z = 40 \text{ mA}$ ? Assume  $V_Z = 12 \text{ V}$  at  $30 \text{ mA}$  and  $Z_Z = 30 \Omega$ .



.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

Faculty of Engineering

4

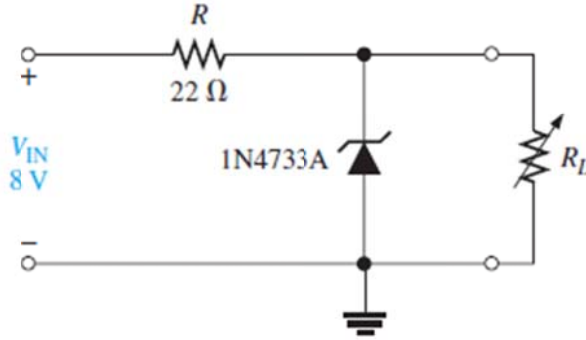A loaded zener regulator is shown in Figure 3–70.  $V_Z = 5.1 \text{ V}$  at  $I_Z = 49 \text{ mA}$ ,  $I_{ZK} = 1 \text{ mA}$ ,  $Z_Z = 7 \Omega$ , and  $I_{ZM} = 70 \text{ mA}$ . Determine the minimum and maximum permissible load currents.



.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....





FACULTY OF ENGINEERING  
AHRAM CANADIAN UNIVERSITY

كلية الهندسة

Faculty of Engineering



جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a dotted horizontal line for writing.



كلية الهندسة

Faculty of Engineering



جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

6

In a certain zener regulator, the output voltage changes 0.2 V when the input voltage goes from 5 V to 10 V. What is the input regulation expressed as a percentage? Refer to Chapter 2, Equation 2-14.

Dotted lines for handwritten answer
















13

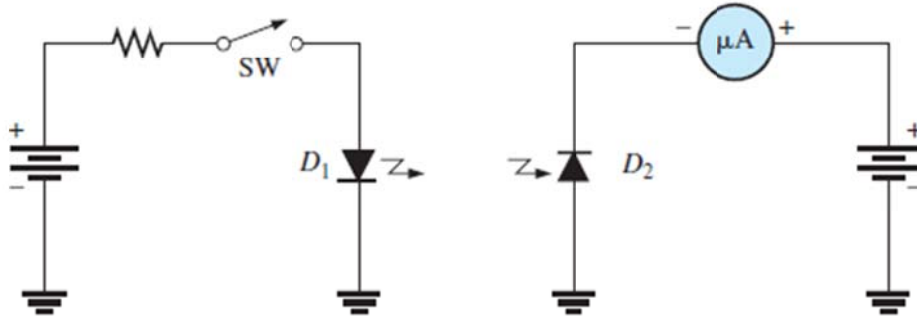When the switch in Figure 3–76 is closed, will the microammeter reading increase or decrease?  
Assume  $D_1$  and  $D_2$  are optically coupled.



.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....