



# Lecture (07) Bipolar Junction Transistor

---

By:

**Dr. Ahmed ElShafee**

Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits I


## Agenda

---



- BJT structure
- BJT operation
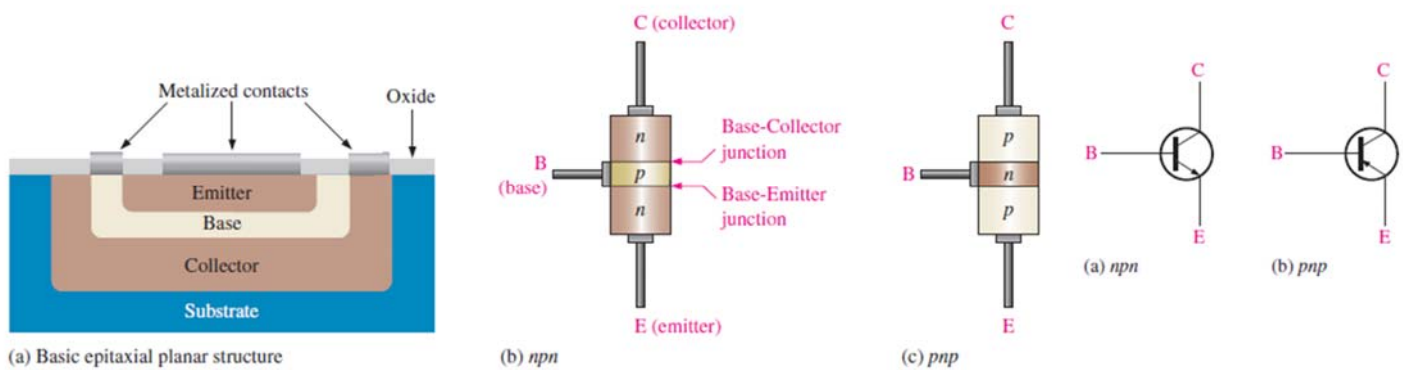
# BJT structure

- The **BJT** is constructed with three doped semiconductor regions
- One type consists of two  $n$  regions separated by a  $p$  region ( $npn$ ), and the other type consists of two  $p$  regions separated by an  $n$  region ( $pnp$ ).
- The term **bipolar** refers to the use of both holes and electrons



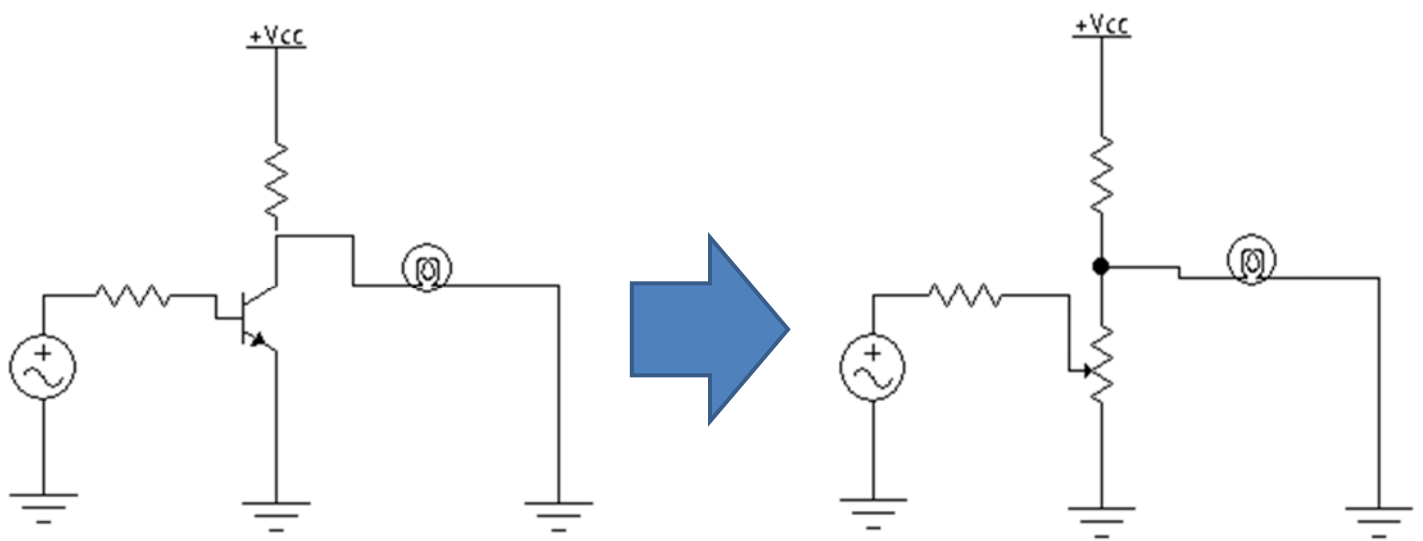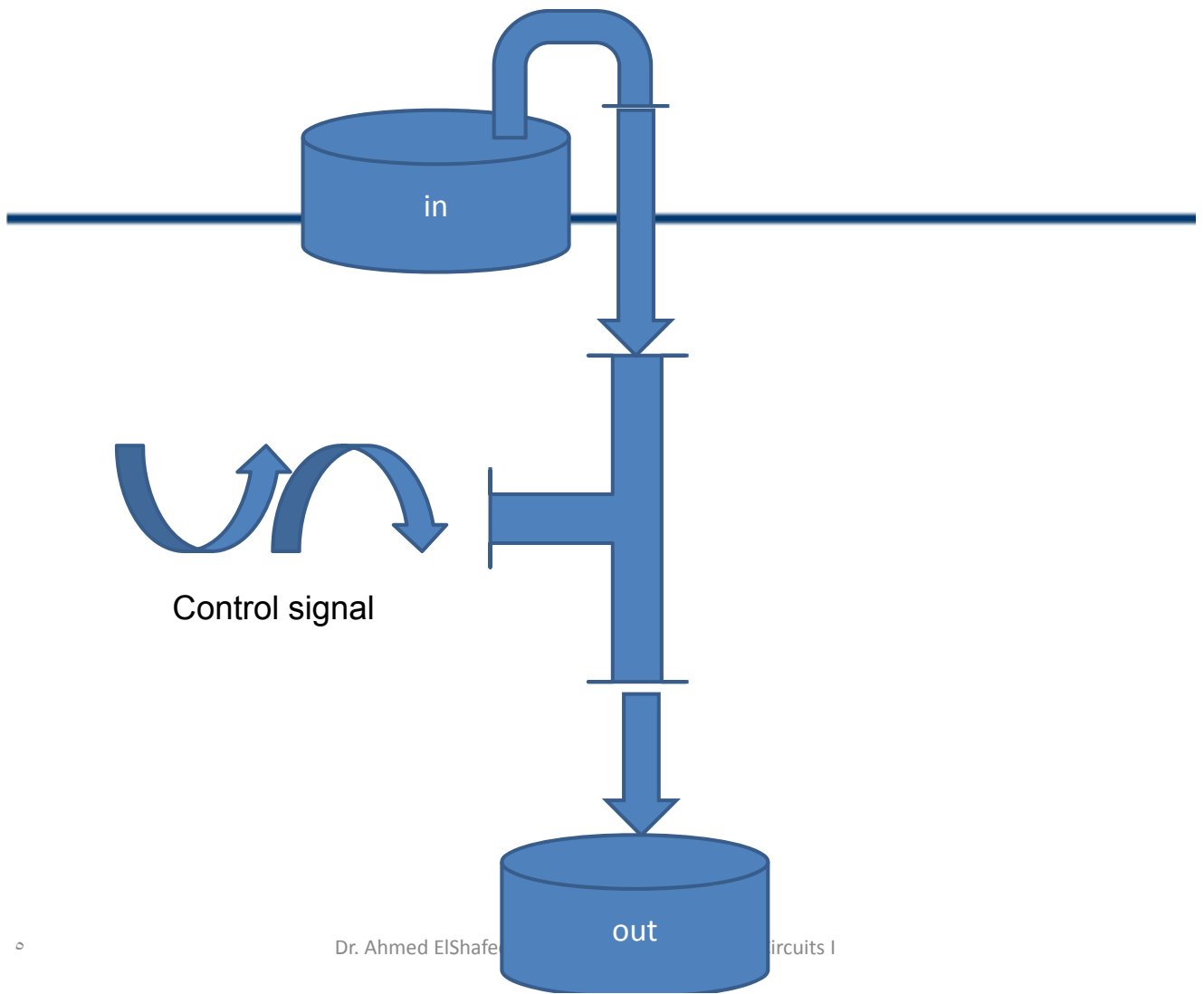- In order for a BJT to operate properly as an amplifier, the two  $pn$  junctions must be correctly biased with external dc voltages.
- In this section, we mainly use the  $npn$  transistor for illustration.
- The operation of the  $pnp$  is the same as for the  $npn$  except that the roles of the electrons and holes, the bias voltage polarities, and the current directions are all reversed.





## Biasing

base-emitter (BE) junction is forward-biased


base-collector (BC) junction is reverse-biased

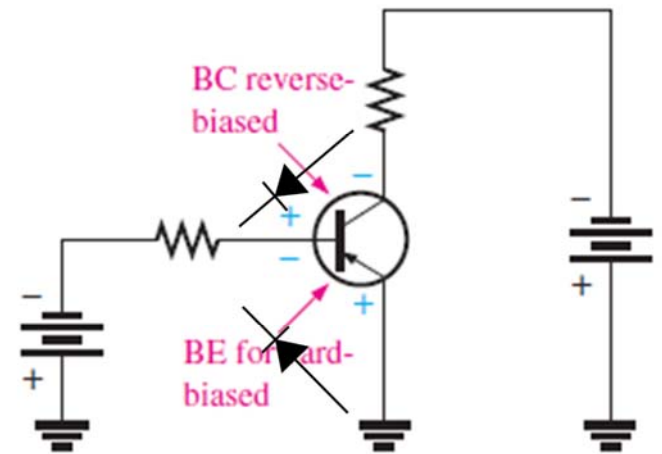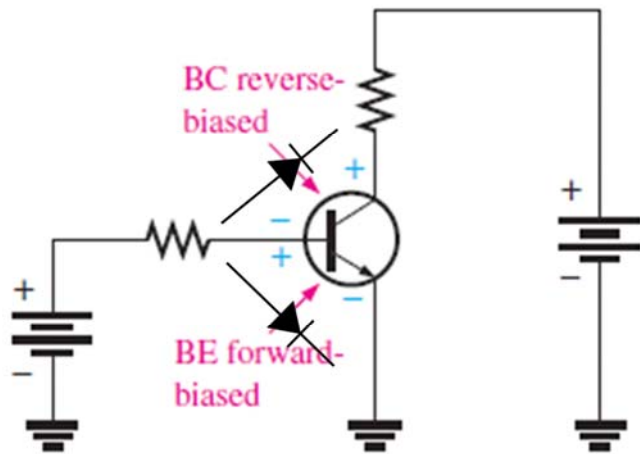This condition is called *forward-reverse bias*


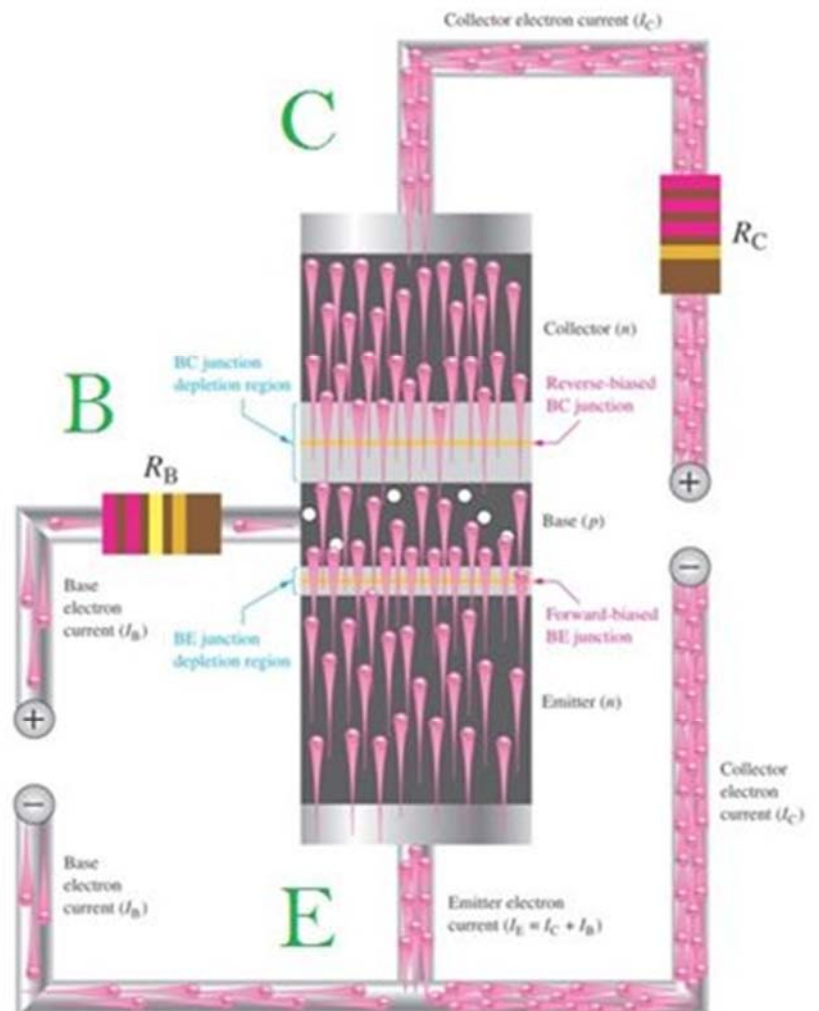
## BJT Operation


- CE battery +ve terminal attract electrons from the collector N-region.
- Collector N-region compensate electrons depletion region, which become more and more wider.



- BE battery +ve terminal start attracting the small amounts of electrons (minority carrier) from base p-type region, then starts attracting electrons from depletion region, which become thinner and thinner, then electrons start to flow from Emitter N-region

9


Dr. Ahmed ElSha

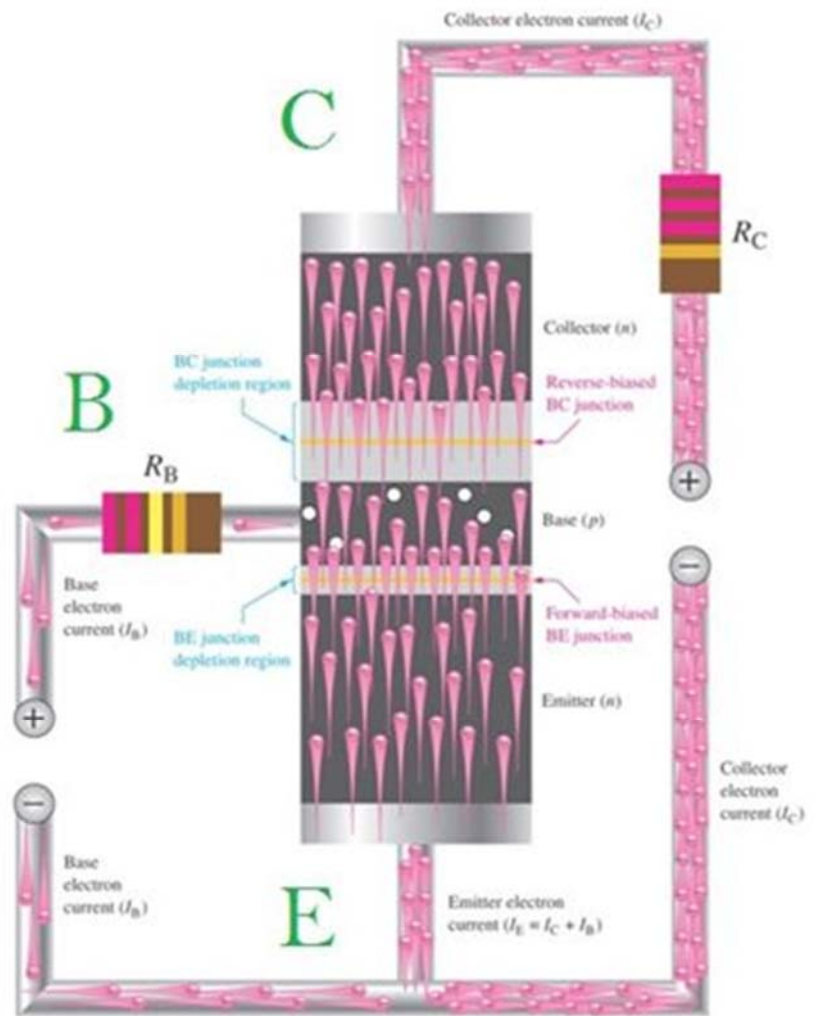

- Now base p-type now how a new electrons being transferred from CE battery -ve terminal through emitter n-type.
- Electrons stream divided between
  - Directly to BE battery +ve terminal
  - CE battery +ve terminal through emitter n-type


10

Dr. Ahmed ElSha

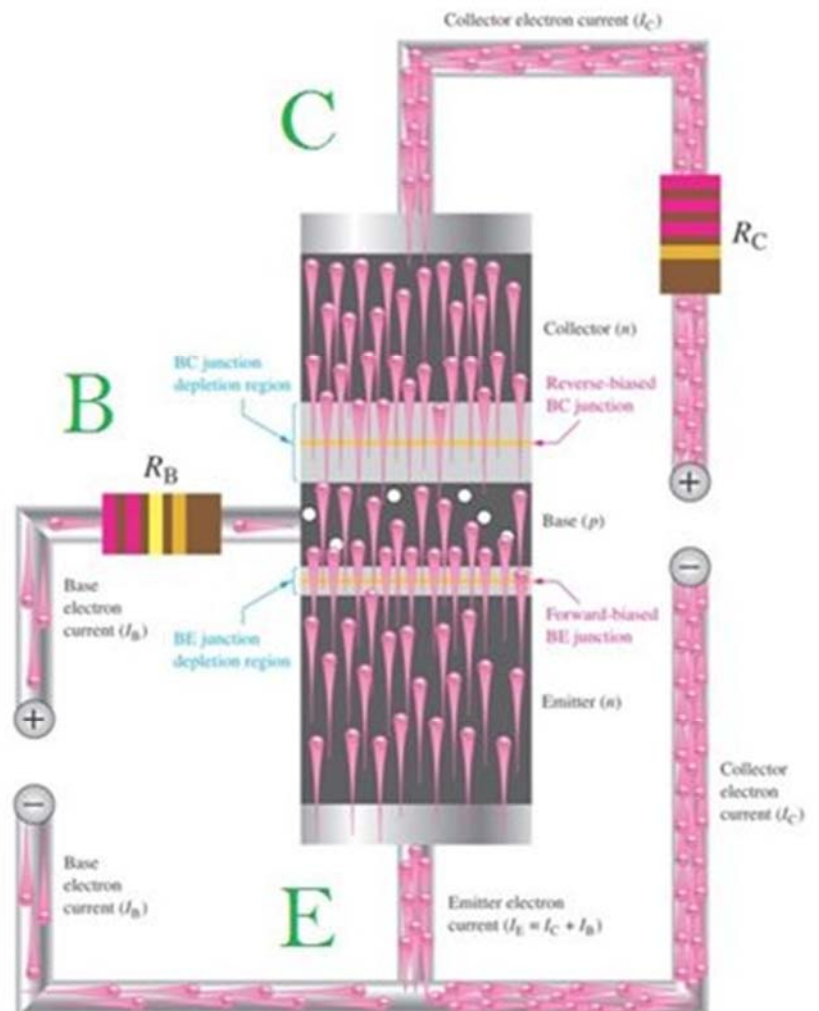



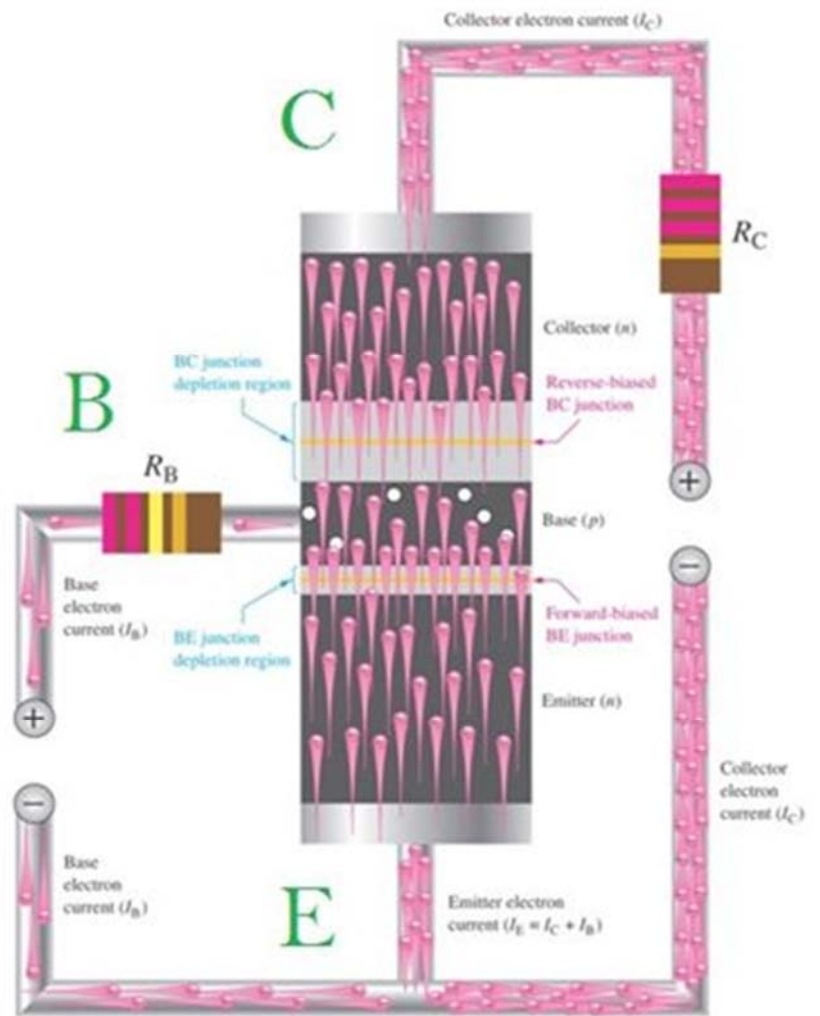- The more +ve potential applied to base from BE battery +ve terminal, a more electrons being transferred from CE battery -ve terminal, through emitter N-region, a more electrons in turn flow to CE battery +ve terminal.




11

Dr. Ahmed ElSha

## Transistor Currents


$$I_E = I_B + I_C$$

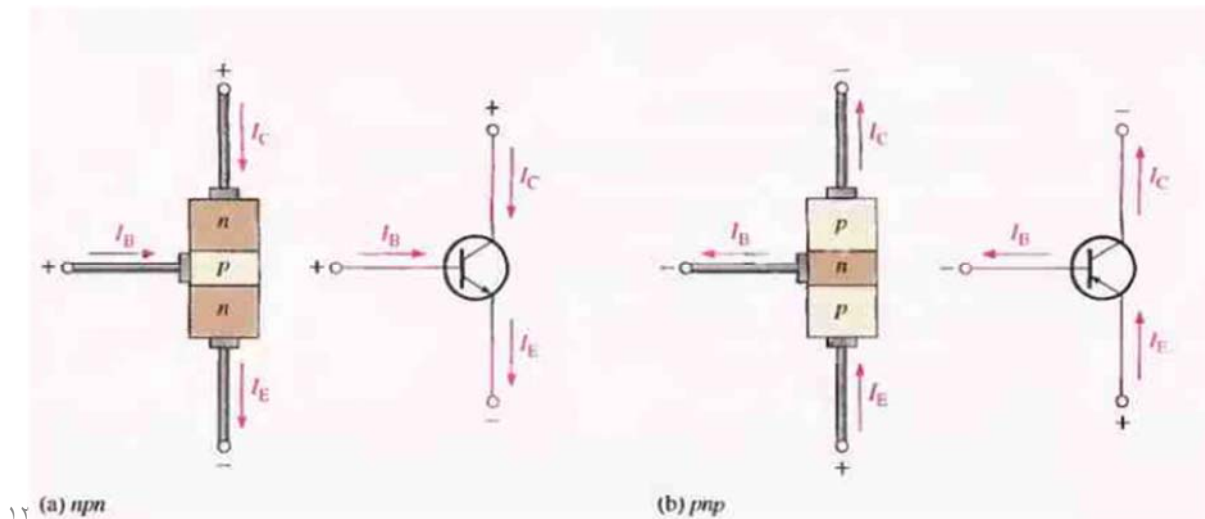


12 (a) npn

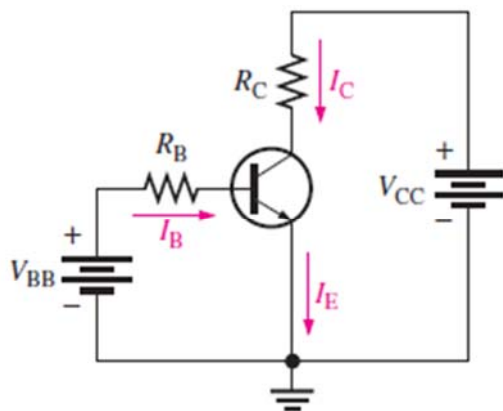(b) pnp

- $V_{BB}$  forward-biases the base-emitter junction,
- $V_{CC}$  reverse-biases the base-collector junction.
- In practice both  $V_{CC}$ , and  $V_{BB}$  derived from single battery with necessarily voltage divider on base terminal



١٣ (a) npn

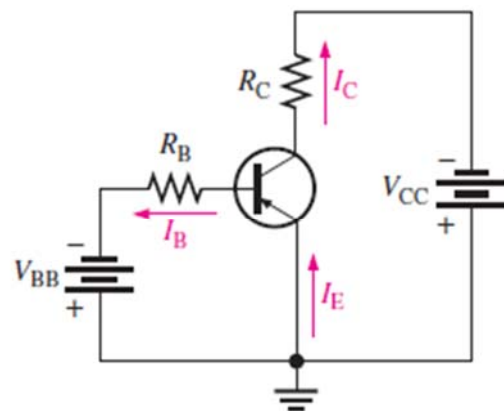

(b) pnp

- **DC Beta ( $\beta_{DC}$ ) and DC Alpha ( $\alpha_{DC}$ )**
- DC gain called ( $\beta_{DC}$ ) is the ratio between  $I_C/I_B$ , which called  $h_{FE}$  in data sheet, range from less than 20 to 200 or higher.

$$\beta_{DC} = \frac{I_C}{I_B}$$


$$h_{FE} = \beta_{DC}$$

- ( $\alpha_{DC}$ ) is the ratio between  $I_C/I_E$ , in range from 0.95 to 0.99 or greater

$$\alpha_{DC} = \frac{I_C}{I_E}$$
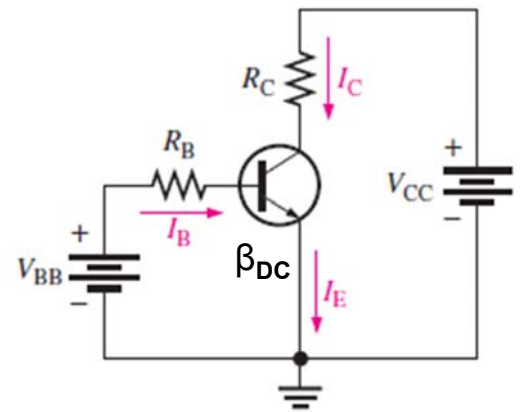
# Example

Determine the dc current gain  $\beta_{DC}$  and the emitter current  $I_E$  for a transistor where  $I_B = 50 \mu\text{A}$  and  $I_C = 3.65 \text{ mA}$ .



10


Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits I

# Example

Determine the dc current gain  $\beta_{DC}$  and the emitter current  $I_E$  for a transistor where  $I_B = 50 \mu\text{A}$  and  $I_C = 3.65 \text{ mA}$ .

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{3.65 \text{ mA}}{50 \mu\text{A}} = 73$$
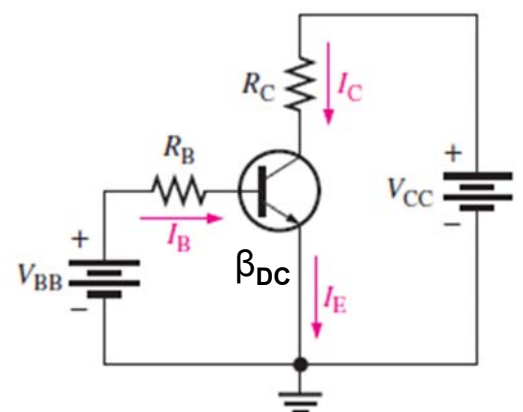
$$I_E = I_C + I_B = 3.65 \text{ mA} + 50 \mu\text{A} = 3.70 \text{ mA}$$




11

Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits I



## Transistor DC Model

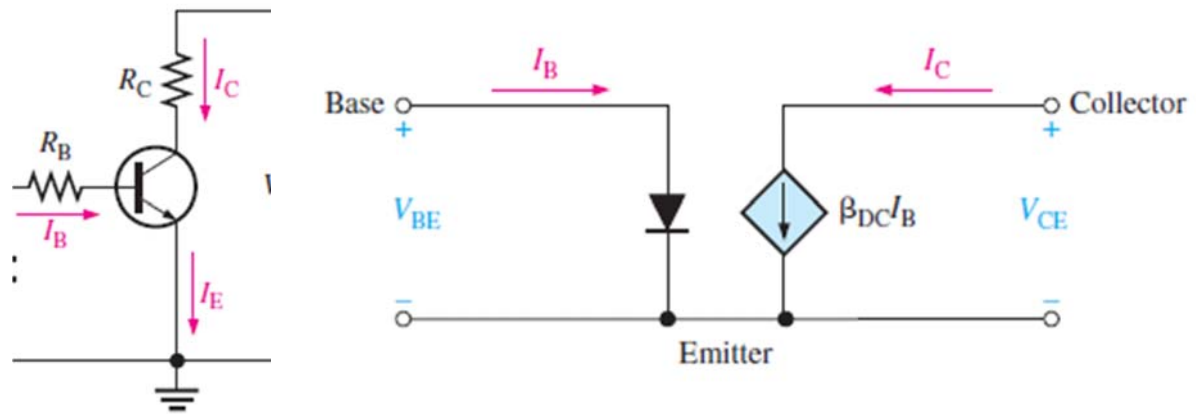

17

Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits I

## BJT Circuit Analysis

- $V_{BB}$ , forward-biases the base-emitter junction, and the collector-bias voltage source,  $V_{CC}$ , reverse-biases the base-collector junction.

$$V_{BE} \cong 0.7 \text{ V}$$

- Kirchhoff's voltage law @1

$$V_{R_B} = V_{BB} - V_{BE}$$

$I_B$ : dc base current


$I_E$ : dc emitter current

$I_C$ : dc collector current

$V_{BE}$ : dc voltage at base with respect to emitter

$V_{CB}$ : dc voltage at collector with respect to base

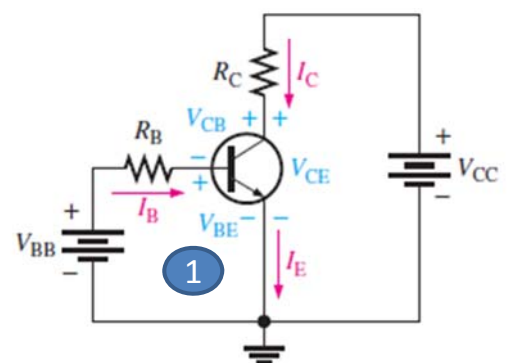$V_{CE}$ : dc voltage at collector with respect to emitter



18

Dr. Ahmed ElShafee, ACU

- Ohm's law

$$V_{R_B} = I_B R_B$$

- Substitute

$$I_B R_B = V_{BB} - V_{BE}$$

- Finally

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

$I_B$ : dc base current


$I_E$ : dc emitter current

$I_C$ : dc collector current

$V_{BE}$ : dc voltage at base with respect to emitter

$V_{CB}$ : dc voltage at collector with respect to base

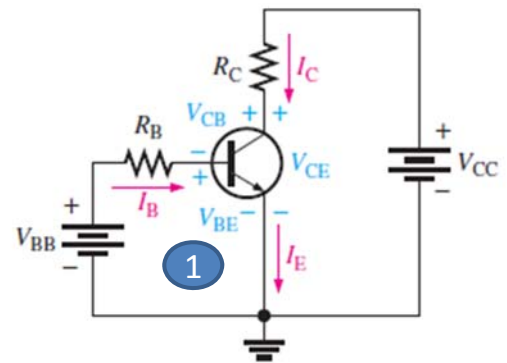$V_{CE}$ : dc voltage at collector with respect to emitter



١٩

Dr. Ahmed ElShafee, ACU

- KVL @ 2

$$-V_{CC} + V_{R_C} + V_{CE} = 0$$

$$V_{CE} = V_{CC} - V_{R_C}$$

- Ohm's

$$V_{R_C} = I_C R_C$$

- Substitute

$$V_{CE} = V_{CC} - I_C R_C$$

- But

$$I_C = \beta_{DC} I_B$$

$I_B$ : dc base current


$I_E$ : dc emitter current

$I_C$ : dc collector current

$V_{BE}$ : dc voltage at base with respect to emitter

$V_{CB}$ : dc voltage at collector with respect to base

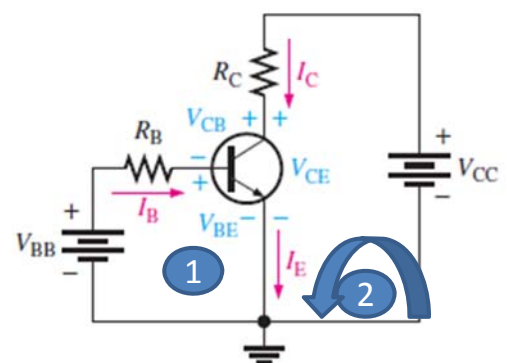$V_{CE}$ : dc voltage at collector with respect to emitter




٢٠

Dr. Ahmed ElShafee, ACU

- Consider the transistor itself


$$V_{CE} = V_{CB} + V_{BE}$$

$$V_{CB} = V_{CE} - V_{BE}$$

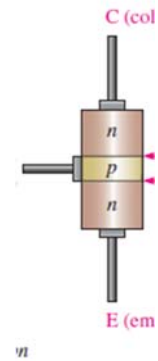
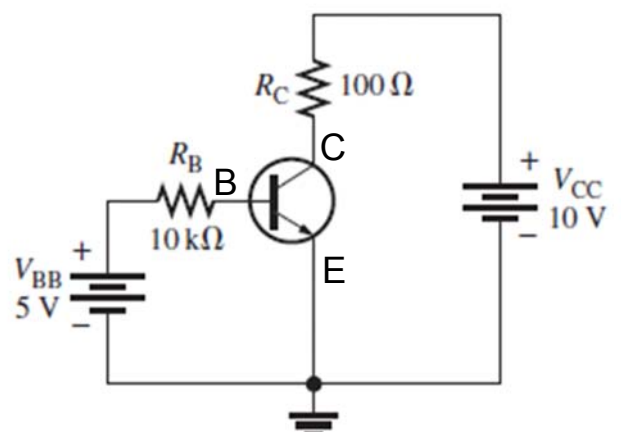
## Example 02

Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$ , and  $V_{CB}$  in the circuit of Figure . The transistor has a  $\beta_{DC} = 150$ .



# Example 02

Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$ , and  $V_{CB}$  in the circuit of Figure . The transistor has a  $\beta_{DC} = 150$ .


Answer

$$V_{BE} \cong 0.7 \text{ V.}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 430 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (150)(430 \mu\text{A}) = 64.5 \text{ mA}$$
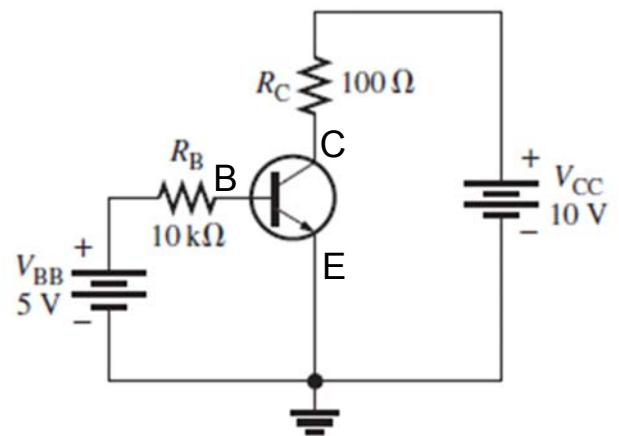
$$I_E = I_C + I_B = 64.5 \text{ mA} + 430 \mu\text{A} = 64.9 \text{ mA}$$



٢٣

Dr. Ahmed ElShafee, ACU : Fall 2017


# Example 02

Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$ , and  $V_{CB}$  in the circuit of Figure . The transistor has a  $\beta_{DC} = 150$ .

Answer

$$V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (64.5 \text{ mA})(100 \Omega) = 10 \text{ V} - 6.45 \text{ V} = 3.55 \text{ V}$$
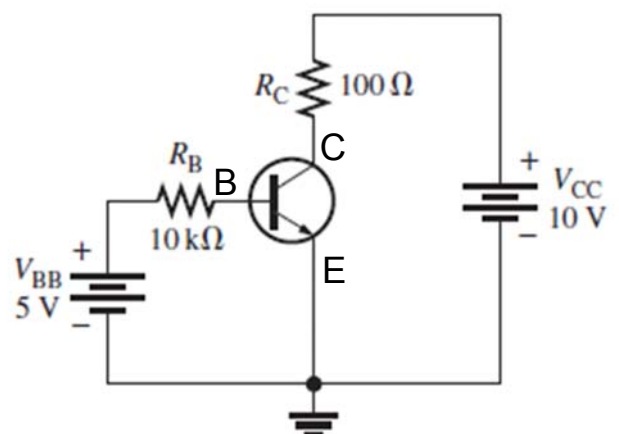
$$V_{CB} = V_{CE} - V_{BE} = 3.55 \text{ V} - 0.7 \text{ V} = 2.85 \text{ V}$$



٢٤

Dr. Ahmed ElShafee, ACU : Fall 2017



**Thanks,..**  
**See you next week (ISA),...**

Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits I