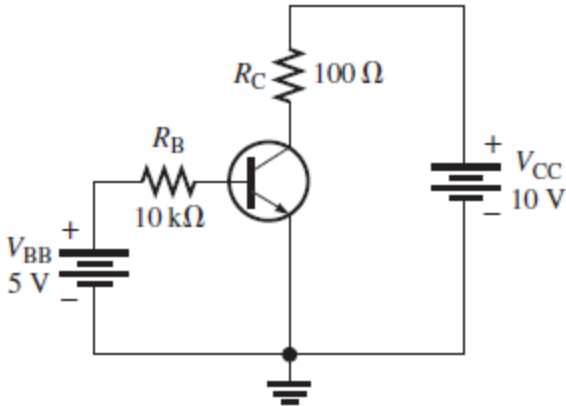
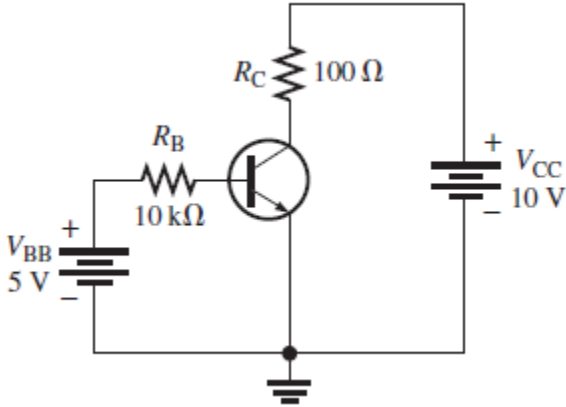
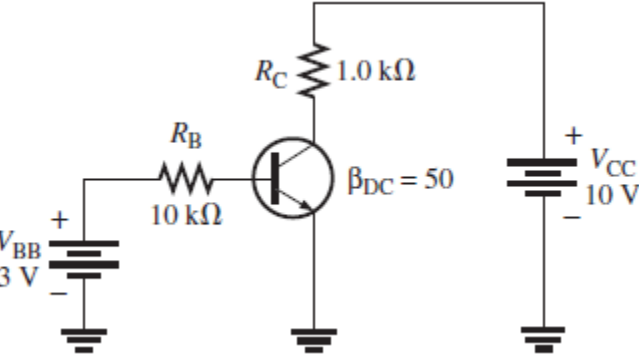


Electronic Circuits - Tutorial 07

BJT transistor 1

#	Question	
1	A bipolar junction transistor has three terminals.	T
2	For operation in the linear or active region, the base-emitter junction of a transistor is forward biased.	T
3	The base current and collector current are approximately equal.	F
4	DC and hFE are two different transistor parameters.	F

MCQ

#	Question	
1	 <p>If a transistor with a higher β_{DC} is used in Figure, the collector current will (a) increase (b) decrease (c) not change</p>	a
2	 <p>If a transistor with a higher β_{DC} is used in Figure, the base current will (a) increase (b) decrease (c) not change</p>	c
3	 <p>If V_{CC} in Figure is increased, the base current will (a) increase (b) decrease (c) not change</p>	c



Faculty of Engineering

FACULTY OF ENGINEERING
AHRAM CANADIAN UNIVERSITY

4	The three terminals of a bipolar junction transistor are called (a) p, n, p (b) n, p, n (c) input, output, ground (d) base, emitter, collector	d
5	For operation as an amplifier, the base of an npn transistor must be (a) positive with respect to the emitter (b) negative with respect to the emitter (c) positive with respect to the collector (d) 0 V	a
6	The β_{DC} of a transistor is its (a) current gain (b) voltage gain (c) power gain (d) internal resistance	a



Faculty of Engineering

FACULTY OF ENGINEERING
AHRAM CANADIAN UNIVERSITY

Q5	For normal operation of a <i>pnp</i> transistor, the base must be (+ or -) with respect to the emitter, and (+ or -) with respect to the collector.
Sol 5 Negative, positive



Faculty of Engineering

Q7	What is the α_{DC} when $I_C = 8.23 \text{ mA}$ and $I_E = 8.69 \text{ mA}$?
Sol 7 0.947

