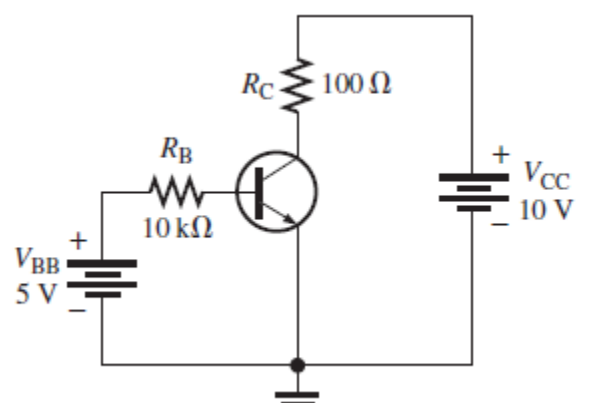
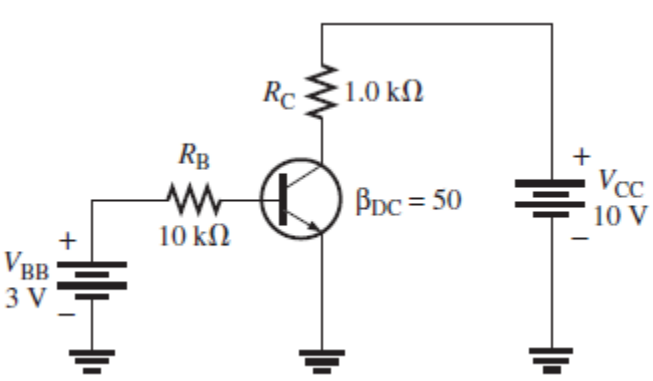


# Electronic Circuits - Tutorial 08

## BJT transistor 2

#	Question	
1	Amplification is the output voltage divided by the input current.	F
2	The three regions of a BJT are base, emitter, and cathode.	F
3	Two types of BJT are npn and pnp.	T
4	The dc voltage gain of a transistor is designated $b_{DC}$ .	F

MCQ

#	Question	
1	The approximate voltage across the forward-biased base-emitter junction of a silicon BJT is (a) 0 V (b) 0.7 V (c) 0.3 V (d) $V_{BB}$	b
2	If the output of a transistor amplifier is 5 V rms and the input is 100 mV rms, the voltage gain is (a) 5 (b) 500 (c) 50 (d) 100	c
3	 <p>If a transistor with a higher <math>\beta_{DC}</math> is used in Figure, the emitter current will (a) increase (b) decrease (c) not change</p>	a
4	 <p>If <math>V_{BB}</math> is reduced in Figure, the collector current will (a) increase (b) decrease (c) not change</p>	b
5	In a <i>npn</i> transistor, the <i>p</i> regions are (a) base and emitter (b) base and collector (c) emitter and collector	c
6	The emitter current is always (a) greater than the base current (b) less than the collector current (c) greater than the collector current (d) answers (a) and (c)	d
7	If $I_C$ is 50 times larger than $I_B$ , then is $\beta_{DC}$ (a) 0.02 (b) 100 (c) 50 (d) 500	c
8	The bias condition for a transistor to be used as a linear amplifier is called (a) forward-reverse (b) forward-forward (c) reverse-reverse (d) collector bias	a
9	When a lowercase is used in relation to a transistor, it refers to (a) a low resistance (b) a wire resistance (c) an internal ac resistance (d) a source resistance	c










Faculty of Engineering

Q4

A base current of  $50 \mu\text{A}$  is applied to the transistor in Figure 4–53, and a voltage of 5 V is dropped across  $R_C$ . Determine the  $\beta_{DC}$  of the transistor.

FIGURE 4–53

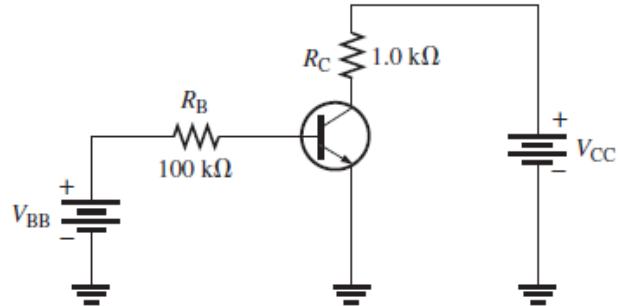

Sol  
4

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....




Q5

Calculate  $\alpha_{DC}$  for the transistor in

A base current of  $50 \mu A$  is applied to the transistor in Figure 4–53, and a voltage of 5 V is dropped across  $R_C$ . Determine the  $\beta_{DC}$  of the transistor.

FIGURE 4–53

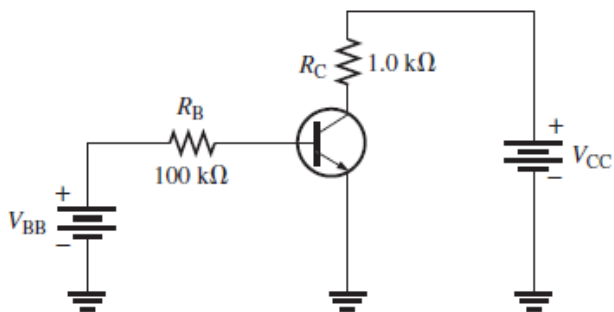

Sol  
5

.....  
.....  
..... 0.99 .....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....







