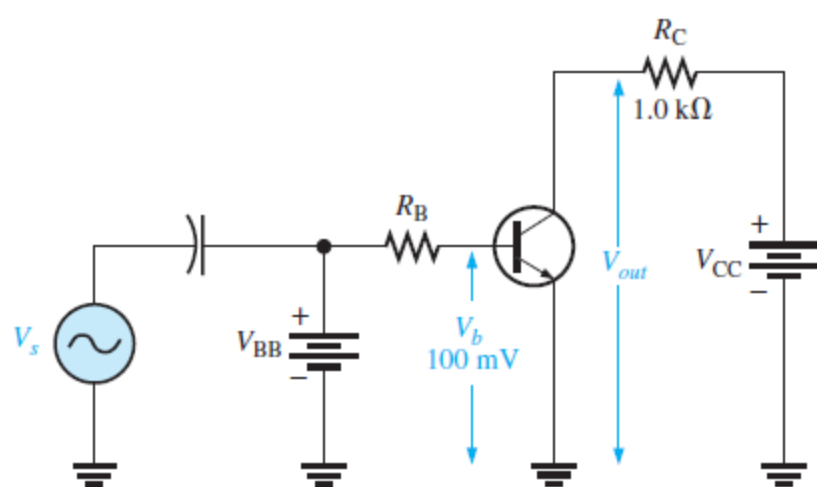
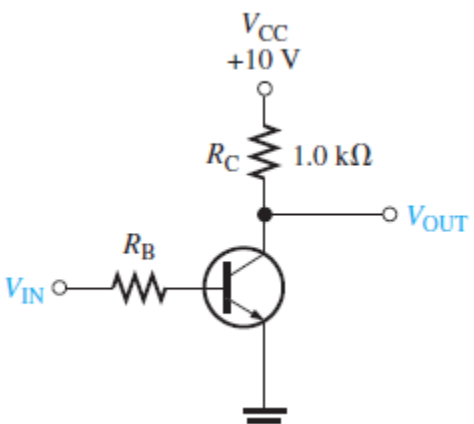




Electronic Circuits - Tutorial 08

BJT transistor 2

#	Question	
1	cutoff and saturation are the two normal states of a linear transistor amplifier.	F
2	When a transistor is saturated, the collector current is maximum.	T
3	Voltage gain of a transistor amplifier depends on the collector resistor and the internal acresistance.	T
4	A transistor in cutoff acts as an open switch.	T

MCQ

#	Question	
1	 <p>If the amplitude of V_{in} in Figure is decreased, the ac output voltage amplitude will (a) increase (b) decrease (c) not change</p>	b
2	 <p>R_C in Figure is reduced in value, the value of $I_{C(sat)}$ will (a) increase (b) decrease (c) not change</p>	a

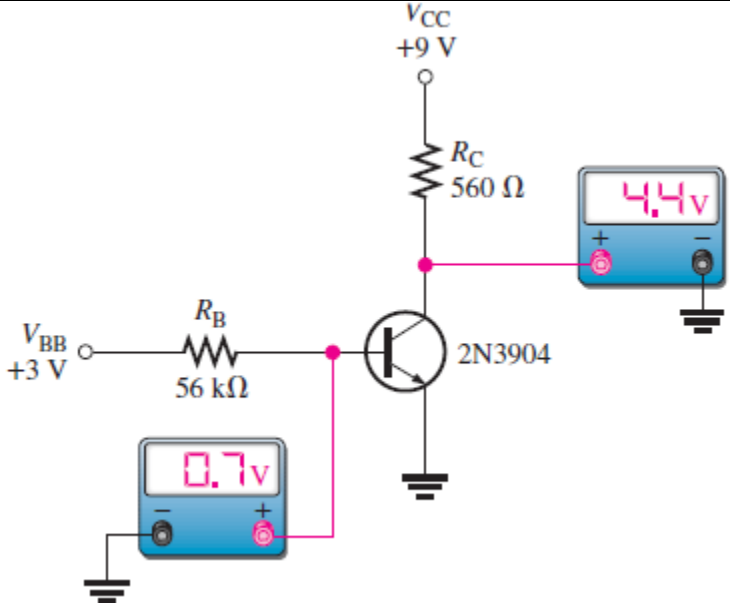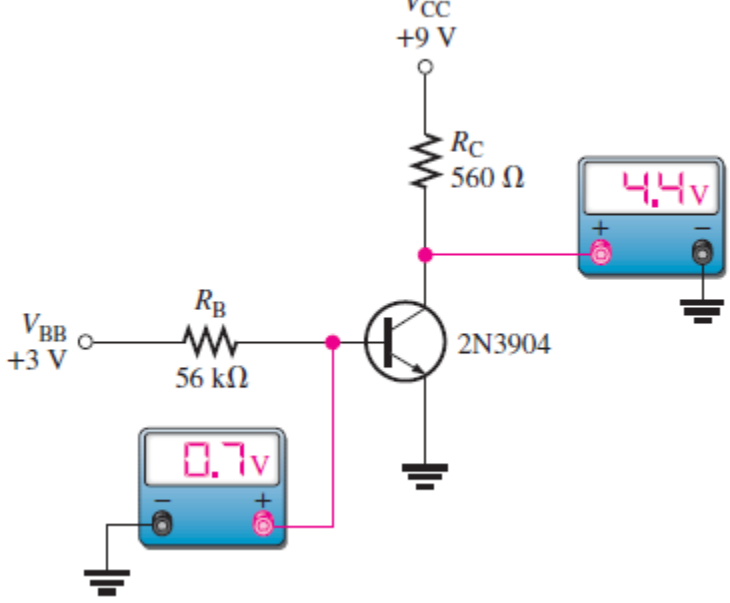3	 <p>If the transistor in Figure is open from collector to emitter, the collector voltage will (a) increase (b) decrease (c) not change</p>	a
4	 <p>If the emitter in Figure becomes disconnected from ground, the collector voltage will (a) increase (b) decrease (c) not change</p>	a
5	<p>When operated in cutoff and saturation, the transistor acts like a (a) linear amplifier (b) switch (c) variable capacitor (d) variable resistor</p>	b
6	<p>In saturation, V_{CE} is (a) 0.7 V (b) equal to V_{CC} (c) minimum (d) maximum</p>	c
7	<p>Once in saturation, a further increase in base current will (a) cause the collector current to increase (b) not affect the collector current (c) cause the collector current to decrease (d) turn the transistor off</p>	b
8	<p>The relationship between the collector current and a light-generated base current is (a) $I_C = \beta_{DC} I_\lambda$ (b) $I_C = \alpha_{DC} I_\lambda$ (c) $I_C = \lambda I_\lambda$ (d) $I_C = \beta_{DC}^2 I_\lambda$</p>	a



كلية الهندسة



جامعة الأهرام الكندية
AHRAM CANADIAN UNIVERSITY

FACULTY OF ENGINEERING
AHRAM CANADIAN UNIVERSITY

Faculty of Engineering

9	In a transistor amplifier, if the base-emitter junction is open, the collector voltage is (a) V_{CC} (b) 0 V (c) floating (d) 0.2 V	a
---	--	---

