

Electronic Circuits II – Laboratory 03

2 stages AC Amplifier


#	Student ID	Student Name	Grade (10)	Instructor signature
1				
2				
3				
4				
5				

Delivery Date	
---------------	--

The main circuit Common collector circuit


Circuit diagram

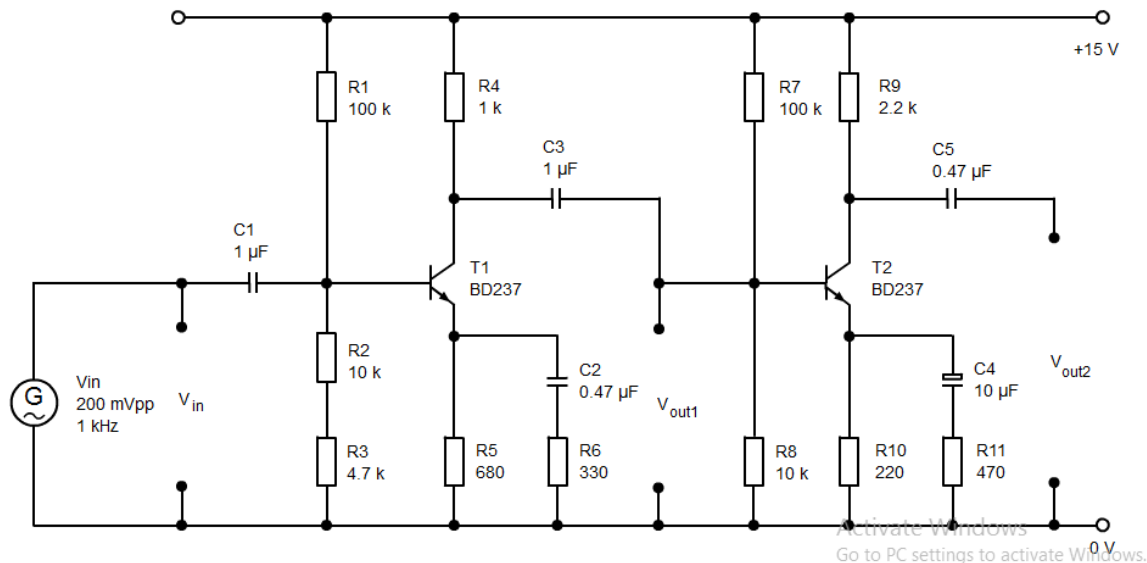This experiment is based on the following circuit:




Equipment

The following equipment is needed for this experiment and should be configured as shown:

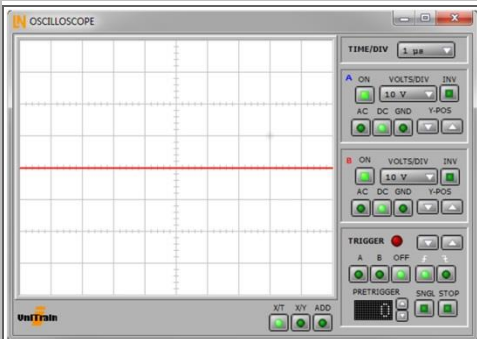Equipment	Settings		
			
		Channel A	Channel B
	Sensitivity	100 mV/div	100 mV/div
	Coupling	AC	AC
	Polarity	Normal	Normal
	Y-pos	0	0
	Time base	200 µs/div	
	Mode	X/T	
	Trigger channel	A	
Trigger edge	Positive		



Waveform	Sine
Amplitude	200 mVpp (1%)
Frequency factor	1 k
Frequency	1 kHz

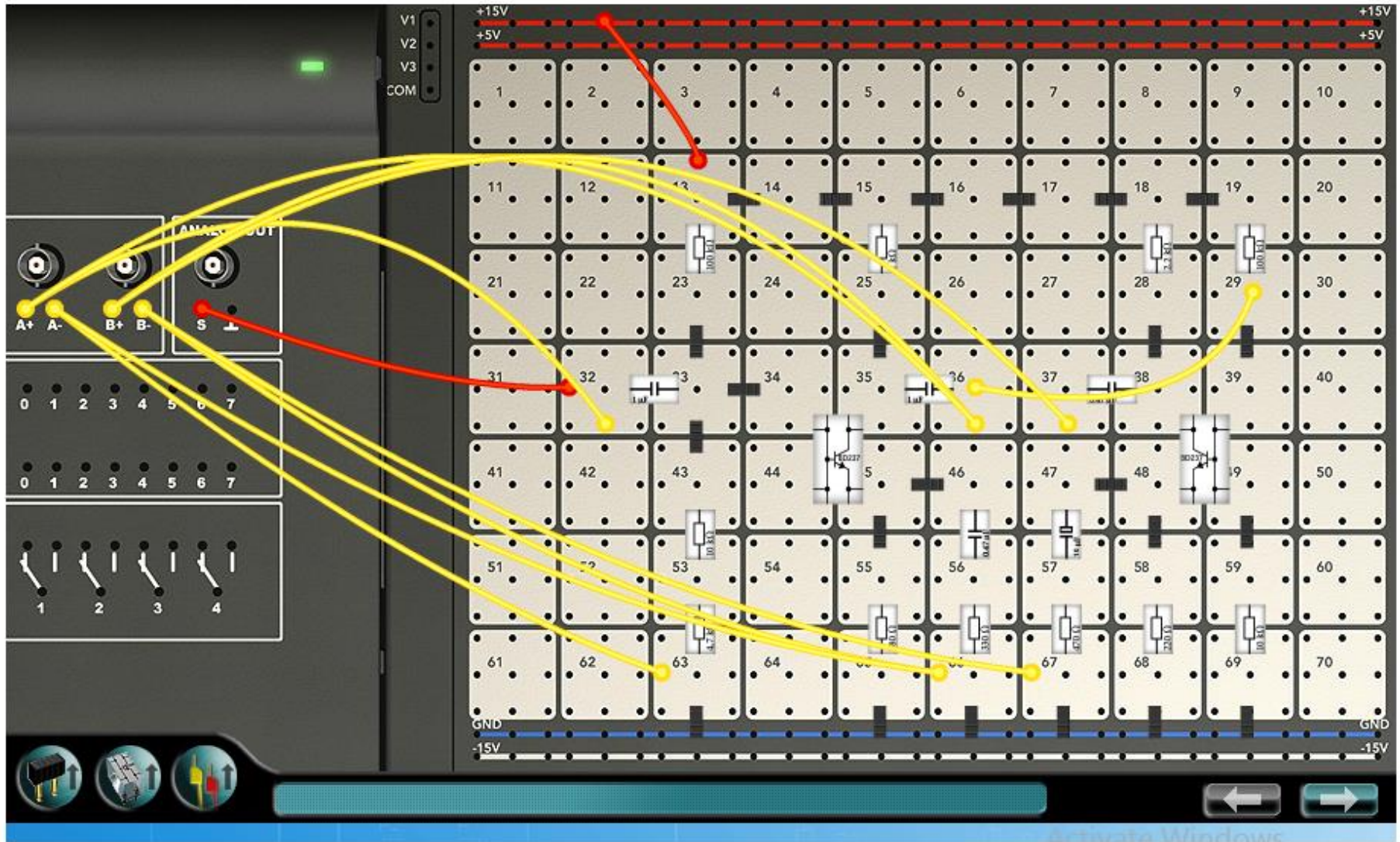

Experiment procedure and exercises

A sinusoidal AC voltage of 200 mV_{PP} with a frequency of 1 kHz is applied to the input V_{in}. Connect sets of leads numbers 1 and 2 to make these measurements.

Measure the input voltage V_{in} and the output voltage of the first stage V_{out1} and calculate the voltage gain.

$$V_{in} = \boxed{} \text{ mV}_{PP}$$

$$V_{out1} = \boxed{} \text{ mV}_{PP}$$

$$\text{Voltage gain } G_{\text{stage 1}} = \boxed{}$$

Now remove capacitor C₂.

Measure the input voltage V_{in} once again, as well as the output voltage V_{out1} of the first stage, in order to determine the voltage gain of the first stage without AC current feedback.

$$V_{in} = \boxed{} \text{ mV}_{PP}$$

$$V_{out1} = \boxed{} \text{ mV}_{PP}$$

$$\text{Voltage gain } G_{\text{stage 1 minus C2}} = \boxed{}$$

Next, put the capacitor C₂ back. The following measurements are to be made with sets of leads numbers 3 and 4.

Now determine the voltage gain of the second stage by measuring the input voltage for stage 2 = V_{out1} and the output voltage for stage 2 = V_{out2}.

$$V_{out1} = \boxed{} \text{ mV}_{PP}$$

$$V_{out2} = \boxed{} \text{ V}_{PP}$$

$$\text{Voltage gain } G_{\text{stage 2}} = \boxed{}$$

Calculate the total voltage for the circuit by two different means:

1. The ratio of the overall output voltage to the input voltage.
2. By multiplying the individual gain factors of the separate stages.

Method 1: Voltage gain $G_{\text{total}} =$

Method 2: Voltage gain $G_{\text{total}} =$

Now change the frequency of the function generators from 1 kHz to 200 Hz, keeping the voltage the same at 200 mV_{PP} and alter the oscilloscope time base from 200 μs/div to 1 ms/div in order to display two periods (two full waves).

Measure the input voltage V_{in} and the output voltage of the first stage V_{out1} , then calculate the voltage gain.

$V_{\text{in-200Hz}} =$ mV_{PP}

$V_{\text{out1-200Hz}} =$ mV_{PP}

Voltage gain $G_{\text{stage 1-200Hz}} =$

Now determine the voltage gain of the second stage at $f = 200$ Hz by measuring the input to stage 2 = V_{out1} and the output voltage of stage 2 = V_{out2} .

$V_{\text{out1-200Hz}} =$ mV_{PP}

$V_{\text{out2-200Hz}} =$ V_{PP}

Voltage gain $G_{\text{stage 2-200Hz}} =$

Calculate the total voltage for the circuit at $f = 200$ Hz by two different means:

1. The ratio of the overall output voltage to the input voltage.
2. By multiplying the individual gain factors of the separate stages.

Method 1: Voltage gain $G_{\text{total-200Hz}} =$

Method 2: Voltage gain $G_{\text{total-200Hz}} =$

