



Lecture (07)

BJT Amplifiers 4



By:

Dr. Ahmed ElShafee

Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits II


THE COMMON-BASE AMPLIFIER

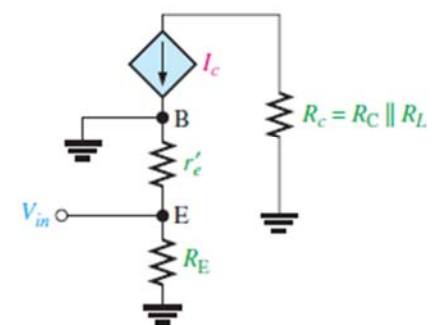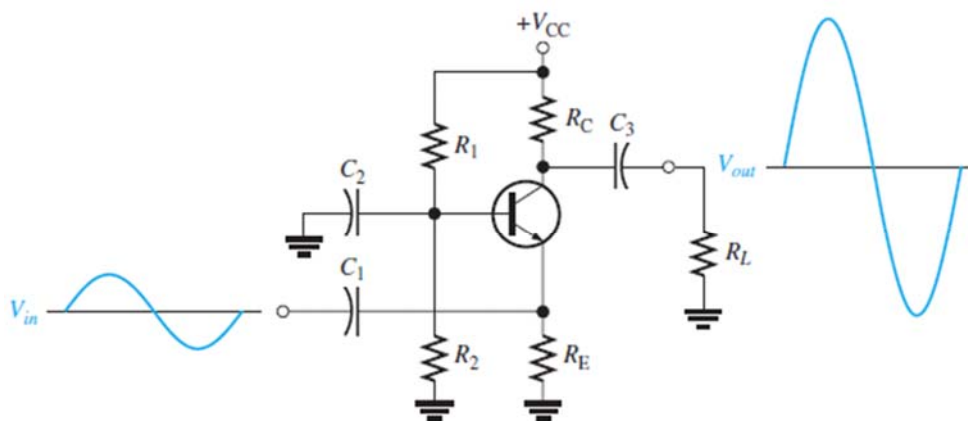- The base is the common terminal and is at ac ground because of capacitor C_2
- The input signal is capacitively coupled to the emitter.
- The output is capacitively coupled from the collector to a load resistor.




Voltage Gain

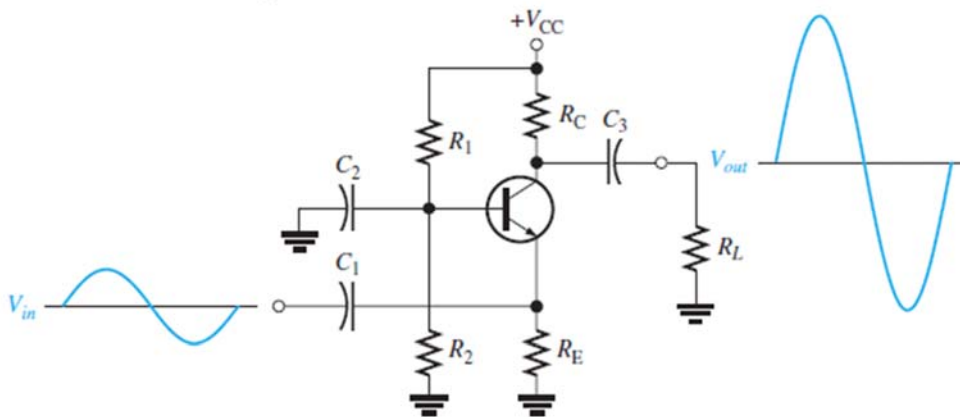- $V_{in} = V_e, V_{out} = V_c$
- $A_v = \frac{V_{out}}{V_{in}} = \frac{V_c}{V_e} = \frac{I_c R_c}{I_e (r'_e \parallel R_E)} \cong \frac{I_e R_c}{I_e (r'_e \parallel R_E)}$
- If $R_E \gg r'_e$, then
- $A_v \cong \frac{R_c}{r'_e}$



(a) Complete circuit with load

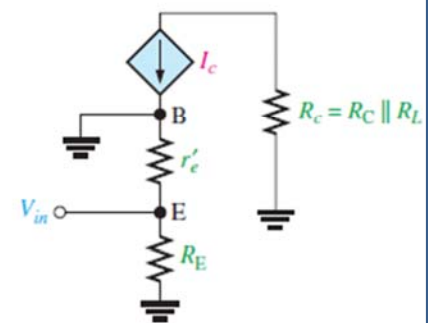


(b) AC equivalent model

Input Resistance

- $R_{in(emitter)} = \frac{V_{in}}{I_{in}} = \frac{V_e}{I_e} = \frac{I_e (r'_e \parallel R_E)}{I_e}$

If $R_E \gg r'_e$, then


$$R_{in(emitter)} \cong r'_e$$

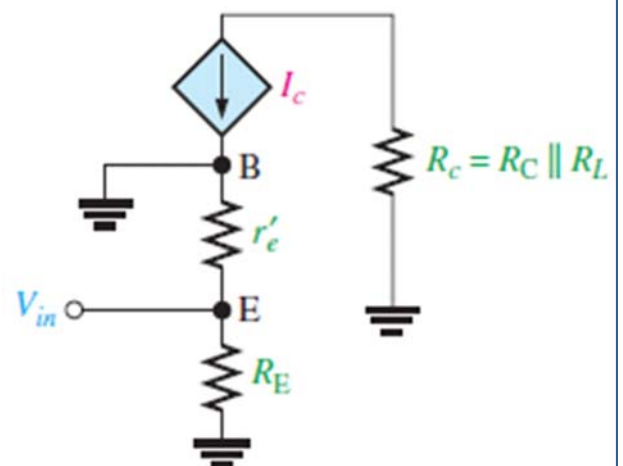

Output Resistance

- r'_c appears in parallel with R_C
- than R_C , r'_c is typically much larger

$$R_{out} \cong R_C$$

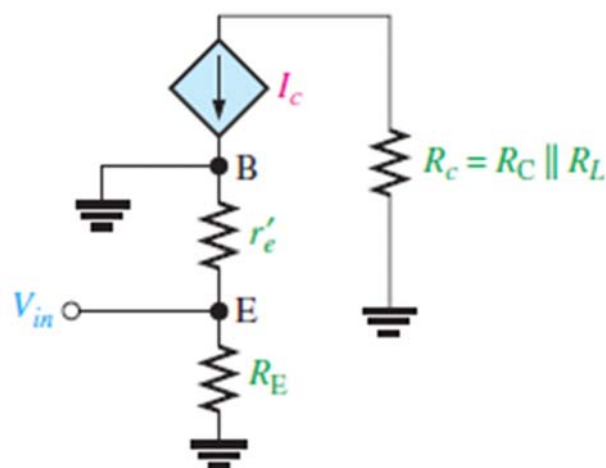


o

Dr. Ahmed ElShafee, ACU : Fall 2017, Elec

Current Gain

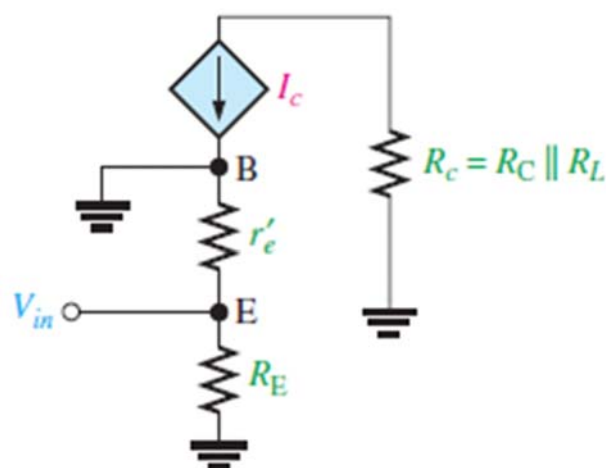- The current gain is the output current divided by the input current.
- I_c is the ac output current, and I_e is the ac input current.
- Since $I_c \cong I_e$,




7

Dr. Ahmed ElShafee, ACU : Fall 2017, Elec

Power Gain

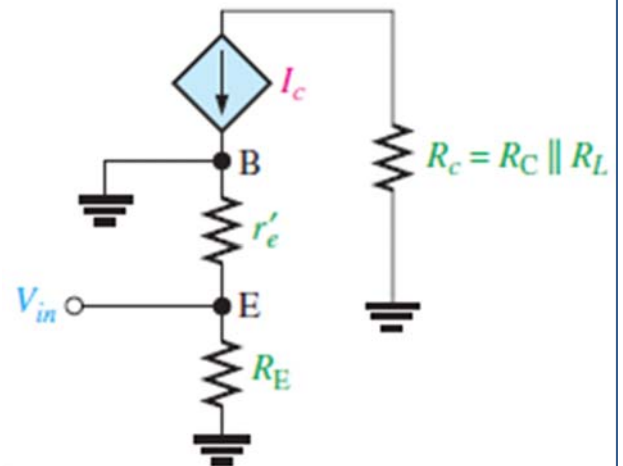- Since the current gain is approximately 1
- $A_p = A_v A_i$
- $A_p \cong A_v$




Y

Dr. Ahmed ElShafee, ACU : Fall 2017, Elec

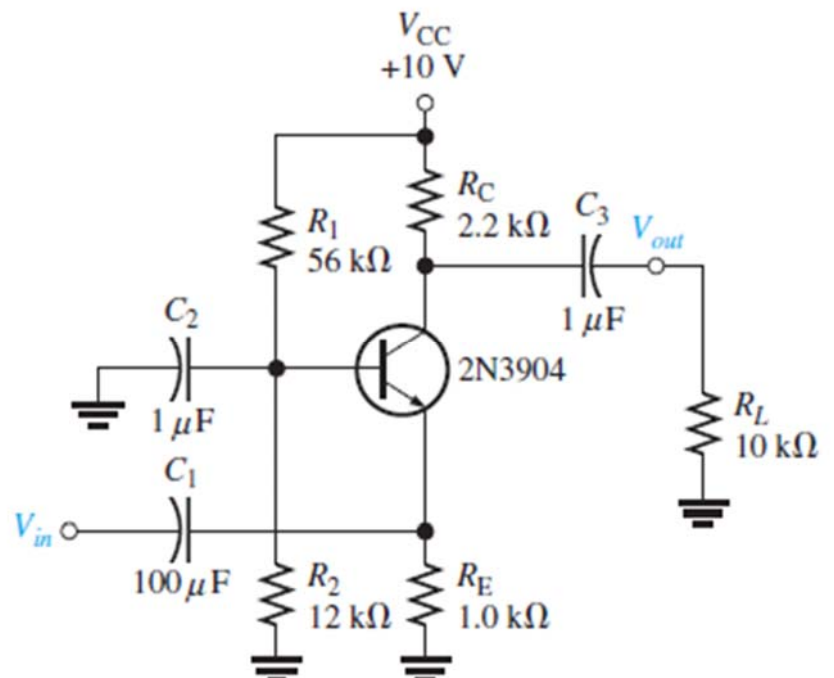Example 01

Find the input resistance, voltage gain, current gain, and power gain for the amplifier in Figure $\beta_{DC} = 250$.



A

Dr. Ahmed ElShaf


Example 01

First, find I_E so that you can determine r'_e . Then $R_{in} \cong r'_e$.

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(56 \text{ k}\Omega)(12 \text{ k}\Omega)}{56 \text{ k}\Omega + 12 \text{ k}\Omega} = 9.88 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{12 \text{ k}\Omega}{56 \text{ k}\Omega + 12 \text{ k}\Omega} \right) 10 \text{ V} = 1.76 \text{ V}$$
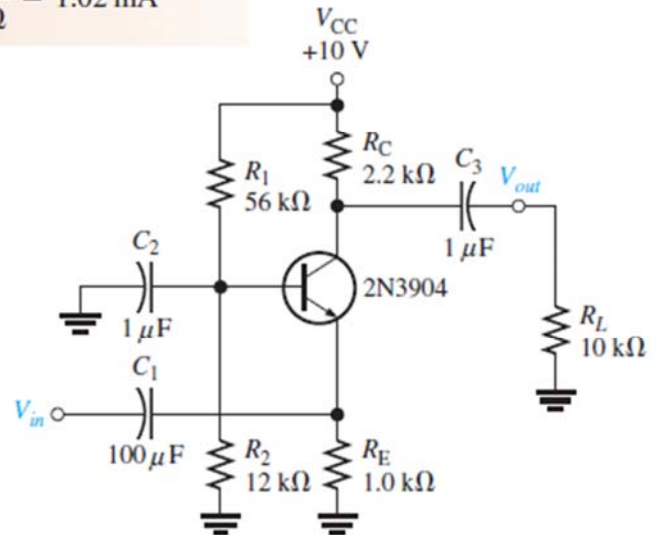
$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH}/\beta_{DC}} = \frac{1.76 \text{ V} - 0.7 \text{ V}}{1.0 \text{ k}\Omega + 39.5 \Omega} = 1.02 \text{ mA}$$



9

Dr. Ahmed ElShafee, ACU : Fall 2017

$$R_{in(emitter)} \cong r'_e$$

$$A_v \cong \frac{R_c}{r'_e} \quad A_p \cong A_v$$

Therefore,


$$R_{in} \cong r'_e = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{1.02 \text{ mA}} = 24.5 \Omega$$

Calculate the voltage gain as follows:

$$R_c = R_C \parallel R_L = 2.2 \text{ k}\Omega \parallel 10 \text{ k}\Omega = 1.8 \text{ k}\Omega$$

$$A_v = \frac{R_c}{r'_e} = \frac{1.8 \text{ k}\Omega}{24.5 \Omega} = 73.5$$

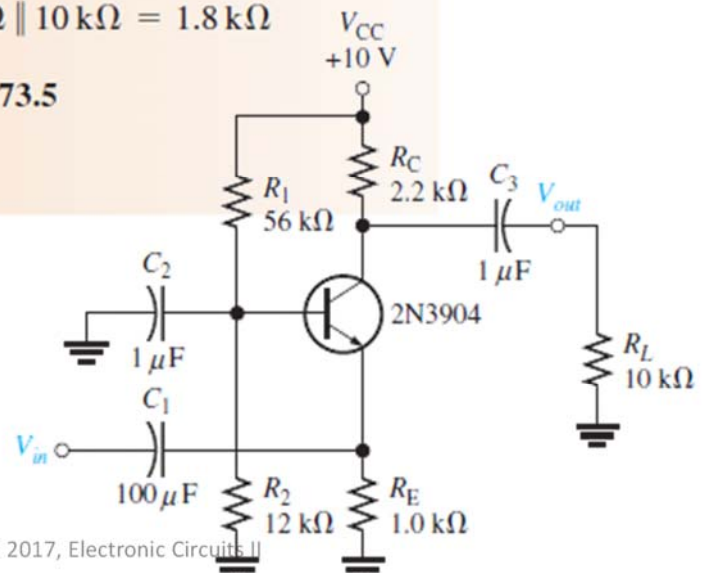Also, $A_i \cong 1$ and $A_p \cong A_v = 76.3$.




10

Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits II

Multistage Amplifier

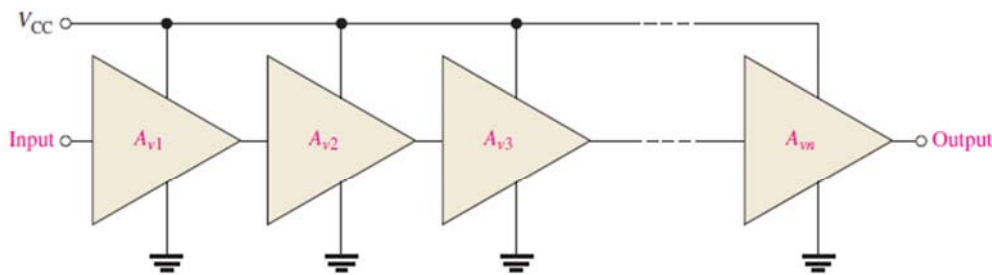- The overall voltage gain A'_v , of cascaded amplifiers,



$$A'_v = A_{v1}A_{v2}A_{v3} \dots A_{vn}$$

- Amplifier voltage gain is often expressed in **decibels (dB)** as follows:

$$A_{v(\text{dB})} = 20 \log A_v$$

11

Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits II

-
- This is particularly useful in **multistage** systems because the overall voltage gain in dB is the *sum* of the individual voltage gains in dB

$$A'_{v(\text{dB})} = A_{v1(\text{dB})} + A_{v2(\text{dB})} + \dots + A_{vn(\text{dB})}$$

12

Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits II

Example 02

A certain cascaded amplifier arrangement has the following voltage gains: $A_{v1} = 10$, $A_{v2} = 15$, and $A_{v3} = 20$. What is the overall voltage gain? Also express each gain in decibels (dB) and determine the total voltage gain in dB.

$$A'_v = A_{v1}A_{v2}A_{v3} = (10)(15)(20) = 3000$$

$$A_{v1(\text{dB})} = 20 \log 10 = 20.0 \text{ dB}$$

$$A_{v2(\text{dB})} = 20 \log 15 = 23.5 \text{ dB}$$


$$A_{v3(\text{dB})} = 20 \log 20 = 26.0 \text{ dB}$$

$$A'_{v(\text{dB})} = 20.0 \text{ dB} + 23.5 \text{ dB} + 26.0 \text{ dB} = 69.5 \text{ dB}$$

- $A_v = 10^{A_{v(\text{dB})}/20} = 10^{(69.5/20)} = 2985.38$

Capacitively-Coupled Multistage Amplifier

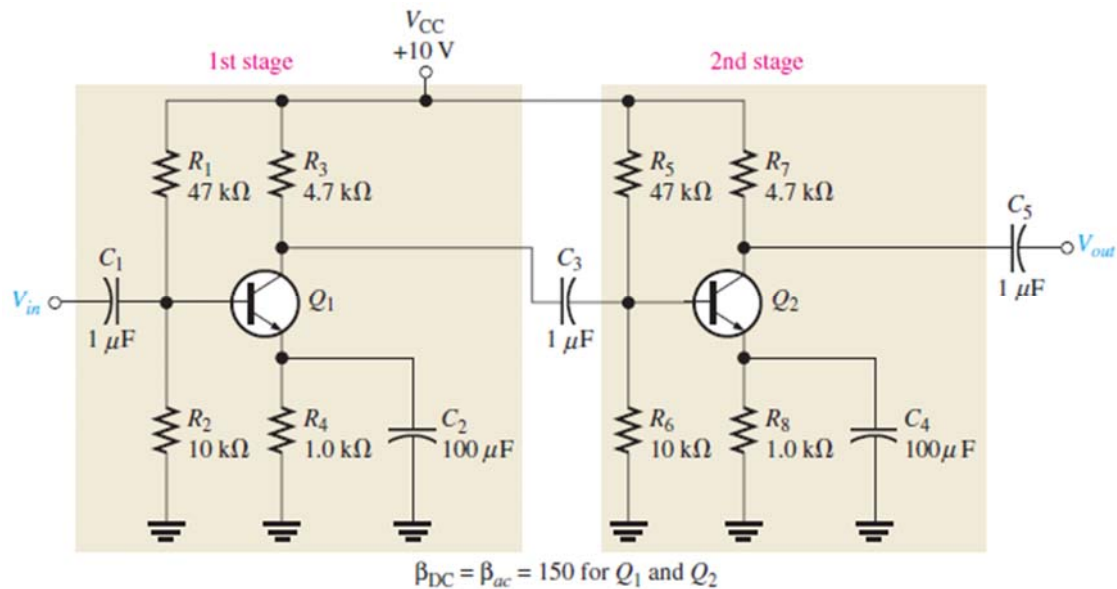
- we will use the two-stage capacitively coupled amplifier in Figure
- The output of the first stage capacitively coupled to the input of the second stage.



- Capacitive coupling prevents the dc bias of one stage from affecting that of the other but allows the ac signal to pass without attenuation $X_C = \infty$

Loading Effects

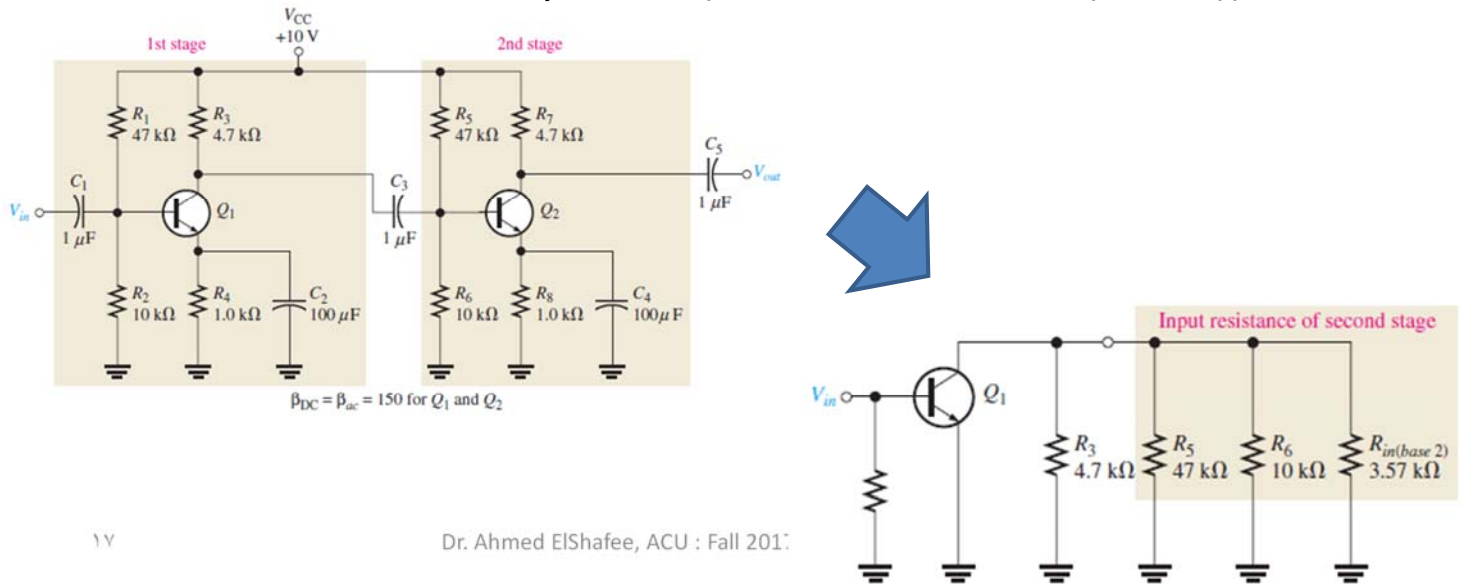- the total input resistance of the second stage presents an ac load to the first stage.
- the effective ac collector resistance of Q_1 is the total of all these resistances in parallel ($R_3, R_5, R_6,$ and $R_{in(base2)}$)



١٧

Dr. Ahmed ElShafee, ACU : Fall 2017

- The ac collector resistance of the first stage is

$$R_{c1} = R_3 \parallel R_5 \parallel R_6 \parallel R_{in(base2)}$$

$$R_{c1} = 4.7\text{ k}\Omega \parallel 47\text{ k}\Omega \parallel 10\text{ k}\Omega \parallel 3.57\text{ k}\Omega = 1.63\text{ k}\Omega$$

- You can verify that $I_E = 1.05\text{ mA}$, $r'_e = 23.8\text{ }\Omega$, and $R_{in(base2)} = 3.57\text{ k}\Omega$.
- Therefore, the base-to-collector voltage gain of the first stage is

$$A_{v1} = \frac{R_{c1}}{r'_e} = \frac{1.63\text{ k}\Omega}{23.8\text{ }\Omega} = 68.5$$

- **Voltage Gain of the Second Stage;** The second stage has no load resistor, so the ac collector resistance is R_7 , and the gain is

$$A_{v2} = \frac{R_7}{r'_e} = \frac{4.7\text{ k}\Omega}{23.8\text{ }\Omega} = 197$$

١٨

Dr. Ahmed ElShafee, ACU : Fall 2017, Electronic Circuits II

- **Overall Voltage Gain**

$$A'_v = A_{v1}A_{v2} = (68.5)(197) \cong 13,495$$

- If an input signal of 100uv , then output voltage is = (100 mV)(13,495) =1.35 V

$$A'_{v(\text{dB})} = 20 \log (13,495) = 82.6 \text{ dB}$$

DC Voltages in the Capacitively Coupled Multistage Amplifier

- Since both stages are identical, the dc voltages for Q1 and Q2 are the same.
- $\beta_{DC}R4 \gg R2, \beta_{DC}R8 \gg R6$


$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{10 \text{ k}\Omega}{57 \text{ k}\Omega} \right) 10 \text{ V} = 1.75 \text{ V}$$

$$V_E = V_B - 0.7 \text{ V} = 1.05 \text{ V}$$

$$I_E = \frac{V_E}{R_4} = \frac{1.05 \text{ V}}{1.0 \text{ k}\Omega} = 1.05 \text{ mA}$$

$$I_C \cong I_E = 1.05 \text{ mA}$$

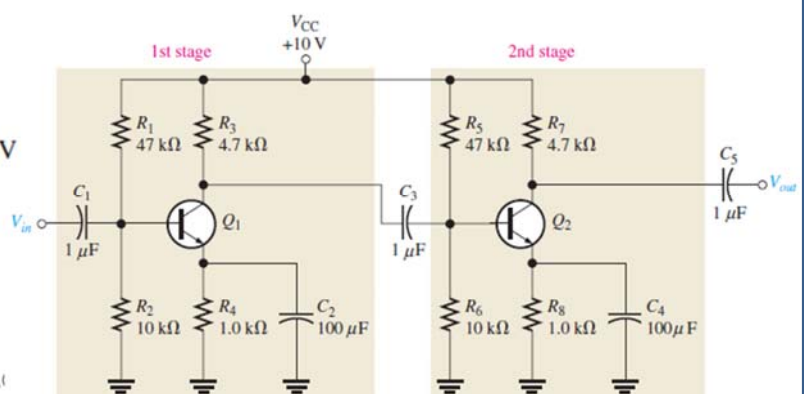
$$V_C = V_{CC} - I_C R_3 = 10 \text{ V} - (1.05 \text{ mA})(4.7 \text{ k}\Omega) = 5.07 \text{ V}$$



$\beta_{DC} = \beta_{ac} = 150$ for Q1 and Q2

Direct-Coupled Multistage Amplifiers

- no coupling or bypass capacitors in this circuit.
- The dc collector voltage of the first stage provides the base-bias voltage for the second stage.
- Because of the direct coupling, this type of amplifier has a better low-frequency response (Direct-coupled amplifiers can be used to amplify low frequencies all the way down to dc (0 Hz)) than the capacitively coupled.
- The increased reactance of capacitors at lower frequencies produces gain reduction in capacitively coupled amplifiers.

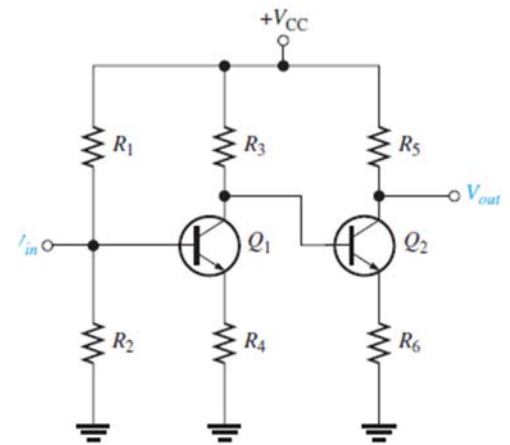

Thanks,..
See you next week (ISA),...