



كلية الهندسة

Faculty of Engineering





جامعة الأهرام الكندية
AHRAM CANADIAN UNIVERSITY

Electronic Circuits II – Tutorial


01

1	The linear region of a transistor's operation lies between saturation and cutoff.	T
---	---	---

MCQ

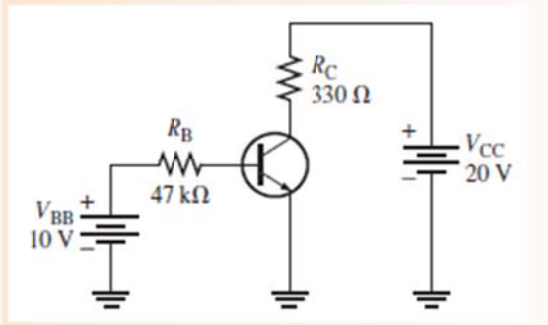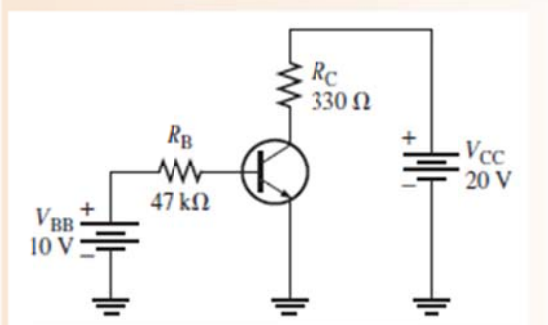
#	Question	
1	<p>If V_{BB} in Figure is increased, the Q-point value of collector current will</p>  <p>(a) increase (b) decrease (c) not change</p>	a
2	<p>If V_{BB} in Figure is increased, the Q-point value of V_{CE} will</p>  <p>(a) increase (b) decrease (c) not change</p>	b

Problems

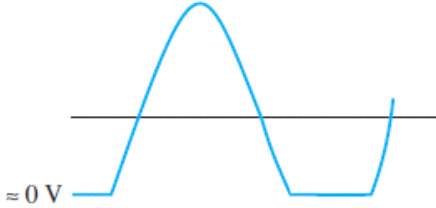Q1	<p>The output (collector voltage) of a biased transistor amplifier is shown in Figure . Is the transistor biased too close to cutoff or too close to saturation?</p> 
Sol 1	<p>.....</p> <div style="border: 1px solid black; width: 500px; height: 40px; margin: 10px auto;"></div> <p>.....</p>

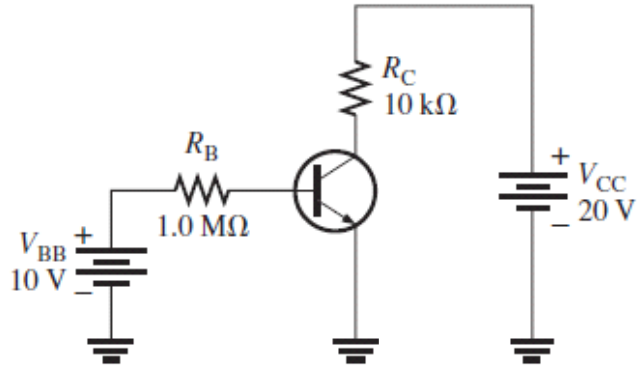
Q
2

Determine the intercept points of the dc load line on the vertical and horizontal axes of collector-characteristic curves for the circuit in Figure




So
12

.....
 $V_{CE} = 20 \text{ V}; I_{C(\text{sat})} = 2 \text{ mA}$

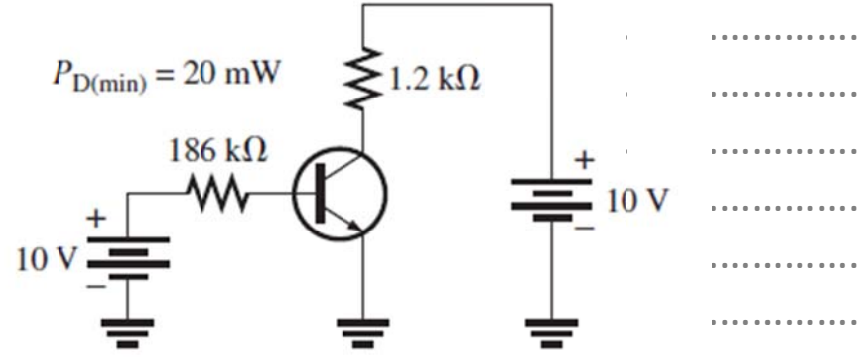Q3	<p>Design a biased-transistor circuit using $V_{BB} = V_{CC} = 10 \text{ V}$ for a Q-point of $I_C = 5 \text{ mA}$ and $V_{CE} = 4 \text{ V}$. Assume $\beta_{DC} = 100$. The design involves finding R_B, R_C, and the <i>minimum</i> power rating of the transistor. (The actual power rating should be greater.) Sketch the circuit.</p>
Sol 3	<p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p>  <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p>

Q4

► FIGURE

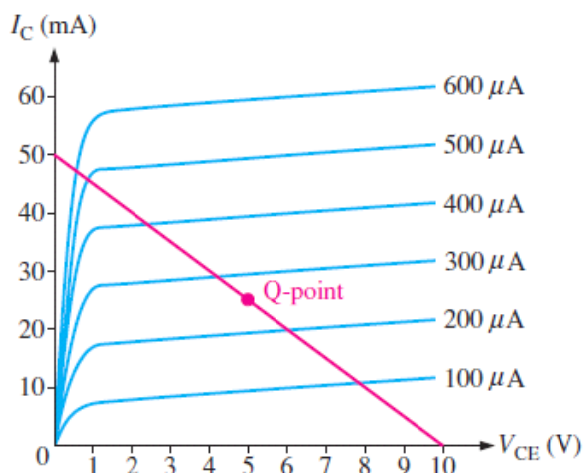

From the collector characteristic curves and the dc load line in Figure , determine the following:

- (a) Collector saturation current
- (b) V_{CE} at cutoff
- (c) Q-point values of I_B , I_C , and V_{CE}

Sol
4

-
- ... (a) $I_{C(sat)} = 50 \text{ mA}$
- ... (b) $V_{CE(CUTOFF)} = 10 \text{ V}$
- ... (c) $I_B = 250 \mu A; I_C = 25 \text{ mA}; V_{CE} = 5 \text{ V}$
-
-
-