


Electronic Circuits II - Tutorial 05



BJT Amplifiers 2

T & F


#		
1	In an amplifier, a coupling capacitor should appear ideally as a short to the signal.	T
2	r parameters include	T
3	h parameters are never specified on a datasheet.	F
4	The r parameter is the same as the h parameter hfe.	T
5	A bypass capacitor in a CE amplifier decreases the voltage gain.	F
6	If RC in a CE amplifier is increased, the voltage gain is reduced.	F
7	The load is the amount of current drawn from the output of an amplifier.	T
8	In a CE amplifier, the gain can be stabilized by using a swamping resistor.	T

MCQ
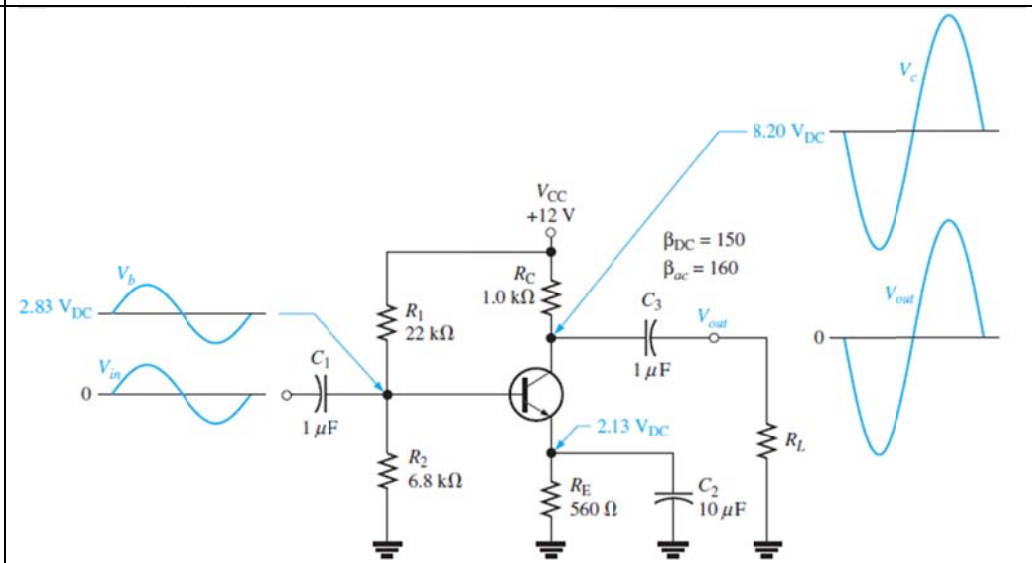
#	Question	Answer
1	 <p>If the transistor in Figure is exchanged for one with higher betas, Vout will (a) increase (b) decrease (c) not change</p>	a

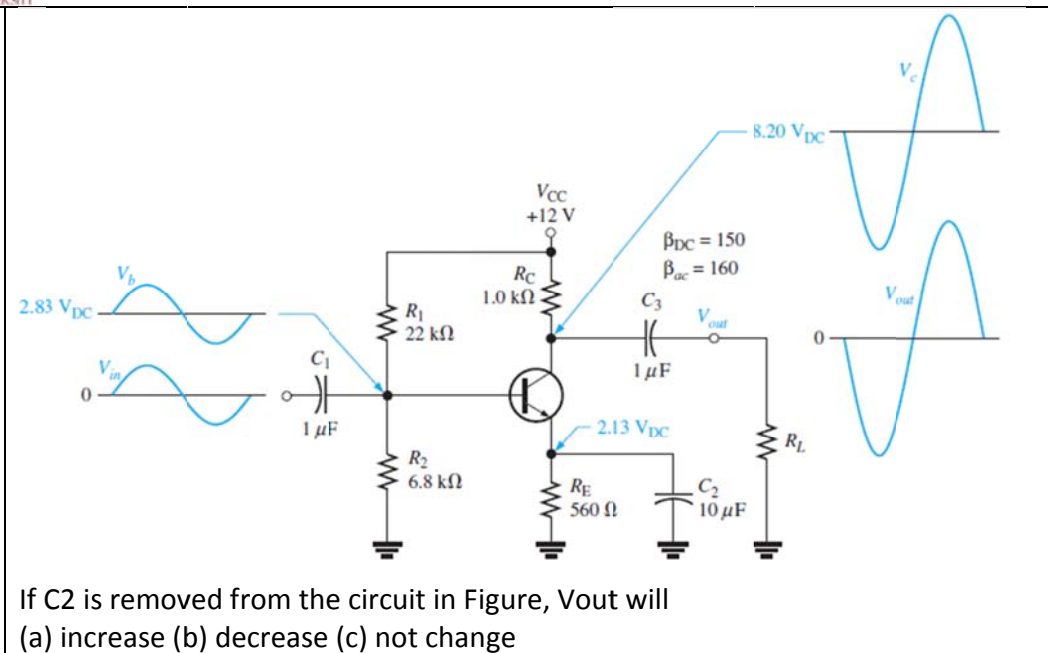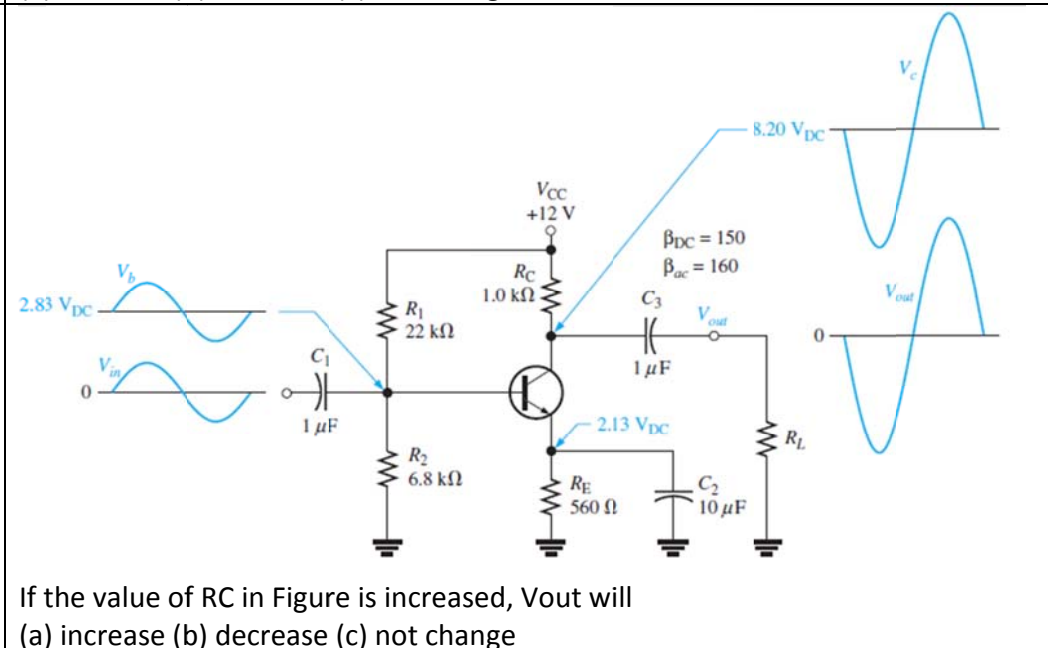2	 <p>If C2 is removed from the circuit in Figure, Vout will (a) increase (b) decrease (c) not change</p>	b
3	 <p>If the value of RC in Figure is increased, Vout will (a) increase (b) decrease (c) not change</p>	a


4

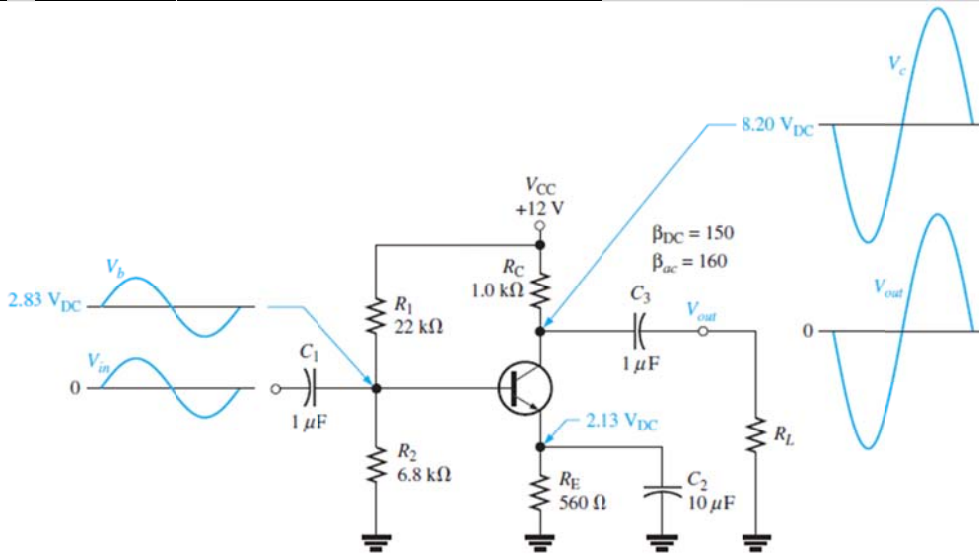

b



If the amplitude of V_{in} in Figure is decreased, V_{out} will
 (a) increase (b) decrease (c) not change

Q2

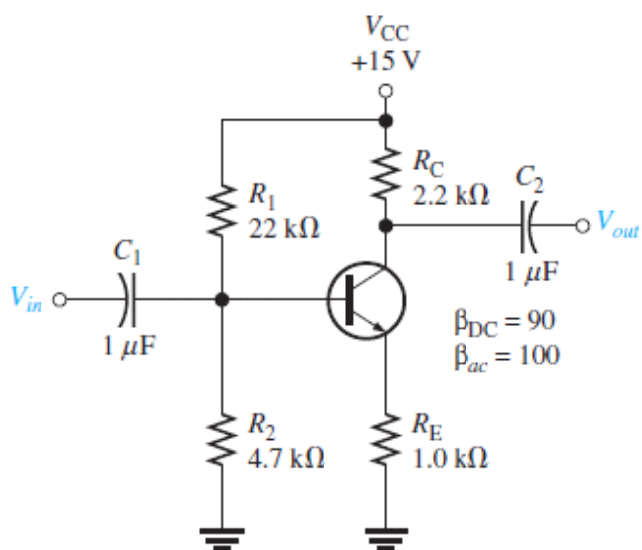

Draw the dc equivalent circuit and the ac equivalent circuit for the unloaded amplifier in Figure

Sol
2

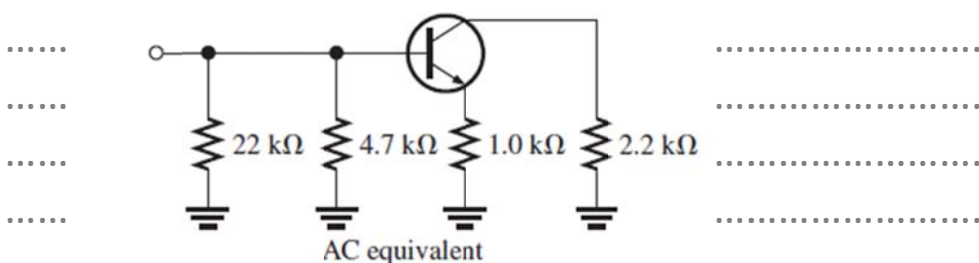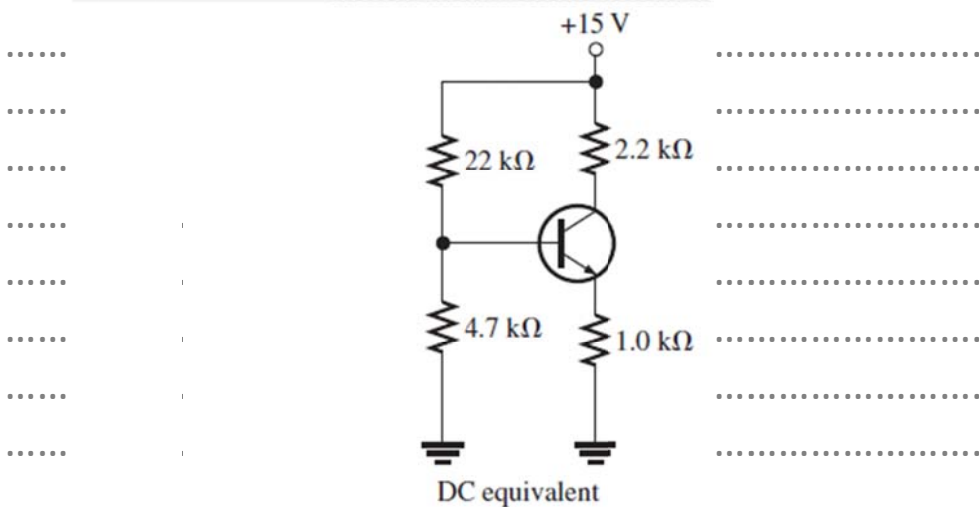



كلية الهندسة

Faculty of Engineering

FACULTY OF ENGINEERING
AHRAM CANADIAN UNIVERSITY



جامعة الأهرام الكندية
AHRAM CANADIAN UNIVERSITY

A large rectangular area with horizontal dotted lines for writing.



كلية الهندسة


Faculty of Engineering



جامعة الأهرام الكندية
AHRAM CANADIAN UNIVERSITY

A large rectangular area with horizontal dotted lines, intended for student answers or notes.

Q4

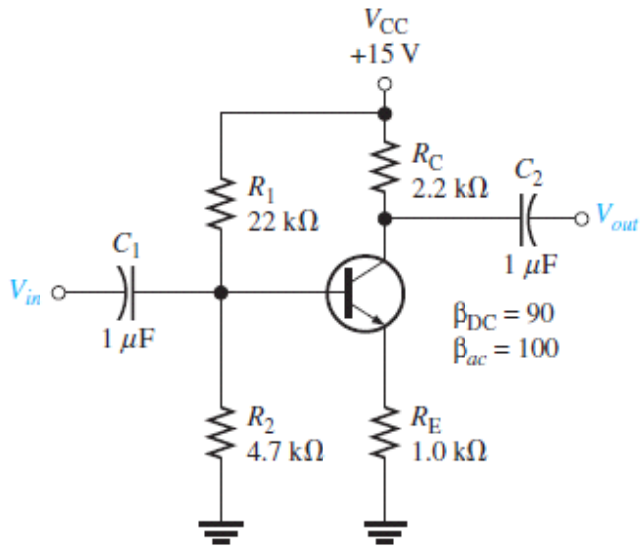


Calculate the quiescent power dissipation in Figure

Sol
4

..... 37.5 mW

Q6

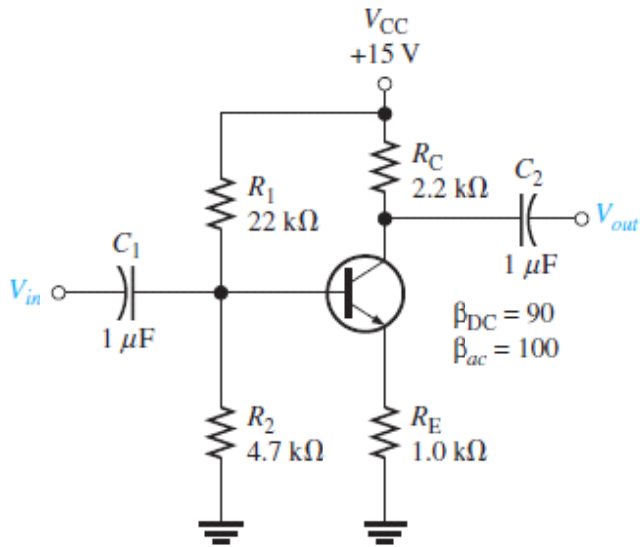

Connect a bypass capacitor across R_E in Figure , and repeat

(a) $R_{in(base)}$ (b) $R_{in(tot)}$ (c) A_v

Sol
6

... (a) 1.29kΩ (b) 968 Ω (c) 171



كلية الهندسة

Faculty of Engineering



جامعة الأهرام الكندية
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a dotted line border, intended for student answers or notes.



كلية الهندسة

Faculty of Engineering



جامعة الأهرام الكندية
AHRAM CANADIAN UNIVERSITY

A large rectangular area with a dotted line pattern, intended for handwritten notes or answers.