

Electronic Circuits II - Tutorial 08

#		
1	The JFET always operates with a reverse-biased gate-to-source pn junction.	T
2	The channel resistance of a JFET is a constant.	F
3	The gate-to-source voltage of an n -channel JFET must be negative.	T
4	I_D becomes zero at the pinch-off voltage.	F
5	V_{GS} has no effect on I_D .	F
6	$V_{GS(off)}$ and V_P are always equal in magnitude but opposite in polarity.	T
7	The JFET is a square-law device because of the mathematical expression of its transfer characteristic curve	T
8	Forward transconductance is the change in drain voltage for a given change in gate voltage.	F

MCQ


#	Question	Answer
1	1. The JFET is (a) a unipolar device (b) a voltage-controlled device (c) a current-controlled device (d) answers (a) and (c) (e) answers (a) and (b)	e
2	The channel of a JFET is between the (a) gate and drain (b) drain and source (c) gate and source (d) input and output	b
3	A JFET always operates with (a) the gate-to-source pn junction reverse-biased (b) the gate-to-source pn junction forward-biased (c) the drain connected to ground (d) the gate connected to the source	a
4	I_{DSS} is (a) the drain current with the source shorted (b) the drain current at cutoff (c) the maximum possible drain current (d) the midpoint drain current	c
5	Drain current in the constant-current region increases when (a) the gate-to-source bias voltage decreases (b) the gate-to-source bias voltage increases (c) the drain-to-source voltage increases (d) the drain-to-source voltage decreases	a



6	A certain JFET datasheet gives $V_{GS(off)} = -4 \text{ V}$. The pinch-off voltage, V_P , (a) cannot be determined (b) is -4 V (c) depends on V_{GS} (d) is $+4 \text{ V}$	d
7	The JFET in Question <input type="text" value="6"/> (a) is an n channel (b) is a p channel (c) can be either	a
8	For a certain JFET, $I_{GSS} = 10 \text{ nA}$ at $V_{GS} = 10 \text{ V}$. The input resistance is (a) $100 \text{ M}\Omega$ (b) $1 \text{ M}\Omega$ (c) $1000 \text{ M}\Omega$ (d) $1000 \text{ M}\Omega$	C
9	<p>If the value of R_D in Figure is increased, I_D will (a) increase (b) decrease (c) not change</p>	b
10	For a certain p -channel JFET, $V_{GS(off)} = 8 \text{ V}$. The value of V_{GS} for an approximate midpoint bias is (a) 4 V (b) 0 V (c) 1.25 V (d) 2.34 V	d
11	The drain-to-source resistance in the ohmic region depends on (a) V_{GS} (b) the Q-point values (c) the slope of the curve at the Q-point (d) all of these	d




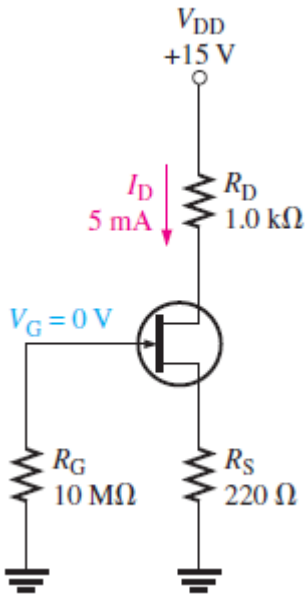12 If the drain current in Figure 8-17 is increased, V_{DS} will



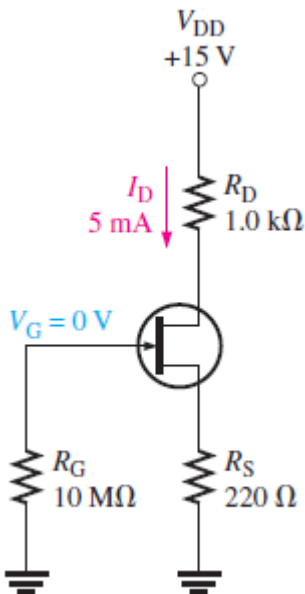
(a) increase (b) decrease (c) not change

13 If the drain current in Figure is increased, V_{GS} will



(a) increase (b) decrease (c) not change

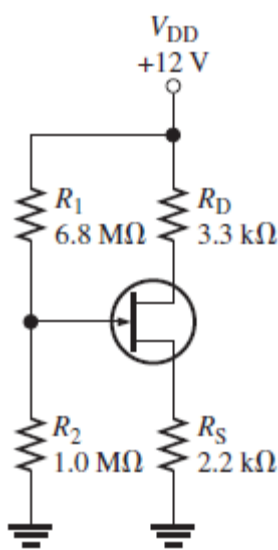

14	For $V_{GS} = 0$ V, the drain current becomes constant when V_{DS} exceeds (a) cutoff (b) V_{DD} (c) V_P (d) 0 V	a
15	The constant-current region of a FET lies between (a) cutoff and saturation (b) cutoff and pinch-off (c) 0 and V_{DS} (d) pinch-off and breakdown	c
16	In a certain FET circuit, $V_{GS} = 0$ V, $V_{DD} = 15$ V, $I_{DSS} = 15$ mA, and $R_D = 470$ Ω . If R_D is decreased to 330 Ω , I_{DSS} is (a) 19.5 mA (b) 10.5 mA (c) 15 mA (d) 1 mA	c
17	At cutoff, the JFET channel is (a) at its widest point (b) completely closed by the depletion region (c) extremely narrow (d) reverse-biased	b
18	 <p>If the value of R_2 in Figure is decreased, V_G will (a) increase (b) decrease (c) not change</p>	b
19	In a self-biased JFET, the gate is at (a) a positive voltage (b) 0 V (c) a negative voltage (d) ground	b





20	To be used as a variable resistor, a JFET must be (a) an n -channel device (b) a p -channel device (c) biased in the ohmic region (d) biased in saturation	c
21	When a JFET is biased at the origin, the ac channel resistance is determined by (a) the Q-point values (b) V_{GS} (c) the transconductance (d) answers (b) and (c)	d



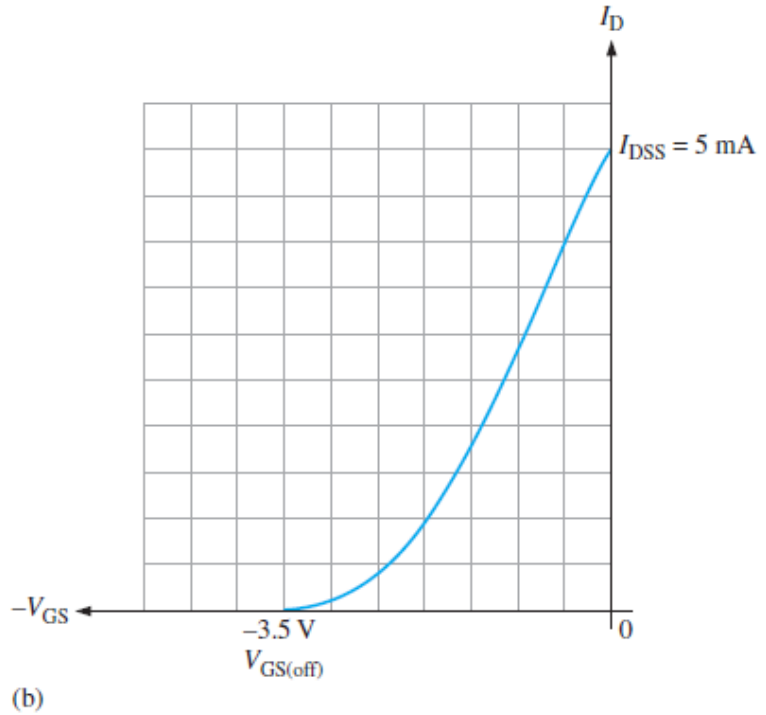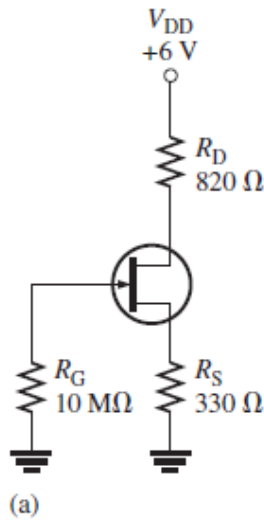Q1
2

Graphically determine the Q-point for the circuit in Figure (a) using the transfer characteristic curve in Figure (b).



Sol
12

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....



.....

.....



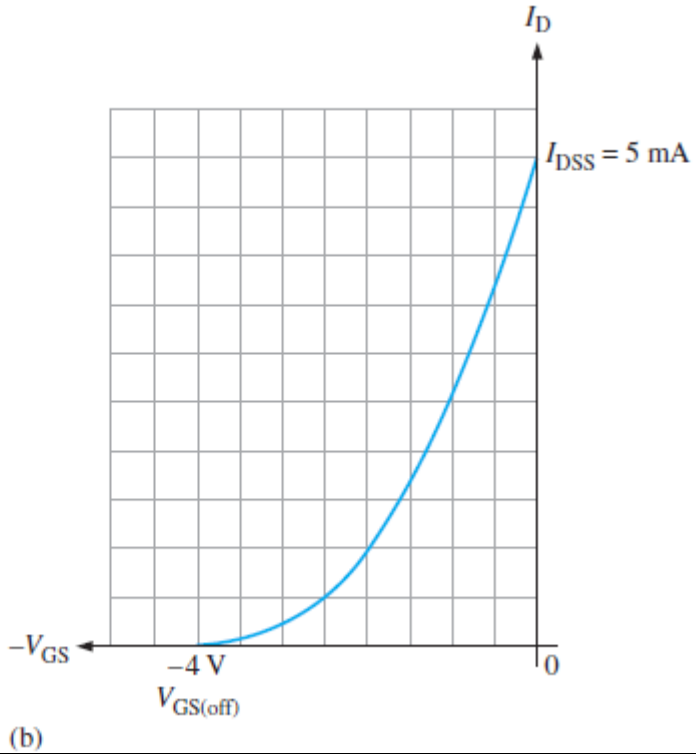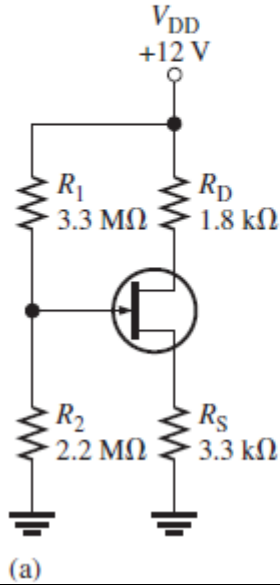Q29

. Find the Q-point values for the JFET with voltage-divider bias in Figure



Sol
29

.....

 $I_D \cong 1.9 \text{ mA}, V_{GS} \cong -1.5 \text{ V}$

