



Lecture (01)

Transistor operating point & DC Load line




By:

Dr. Ahmed ElShafee

Dr. Ahmed ElShafee, ACU : Fall 2018, Electronic Circuits II

BJT Characteristic

Collector Characteristic Curves

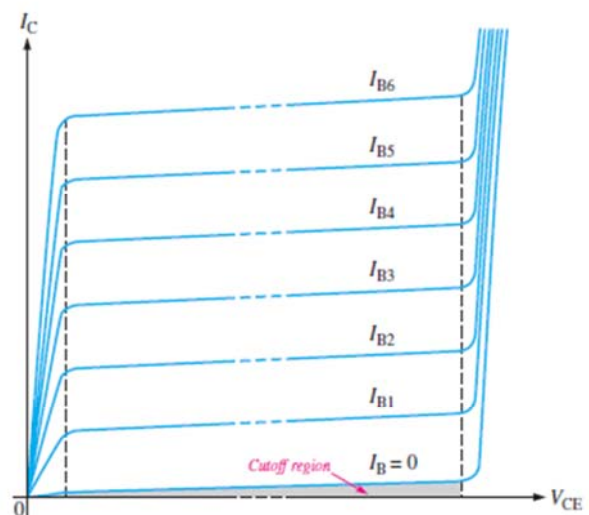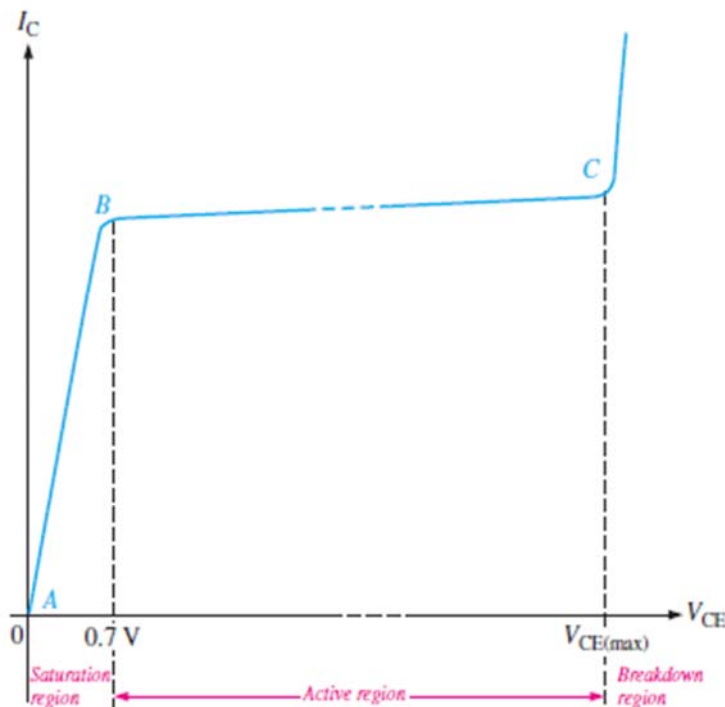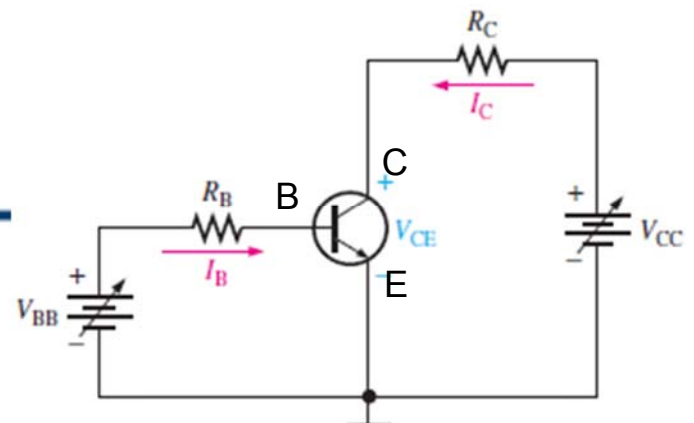

(c) Family of I_C versus V_{CE} curves for several values of I_B ($I_{B1} < I_{B2} < I_{B3}$, etc.)

BJT modes of operation



- **Conditions in Cutoff**

$$V_{CE(\text{cutoff})} = V_{CC}$$

- **Conditions in Saturation**

$$I_{C(\text{sat})} = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C}$$

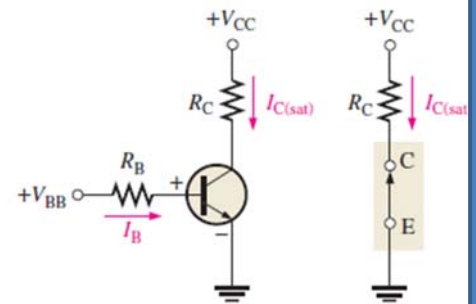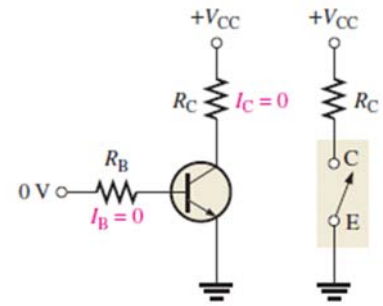
$$I_{B(\text{min})} = \frac{I_{C(\text{sat})}}{\beta_{DC}}$$



r

DC Bias

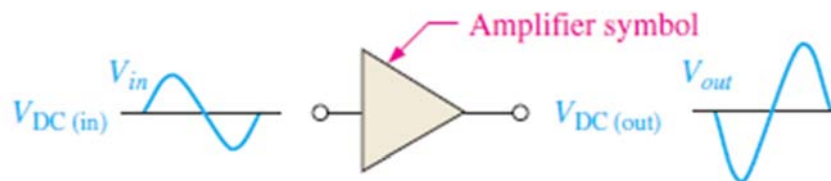- Following Figure shows the effects of proper and improper dc biasing of an inverting amplifier.




(a) Linear operation: larger output has same shape as input except that it is inverted

which means that it is out of phase with the input. The output signal swings equally above and below the dc bias level of the output, $V_{DC}(\text{out})$.

ε

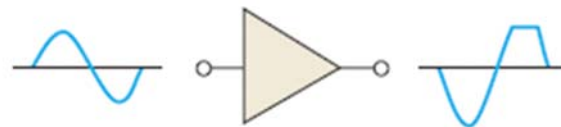-
- If an amplifier is not biased with correct dc voltages on the input and output, it can go into saturation or cutoff when an input signal is applied
 - Improper biasing can cause distortion in the output signal




(b) Nonlinear operation: output voltage limited (clipped) by cutoff

Figure illustrates limiting of the positive portion of the output voltage as a result of a Q-point (dc operating point) being too close to cutoff

◦

Dr. Ahmed ElShafee, ACU : Fall 2018, Electronic Circuits II

•

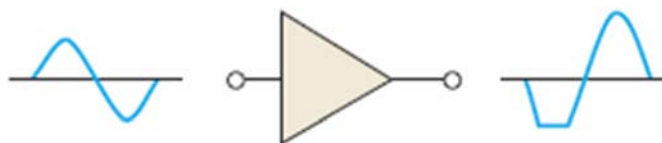


(c) Nonlinear operation: output voltage limited (clipped) by saturation

limiting of the negative portion of the output voltage as a result of a dc operating point being too close to saturation.


7

Dr. Ahmed ElShafee, ACU : Fall 2018, Electronic Circuits II

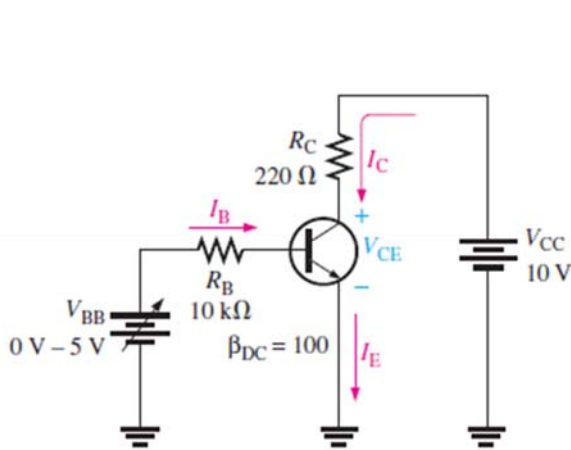- The transistor in Figure is biased with V_{CC} and V_{BB} to obtain certain values of I_B , I_C , and V_{CE} .



(a) DC biased circuit

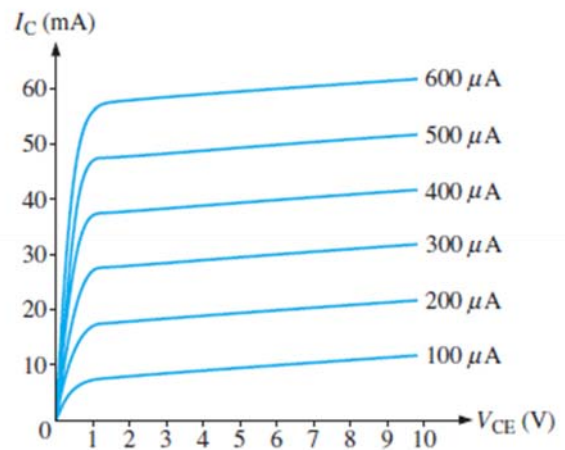


(b) Collector characteristic curves

Y


Dr. Ahmed ElShafee, ACU : Fall 2018, Electronic Circuits II

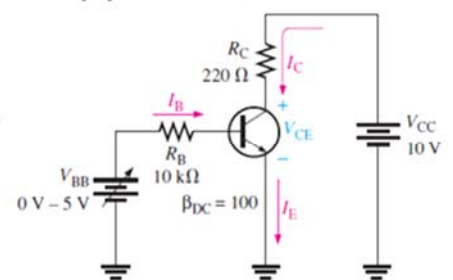- assign three values to I_B and observe what happens to I_C and V_{CE} .
- V_{BB} is adjusted to produce an I_B of $200 \mu\text{A}$
- Since $I_C = \beta I_B$
- the collector current is 20 mA ,




$$V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (20 \text{ mA})(220 \Omega) = 10 \text{ V} - 4.4 \text{ V} = 5.6 \text{ V}$$

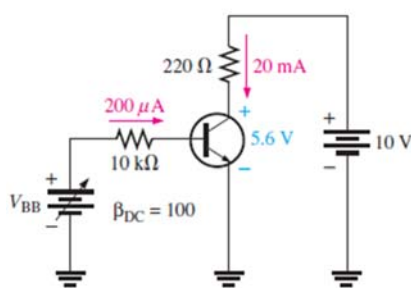- This Q-point is shown on the graph of Figure




(a) $I_B = 200 \mu\text{A}$

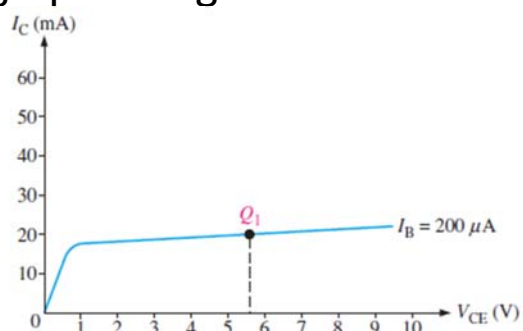



A

- V_{BB} is increased to produce an I_B of 300 μA and an I_C of 30 mA.
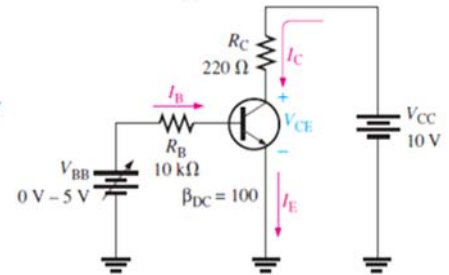
$$V_{CE} = 10\text{ V} - (30\text{ mA})(220\ \Omega) = 10\text{ V} - 6.6\text{ V} = 3.4\text{ V}$$




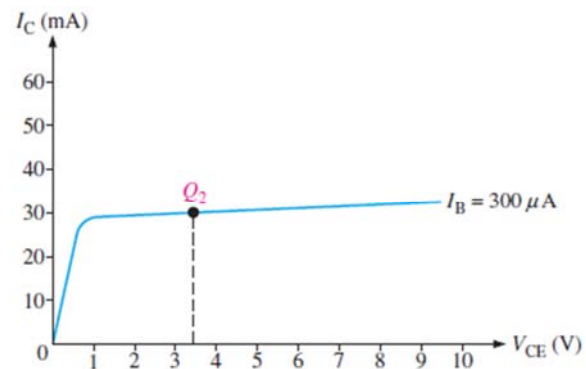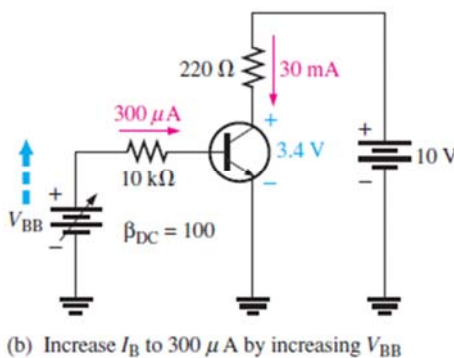- The Q-point for this condition is indicated by Q_2 on the graph






- V_{BB} is increased to give an I_B 400 μA of and an I_C of 40 mA.
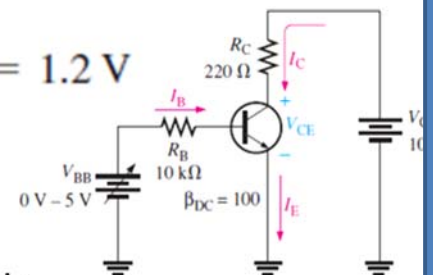
$$V_{CE} = 10\text{ V} - (40\text{ mA})(220\ \Omega) = 10\text{ V} - 8.8\text{ V} = 1.2\text{ V}$$



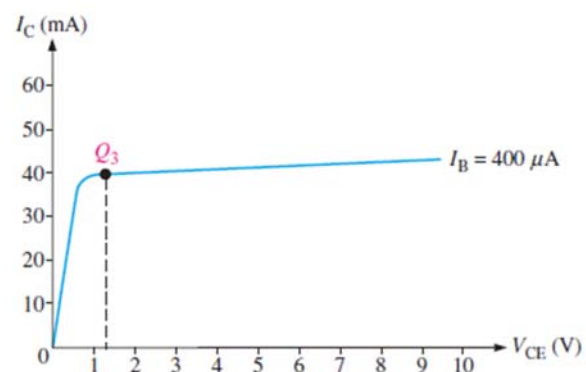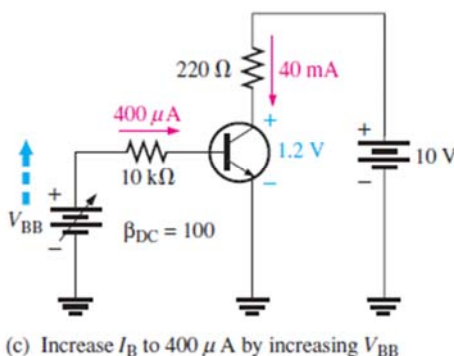- Q_3 is the corresponding Q-point on the graph.



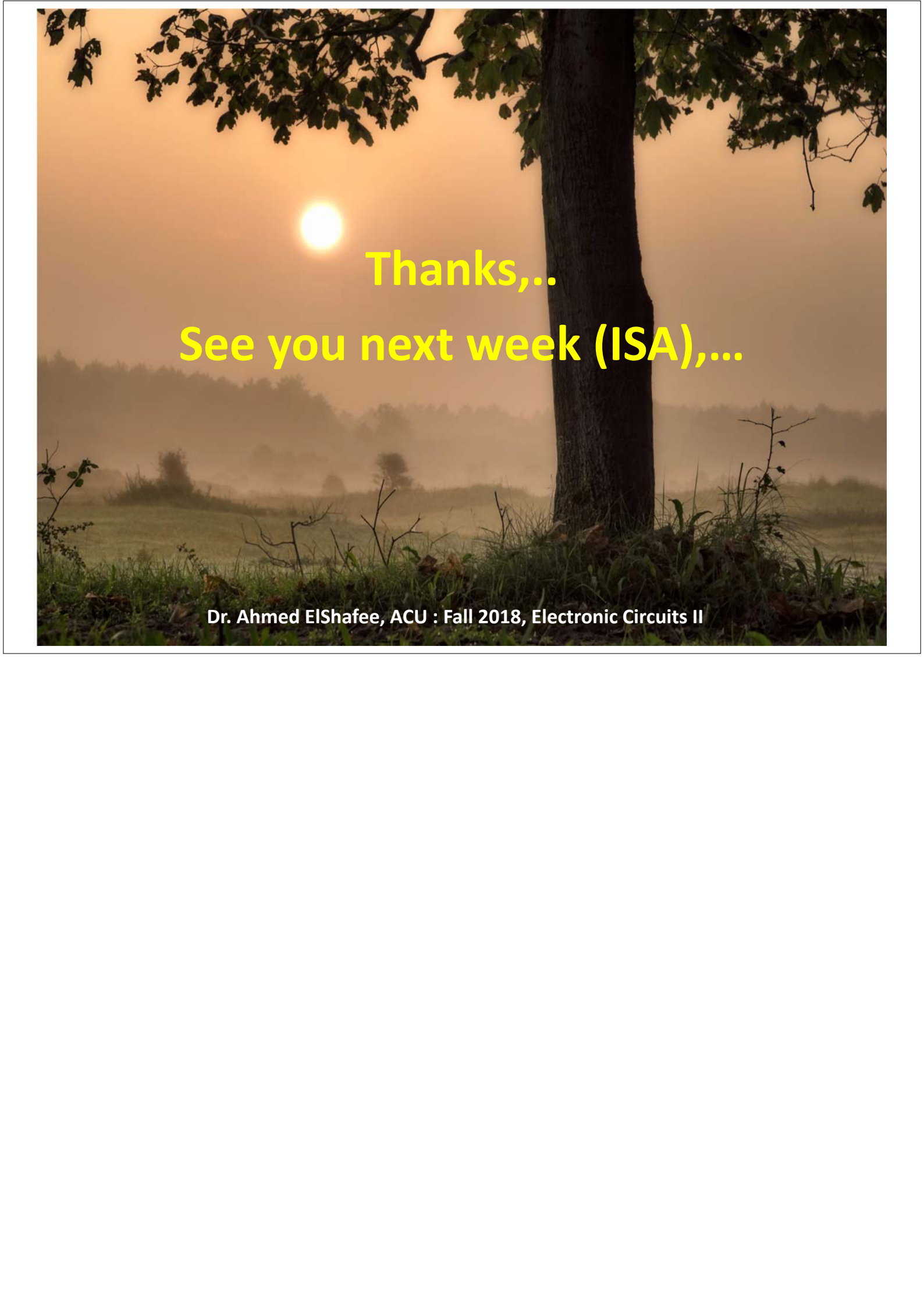

Thanks,..
See you next week (ISA),...

Dr. Ahmed ElShafee, ACU : Fall 2018, Electronic Circuits II