



جامعة الاهرام الكندية

Faculty of Engineering

FACULTY OF ENGINEERING
AHRAM CANADIAN UNIVERSITY



Electric Circuits II – Assignment

04

#	Student ID	Student Name	Grade (10)
-			

Delivery Date	
---------------	--


١. يتم تسليم التمرين محلولا في خلال أسبوع من تاريخ التمرين، و يتم حذف درجتين من التمرين عن كل أسبوع تأخير
٢. يتم التسليم لمعيد المقرر مباشرة
٣. تتم أجابه التمرين في نفس ورق الأسئلة

Faculty of Engineering

Q1

In the circuit of Fig. , find:

- $v(0^+)$ and $i(0^+)$,
- $dv(0^+)/dt$ and $di(0^+)/dt$,
- $v(\infty)$ and $i(\infty)$.

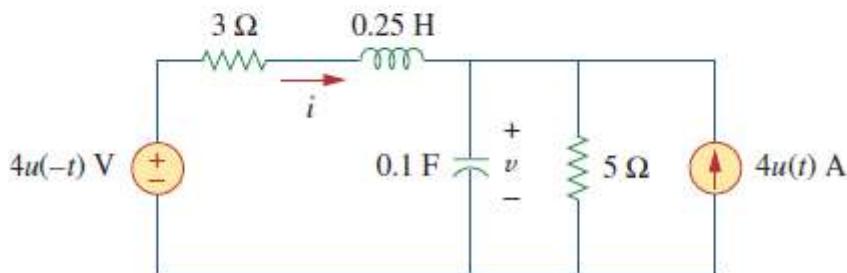


Sol 1

(a) At $t = 0^-$, $u(-t) = 1$ and $u(t) = 0$ so that the equivalent circuit is shown in Figure (a).


$$i(0^-) = 40/(3 + 5) = 5\text{A}, \text{ and } v(0^-) = 5i(0^-) = 25\text{V}.$$

$$\text{Hence, } i(0^+) = i(0^-) = 5\text{A}$$

$$v(0^+) = v(0^-) = 25\text{V}$$

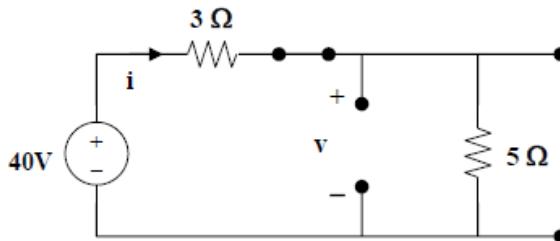

(a)

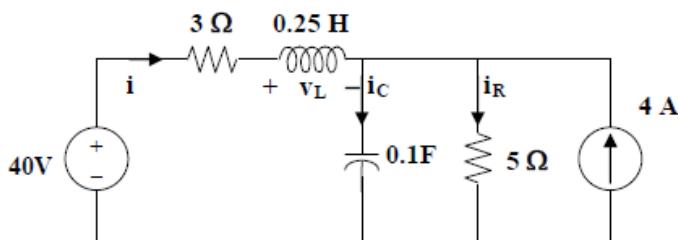

(b)

Faculty of Engineering

$$(b) \quad i_C = Cdv/dt \text{ or } dv(0^+)/dt = i_C(0^+)/C$$

For $t = 0^+$, $4u(t) = 4$ and $4u(-t) = 0$. The equivalent circuit is shown in Figure (b). Since i and v cannot change abruptly,

$$i_R = v/5 = 25/5 = 5A, \quad i(0^+) + 4 = i_C(0^+) + i_R(0^+)$$

$$5 + 4 = i_C(0^+) + 5 \text{ which leads to } i_C(0^+) = 4$$

$$dv(0^+)/dt = 4/0.1 = 40 \text{ V/s}$$


Similarly, $v_L = Ldi/dt$ which leads to $di(0^+)/dt = v_L(0^+)/L$

$$3i(0^+) + v_L(0^+) + v(0^+) = 0$$

$$15 + v_L(0^+) + 25 = 0 \text{ or } v_L(0^+) = -40$$

$$di(0^+)/dt = -40/0.25 = -160 \text{ A/s}$$

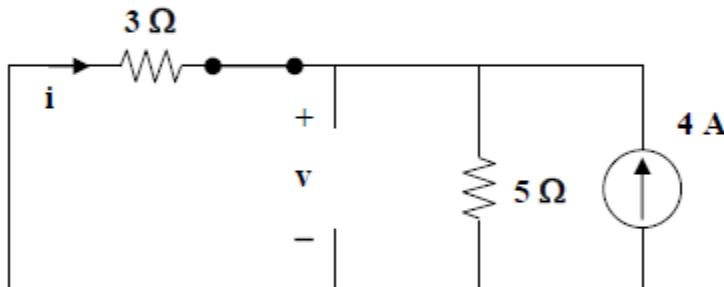(c) As t approaches infinity, we have the equivalent circuit in Figure (c).



(c)

$$i(\infty) = -5(4)/(3 + 5) = -2.5 \text{ A}$$

$$v(\infty) = 5(4 - 2.5) = 7.5 \text{ V}$$



FACULTY OF ENGINEERING
AHRAM CANADIAN UNIVERSITY

جامعة الامم الكندية

Faculty of Engineering



Q2

The current in an *RLC* circuit is described by

$$\frac{d^2i}{dt^2} + 10\frac{di}{dt} + 25i = 0$$

If $i(0) = 10$ A and $di(0)/dt = 0$, find $i(t)$ for $t > 0$.

Sol 2

...
... $s^2 + 10s + 25 = 0$, thus $s_{1,2} = \frac{-10 \pm \sqrt{100 - 100}}{2} = -5$, repeated roots. ...

...

... $i(t) = [(A + Bt)e^{-5t}]$, $i(0) = 10 = A$...

... $di/dt = [Be^{-5t}] + [-5(A + Bt)e^{-5t}]$...

... $di(0)/dt = 0 = B - 5A = B - 50$ or $B = 50$

... Therefore, $i(t) = [(10 + 50t)e^{-5t}]$ A ...

...

...

...

...

...

...

...

...

...

...


...



Faculty of Engineering

Q3

In the circuit of Fig. , the switch instantaneously moves from position A to B at $t = 0$. Find $v(t)$ for all $t \geq 0$.

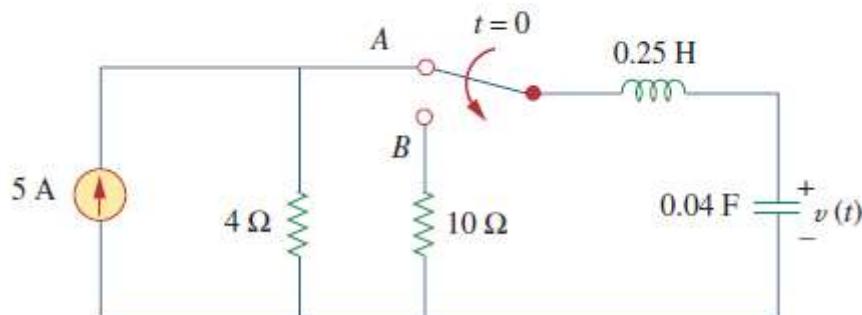

Sol 3

$$\dots i(0) = I_0 = 0, v(0) = V_0 = 4 \times 5 = 20$$

$$\dots \frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + V_0) = -4(0 + 20) = -80$$

$$\dots \omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \frac{1}{25}}} = 10$$

$$\dots \alpha = \frac{R}{2L} = \frac{10}{2 \frac{1}{4}} = 20, \text{ which is } > \omega_o.$$

$$\dots s = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -20 \pm \sqrt{300} = -20 \pm 10\sqrt{3} = -2.679, -37.32$$

$$\dots i(t) = A_1 e^{-2.679t} + A_2 e^{-37.32t}$$

$$\dots i(0) = 0 = A_1 + A_2, \frac{di(0)}{dt} = -2.679A_1 - 37.32A_2 = -80$$

$$\dots \text{This leads to } A_1 = -2.309 = -A_2$$

$$\dots i(t) = 2.309(e^{-37.32t} - e^{-2.679t})$$

$$\dots \text{Since, } v(t) = \frac{1}{C} \int_0^t i(t) dt + 20, \text{ we get}$$


$$\dots v(t) = [21.55e^{-2.679t} - 1.55e^{-37.32t}] \text{ V}$$



Faculty of Engineering

Q4

Find the voltage across the capacitor as a function of time for $t > 0$ for the circuit in Fig. Assume steady-state conditions exist at $t = 0^-$.

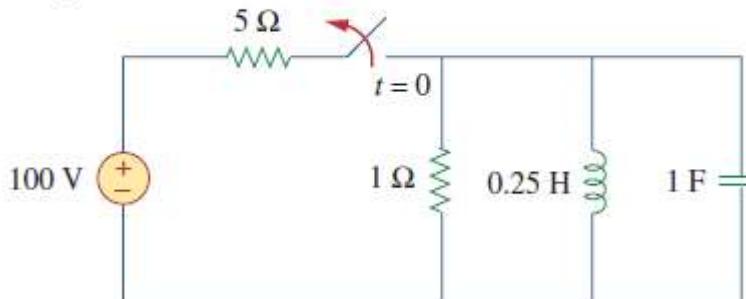

Sol 4

.....
.....
When the switch is off, we have a source-free parallel RLC circuit.

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.25 \times 1}} = 2, \quad \alpha = \frac{1}{2RC} = 0.5$$

$$\alpha < \omega_o \quad \longrightarrow \quad \text{underdamped case} \quad \omega_d = \sqrt{\omega_o^2 - \alpha^2} = \sqrt{4 - 0.25} = 1.936$$

$$I_o(0) = i(0) = \text{initial inductor current} = 100/5 = 20 \text{ A}$$

$$V_o(0) = v(0) = \text{initial capacitor voltage} = 0 \text{ V}$$

$$v(t) = e^{-\alpha t} (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) = e^{-0.5at} (A_1 \cos(1.936t) + A_2 \sin(1.936t))$$

$$v(0) = 0 = A_1$$

$$\frac{dv}{dt} = e^{-0.5at} (-0.5)(A_1 \cos(1.936t) + A_2 \sin(1.936t)) + e^{-0.5at} (-1.936A_1 \sin(1.936t) + 1.936A_2 \cos(1.936t))$$

$$\frac{dv(0)}{dt} = -\frac{(V_o + RI_o)}{RC} = -\frac{(0 + 20)}{1} = -20 = -0.5A_1 + 1.936A_2 \quad \longrightarrow \quad A_2 = -10.333$$

Thus,

$$\underline{v(t) = [-10.333e^{-0.5t} \sin(1.936t)] \text{volts}}$$

