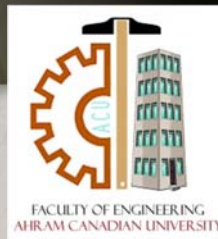




Lecture (02) First order Circuit (continue,...)


By:

Dr. Ahmed ElShafee



The Source-Free RL Circuit

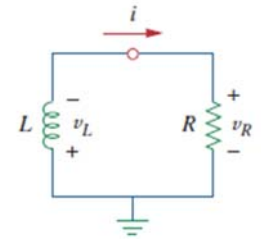- Consider the series connection of a resistor and an inductor
- Goal is to determine the current flow through the inductor $i(t)$,
- At $t=0$, assume the initial current = I_0



$$i(0) = I_0$$

- with the corresponding energy stored in the inductor as

$$w(0) = \frac{1}{2} L I_0^2$$

- Applying KVL around the loop

$$v_L + v_R = 0$$

- Ohm:

$$v_L = L di/dt \text{ and } v_R = iR.$$


- Then:

$$L \frac{di}{dt} + Ri = 0$$

$$\frac{di}{dt} + \frac{R}{L}i = 0$$

- Rearranging terms and integrating gives
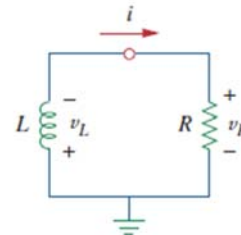
$$\int_{I_0}^{i(t)} \frac{di}{i} = - \int_0^t \frac{R}{L} dt$$



- From integration table: $\int \frac{1}{x} dx = \ln|x|$ $\int_{I_0}^{i(t)} \frac{di}{i} = - \int_0^t \frac{R}{L} dt$

$$\ln i \Big|_{I_0}^{i(t)} = - \frac{Rt}{L} \Big|_0^t \Rightarrow \ln i(t) - \ln I_0 = - \frac{Rt}{L} + 0$$

- so

$$\ln \frac{i(t)}{I_0} = - \frac{Rt}{L}$$


- Taking the powers of e $i(t) = I_0 e^{-Rt/L}$
- This shows that the natural response of the RL circuit is an exponential decay of the initial current

- the time constant for the RL circuit is

$$\tau = \frac{L}{R}$$

$$i(t) = I_0 e^{-t/\tau}$$

$$i(t) = I_0 e^{-t/\tau}$$

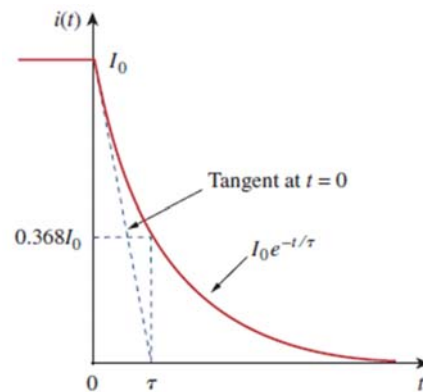

- voltage across the resistor $v_R(t) = iR = I_0 R e^{-t/\tau}$
- The power dissipated in the resistor is

$$p = v_R i = I_0^2 R e^{-2t/\tau}$$

- The energy absorbed by the resistor is

$$w_R(t) = \int_0^t p(\lambda) d\lambda = \int_0^t I_0^2 R e^{-2\lambda/\tau} d\lambda$$

$$w_R(t) = -\frac{\tau}{2} I_0^2 R e^{-2\lambda/\tau} \Big|_0^t$$


- But $\tau = \frac{L}{R}$

- then $w_R(t) = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau})$

Note that as $t \rightarrow \infty$, $w_R(\infty) \rightarrow \frac{1}{2} L I_0^2$, which is the same as $w_L(0)$,

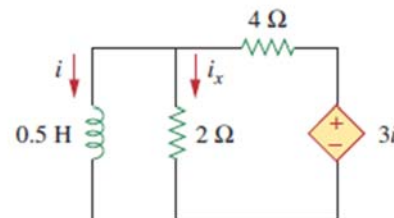Example 01

Assuming that $i(0) = 10$ A, calculate $i(t)$ and $i_x(t)$ in the circuit of Fig.




- Firstly, The equivalent resistance is the same as the Thevenin resistance at the inductor terminals. Because of the dependent source, we insert a voltage source with $V_0=1V$ at the inductor terminals $a-b$,
- Applying KVL to the two loops results in
- Left loop:

$$2(i_1 - i_2) + 1 = 0$$


$$i_1 - i_2 = -\frac{1}{2} \quad \times 6$$

$$6i_1 - 6i_2 = 3$$

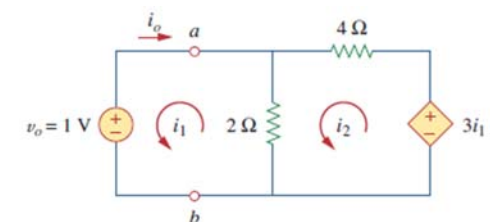

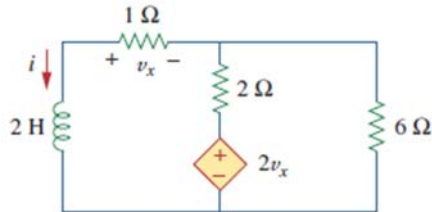Example 02


Find i and v_x in the circuit of Fig. 7.15. Let $i(0) = 12 \text{ A}$.



- Right loop

$$2(i_2 - i_1) - 3i_1 + 4i_2 = 0$$

$$-5i_1 + 6i_2 = 0$$

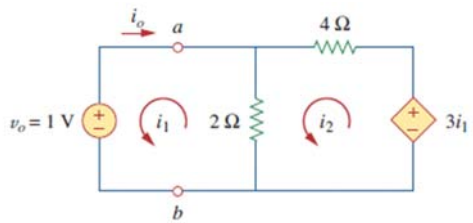

- Add both equations

$$i_1 = -3$$


$$i_1 = -3 \text{ Amp}$$

$$i_0 = 3 \text{ Amp}$$

$$R_{th} = R_{eq} = \frac{1}{3} \text{ Ohm}$$

$$\tau = \frac{L}{R_{eq}} = \frac{3}{2} \text{ s}$$
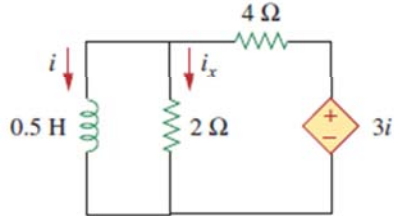
$$i(t) = i(0)e^{-t/\tau} = 10e^{-(2/3)t} \text{ A}, \quad t > 0$$



- Ohm

$$V_x = 1 \times I$$
- KCL @1

$$I_1 + 2(I_1 - I_2) + 2V_x - 1 = 0$$

$$I_1 + 2I_1 - 2I_2 + 2I_1 = 1$$



$$5I_1 - 2I_2 = 1 \quad \times 4$$

$$20I_1 - 8I_2 = 4 \rightarrow 1$$
- KCL @2

$$2(I_2 - I_1) - 2V_x + 6I_2 = 0$$

$$2I_2 - 2I_1 - 2I_1 + 6I_2 = 0$$
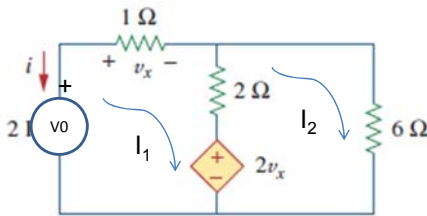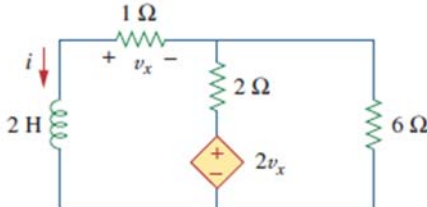
$$-4I_1 + 8I_2 = 0 \rightarrow 2$$
- Add 1,2



$$16 - I_1 = 4$$

$$I_1 = \frac{4}{16} = \frac{2}{12} = \frac{1}{4} \text{ Amp}$$

$$I_0 = I_1 = 1/4 \text{ Amp}$$



$$R_{eq} = \frac{V_0}{I_0} = 4 \text{ Ohm}$$

- coil

$$I(t) = I_0 e^{-tR/L} = 12 e^{-4t/2}$$


$$= 12 e^{-2t}$$
- ohm

$$V_x = -1 \times I(t) = -12e^{-2t}$$

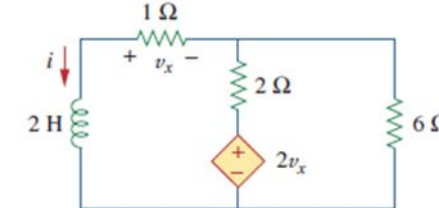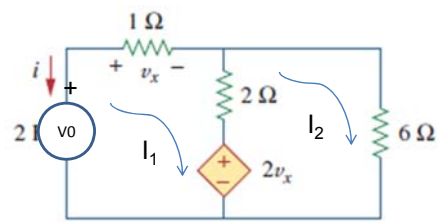

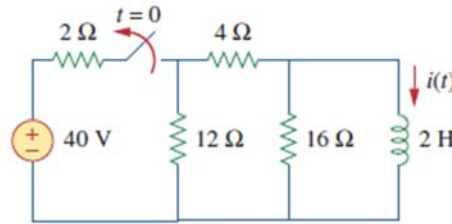
Example 03

The switch in the circuit of Fig. has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$.



- Step 1, to find $i(0)$
- @ $t < 0$ the switch is closed, and the inductor acts as a short circuit to dc. 16 ohm resistance is short circuit
- 4 in parallel with 12 \rightarrow 3 ohm
- 3 in series with 2 \rightarrow 5 ohm
- Ohm :

$$i_1 = \frac{40}{5} = 8 \text{ amp}$$

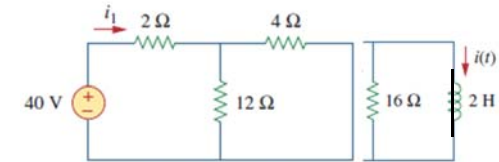

- C.D.

$$i(0) = 8 \times \frac{12}{4 + 12} = 6 \text{ Amp}$$

13



Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

14

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II


- @ $t > 0$ the switch is open and the voltage source is disconnected. We now have the source-free RL
- 12 in series with 4 \rightarrow 16 ohm
- 16 in series with 16 \rightarrow 8 ohm

$$i(t) = i_0 e^{-tR/L} = 6 e^{-8t/2} = 6e^{-4t}$$

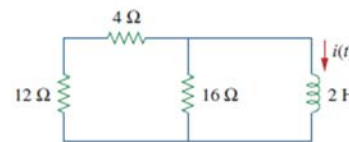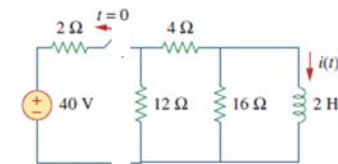

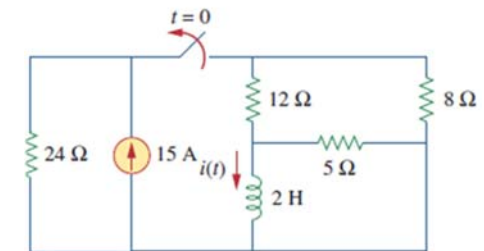Example 04

For the circuit in Fig. , find $i(t)$ for $t > 0$.




15

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

16


Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

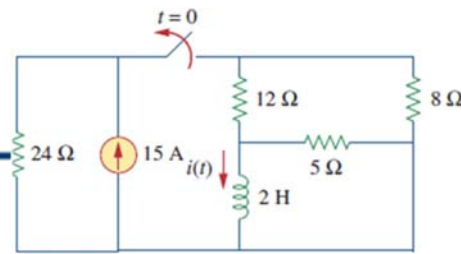- At $t < 0$, switch is closed, coil is short
8 in parallel with 24
→ 6 ohm




- Current division
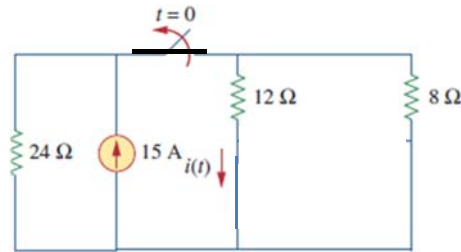
$$I_{12ohm} = I(0) = 15 \times \frac{6}{12 + 6} = 5 \text{ Amp}$$



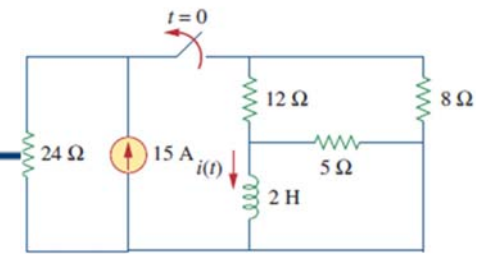- At $t > 0$, switch is opened
- Use thevenin theorem to find Req as seen by coil, by replacing coil with voltage source $V_0 = 1$ volt




- KVL@1

$$-1 + 5(I_1 - I_2) = 0$$

$$5I_1 - 5I_2 = 1 \quad \times 5$$

$$25I_1 - 25I_2 = 5 \rightarrow 1$$

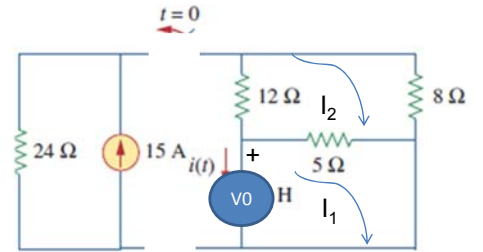

- KVL@2

$$20I_2 + 5(I_2 - I_1) = 0$$

$$20I_2 + 5I_2 - 5I_1 = 0$$

$$-5I_1 + 25I_2 = 0 \rightarrow 2$$

- Add 1,2


$$20I_1 = 5$$

$$I_1 = \frac{5}{20} = \frac{1}{4}$$

- Req


$$Req = R_{th} = \frac{V_0}{I_0} = 4 \text{ ohm}$$

$$I(t) = I_0 e^{-tR/L} = 5e^{-4t/2} = 5e^{-2t}$$

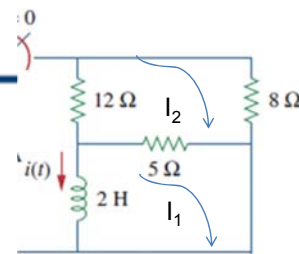

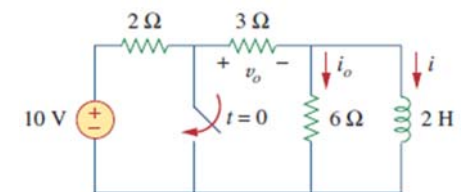Example 05

In the circuit shown in Fig. , find i_o , v_o , and i for all time, assuming that the switch was open for a long time.



$$i_o(t) = \begin{cases} 0 \text{ A}, & t < 0 \\ -\frac{2}{3}e^{-t} \text{ A}, & t > 0 \end{cases} \quad v_o(t) = \begin{cases} 6 \text{ V}, & t < 0 \\ 4e^{-t} \text{ V}, & t > 0 \end{cases}$$

$$i(t) = \begin{cases} 2 \text{ A}, & t < 0 \\ 2e^{-t} \text{ A}, & t \geq 0 \end{cases}$$

- At $t < 0$, switch is opened, coil is shorted



$$I_0(0) = 0$$

- V.D.



$$V_0(0) = 10 \times \frac{3}{2+3} = \frac{30}{5} = 6 \text{ Volt}$$

- Ohm

$$i(0) = \frac{10}{5} = 1 \text{ Amp}$$

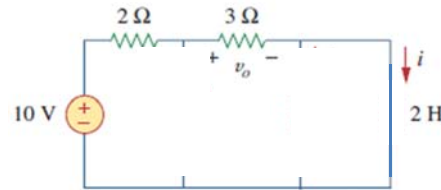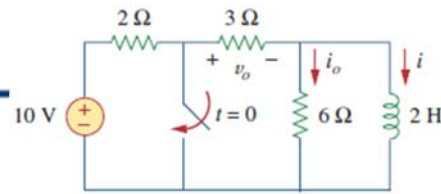

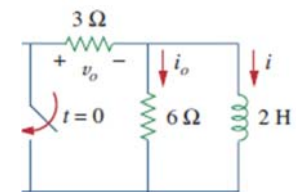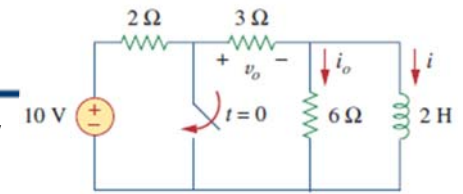- @ $t > 0$ Switch is closed, so the 10v supply and 2 ohm resistor is independent circuit, has nothing to do with the rest of circuit that contains coil under consideration



- Use thevenin theorem

$R_{th} = R_{eq} = 3$ in parallel with 6

$$= \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2 \text{ ohm}$$

$$i(t) = i(0)e^{-tR/L} = 2e^{-2t/2} = 2e^{-t}$$


- Ohm

$$Vl(t) = \frac{Ldi}{dt} = 4 \frac{d}{dt} e^{-t} = 4e^{-t} \text{ volt}$$

$$V_0(t) = Vl = -4e^{-t} \text{ volt}$$

- Ohm
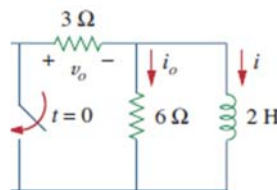
$$I_0(t) = \frac{V_0}{6} = -\frac{2}{3}e^{-t} \text{ Amp}$$



Summery

RC

$$V = V_0 e^{-t/RC}$$

$$\tau = RC$$

$$V = V_0 e^{-t/\tau}$$

$$p(t) = vi_R = \frac{V_0^2}{R} e^{-2t/\tau}$$

$$w_R(t) = \frac{1}{2} CV_0^2 (1 - e^{-2t/\tau})$$

RL

$$I = I_0 e^{-tR/L}$$

$$\tau = \frac{L}{R}$$

$$I = I_0 e^{-t/\tau}$$

$$p = v_R i = I_0^2 R e^{-2t/\tau}$$

$$w_R(t) = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau})$$

Singularity Functions

- Singularity functions (also called *switching functions*) are good approximations to the switching signals that arise in circuits with switching operations.

٢٥


Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

unit step function

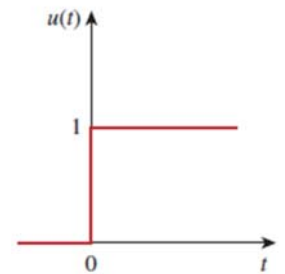1. *unit step*, the *unit impulse*, and the *unit ramp* functions.

- The unit step function $u(t)$ is 0 for negative values of t and 1 for positive values of t .

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$



- The unit step function is undefined at where it changes abruptly from 0 to 1.



٢٦

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- The unit step function may be delayed or stepped by t_0 .

$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$
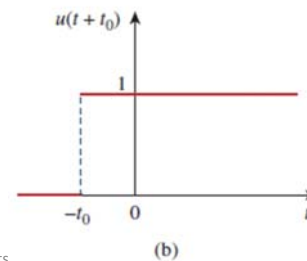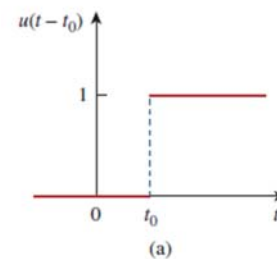
$$u(t + t_0) = \begin{cases} 0, & t < -t_0 \\ 1, & t > -t_0 \end{cases}$$



٢٧

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- We use the step function to represent an abrupt (sudden) change in voltage or current, like the changes that occur in the circuits of control systems and digital computers

$$v(t) = \begin{cases} 0, & t < t_0 \\ V_0, & t > t_0 \end{cases}$$

- may be expressed in terms of the unit step function as

$$v(t) = V_0 u(t - t_0)$$


٢٨

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

Unit Impulse function (delta)

The derivative of the unit step function $u(t)$ is the *unit impulse function* $\delta(t)$, which we write as

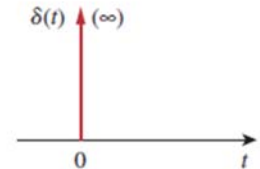
$$\delta(t) = \frac{d}{dt}u(t) = \begin{cases} 0, & t < 0 \\ \text{Undefined}, & t = 0 \\ 0, & t > 0 \end{cases}$$




- The unit impulse function—also known as the *delta* function—

The **unit impulse function** $\delta(t)$ is zero everywhere except at $t = 0$, where it is undefined.

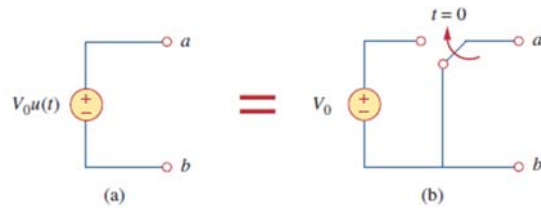- If we let $t=t_0$, then $v(t)$, is simply the step voltage $v_0u(t)$.



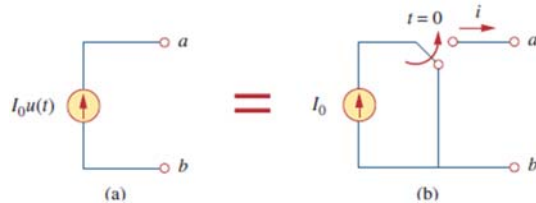- If we let $t=t_0$, then $i(t)$, is simply the step current $i_0u(t)$.




- Impulsive currents and voltages occur in electric circuits as a result of switching operations or impulsive sources.
- the unit impulse function is not physically realizable (just like ideal sources, ideal resistors, etc.), it is a very useful mathematical tool.
- It may be visualized as a very short duration pulse of unit area

$$\int_{0^-}^{0^+} \delta(t) dt = 1$$


where $t = 0^-$ denotes the time just before $t = 0$ and $t = 0^+$ is the time just after $t = 0$.

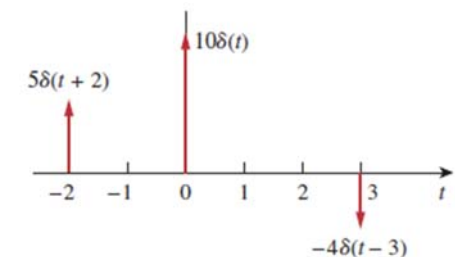- The unit area is known as the *strength* of the impulse function.
- When an impulse function has a strength other than unity, the area of the impulse is equal to its strength.
- For example $10\delta(t)$, an impulse function has an area of 10.



- To illustrate how the impulse function affects other functions, let us evaluate the integral

$$\int_a^b f(t)\delta(t - t_0) dt$$

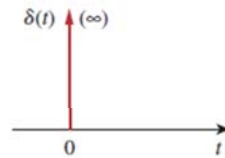

where $a < t_0 < b$. Since $\delta(t - t_0) = 0$ except at $t = t_0$, the integrand is zero except at t_0 . Thus,

$$\begin{aligned} \int_a^b f(t)\delta(t - t_0) dt &= \int_a^b f(t_0)\delta(t - t_0) dt \\ &= f(t_0) \int_a^b \delta(t - t_0) dt = f(t_0) \end{aligned}$$

٣٣

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- This shows that when a function is integrated with the impulse function, we obtain the value of the function at the point where the impulse occurs.
- This is a highly useful property of the impulse function known as the *sampling*
- Special case when $t_0=0$.

$$\int_{0^-}^{0^+} f(t)\delta(t) dt = f(0)$$

٣٤

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II



unit ramp function

- Integrating the unit step function results in the *unit ramp function* we write

$$r(t) = \int_{-\infty}^t u(\lambda) d\lambda = tu(t)$$

$$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t \geq 0 \end{cases}$$

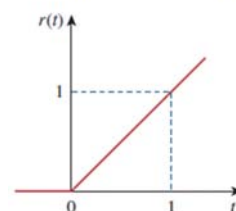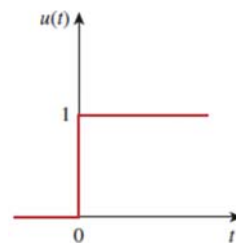The **unit ramp function** is zero for negative values of t and has a unit slope for positive values of t .




٣٥


Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- For the delayed unit ramp function
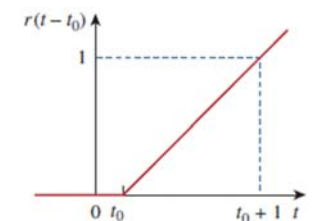
$$r(t - t_0) = \begin{cases} 0, & t \leq t_0 \\ t - t_0, & t \geq t_0 \end{cases}$$


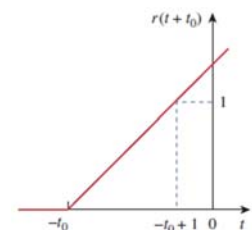
$$r(t + t_0) = \begin{cases} 0, & t \leq -t_0 \\ t + t_0, & t \geq -t_0 \end{cases}$$




٣٦

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

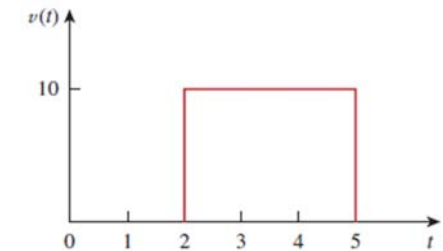Example 06

Express the voltage pulse in Fig. in terms of the unit step. Calculate its derivative and sketch it.



- We should keep in mind that the three singularity functions (impulse, step, and ramp) are related by differentiation as

$$\delta(t) = \frac{du(t)}{dt}, \quad u(t) = \frac{dr(t)}{dt}$$

- or by integration as

$$u(t) = \int_{-\infty}^t \delta(\lambda) d\lambda, \quad r(t) = \int_{-\infty}^t u(\lambda) d\lambda$$


٣٧

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

٣٨

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

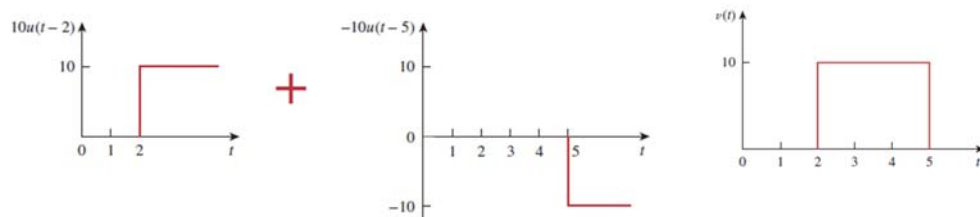switches on at $t = 2$ s and switches off at $t = 5$ s. It consists of the sum of two unit step functions



$$v(t) = 10u(t-2) - 10u(t-5) = 10[u(t-2) - u(t-5)]$$

٣٩

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

٤٠




Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- Taking the derivative of this gives

$$\frac{dv}{dt} = 10[\delta(t-2) - \delta(t-5)]$$

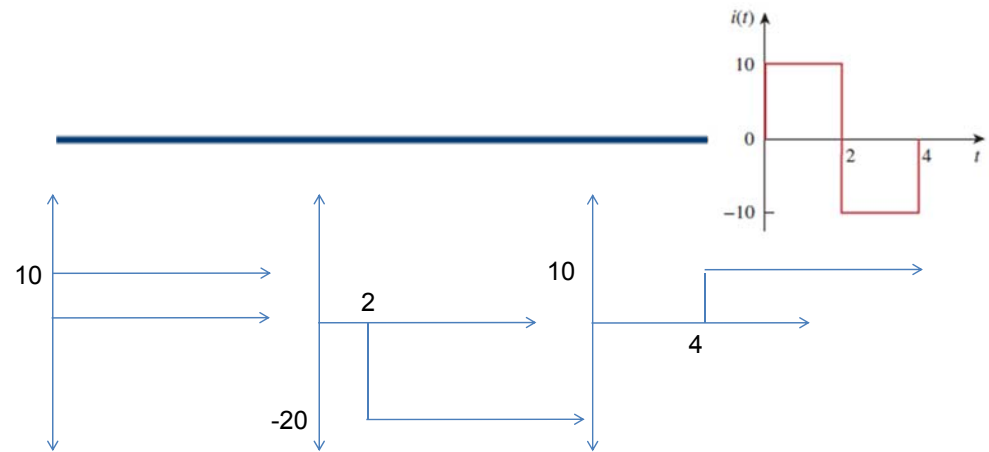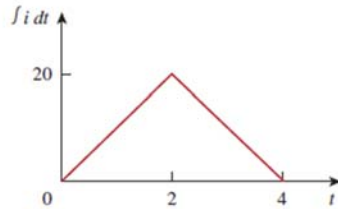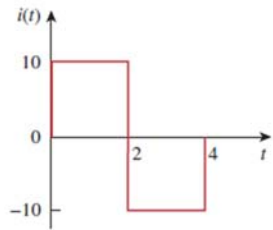Example 07

Express the current pulse in Fig. in terms of the unit step. Find its integral and sketch it.




$$f(t) = 10 u(t) - 20 u(t - 2) + 10 u(t - 4)$$

$$r(t) = \int_{-\infty}^t u(\lambda) d\lambda$$

$$f(t) = 10 u(t) - 20 u(t - 2) + 10 u(t - 4)$$

$$f'(t) = 10r(t) - 20r(t - 2) + 10r(t - 4)$$

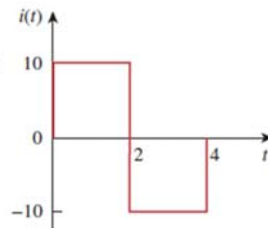

Example 2
Part 2


$\text{slope} = \frac{y_2 - y_1}{x_2 - x_1} = \frac{20 - 0}{2 - 0} = 10 = \frac{y - 0}{x - 0} \Rightarrow 10x - 20 = y - 20 \Rightarrow 10t - 20 = \int i dt - 20$
 $\frac{20}{2} = \frac{y - 20}{x - 2} = 10 = \frac{y - 20}{x - 2} \Rightarrow 10x - 20 = y - 20 \Rightarrow 10t - 20 = \int i dt - 20$
 $\frac{20}{-2} = \frac{y - 20}{x - 2} = -10 = \frac{y - 20}{x - 2} \Rightarrow -10t - 20 = \int i dt - 20$

$\int i dt = \begin{cases} 10t & 0 < t < 2 \\ -10t & 2 < t < 4 \\ 0 & \text{elsewhere} \end{cases}$



$\int i dt = 10t [u(t) - u(t-2)] - 10t [u(t-2) - u(t-4)]$
 $10t [u(t) - u(t-2) - u(t-2) + u(t-4)]$
 but $u(t)t = r(t)$
 $= 10r(t) - 20r(t-2) + 10r(t-4)$

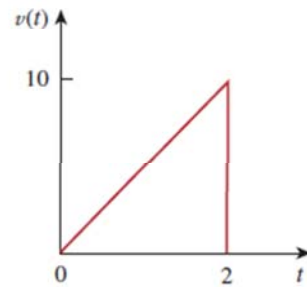Example 08

Express the *sawtooth* function shown in Fig. in terms of singularity functions.




• Method 1, addition

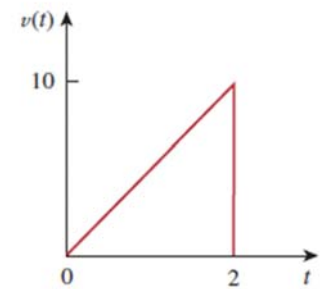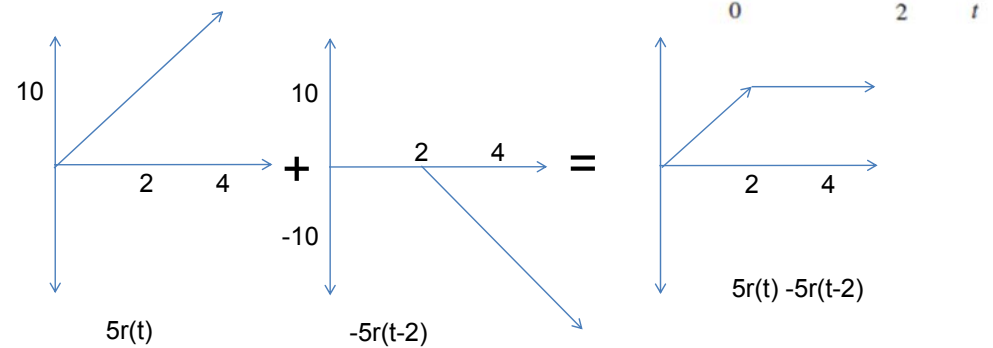


٤٥

٤٦

•

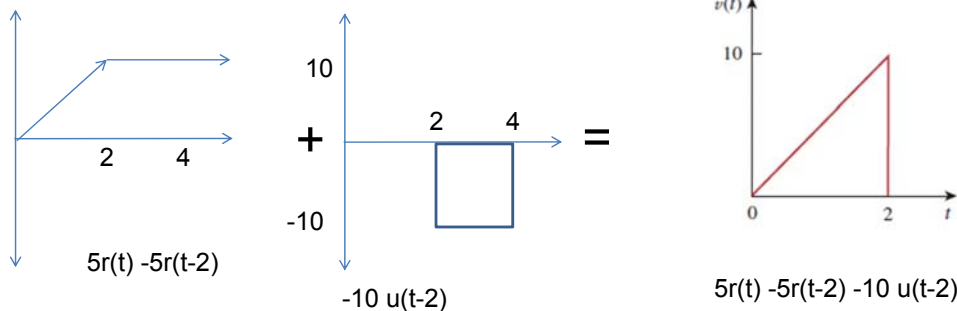

example 03
method 2

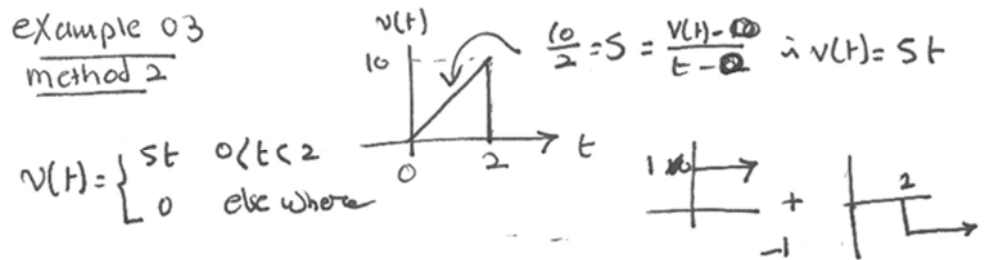


$$\begin{aligned}
 v(t) &= 5t [u(t) - u(t-2)] \\
 &= 5t u(t) - 5t u(t-2) \\
 &= 5t u(t) - 5(t-2+2) u(t-2) \\
 &= 5t u(t) - 5(t-2) u(t-2) - 10 u(t-2) \\
 &\text{but } t u(t) = r(t) \\
 &= 5r(t) - 5r(t-2) - 10 u(t-2)
 \end{aligned}$$

٤٧

٤٨

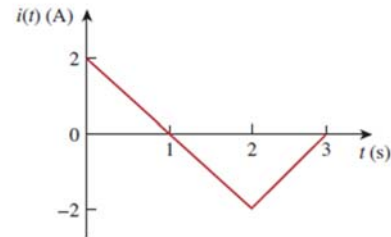Example 09

- Refer to Fig Express $i(t)$ in terms of singularity functions.



$$i(t) = \begin{cases} 2t-2 & 0 < t < 2 \\ 2t-6 & 2 < t < 3 \\ 0 & \text{elsewhere} \end{cases}$$

$$i(t) = (2t-2)[u(t)-u(t-2)] + (2t-6)[u(t-2)-u(t-3)]$$



Thanks,..
See you next week (ISA),...