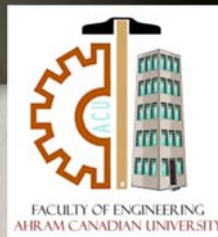




Lecture (03) First order Circuit (continue,...)

By:

Dr. Ahmed ElShafee



Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

Step Response of an RC Circuit

- When the dc source of an RC circuit is suddenly applied, the voltage or current source can be modeled as a step function, and the response is known as a step response.

The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.

۳

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II


- We assume an initial voltage V_0 on the capacitor . $v(0^-) = v(0^+) = V_0$
- Applying KCL,

$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0$$

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC} u(t)$$

- For $t > 0$
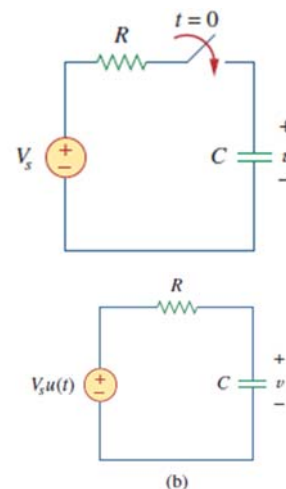
$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC}$$



۳

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- Rearranging terms gives

$$\frac{dv}{dt} = -\frac{v - V_s}{RC}$$

$$\frac{dv}{v - V_s} = -\frac{dt}{RC}$$

- From integration table

$$\int \frac{1}{x} dx = \ln |x|$$

- Integrating both sides and introducing the initial conditions

$$\ln(v - V_s) \Big|_{V_0}^{v(t)} = -\frac{t}{RC} \Big|_0^t$$

۴

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

$$\ln(v(t) - V_s) - \ln(V_0 - V_s) = -\frac{t}{RC} + 0$$

$$\ln \frac{v - V_s}{V_0 - V_s} = -\frac{t}{RC}$$


- Taking the exponential of both sides

$$\frac{v - V_s}{V_0 - V_s} = e^{-t/\tau}, \quad \tau = RC$$

$$v - V_s = (V_0 - V_s)e^{-t/\tau}$$

$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$$
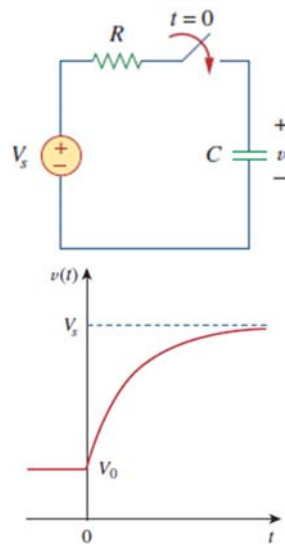
$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$



Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- capacitor is uncharged initially,

$$v(t) = \begin{cases} 0, & t < 0 \\ V_s(1 - e^{-t/\tau}), & t > 0 \end{cases}$$



$$v(t) = V_s(1 - e^{-t/\tau})u(t)$$

- Calculating current

$$i(t) = C \frac{dv}{dt}$$

$$i(t) = C \frac{dv}{dt} = \frac{C}{\tau} V_s e^{-t/\tau}, \quad \tau = RC, \quad t > 0$$
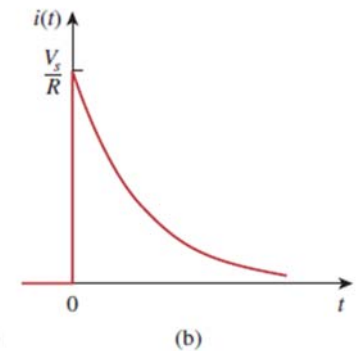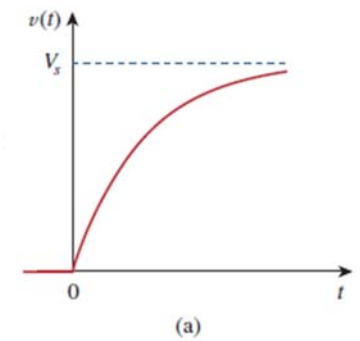
$$i(t) = \frac{V_s}{R} e^{-t/\tau} u(t)$$



Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Ci

$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$$

- $v(t)$ has two components:

- “natural response
- Forced response”

$$v = v_n + v_f \quad \text{Complete response} = \underset{\text{stored energy}}{\text{natural response}} + \underset{\text{independent source}}{\text{forced response}}$$

$$v_n = V_0 e^{-t/\tau}$$

$$v_f = V_s(1 - e^{-t/\tau})$$

- *forced* response because it is produced by the circuit when an external “force” (a voltage source in this case) is applied.

- Forced response break to

- “transient response
- steady-state response.”

- Dies:

- natural response eventually
- transient component of the forced response, I

- Leaving only

- the steady state component of the forced response.

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- Another way to present complete response

Complete response = transient response + steady-state response
temporary part permanent part

$$v = v_t + v_{ss}$$

$$v_t = (V_o - V_s)e^{-t/\tau}$$

$$v_{ss} = V_s$$

The **transient response** is the circuit's temporary response that will die out with time.

The **steady-state response** is the behavior of the circuit a long time after an external excitation is applied.

9

- $v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

1. The initial capacitor voltage $v(0)$.
2. The final capacitor voltage $v(\infty)$.
3. The time constant τ .

10


- Note that if the switch changes position at time t_0 instead of $t=0$

$$v(t) = v(\infty) + [v(t_0) - v(\infty)]e^{-(t-t_0)/\tau}$$

11

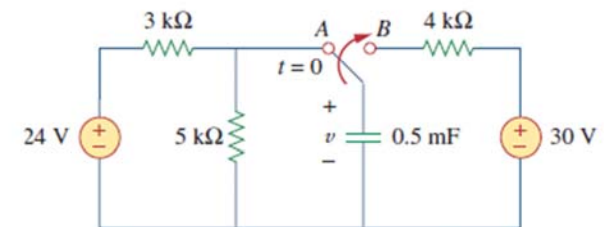Example 01

The switch in Fig. has been in position A for a long time. At $t = 0$, the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 1$ s and 4 s.





12

- @ $t < 0$, switch @ A
- voltage division

$$v(0^-) = \frac{5}{5 + 3}(24) = 15 \text{ V}$$

- capacitor voltage cannot change instantaneously
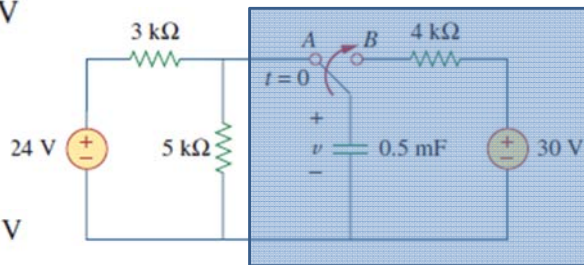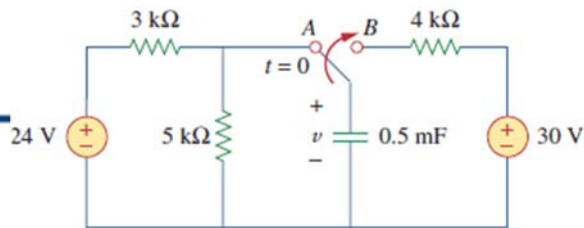
$$v(0) = v(0^-) = v(0^+) = 15 \text{ V}$$



- $t > 0$, switch @ B

- Use thevenin theorem to find Req connected to Cap

$$R_{Th} = 4 \text{ k}\Omega,$$


- Time constant

$$\tau = R_{Th}C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ s}$$

- Cap act ac open circuit @ steady state,
- $$v(\infty) = 30 \text{ V}.$$

- as
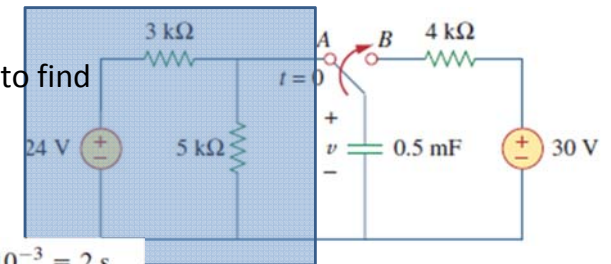
$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$




$$v(t) = 30 + (15 - 30)e^{-t/2} = (30 - 15e^{-0.5t}) \text{ V}$$

$$\text{At } t = 1, \quad v(1) = 30 - 15e^{-0.5} = 20.9 \text{ V}$$

$$\text{At } t = 4, \quad v(4) = 30 - 15e^{-2} = 27.97 \text{ V}$$

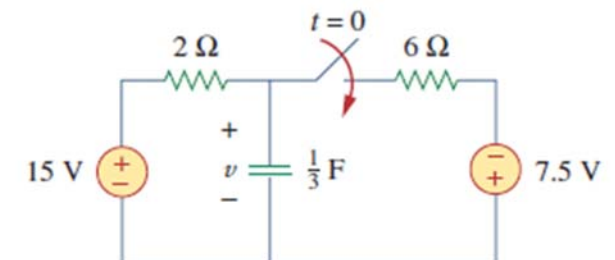Example 02

Find $v(t)$ for $t > 0$ in the circuit of Fig. Assume the switch has been open for a long time and is closed at $t = 0$. Calculate $v(t)$ at $t = 0.5$.



- For $t < 0$, switch is open, cap is open

$$v(0^-) = v(0^+) = v(0) = 15$$

- For $t > 0$
- Find Req

$$R_{th} = 2 \parallel 6 = \frac{3}{2} \Omega,$$


- Find time constant

$$\tau = R_{th}C = \frac{3}{2} \times \frac{1}{3} = \frac{1}{2}$$

- Find $v(\infty)$, the current flow through cap=0 (open) then

$$[(v(\infty) - 15)/2] + [(v(\infty) - (-7.5))/6] = 0$$

$$v(\infty) = 9.375 \text{ V}$$

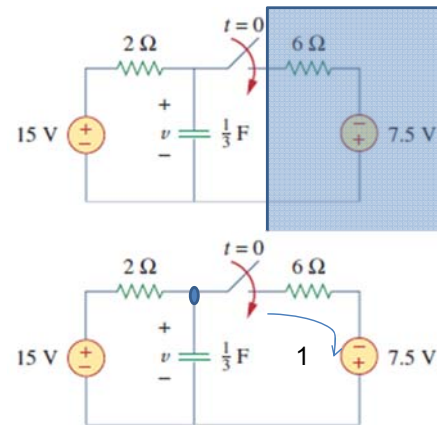


$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$v(t) = 9.375 + (15 - 9.375)e^{-2t}$$

$$\text{At } t = 0.5, \quad v(0.5) = 6.25 + 3.75e^{-1} = 6.25 + 1.3795 = 7.63 \text{ V}$$

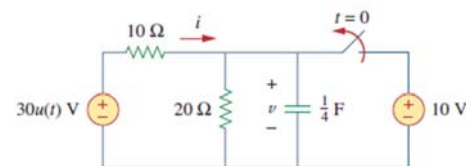Example 03

In Fig. , the switch has been closed for a long time and is opened at $t = 0$. Find i and v for all time.



- For $t < 0$

$$v = 10 \text{ V}, \quad i = -\frac{v}{10} = -1 \text{ A}$$

$$v(0) = v(0^-) = 10 \text{ V}$$


- For $t > 0$

- Find $v(\infty)$ Use V.D.

$$v(\infty) = \frac{20}{20 + 10}(30) = 20 \text{ V}$$


- The Thevenin resistance at the capacitor terminals

$$R_{Th} = 10 \parallel 20 = \frac{10 \times 20}{30} = \frac{20}{3} \Omega$$

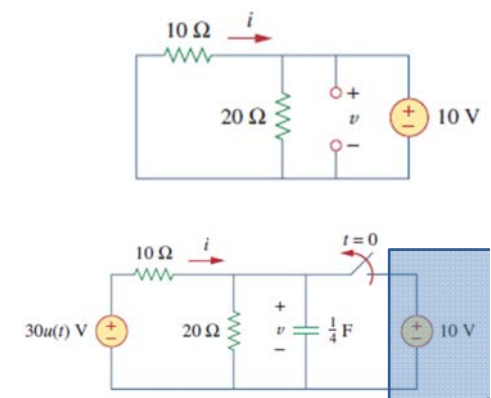

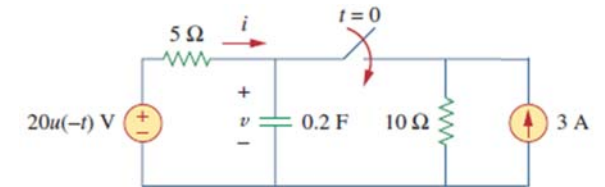Example 04

The switch in Fig. is closed at $t = 0$. Find $i(t)$ and $v(t)$ for all time. Note that $u(-t) = 1$ for $t < 0$ and 0 for $t > 0$. Also, $u(-t) = 1 - u(t)$.



٢٢

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- Time constant

$$\tau = R_{Th}C = \frac{20}{3} \cdot \frac{1}{4} = \frac{5}{3} \text{ s}$$


$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} = 20 + (10 - 20)e^{-(3/5)t} = (20 - 10e^{-0.6t}) \text{ V}$$

- To find current, that i is the sum of the currents through the resistor and the capacitor;

$$i = \frac{v}{20} + C \frac{dv}{dt} = 1 + 0.25(-0.6)(-10)e^{-0.6t} = (1 + e^{-0.6t}) \text{ A}$$

$$v = \begin{cases} 10 \text{ V}, & t < 0 \\ (20 - 10e^{-0.6t}) \text{ V}, & t \geq 0 \end{cases}$$
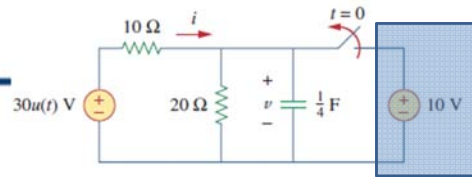
$$i = \begin{cases} -1 \text{ A}, & t < 0 \\ (1 + e^{-0.6t}) \text{ A}, & t > 0 \end{cases}$$



٢١

Spring 2016, Electric Circuits II

- For $t < 0$, switch is open, Cap is open

$$v(0^-) = v(0^+) = v(0) = 20, \quad i(0) = 0$$

- For $t > 0$, switch is on, voltage source = 0


- Find $v(\infty)$, CD

$$I_{5ohm} = 3 \times \frac{10}{15} = 2$$

- ohm

$$V(\infty) = 2 \times 5 = 10 \text{ v}$$
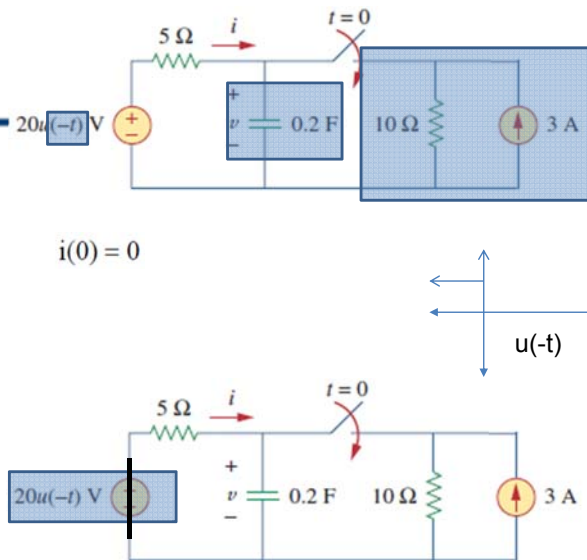
$$R_{th} = 5 \parallel 10 = \frac{10}{3} \Omega$$



- Time constant

$$\tau = R_{th}C = \frac{10}{3} \times 0.2 = \frac{2}{3}$$


$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} = 10 + (20 - 10)e^{-3t/2} = 10(1 + e^{-1.5t})$$

- current

$$i(t) = \frac{-v(t)}{5} = -2(1 + e^{-1.5t})$$

$$i(t) = \begin{cases} 0 & t < 0 \\ -2(1 + e^{-1.5t}) \text{ A} & t > 0 \end{cases}$$
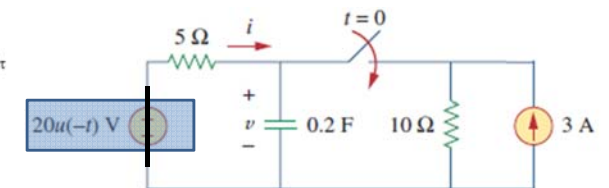
$$v(t) = \begin{cases} 20 \text{ V} & t < 0 \\ 10(1 + e^{-1.5t}) \text{ V} & t > 0 \end{cases}$$



٢٣

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

٢٤

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

Step Response of an RL Circuit


- Complete response = transient response + steady-state response
temporary part permanent part

$$i = i_t + i_{ss}$$


$$i_t = Ae^{-t/\tau}, \quad \tau = \frac{L}{R}$$

$$i_{ss} = \frac{V_s}{R}$$

$$i = Ae^{-t/\tau} + \frac{V_s}{R}$$

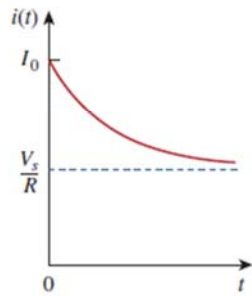

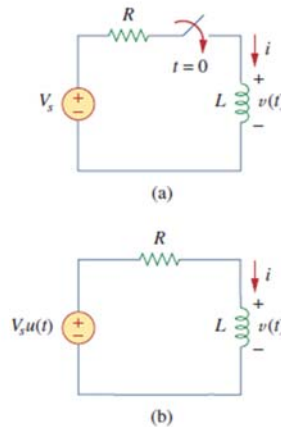Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II



- At $t=0$ $I_0 = A + \frac{V_s}{R}$
- we obtain A as $A = I_0 - \frac{V_s}{R}$
- Substituting for A

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

٢٦

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- This is the complete response of the RL circuit

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

- The initial inductor current $i(0)$ at $t = 0$.
- The final inductor current $i(\infty)$.
- The time constant τ .


- if the switching takes place at time $t = t_0$ instead of $t = 0$,

$$i(t) = i(\infty) + [i(t_0) - i(\infty)]e^{-(t-t_0)/\tau}$$

- If $I_0=0$

$$i(t) = \begin{cases} 0, & t < 0 \\ \frac{V_s}{R}(1 - e^{-t/\tau}), & t > 0 \end{cases}$$
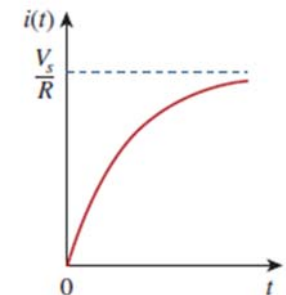
$$i(t) = \frac{V_s}{R}(1 - e^{-t/\tau})u(t)$$



٢٧


Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

٢٨

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

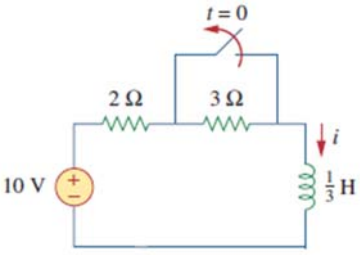Example 05


Find $i(t)$ in the circuit of Fig. for $t > 0$. Assume that the switch has been closed for a long time.



The voltage across the inductor is

$$v(t) = L \frac{di}{dt} = V_s \frac{L}{\tau R} e^{-t/\tau}, \quad \tau = \frac{L}{R}, \quad t > 0$$

$$v(t) = V_s e^{-t/\tau} u(t)$$

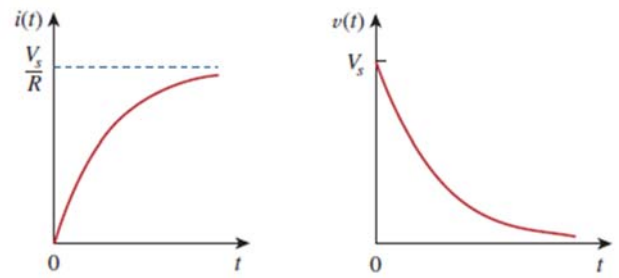


$t < 0$, switch on, 3 ohm is neglected, coil is short

$$i(0^-) = \frac{10}{2} = 5 \text{ A}$$

$t > 0$, switch is off
Calculate current using ohm law, coil is short

$$i(\infty) = \frac{10}{2 + 3} = 2 \text{ A}$$

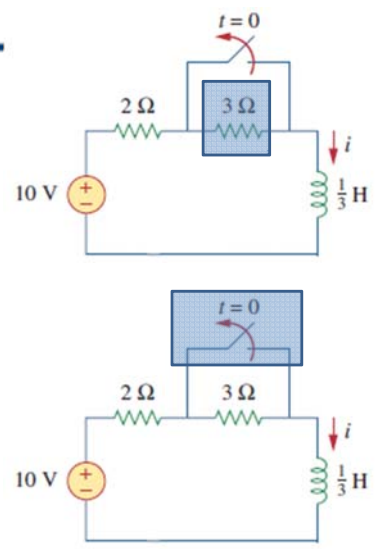Calculate R_{th}
 $R_{Th} = 2 + 3 = 5 \Omega$



Calculate time constant


$$\tau = \frac{L}{R_{Th}} = \frac{\frac{1}{3}}{5} = \frac{1}{15} \text{ s}$$

Complete response


$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} = 2 + (5 - 2)e^{-15t} = 2 + 3e^{-15t} \text{ A}, \quad t > 0$$

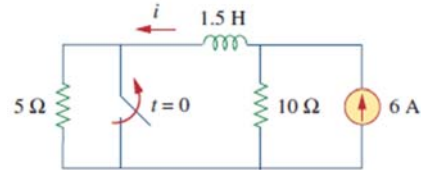Example 06

The switch in Fig. has been closed for a long time. It opens at $t = 0$. Find $i(t)$ for $t > 0$.



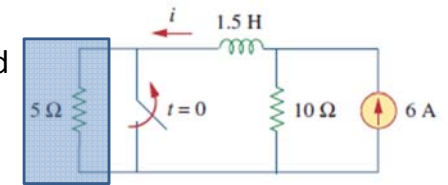- At $t < 0$, the switch is closed so that the 5 ohm resistor is short circuited
 $I(0) = 6 \text{ Amp}$




- At $t > 0$, switch is on,
- Find current using CD:

$$I(5\text{ohm}) = 6 \times \frac{10}{15} = 4 \text{ Amp}$$

- Find Req

$$R_{th} = 10 + 5 = 15 \text{ ohm}$$

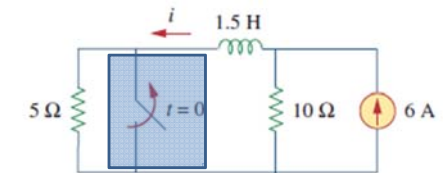


$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 4 + (6 - 4)e^{-10t}$$

$$i(t) = (4 + 2e^{-10t}) \text{ A for all } t > 0$$

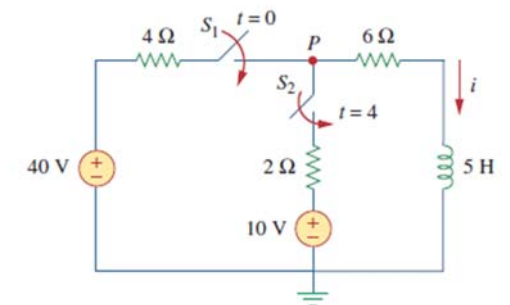
Example 07

At $t = 0$, switch 1 in Fig. is closed, and switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2 \text{ s}$ and $t = 5 \text{ s}$.



- $t < 0$

$$i(0^-) = i(0) = i(0^+) = 0$$

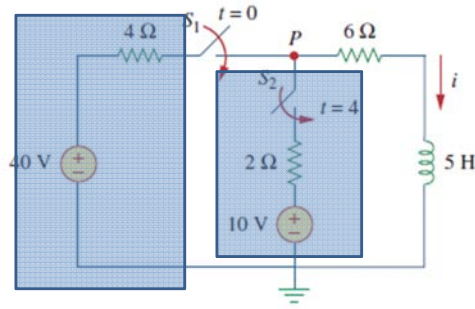

٣٧


Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- $0 < t < 4$

$$i(\infty) = \frac{40}{4 + 6} = 4 \text{ A,}$$

$$R_{Th} = 4 + 6 = 10 \Omega$$
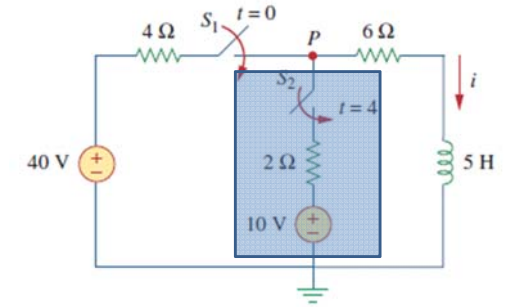
$$\tau = \frac{L}{R_{Th}} = \frac{5}{10} = \frac{1}{2} \text{ s}$$



$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$= 4 + (0 - 4)e^{-2t} = 4(1 - e^{-2t}) \text{ A,} \quad 0 \leq t \leq 4$$

٣٨

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

For $t \geq 4$,

$$i(t) = 4(1 - e^{-2t}) \text{ A,}$$

$$i(4) = i(4^-) = 4(1 - e^{-8}) = 4 \text{ A}$$


- Use KCL @ p

$$\frac{40 - v}{4} + \frac{10 - v}{2} = \frac{v}{6}$$

$$v = \frac{180}{11} \text{ V}$$

$$i(\infty) = \frac{v}{6} = \frac{30}{11} = 2.727 \text{ A}$$
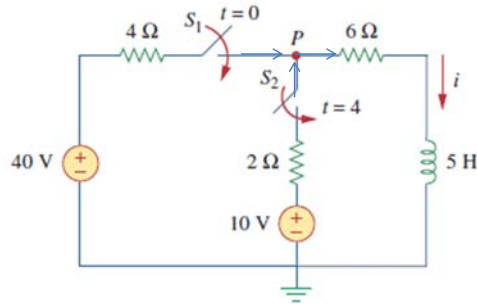
$$R_{Th} = 4 \parallel 2 + 6 = \frac{4 \times 2}{6} + 6 = \frac{22}{3} \Omega$$



٣٩

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

$$\tau = \frac{L}{R_{Th}} = \frac{5}{\frac{22}{3}} = \frac{15}{22} \text{ s}$$

$$i(t) = i(\infty) + [i(4) - i(\infty)]e^{-(t-4)/\tau}, \quad t \geq 4$$

$$i(t) = 2.727 + (4 - 2.727)e^{-(t-4)/\tau}, \quad \tau = \frac{15}{22}$$

$$= 2.727 + 1.273e^{-1.4667(t-4)}, \quad t \geq 4$$

Putting all this together,

$$i(t) = \begin{cases} 0, & t \leq 0 \\ 4(1 - e^{-2t}), & 0 \leq t \leq 4 \\ 2.727 + 1.273e^{-1.4667(t-4)}, & t \geq 4 \end{cases}$$

At $t = 2$,

$$i(2) = 4(1 - e^{-4}) = 3.93 \text{ A}$$

At $t = 5$,


$$i(5) = 2.727 + 1.273e^{-1.4667} = 3.02 \text{ A}$$

٤٠

٤١

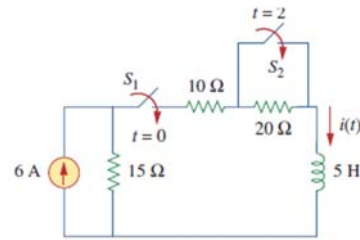Example 08

Switch S_1 in Fig. is closed at $t = 0$, and switch S_2 is closed at $t = 2$ s. Calculate $i(t)$ for all t . Find $i(1)$ and $i(3)$.



٤١

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

• At $t < 0$, S_1, S_2 are open
 $i(0^-) = 0$

• At $0 < t < 2$, S_1 close, S_2 open

• Calculate current using CD

$$I(\infty) = 6 \times \frac{15}{10 + 15 + 20} = 2 \text{ Amp}$$

$$R_{th} = 45 \Omega$$

$$\tau = \frac{L}{R_{th}} = \frac{5}{45} = \frac{1}{9}$$



$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 2 + (0 - 2)e^{-9t}$$

$$i(t) = 2(1 - e^{-9t}) \text{ A}$$

٤٢

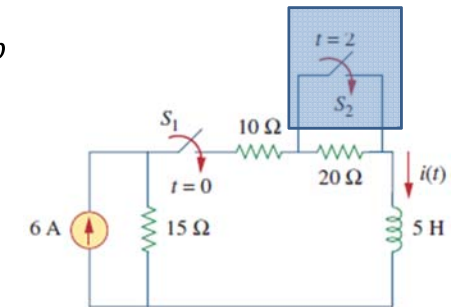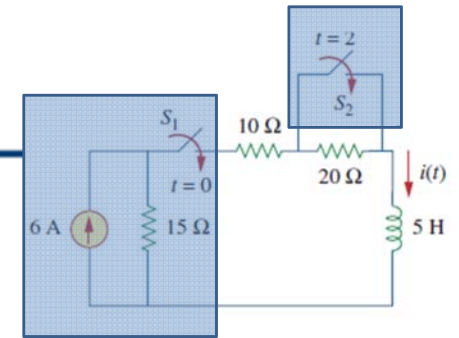Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II



• At $t > 2$,
 $i(t) = 2(1 - e^{-9t}) \text{ A}$

$$i(2^+) = i(2^-) = 2(1 - e^{-18}) \cong 2$$

• Calculate $I(\infty)$, using CD

$$I(\infty) = 6 \times \frac{15}{15 + 10} = 3.6 \text{ Amp}$$

$$R_{th} = 25 \Omega, \quad \tau = \frac{5}{25} = \frac{1}{5}$$

$$i(t) = i(\infty) + [i(2^+) - i(\infty)] e^{-(t-2)/\tau}$$

$$i(t) = 3.6 + (2 - 3.6)e^{-5(t-2)}$$

$$i(t) = 3.6 - 1.6e^{-5(t-2)}$$

٤٣

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II


$$\text{Thus, } i(t) = \begin{cases} 0 & t < 0 \\ 2(1 - e^{-9t}) \text{ A} & 0 < t < 2 \\ 3.6 - 1.6e^{-5(t-2)} \text{ A} & t > 2 \end{cases}$$


$$\text{At } t = 1, \quad i(1) = 2(1 - e^{-9}) = 1.9997 \text{ A}$$

$$\text{At } t = 3, \quad i(3) = 3.6 - 1.6e^{-5} = 3.589 \text{ A}$$

٤٤

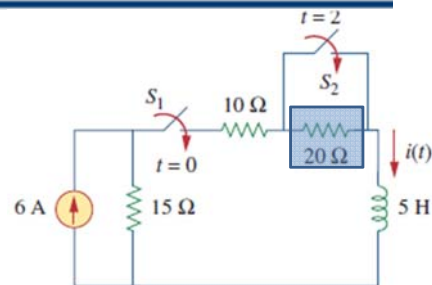Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II



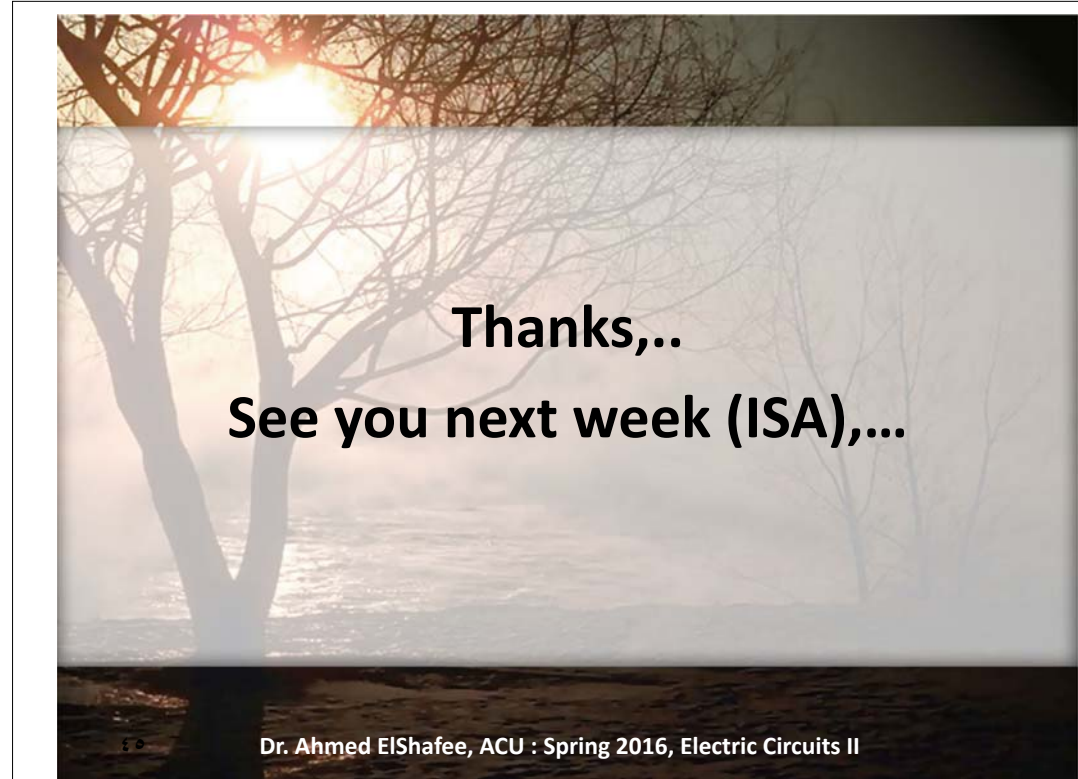

**Thanks,..
See you next week (ISA),...**

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II