


Lecture (04) Second Order Circuits I

By:
Dr. Ahmed ElShafee


Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

Introduction

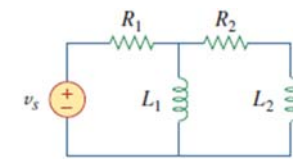
- we will consider circuits containing two storage elements. These are known as *second-order* circuits because their responses are described by differential equations that contain second derivatives.
- that a second-order circuit may have two storage elements of different type or the same type




(c)

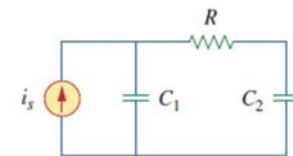

(d)

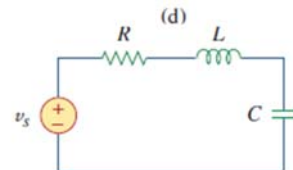

(a)

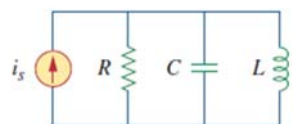

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circu

Finding Initial and Final Values


- The goal is to find, $v(0)$, $i(0)$, $dv(0)/dt$, $di(0)/dt$, $i(\infty)$, $v(\infty)$.
- we must carefully handle the polarity of voltage across the capacitor and the direction of the current through the inductor
- keep in mind that the capacitor voltage is always continuous, and the inductor current is always continuous

$$v(0^+) = v(0^-)$$

$$i(0^+) = i(0^-)$$

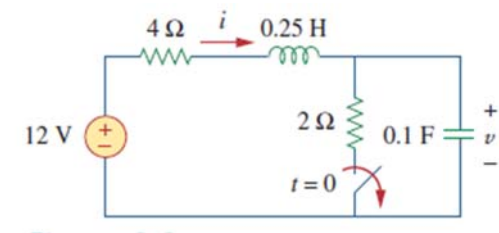Example 01

The switch in Fig. has been closed for a long time. It is open at $t = 0$. Find: (a) $i(0^+)$, $v(0^+)$, (b) $di(0^+)/dt$, $dv(0^+)/dt$, (c) $i(\infty)$, $v(\infty)$.



- Before $t < 0$, circuit reached steady state

- ohm


$$i(0^-) = \frac{12}{4 + 2} = 2 \text{ A,}$$

- Ohm

$$v(0^-) = 2i(0^-) = 4 \text{ V}$$

- As the inductor current and the capacitor voltage cannot change suddenly
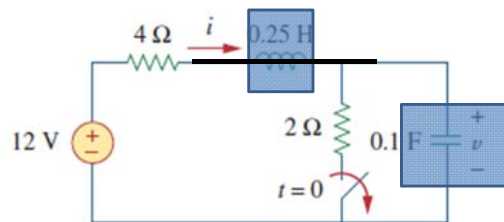
$$i(0^+) = i(0^-) = 2 \text{ A,} \quad v(0^+) = v(0^-) = 4 \text{ V}$$



- $t > 0$, switch is open

$$i(0^+) = i(0^-) = 2 \text{ A,} \quad v(0^+) = v(0^-) = 4 \text{ V}$$

- Capacitor ohm's law

$$C \frac{dv}{dt} = i_C, \quad \frac{dv}{dt} = i_C / C,$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{2}{0.1} = 20 \text{ V/s}$$

- KVL


$$-12 + 4i(0^+) + v_L(0^+) + v(0^+) = 0$$

$$v_L(0^+) = 12 - 8 - 4 = 0$$

- Coil ohm's law

$$L \frac{di}{dt} = v_L, \quad \frac{di}{dt} = v_L / L.$$

$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{0}{0.25} = 0 \text{ A/s}$$


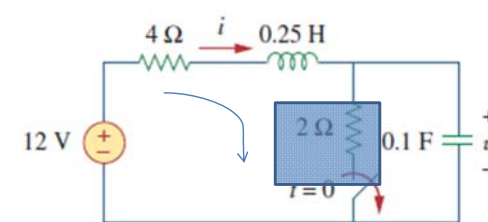


Example 02

The switch in Fig. was open for a long time but closed at $t = 0$. Determine: (a) $i(0^+)$, $v(0^+)$, (b) $di(0^+)/dt$, $dv(0^+)/dt$, (c) $i(\infty)$, $v(\infty)$.

- $t \rightarrow \infty$ the circuit reaches steady state again. The inductor acts like a short circuit and the capacitor like an open circuit,
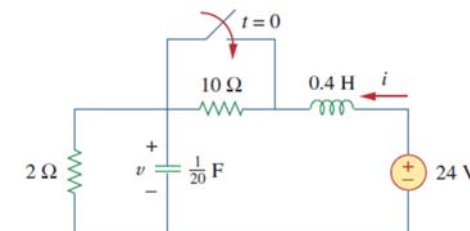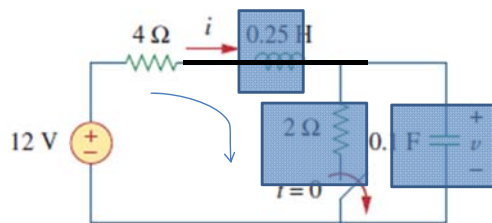
$$i(\infty) = 0 \text{ A,} \quad v(\infty) = 12 \text{ V}$$




- At $t < 0$ ($t(0^-)$)

- KVL

$$i(0^-) = 24 / (2 + 10) = 2 \text{ A,}$$

$$v(0^-) = 2i(0^-) = 4 \text{ V}$$
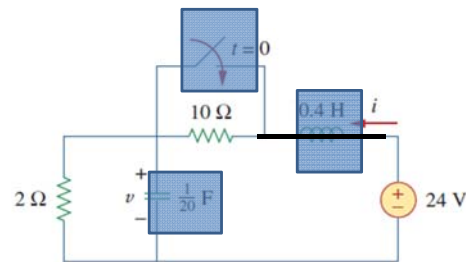
$$\text{hence, } v(0^+) = v(0^-) = 4 \text{ V.}$$



9

- At $t > 0$ ($t(0^+)$)

$$v(0^+) = v(0^-) = 4 \text{ V.}$$

- KVL @ right

$$v_C(0^+) + v_L(0^+) = 24$$


$$24 = 4 + v_L(0^+),$$

$$v_L(0^+) = 20 \text{ V}$$

- Coil ohm's law

$$L(di/dt) = v_L, \text{ leads to } (di/dt) = v_L/L$$
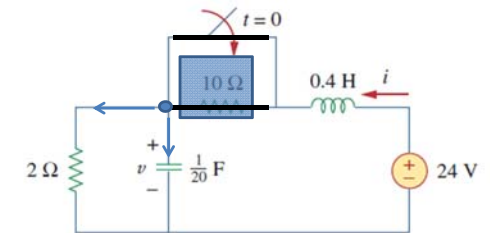
$$(di(0^+)/dt) = 20/0.4 = 50 \text{ A/s}$$



10


- KCL @ node

$$i(0^+) = i_C(0^+) + v(0^+)/2$$

$$2 = i_C(0^+) + 4/2$$

$$i_C(0^+) = 0,$$

$$(dv(0^+)/dt) = 0 \text{ V/s}$$

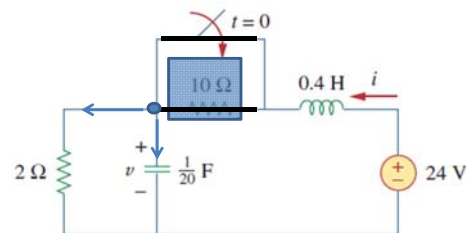


11

- @ $t >> 0$ $t \rightarrow \infty$

- Ohm's law

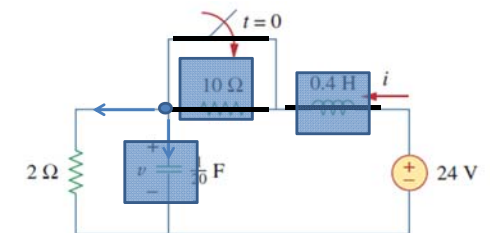
$$v(\infty) = 24 \text{ V, and } i(\infty) = 12 \text{ A.}$$



12

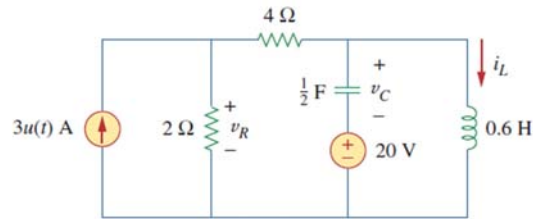Example 03

In the circuit of Fig. , calculate: (a) $i_L(0^+)$, $v_C(0^+)$, $v_R(0^+)$, (b) $di_L(0^+)/dt$, $dv_C(0^+)/dt$, $dv_R(0^+)/dt$, (c) $i_L(\infty)$, $v_C(\infty)$, $v_R(\infty)$.




• @ $t < 0$

$$3u(t) = 0$$

$$i_L(0^-) = 0$$

$$v_R(0^-) = 0$$

$$v_C(0^-) = -20 \text{ V}$$

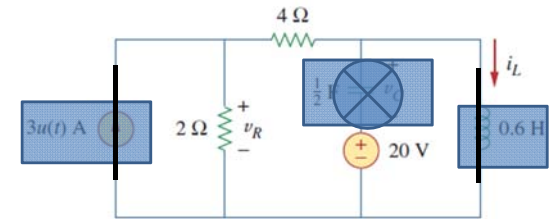

• For $t > 0$

$$3u(t) = 3$$

• inductor current and capacitor voltage cannot change immediately


$$i_L(0^+) = i_L(0^-) = 0$$

$$v_C(0^+) = v_C(0^-) = -20 \text{ V}$$

• Applying KCL at node a

$$3 = \frac{v_R(0^+)}{2} + \frac{V_{4\Omega}}{4} \quad \times 4$$
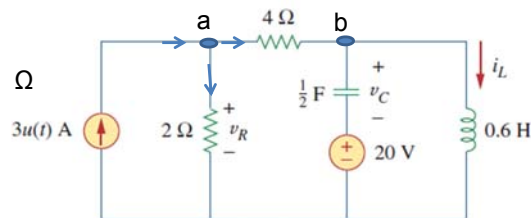
$$-2v_R(0^+) - V_{4\Omega}(0^+) = -12 \rightarrow 1$$



• Applying KVL to the middle mesh

$$-v_R(0^+) + V_{4\Omega}(0^+) + v_C(0^+) + 20 = 0$$

• While $v_C(0^+) = -20 \text{ V}$

$$-v_R(0^+) + V_{4\Omega}(0^+) = 0 \rightarrow 2$$


• Add 1,2

$$-3v_R(0^+) = -12$$

$$v_R(0^+) = 4 \text{ V}$$

• Substitute in 2

$$V_{4\Omega}(0^+) = 4 \text{ V}$$

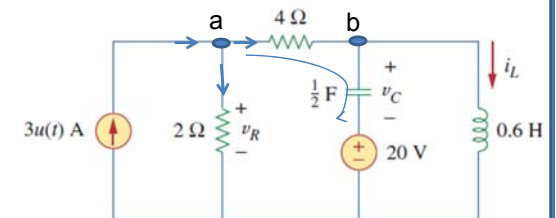

- applying KVL to the right mesh

$$v_L(0^+) - v_C(0^+) - 20 = 0$$

$$v_C(0^+) = -20 \text{ V}$$


$$v_L(0^+) = 0$$

- Apply Ohm's law on coil

$$L \frac{di_L}{dt} = v_L$$

$$\frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L}$$

$$\frac{di_L(0^+)}{dt} = 0$$

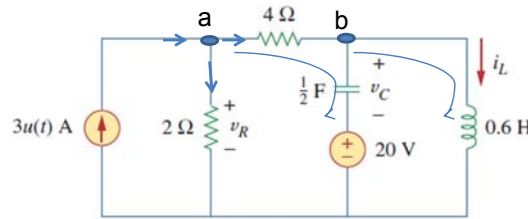

17

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- Apply KCL @ b

$$\frac{V_{4\Omega}}{4} = i_C(0^+) + i_L(0^+)$$

- while $V_{4\Omega}(0^+) = 4 \text{ V}$

- And $i_L(0^+) = i_L(0^-) = 0$,


$$i_C(0^+) = 4/4 = 1 \text{ A.}$$

- Ohm's law on capacitor

$$C \frac{dv_C}{dt} = i_C$$

$$\frac{dv_C}{dt} = i_C/C$$
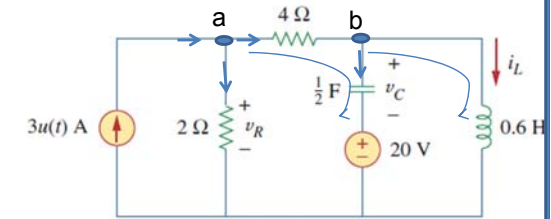
$$\frac{dv_C(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{1}{0.5} = 2 \text{ V/s}$$



18

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

To get $dv_R(0^+)/dt$,

- apply KCL to node a and obtain

$$3 = \frac{v_R(0^+)}{2} + \frac{V_{4\Omega}}{4}$$


- Taking the derivative of each term

$$0 = 2 \frac{dv_R(0^+)}{dt} + \frac{dV_{4\Omega}(0^+)}{dt} \rightarrow 1$$

- Applying KVL to the middle mesh

$$-v_R(0^+) + V_{4\Omega}(0^+) + v_C(0^+) + 20 = 0$$

- taking the derivative of each term

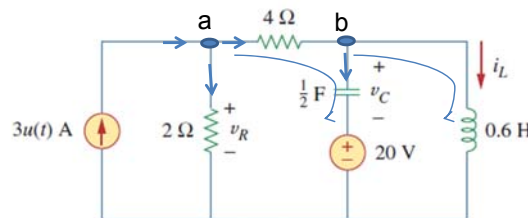

19

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- To find $di_R(0^+)/dt$


$$0 = 2 \frac{dv_R(0^+)}{dt} + \frac{dV_{4\Omega}(0^+)}{dt}$$

$$0 = 2 + \frac{dV_{4\Omega}(0^+)}{dt} - \frac{dv_R(0^+)}{dt}$$

$$\frac{dv_R}{dt} = \frac{2}{3}$$

- From ohm $V_R = 2 IR$
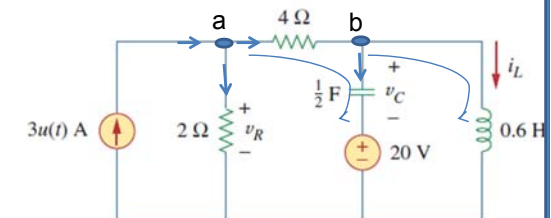
$$\frac{di_R(0^+)}{dt} = \frac{1}{2} \frac{dv_R(0^+)}{dt} = \frac{1}{2} \frac{2}{3} = \frac{1}{3} \text{ A/s}$$



20


Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- At $t \rightarrow \infty$

$$i_L(\infty) = \frac{2}{2+4} 3 \text{ A} = 1 \text{ A}$$

$$v_R(\infty) = \frac{4}{2+4} 3 \text{ A} \times 2 = 4 \text{ V},$$

$$v_C(\infty) = -20 \text{ V}$$

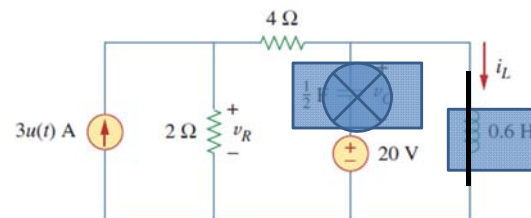

٢١

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

Source-Free Series RLC Circuit

$$v(0) = \frac{1}{C} \int_{-\infty}^0 i dt = v(0)$$

$$i(0) = I_0$$

- Apply KVL to get

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = 0$$

- Differentiate again


$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

- Need two initial conditions

$$i(0) \text{ and } \frac{di(0)}{dt}$$

- Assume

$$i = A e^{st}$$

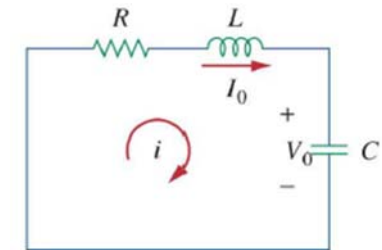

٢٢

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- Substitute

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- The roots will give us the natural frequencies s_1, s_2

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \text{ and } s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{where } \alpha = \frac{R}{2L} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$

- General solution will be

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

٢٣

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \text{ and } s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

The roots s_1 and s_2 are called *natural frequencies*, measured in nepers per second (Np/s), because they are associated with the natural response of the circuit;

$$\alpha = \frac{R}{2L} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$

response of the circuit; ω_0 is known as the *resonant frequency* or strictly as the *undamped natural frequency*, expressed in radians per second (rad/s);

and α is the *neper frequency* or the *damping factor*, expressed in nepers per second.

٢٤


Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- Case 1: Overdamped ($\alpha > \omega_0$)

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

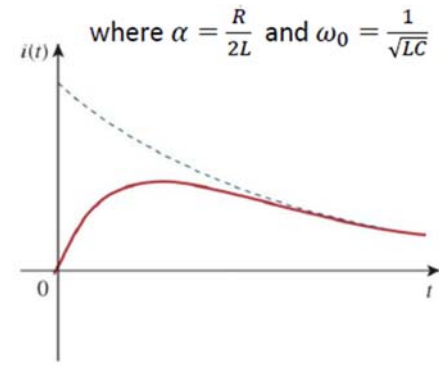


- Case 2: Critically damped ($\alpha = \omega_0$)

$$s_1 = s_2 = -\alpha$$

$$\text{where } \alpha = \frac{R}{2L}$$

$$i(t) = (A_1 t + A_2) e^{-\alpha t}$$

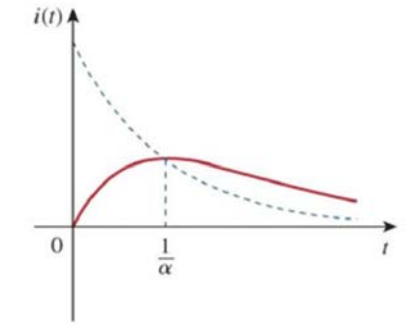

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \text{ and } s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{where } \alpha = \frac{R}{2L} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$


- Case 3: Underdamped ($\alpha < \omega_0$)

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$i(t) = e^{-\alpha t} (A_1 \cos(\sqrt{\omega_0^2 - \alpha^2} t) + A_2 \sin(\sqrt{\omega_0^2 - \alpha^2} t))$$

$$s_{1,2} = -\alpha \pm j\omega_d \text{ where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

ω_d : damping frequency

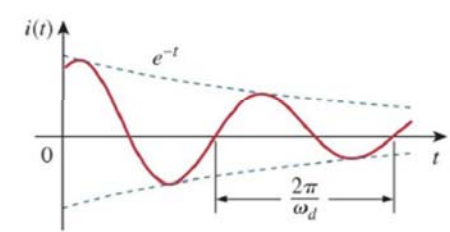

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


- To find A1, and A2, use initial conditions $I(0)$, $di(0)/dt$

$$\text{At } t = 0, \quad i(0) = 1 = A_1 + A_2$$

$$R i(0) + L \frac{di(0)}{dt} + V_0 = 0$$


$$\frac{di(0)}{dt} = -\frac{1}{L} (R I_0 + V_0)$$

- Sub $di(0)/dt$ and A1 in $i(t)$ to find A2

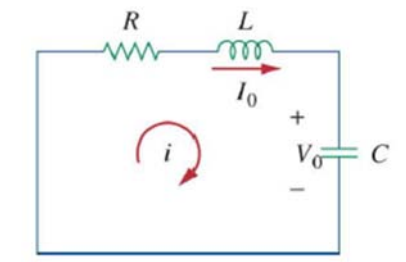

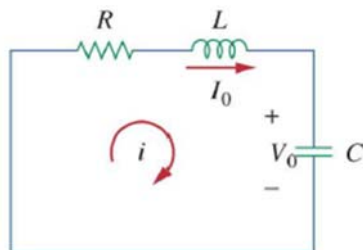Example 05

In Fig. $R = 40 \Omega$, $L = 4 \text{ H}$, and $C = 1/4 \text{ F}$. Calculate the characteristic roots of the circuit. Is the natural response overdamped, underdamped, or critically damped?



٢٩

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \text{ and } s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{where } \alpha = \frac{R}{2L} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$

$R = 40 \Omega$, $L = 4 \text{ H}$, and $C = 1/4 \text{ F}$.

$$\alpha = \frac{R}{2L} = \frac{40}{2(4)} = 5.$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \times \frac{1}{4}}} = 1$$

Since $\alpha > \omega_0$, we conclude that the response is overdamped.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5 \pm \sqrt{25 - 1}$$


$$s_1 = -0.101, \quad s_2 = -9.899$$

٣٠

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

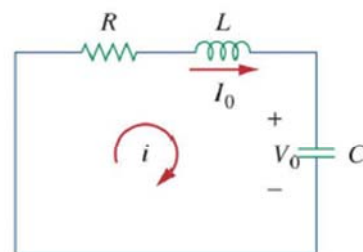Example 06

If $R = 10 \Omega$, $L = 5 \text{ H}$, and $C = 2 \text{ mF}$ in Fig. find α , ω_0 , s_1 , and s_2 . What type of natural response will the circuit have?



٣١

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

$$\text{where } \alpha = \frac{R}{2L} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$

$R = 10 \Omega$, $L = 5 \text{ H}$, and $C = 2 \text{ mF}$

$$\alpha = R/(2L) = 10/(2 \times 5) = 1,$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{5 \times 2 \times 10^{-2}} = 10$$

Underdamped ($\alpha < \omega_0$)

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -1 \pm \sqrt{1 - 100} = -1 \pm j9.95.$$


$$i(t) = e^{-t}(A_1 \cos(9.95t) + A_2 \sin(9.95t))$$

٣٢

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

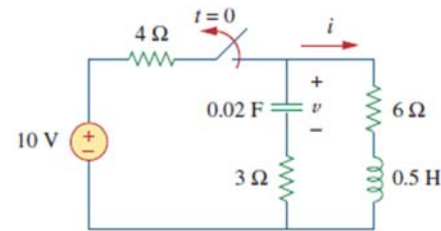Example 07

Find $i(t)$ in the circuit of Fig. . Assume that the circuit has reached steady state at $t = 0^-$.




- For $t < 0$, the switch is closed. The capacitor acts like an open circuit while the inductor acts like a shunted circuit

• C.D.

$$i(0) = \frac{10}{4 + 6} = 1 \text{ A.}$$

• Ohm

$$v(0) = 6i(0) = 6 \text{ V}$$

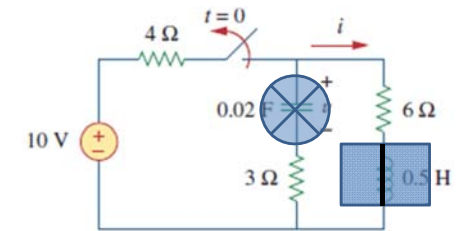

$$\text{where } \alpha = \frac{R}{2L} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$

- For $t > 0$ the switch is opened and the voltage source is disconnected.
- Req=9 ohm

$$\alpha = \frac{R}{2L} = \frac{9}{2(\frac{1}{2})} = 9,$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{2} \times \frac{1}{30}}} = 10$$

the response is underdamped ($\alpha < \omega$);

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -9 \pm \sqrt{81 - 100}$$

$$s_{1,2} = -9 \pm j4.359$$
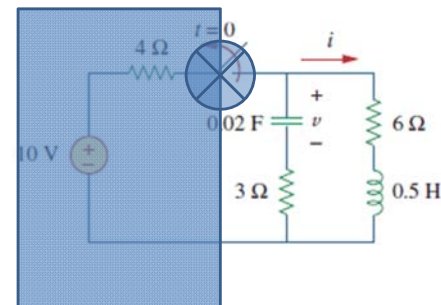
$$i(t) = e^{-9t}(A_1 \cos 4.359t + A_2 \sin 4.359t)$$



- We now obtain A1, A2 using the initial conditions

$$\text{At } t = 0, \quad i(0) = 1 = A_1$$

- But $\frac{di(0)}{dt} = -\frac{1}{L}(Ri_0 + V_0)$

• Then

$$\left. \frac{di}{dt} \right|_{t=0} = -\frac{1}{L}[Ri(0) + v(0)] = -2[9(1) - 6] = -6 \text{ A/s}$$

- Taking the derivative of $i(t) = e^{-9t}(A_1 \cos 4.359t + A_2 \sin 4.359t)$

$$\frac{di}{dt} = -9e^{-9t}(A_1 \cos 4.359t + A_2 \sin 4.359t) + e^{-9t}(4.359)(-A_1 \sin 4.359t + A_2 \cos 4.359t)$$


- Substituting di/dt from previous equation at $t=0$

$$-6 = -9 + 4.359A_2 \Rightarrow A_2 = 0.6882$$

$$i(t) = e^{-9t}(\cos 4.359t + 0.6882 \sin 4.359t) \text{ A}$$

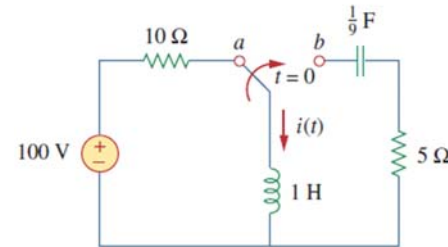Example 08

The circuit in Fig. has reached steady state at $t = 0^-$. If the make-before-break switch moves to position b at $t = 0$, calculate $i(t)$ for $t > 0$.




٣٧

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- For $t < 0$, the inductor is connected to the voltage source and when the circuit reaches steady state, the inductor acts like a short circuit

$$i(0^-) = 50/10 = 5 = i(0^+) = i(0)$$

$$0 = v(0^-) = v(0^+) = v(0).$$

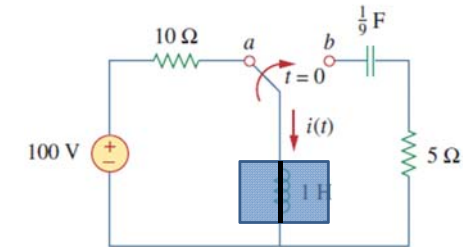

٣٨

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- For $t > 0$, we have a source-free RLC circuit


$$\alpha = R/(2L) = 5/(2 \times 1) = 2.5$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{1 \times \frac{1}{9}} = 3$$

- Since $\alpha < \omega_0$, we have an underdamped case

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -2.5 \pm \sqrt{6.25 - 9} = -2.5 \pm j1.6583$$
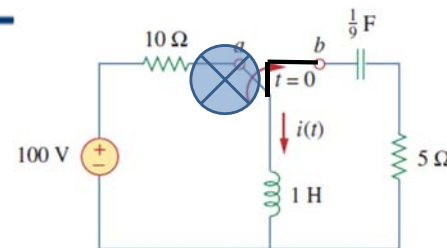
$$i(t) = e^{-2.5t} [A_1 \cos(1.6583t) + A_2 \sin(1.6583t)]$$



٣٩

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- We now determine A_1 and A_2 .

$$i(0) = 10 = A_1$$

- Sub in

$$di(0)/dt = -(1/L)[Ri(0) + v(0)] = -1[5 \times 10 + 0] = -1[50] = -50$$

- Differentiate

$$i(t) = e^{-2.5t} [A_1 \cos(1.6583t) + A_2 \sin(1.6583t)]$$

$$di/dt = -2.5 \{ e^{-2.5t} [A_1 \cos(1.6583t) + A_2 \sin(1.6583t)] \} + 1.6583 e^{-2.5t} [-A_1 \sin(1.6583t) + A_2 \cos(1.6583t)]$$

- Sub $di(0)/dt$ from previous, set $t=0$


$$-2.5(10) + 1.6583A_2 = -50$$

$$A_2 = -15.076$$

$$i(t) = e^{-2.5t} [10 \cos(1.6583t) - 15.076 \sin(1.6583t)] \text{ A}$$

٤٠

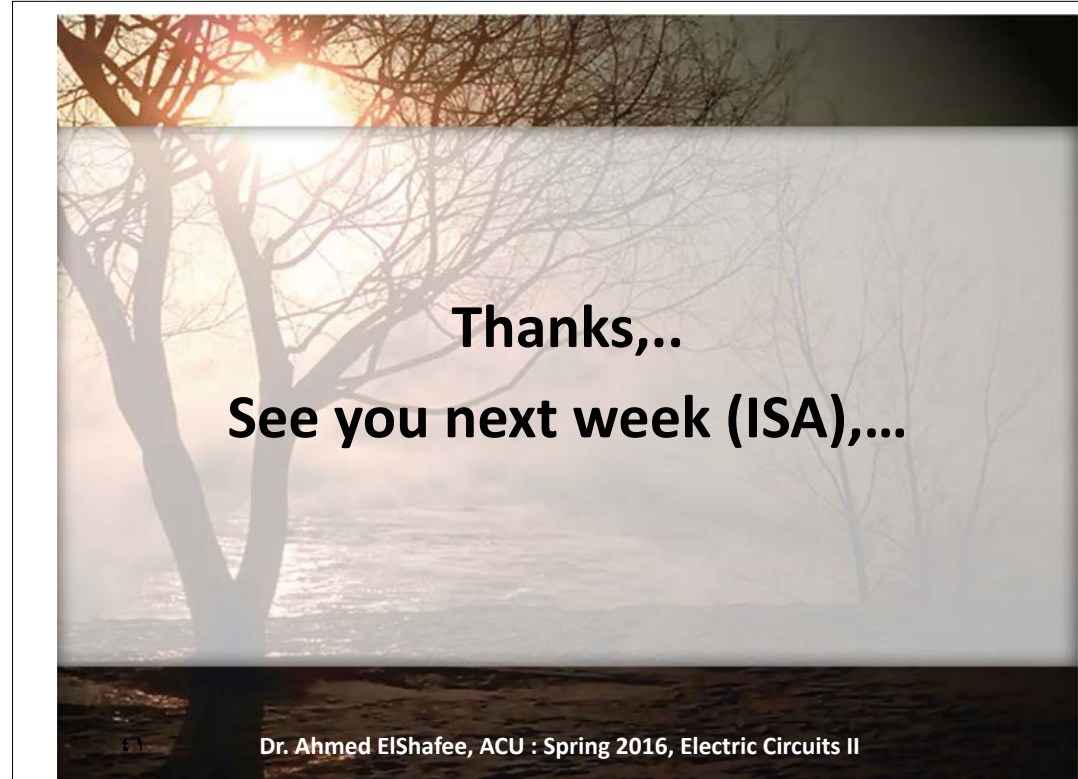Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II



Thanks,..
See you next week (ISA),...

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II