




# Lecture (05)

## Step Response of a RLC

By:

Dr. Ahmed ElShafee

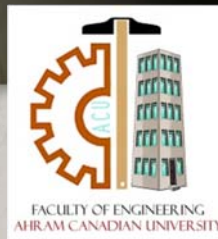

## Source Free RLC parallel circuit

$$i(0) = I_0 = \frac{1}{L} \int_{-\infty}^0 v(t) dt$$


$$v(0) = V_0$$

- Applying KCL @ V

$$\frac{v}{R} + \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau + C \frac{dv}{dt} = 0$$

- Divide by C and Take the derivative to get
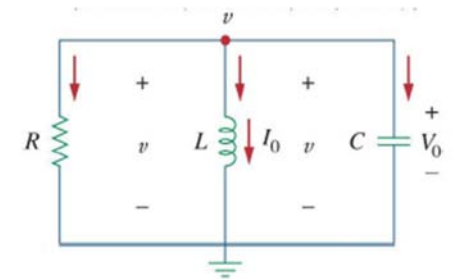
$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$



$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

- Need two initial conditions  $v(0)$  and  $\frac{dv(0)}{dt}$

Assume  $v = A e^{st}$  to get

- $V(0) = A$
- $\frac{dv}{dt} = A s e^{st}$
- $\frac{dv(0)}{dt} = A s$
- $\frac{d^2v}{dt^2} = A s^2 e^{st}$
- $\frac{d^2v(0)}{dt^2} = A s^2$
- $A \left( s^2 + \frac{1}{RC} s + \frac{1}{LC} \right) = 0$
- $\left( s^2 + \frac{1}{RC} s + \frac{1}{LC} \right) = 0$

- General solution for 2<sup>nd</sup> order polynomial equation

$$ax^2 + bx + c = 0$$

$$(x - x_1)(x - x_2) = 0$$

$$x_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$x_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

- $(s^2 + \frac{1}{RC}s + \frac{1}{LC}) = 0$

- The roots will give us the natural frequencies  $s_{1,2}$ :

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \text{ and } s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

where  $\alpha = \frac{1}{2RC}$  and  $\omega_0 = \frac{1}{\sqrt{LC}}$


- General solution will be

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

- **Case 1: Overdamped ( $\alpha > \omega_0$ )  $L > 4R^2C$ .**

$s_{1,2}$  are real:  $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

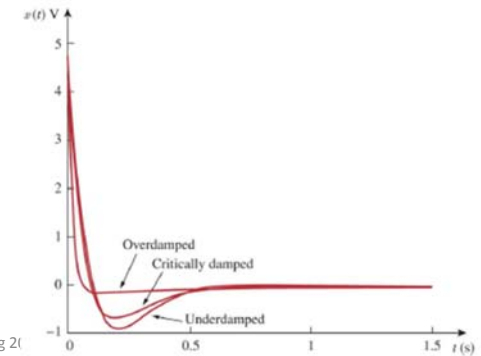
$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$



- **Case 2: Critically damped ( $\alpha = \omega_0$ )  $L = 4R^2C$ .**

$s_1 = s_2 = -\alpha$ :

$$v(t) = (A_1 t + A_2) e^{-\alpha t}$$

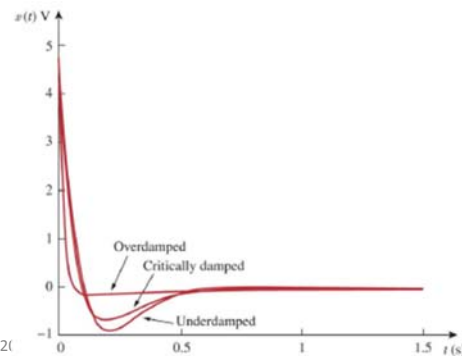


- **Case 3: Underdamped ( $\alpha < \omega_0$ )  $L < 4R^2C$ .**

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$s_{1,2} = -\alpha \pm j\omega_d$  where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ :

$$v(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

$\omega_d$ : damping frequency

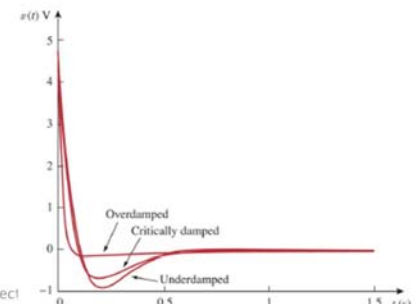

$$v'(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


The constants  $A_1$  and  $A_2$  in each case can be determined from the initial conditions. We need  $v(0)$  and  $dv(0)/dt$ . The first term is known from

$$v(0) = V_0$$

We find the second term by

$$\frac{V_0}{R} + I_0 + C \frac{dv(0)}{dt} = 0$$
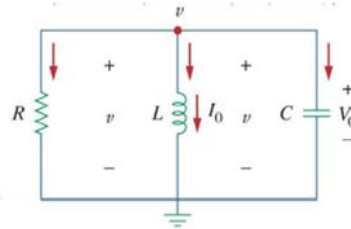
$$\frac{dv(0)}{dt} = -\frac{(V_0 + RI_0)}{RC}$$



Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Cir

## Summary

$$\alpha = \frac{1}{2RC} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad s_{1,2} = -\alpha \pm j\omega_d \text{ where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$s_1 = s_2 = -\alpha$$

- $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$  (Overdamped)  $\alpha > \omega_0$
- $v(t) = (A_1 t + A_2) e^{-\alpha t}$  (Critically damped)  $\alpha = \omega_0$
- $v(t) = (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) e^{-\alpha t}$  (Underdamped)  $\alpha < \omega_0$

$$v'(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v(0) = V_0$$


Init. Cond.

$$\frac{dv(0)}{dt} = -\frac{(V_0 + RI_0)}{RC}$$

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II
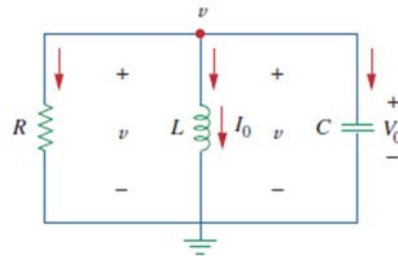
## Example 01

In the parallel circuit of Fig. , find  $v(t)$  for  $t > 0$ , assuming  $v(0) = 5 \text{ V}$ ,  $i(0) = 0$ ,  $L = 1 \text{ H}$ , and  $C = 10 \text{ mF}$ . Consider these cases:  $R = 1.923 \Omega$ ,  $R = 5 \Omega$ , and  $R = 6.25 \Omega$ .



Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

$$v(0) = 5 \text{ V}, i(0) = 0, L = 1 \text{ H}, \text{ and } C = 10 \text{ mF}.$$

$$R = 1.923 \Omega,$$

- Case 1

$$\text{If } R = 1.923 \Omega,$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 1.923 \times 10 \times 10^{-3}} = 26$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10 \times 10^{-3}}} = 10$$

Since  $\alpha > \omega_0$  in this case, the response is overdamped.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -2, -50$$

$$v(t) = A_1 e^{-2t} + A_2 e^{-50t}$$

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

---

We now apply the initial conditions to get  $A_1$  and  $A_2$ .

$$v(0) = 5 = A_1 + A_2$$
$$\frac{dv(0)}{dt} = -\frac{v(0) + Ri(0)}{RC} = -\frac{5 + 0}{1.923 \times 10 \times 10^{-3}} = -260$$

But differentiating  $v(t) = A_1e^{-2t} + A_2e^{-50t}$

$$\frac{dv}{dt} = -2A_1e^{-2t} - 50A_2e^{-50t}$$

At  $t = 0$ ,

$$-260 = -2A_1 - 50A_2$$

١٣

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

---

- $A_1 = -0.2083$

$$A_2 = 5.208.$$

$$v(t) = -0.2083e^{-2t} + 5.208e^{-50t}$$

١٤

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

$v(0) = 5 \text{ V}$ ,  $i(0) = 0$ ,  $L = 1 \text{ H}$ , and  $C = 10 \text{ mF}$ .  
 $R = 1.923 \Omega$ ,

- 
- Case 2:  $R = 5 \Omega$ ,

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 5 \times 10 \times 10^{-3}} = 10$$

while  $\omega_0 = 10$  remains the same. Since  $\alpha = \omega_0 = 10$ , the response is critically damped.

$$s_1 = s_2 = -10,$$

$$v(t) = (A_1 + A_2t)e^{-10t}$$

To get  $A_1$  and  $A_2$ , we apply the initial conditions

$$v(0) = 5 = A_1$$
$$\frac{dv(0)}{dt} = -\frac{v(0) + Ri(0)}{RC} = -\frac{5 + 0}{5 \times 10 \times 10^{-3}} = -100$$

١٥

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

---

But differentiating Eq.  $v(t) = (A_1 + A_2t)e^{-10t}$

$$\frac{dv}{dt} = (-10A_1 - 10A_2t + A_2)e^{-10t}$$

At  $t = 0$ ,

$$-100 = -10A_1 + A_2$$

$A_1 = 5$  and  $A_2 = -50$ . Thus,

$$v(t) = (5 - 50t)e^{-10t} \text{ V}$$

١٦

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

• Case 03 :

When  $R = 6.25 \Omega$ ,

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 6.25 \times 10 \times 10^{-3}} = 8$$

while  $\omega_0 = 10$  remains the same. As  $\alpha < \omega_0$  in this case, the response is underdamped.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -8 \pm j6$$

$$v(t) = (A_1 \cos 6t + A_2 \sin 6t)e^{-8t}$$

17

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

We now obtain  $A_1$  and  $A_2$ , as

$$v(0) = 5 = A_1$$

$$\frac{dv(0)}{dt} = -\frac{v(0) + Ri(0)}{RC} = -\frac{5 + 0}{6.25 \times 10 \times 10^{-3}} = -80$$

But differentiating  $v(t) = (A_1 \cos 6t + A_2 \sin 6t)e^{-8t}$

$$\frac{dv}{dt} = (-8A_1 \cos 6t - 8A_2 \sin 6t - 6A_1 \sin 6t + 6A_2 \cos 6t)e^{-8t}$$

At  $t = 0$ ,

$$-80 = -8A_1 + 6A_2$$



$A_1 = 5$  and  $A_2 = -6.667$ . Thus,

$$v(t) = (5 \cos 6t - 6.667 \sin 6t)e^{-8t}$$

18
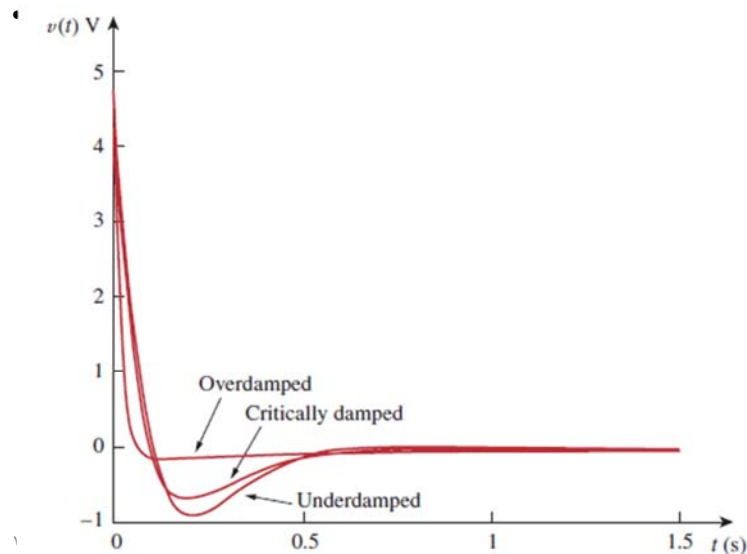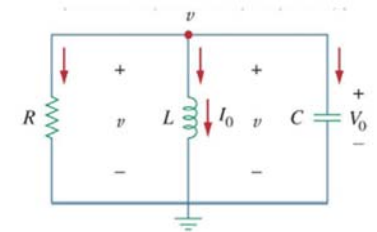
## Example 02

In Fig. , let  $R = 2 \Omega$ ,  $L = 0.4 \text{ H}$ ,  $C = 25 \text{ mF}$ ,  $v(0) = 0$ ,  $i(0) = 50 \text{ mA}$ . Find  $v(t)$  for  $t > 0$ .



19

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

where  $\alpha = \frac{1}{2RC}$  and  $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\alpha = 1/(2RC) = 1/(2 \times 2 \times 25 \times 10^{-3}) = 10$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{0.4 \times 25 \times 10^{-3}} = 10$$

since  $\alpha = \omega_0$ , we have a critically damped response. Therefore,

$$s_1 = s_2 = -\alpha:$$

$$v(t) = (A_1 t + A_2) e^{-\alpha t}$$

$$v(t) = [(A_1 + A_2 t) e^{-10t}]$$

٢١

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

Initial conditions  $v(0) = V_0$   $\frac{dv(0)}{dt} = -\frac{(V_0 + RI_0)}{RC}$

$$v(0) = 0 = A_1 + A_2 \times 0 = A_1, \text{ which leads to } v(t) = [A_2 t e^{-10t}].$$

$$dv(0)/dt = -(v(0) + Ri(0))/(RC) = -2 \times 0.05 / (2 \times 25 \times 10^{-3}) = -2$$

$$v(t) = [(A_1 + A_2 t) e^{-10t}]$$

$$dv/dt = [(A_2 - 10A_2 t) e^{-10t}]$$


$$\text{At } t = 0, \quad -2 = A_2 \text{ therefore, } v(t) = (-2t) e^{-10t} \mathbf{u}(t) \text{ V}$$

٢٢

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II
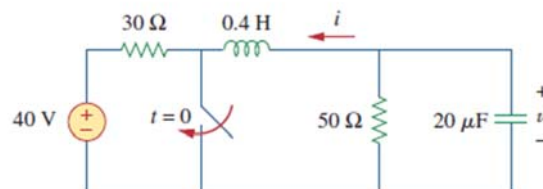
## Example 3


Find  $v(t)$  for  $t > 0$  in the RLC circuit of Fig.



٢٣

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

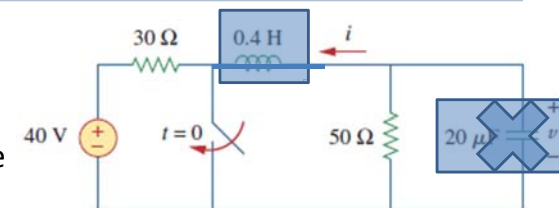When  $t < 0$  the switch is open; the inductor acts like a short circuit while the capacitor behaves like an open circuit.




$$v(0) = \frac{50}{30 + 50} (40) = \frac{5}{8} \times 40 = 25 \text{ V}$$

$$i(0) = -\frac{40}{30 + 50} = -0.5 \text{ A}$$

٢٤

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

- When  $t > 0$ , the switch is closed.

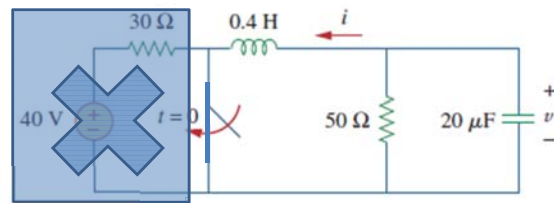

where  $\alpha = \frac{1}{2RC}$  and  $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 50 \times 20 \times 10^{-6}} = 500$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.4 \times 20 \times 10^{-6}}} = 354$$

Case 1: Overdamped ( $\alpha > \omega_0$ )  $L > 4R^2C$ .

$$s_{1,2} \text{ are real: } v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

٢٥

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -500 \pm \sqrt{250,000 - 124,997.6} = -500 \pm 354$$

$$s_1 = -854, \quad s_2 = -146$$

$$v(t) = A_1 e^{-854t} + A_2 e^{-146t}$$

- Initial conditions  $v(0) = V_0$   $\frac{dv(0)}{dt} = -\frac{(V_0 + RI_0)}{RC}$

At  $t = 0$ ,

$$v(0) = 25 = A_1 + A_2 \Rightarrow A_2 = 25 - A_1$$

٢٦

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

$$\frac{dv}{dt} = -854A_1 e^{-854t} - 146A_2 e^{-146t}$$

$$\frac{dv(0)}{dt} = -\frac{v(0) + Ri(0)}{RC} = -\frac{25 - 50 \times 0.5}{50 \times 20 \times 10^{-6}} = 0$$

$$0 = 854A_1 + 146A_2$$

$$A_1 = -5.156, \quad A_2 = 30.16$$


$$v(t) = -5.156e^{-854t} + 30.16e^{-146t} \text{ V}$$

٢٧

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II
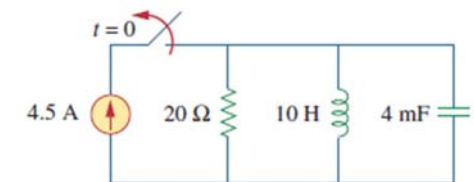
## Example 04

Refer to the circuit in Fig. Find  $v(t)$  for  $t > 0$ .



٢٨

Dr. Ahmed ElShafee, ACU : Spring 2016, Electric Circuits II

For  $t < 0$ , the switch is closed. The inductor acts like a short circuit while the capacitor acts like an open circuit. Hence,

$$i(0) = 4.5\text{A and } v(0) = 0.$$

$$\text{where } \alpha = \frac{1}{2RC} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$


$$\alpha = 1/(2RC) = 1/(2 \times 20 \times 4 \times 10^{-3}) = 6.25$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{10 \times 4 \times 10^{-3}} = 5$$

Since  $\alpha > \omega_0$ , this is an overdamped response.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$
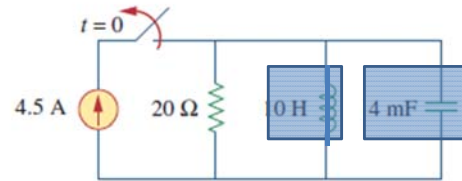
$$= -6.25 \pm \sqrt{(6.25)^2 - 25} = -2.5 \text{ and } -10$$



$$v(t) = A_1 e^{-2.5t} + A_2 e^{-10t}$$

• Initial conditions  $v(0) = V_0$   $\frac{dv(0)}{dt} = -\frac{(V_0 + RI_0)}{RC}$

$$dv(0)/dt = -(v(0) + Ri(0))/(RC) = -(20 \times 4.5)/12.5 = -1125$$

$$\text{But, } dv/dt = -2.5A_1 e^{-2.5t} - 10A_2 e^{-10t}$$

$$\text{At } t = 0, -1125 = -2.5A_1 - 10A_2 = 7.5A_1 \text{ since } A_1 = -A_2$$

$$A_1 = -150, A_2 = 150$$

$$\therefore v(t) = 150(e^{-10t} - e^{-2.5t}) \text{ V}$$



Thanks,..  
See you next week (ISA),...