

Electric Circuits II – Tutorial 01

Source Free RC Circuits


Q1

7.1 In the circuit shown in Fig. 7.81

$$v(t) = 56e^{-200t} \text{ V}, \quad t > 0$$

$$i(t) = 8e^{-200t} \text{ mA}, \quad t > 0$$

- Find the values of R and C .
- Calculate the time constant τ .
- Determine the time required for the voltage to decay half its initial value at $t = 0$.

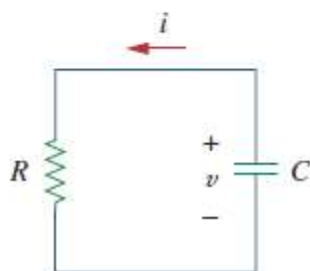

Sol 1

$$(a) \quad \tau = RC = 1/200$$

$$\text{For the resistor, } V = iR = 56e^{-200t} = 8Re^{-200t} \times 10^{-3} \quad \longrightarrow \quad R = \frac{56}{8} = \underline{7 \text{ k}\Omega}$$

$$C = \frac{1}{200R} = \frac{1}{200 \times 7 \times 10^3} = \underline{0.7143 \mu\text{F}}$$

$$(b) \quad \tau = 1/200 = \underline{5 \text{ ms}}$$

(c) If value of the voltage at $t = 0$ is 56 .

$$\frac{1}{2} \times 56 = 56e^{-200t} \quad \longrightarrow \quad e^{200t} = 2$$

$$200t_o = \ln 2 \quad \longrightarrow \quad t_o = \frac{1}{200} \ln 2 = \underline{3.466 \text{ ms}}$$

Q2

7.3 Determine the time constant for the circuit in Fig. 7.83

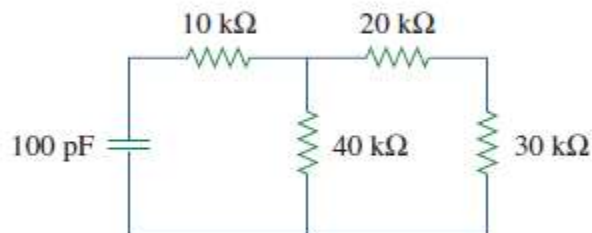


Figure 7.83

For Prob. 7.3.

Sol 2

$$R = 10 + 20 // (20 + 30) = 10 + 40 \times 50 / (40 + 50) = 32.22 \text{ k}\Omega$$

$$\tau = RC = 32.22 \times 10^3 \times 100 \times 10^{-12} = \underline{3.222 \mu\text{S}}$$

Q3

7.5 Using Fig. 7.85, design a problem to help other students better understand source-free RC circuits.

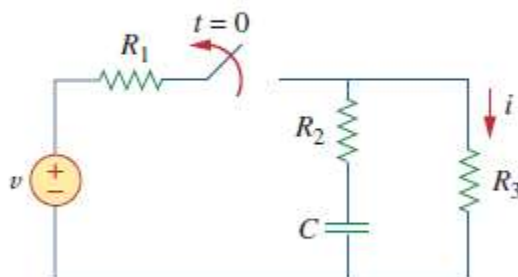


Figure 7.85

For Prob. 7.5.


Sol 3

Let v be the voltage across the capacitor.

For $t < 0$,

$$v(0^-) = \frac{4}{2+4}(24) = 16 \text{ V}$$

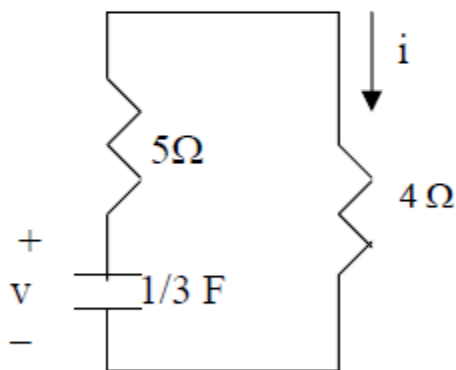For $t > 0$, we have a source-free RC circuit as shown below.



$$\tau = RC = (4+5)\frac{1}{3} = 3\text{s}$$

$$v(t) = v(0)e^{-t/\tau} = 16e^{-t/3} \text{ V}$$

$$i(t) = -C \frac{dv}{dt} = -\frac{1}{3} \left(-\frac{1}{3}\right) 16e^{-t/3} = \underline{1.778e^{-t/3} \text{ A}}$$

Q4

7.7 Assuming that the switch in Fig. 7.87 has been in position *A* for a long time and is moved to position *B* at $t = 0$. Then at $t = 1$ second, the switch moves from *B* to *C*. Find $v_C(t)$ for $t \geq 0$.

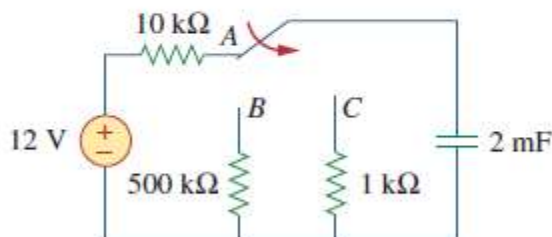


Figure 7.87
For Prob. 7.7.

Sol 4

Step 1. Determine the initial voltage on the capacitor. Clearly it charges to 12 volts when the switch is at position *A* because the circuit has reached steady state.

This then leaves us with two simple circuits, the first a 500 Ω resistor in series with a 2 mF capacitor and an initial charge on the capacitor of 12 volts. The second circuit which exists from $t = 1$ sec to infinity. The initial condition for the second circuit will be $v_C(1)$ from the first circuit. The time constant for the first circuit is $(500)(0.002) = 1$ sec and the time constant for the second circuit is $(1,000)(0.002) = 2$ sec. $v_C(\infty) = 0$ for both circuits.

Step 1.

$$v_C(t) = 12e^{-t} \text{ volts for } 0 < t < 1 \text{ sec and } = 12e^{-1}e^{-2(t-1)} \text{ at } t = 1 \text{ sec, and}$$

$$= 4.415e^{-2(t-1)} \text{ volts for } 1 \text{ sec} < t < \infty.$$

$$12e^{-t} \text{ volts for } 0 < t < 1 \text{ sec, } 4.415e^{-2(t-1)} \text{ volts for } 1 \text{ sec} < t < \infty.$$

Q5

7.9 The switch in Fig. 7.89 opens at $t = 0$. Find v_o for $t > 0$.

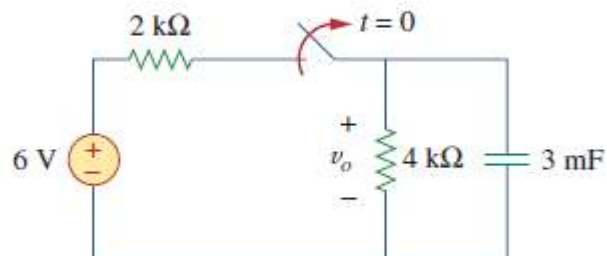


Figure 7.89

for Prob. 7.9.

Sol 5

For $t < 0$, the switch is closed so that

$$v_o(0) = \frac{4}{2+4}(6) = 4 \text{ V}$$

For $t > 0$, we have a source-free RC circuit.

$$\tau = RC = 3 \times 10^{-3} \times 4 \times 10^3 = 12 \text{ s}$$

$$v_o(t) = v_o(0)e^{-t/\tau} = 4e^{-t/12} \text{ V.}$$