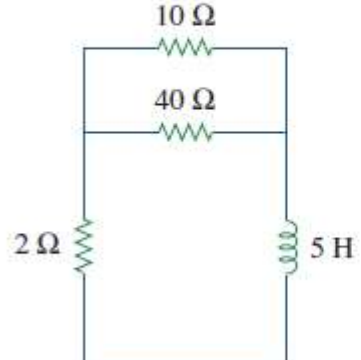
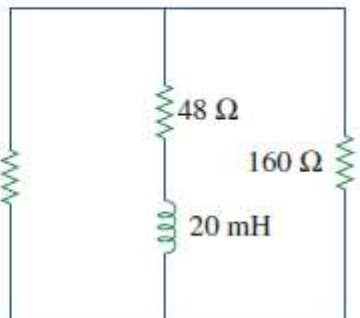
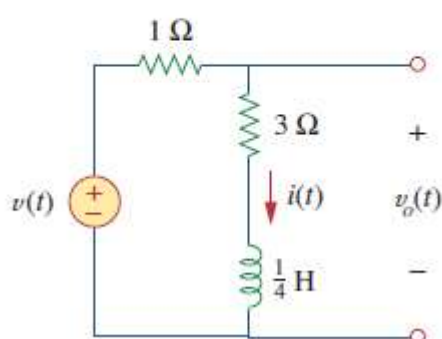


Electric Circuits II – Tutorial 02 - Source Free RL circuit, Singularity functions

#	Student ID	Student Name	Grade (10)
-			

<p>Q1</p>	<p>7.15 Find the time constant for each of the circuits in Fig. 7.95.</p> <div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;">  <p>(a)</p> </div> <div style="text-align: center;">  <p>(b)</p> </div> </div>
<p>Sol 1</p>	<p>(a) $R_{Th} = 2 + 10 // 40 = 10\Omega$, $\tau = \frac{L}{R_{Th}} = 5/10 = \underline{0.5s}$</p> <p>(b) $R_{Th} = 40 // 160 + 48 = 40\Omega$, $\tau = \frac{L}{R_{Th}} = (20 \times 10^{-3})/40 = \underline{0.25 ms}$</p> <p style="text-align: center;">(a) 10 Ω, 500 ms (b) 40 Ω, 250 μs</p>

<p>Q2</p>	<p>Consider the circuit of Fig. 7.97. Find $v_o(t)$ if $i(0) = 6 A$ and $v(t) = 0$.</p> <div style="text-align: center;">  </div>
-----------	---

Sol 2

$$i(t) = i(0)e^{-t/\tau}, \quad \tau = \frac{L}{R_{eq}} = \frac{1/4}{4} = \frac{1}{16}$$


$$i(t) = 6e^{-16t}$$

$$v_o(t) = 3i + L \frac{di}{dt} = 18e^{-16t} + (1/4)(-16)6e^{-16t}$$


$$v_o(t) = -6e^{-16t}u(t) \text{ V}$$

Q3

In the circuit of Fig. 7.99, find $i(t)$ for $t > 0$ if $i(0) = 6 \text{ A}$.

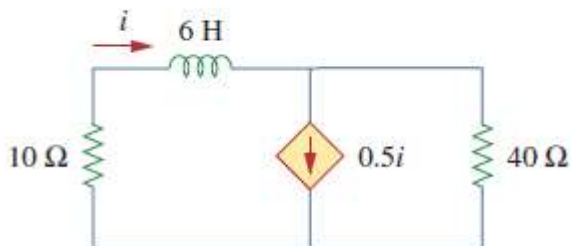

Sol 3

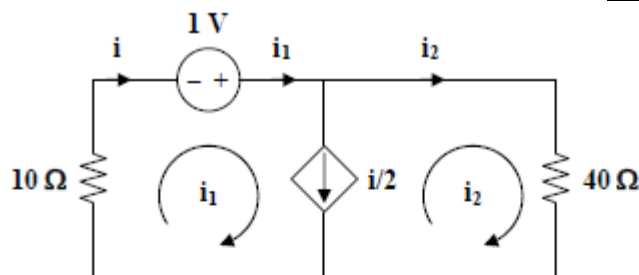

To find R_{th} we replace the inductor by a 1-V voltage source as shown above.

$$10i_1 - 1 + 40i_2 = 0$$

But $i = i_2 + i/2$ and $i = i_1$

i.e. $i_1 = 2i_2 = i$

$$10i - 1 + 20i = 0 \longrightarrow i = \frac{1}{30}$$


$$R_{th} = \frac{1}{i} = 30 \Omega$$

$$\tau = \frac{L}{R_{th}} = \frac{6}{30} = 0.2 \text{ s}$$

$$i(t) = 6e^{-5t}u(t) \text{ A}$$


Q4

In the circuit of Fig. 7.101, find the value of R for which the steady-state energy stored in the inductor will be 1 J.

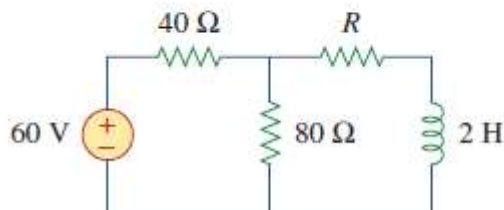

Sol 4

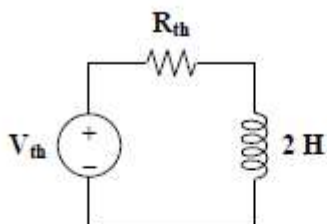The circuit can be replaced by its Thevenin equivalent shown below.



$$V_{th} = \frac{80}{80+40}(60) = 40 \text{ V}$$

$$R_{th} = 40 \parallel 80 + R = \frac{80}{3} + R$$

$$I = i(0) = i(\infty) = \frac{V_{th}}{R_{th}} = \frac{40}{80/3 + R}$$





$$w = \frac{1}{2}LI^2 = \frac{1}{2}(2)\left(\frac{40}{R+80/3}\right)^2 = 1$$

$$\frac{40}{R+80/3} = 1 \longrightarrow R = \frac{40}{3}$$

$$R = 13.333 \Omega$$

Q5

7.26 Express the signals in Fig. 7.104 in terms of singularity functions.

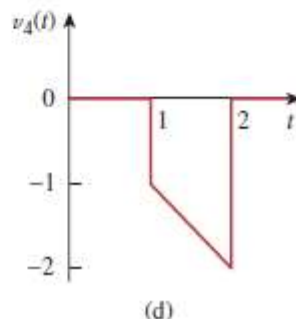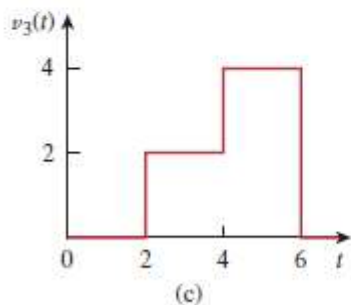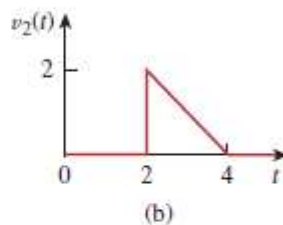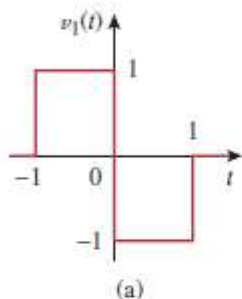

Sol 5

(a) $v_1(t) = u(t+1) - u(t) + [u(t-1) - u(t)]$
 $v_1(t) = u(t+1) - 2u(t) + u(t-1)$

(b) $v_2(t) = (4-t)[u(t-2) - u(t-4)]$
 $v_2(t) = -(t-4)u(t-2) + (t-4)u(t-4)$
 $v_2(t) = 2u(t-2) - r(t-2) + r(t-4)$

(c) $v_3(t) = 2[u(t-2) - u(t-4)] + 4[u(t-4) - u(t-6)]$
 $v_3(t) = 2u(t-2) + 2u(t-4) - 4u(t-6)$

(d) $v_4(t) = -t[u(t-1) - u(t-2)] = -tu(t-1) + tu(t-2)$
 $v_4(t) = (-t+1-1)u(t-1) + (t-2+2)u(t-2)$
 $v_4(t) = -r(t-1) - u(t-1) + r(t-2) + 2u(t-2)$