


Electric Circuits II – Tutorial 04

#	Student ID	Student Name	Grade (10)
-			

Q1

Refer to the circuit shown in Fig. Calculate:


- $i_L(0^+)$, $v_C(0^+)$, and $v_R(0^+)$,
- $di_L(0^+)/dt$, $dv_C(0^+)/dt$, and $dv_R(0^+)/dt$,
- $i_L(\infty)$, $v_C(\infty)$, and $v_R(\infty)$.

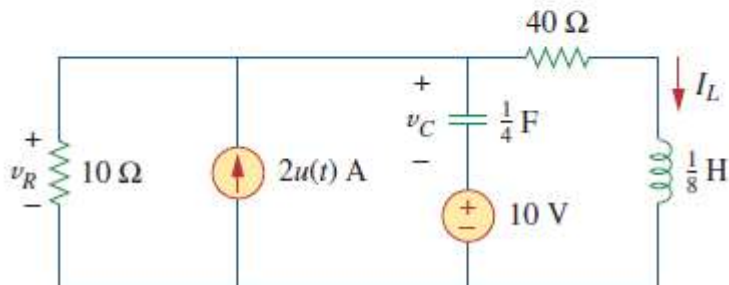

Sol 1

At $t = 0^-$, $u(t) = 0$. Consider the circuit shown in Figure (a). $i_L(0^-) = 0$, and $v_R(0^-) = 0$. But, $-v_R(0^-) + v_C(0^-) + 10 = 0$, or $v_C(0^-) = -10V$.

- At $t = 0^+$, since the inductor current and capacitor voltage cannot change abruptly, the inductor current must still be equal to 0A, the capacitor has a voltage equal to $-10V$. Since it is in series with the $+10V$ source, together they represent a direct short at $t = 0^+$. This means that the entire 2A from the current source flows through the capacitor and not the resistor. Therefore, $v_R(0^+) = 0 V$.
- At $t = 0^+$, $v_L(0^+) = 0$, therefore $L di_L(0^+)/dt = v_L(0^+) = 0$, thus, $di_L/dt = 0A/s$, $i_C(0^+) = 2 A$, this means that $dv_C(0^+)/dt = 2/C = 8 V/s$. Now for the value of $dv_R(0^+)/dt$. Since $v_R = v_C + 10$, then $dv_R(0^+)/dt = dv_C(0^+)/dt + 0 = 8 V/s$.

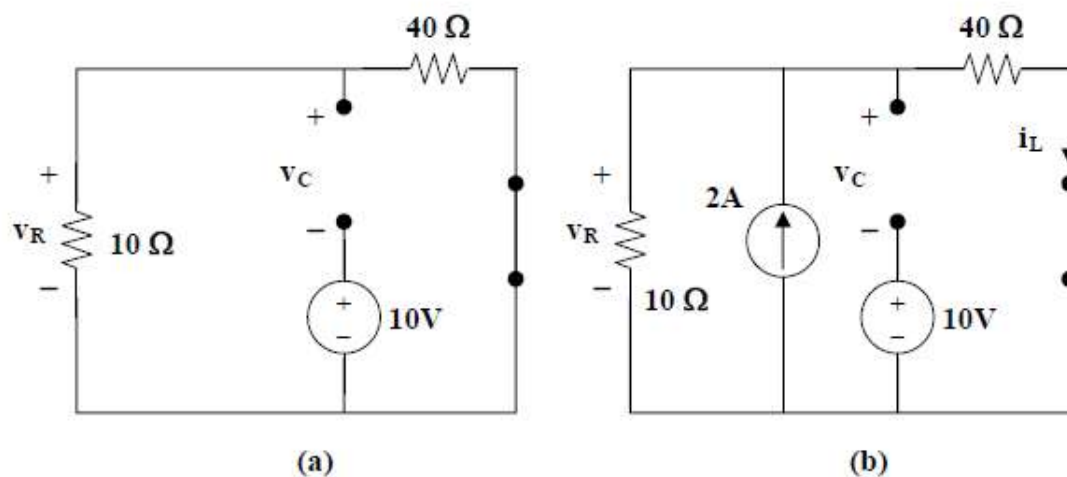

(c) As t approaches infinity, we end up with the equivalent circuit shown in Figure (b).

$$i_L(\infty) = 10(2)/(40 + 10) = 400 \text{ mA}$$


$$v_C(\infty) = 2[10\|40] - 10 = 16 - 10 = 6\text{V}$$

$$v_R(\infty) = 2[10\|40] = 16 \text{ V}$$

Q2


For the circuit in Fig. , find:

- (a) $i(0^+)$ and $v(0^+)$,
- (b) $di(0^+)/dt$ and $dv(0^+)/dt$,
- (c) $i(\infty)$ and $v(\infty)$.

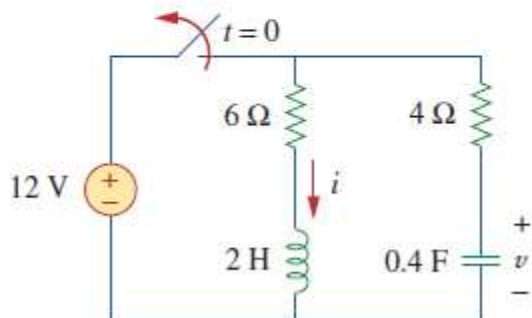


Sol 2

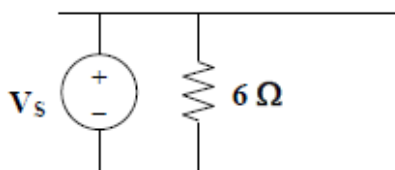(a) At $t = 0^-$, the circuit has reached steady state so that the equivalent circuit is shown in Figure (a).



(a)

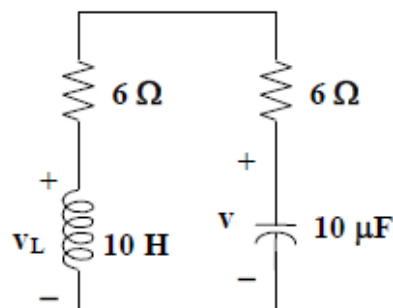

(b)

$$i(0^-) = 12/6 = 2A, v(0^-) = 12V$$

$$\text{At } t = 0^+, i(0^+) = i(0^-) = 2A, v(0^+) = v(0^-) = 12V$$

(b) For $t > 0$, we have the equivalent circuit shown in Figure (b).

$$v_L = Ldi/dt \text{ or } di/dt = v_L/L$$

Applying KVL at $t = 0+$, we obtain,

$$v_L(0+) - v(0+) + 10i(0+) = 0$$

$$v_L(0+) - 12 + 20 = 0, \text{ or } v_L(0+) = -8$$

Hence, $di(0+)/dt = -8/2 = -4 \text{ A/s}$

Similarly, $i_C = Cdv/dt$, or $dv/dt = i_C/C$

$$i_C(0+) = -i(0+) = -2$$

$$dv(0+)/dt = -2/0.4 = -5 \text{ V/s}$$


(c) As t approaches infinity, the circuit reaches steady state.

$$i(\infty) = 0 \text{ A}, \quad v(\infty) = 0 \text{ V}$$

Q3	<p>The differential equation that describes the voltage in an <i>RLC</i> network is</p> $\frac{d^2v}{dt^2} + 5\frac{dv}{dt} + 4v = 0$ <p>Given that $v(0) = 0$, $dv(0)/dt = 10$ V/s, obtain $v(t)$.</p>
Sol 3	$s^2 + 5s + 4 = 0, \text{ thus } s_{1,2} = \frac{-5 \pm \sqrt{25-16}}{2} = -4, -1.$ $v(t) = (Ae^{-4t} + Be^{-t}), v(0) = 0 = A + B, \text{ or } B = -A$ $dv/dt = (-4Ae^{-4t} - Be^{-t})$ $dv(0)/dt = 10 = -4A - B = -3A \text{ or } A = -10/3 \text{ and } B = 10/3.$ <p>Therefore, $v(t) = -(10/3)e^{-4t} + (10/3)e^{-t}$ V</p>

Q4

The switch in Fig. moves from position A to position B at $t = 0$ (please note that the switch must connect to point B before it breaks the connection at A , a make-before-break switch). Let $v(0) = 0$, find $v(t)$ for $t > 0$.

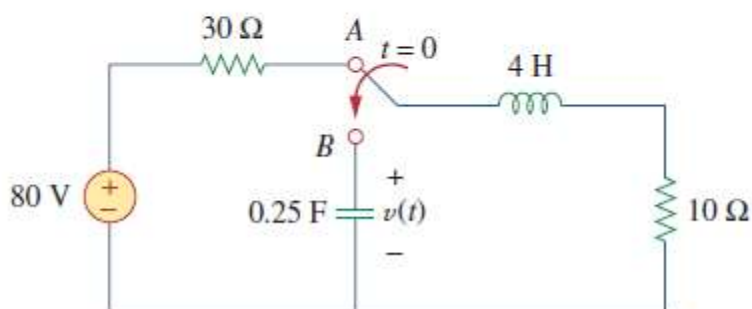

Sol 4

When the switch is in position A , $v(0^-) = 0$ and $i_L(0) = 80/40 = 2$ A. When the switch is in position B , we have a source-free series RCL circuit.

$$\alpha = \frac{R}{2L} = \frac{10}{2 \times 4} = 1.25$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times 4}} = 1$$

When the switch is in position A , $v(0^-) = 0$. When the switch is in position B , we have a source-free series RCL circuit.

$$\alpha = \frac{R}{2L} = \frac{10}{2 \times 4} = 1.25$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times 4}} = 1$$

Since $\alpha > \omega_o$, we have overdamped case.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -1.25 \pm \sqrt{1.5625 - 1} = -0.5 \text{ and } -2 \quad 0.9336$$



$$v(t) = Ae^{-2t} + Be^{-0.5t} \quad (1)$$

$$v(0) = 0 = A + B \quad (2)$$

$$i_C(0) = C(dv(0)/dt) = -2 \text{ or } dv(0)/dt = -2/C = -8.$$

$$\text{But } \frac{dv(t)}{dt} = -2Ae^{-2t} - 0.5Be^{-0.5t}$$


$$\frac{dv(0)}{dt} = -2A - 0.5B = -8 \quad (3)$$

Solving (2) and (3) gives $A = 1.3333$ and $B = -1.3333$

$$v(t) = 5.333e^{-2t} - 5.333e^{-0.5t} \text{ V.}$$

Q5

Find $i(t)$ for $t > 0$ in the circuit of Fig.

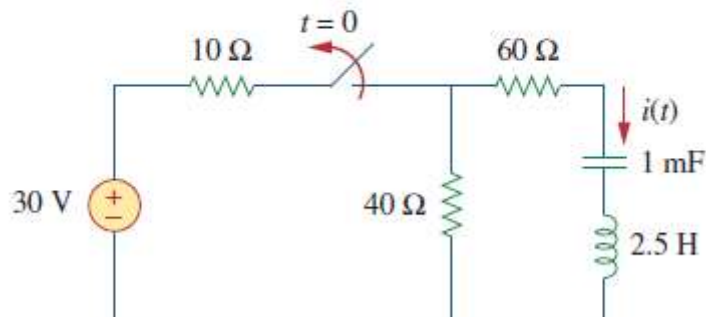

Sol 5

At $t = 0$, $i(0) = 0$, $v_C(0) = 40 \times 30 / 50 = 24V$

For $t > 0$, we have a source-free RLC circuit.

$$\alpha = R/(2L) = (40 + 60)/5 = 20 \text{ and } \omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 2.5}} = 20$$

$\omega_o = \alpha$ leads to critical damping

$$i(t) = [(A + Bt)e^{-20t}], \quad i(0) = 0 = A$$

$$di/dt = \{[Be^{-20t}] + [-20(Bt)e^{-20t}]\},$$

$$\text{but } di(0)/dt = -(1/L)[Ri(0) + v_C(0)] = -(1/2.5)[0 + 24]$$

$$\text{Hence, } \quad B = -9.6 \text{ or } i(t) = [-9.6te^{-20t}] \text{ A}$$