


Electromagnetic Fields – Tutorial 03 & Assignment 03 Transmission Lines Fundamentals

#	Student ID	Student Name	Grade (10)
-			

Delivery Date	
---------------	--

١. يتم تسليم التمرين محلولا في خلال أسبوع من تاريخ التمرين، و يتم حذف درجتين من التمرين عن كل أسبوع تأخير
٢. يتم التسليم لمعيد المقرر مباشرة
٣. تتم أجابه التمرين في نفس ورق الأسئلة

Q1

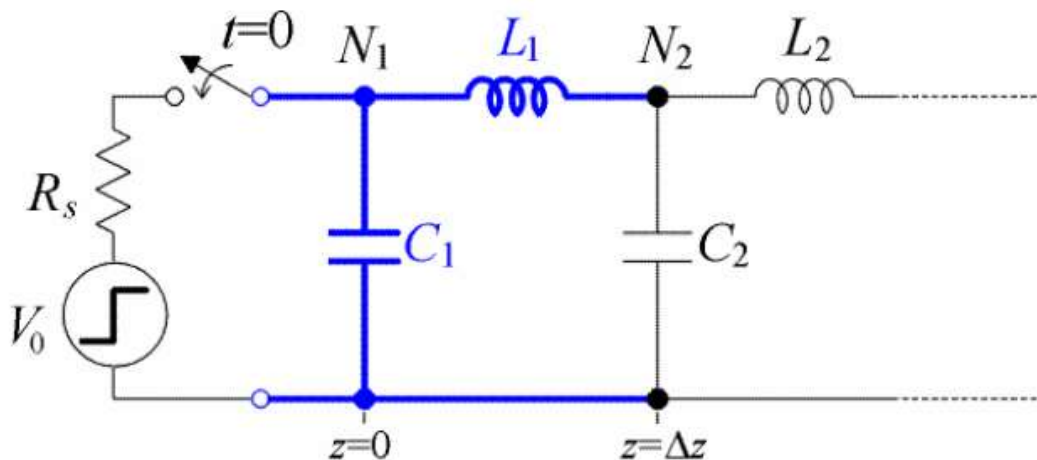

Circuit model of transmission line.

Consider the distributed circuit model of a lossless transmission line shown in Fig.

Assume the line is initially at rest, i.e. $v(z, 0^-) = 0$ (zero voltage for any node N_i at

$t = 0^-$), $i(z, 0^-) = 0$ (zero current for any branch at $t = 0^-$).

Part 2	<p>What is the current along C_1 at $t = 0^+$? What is the voltage of node N_2 at $t = 0^+$, i.e. $v(\Delta z, 0^+)$? (<i>Hint: Borrow the result of Problem a.</i>)</p>
	<div style="border: 1px solid black; padding: 10px; margin: 10px auto; width: 80%;"> <p>At the moment the switch pressed down, the output voltage electron source will first hole to do across the capacitor charge, then you can As access to the first capacitor. Therefore, the flow in the current through the wire and the capacitor will be</p> $I_c = \frac{V_0}{R_s}$ <p>According to</p> $v = L \frac{di}{dt}$ <p>the inductor current change will not be instantaneous change, rising from scratch. So both ends of the inductor L1 at $t=0^+$, not have a voltage difference, the voltage on the N2 is zero.</p> </div>



Part
3

Describe how do node voltages at N_1, N_2, \dots , and branch currents along inductors L_1, L_2, \dots change with time ($t > 0^+$)? Justify the “wave” behavior accordingly.

When the switch is on, the voltage source through a resistor R_s capacitor C_1 is charged, so that the voltage V_1 N_1 gradually rises.

Before charging capacitor C_1 , inductor L_1 no current flows. After capacitor charging, V_1 rises, the inductance L_1 voltage appears across difference, stay off the inductor current I_1 gradually increased.

When current flows through L_1 , the capacitor C_2 can be charged, and so on, will gradually transfer the energy down.

But regardless of capacitance or inductance will take some time to change the voltage across or current. Therefore, the energy transfer must After a time difference. Therefore, the voltage change in the voltage of N_1 and N_2 , there will be a time difference, so the voltage of N_2 And voltage variations N_3 will have the time difference. And after the current through L_1 , it takes some time before through the inductor L_2 , back through the inductor current situation and so on.

In the lossless transmission line, assuming the capacitance and inductance values each segment are the same as the equivalent circuit, the voltage and The current will pass along a particular speed.

Described above can be found in accordance with the transmission line voltage and current having wave characteristics.

Because the values of voltage and current with the changing time and location, and continue to pass along the $+z$ direction.