

# Logic Design– Assignment 06

#	Student ID	Student Name	Grade (10)
-			

Delivery Date	
---------------	--

<p>١. يتم تسليم التمرين محلولا في خلال أسبوع من تاريخ التمرين، و يتم حذف درجتين من التمرين عن كل أسبوع تأخير</p> <p>٢. يتم التسليم لمعيد المقرر مباشرة</p> <p>٣. تتم أجابه التمرين في نفس ورق الأسئلة</p>
---



Q1

A combinational circuit has four inputs ( $A, B, C, D$ ) and four outputs ( $W, X, Y, Z$ ).  $WXYZ$  represents an excess-3 coded number whose value equals the number of 1's at the input. For example, if  $ABCD = 1101$ ,  $WXYZ = 0110$ .

- (a) Find the minterm expansions for  $X, Y$ , and  $Z$ .
- (b) Find the maxterm expansions for  $Y$  and  $Z$ .

Sol  
1

$ABCD$	$WXYZ$
0000	0011
0001	0100
0010	0100
0011	0101
0100	0100
0101	0101
0110	0101
0111	0110
1000	0100
1001	0101
1010	0101
1011	0110
1100	0101
1101	0110
1110	0110
1111	0111

$$\begin{aligned}
 X = & A'B'C'D + A'B'CD' + A'B'CD + A'BC'D' + A'BC'D + A'BCD' \\
 & + A'BCD + AB'C'D' + AB'C'D + AB'CD' + AB'CD + ABC'D' + ABC'D + ABCD' + ABCD
 \end{aligned}$$

$$\begin{aligned}
 Y = & A'B'C'D' + A'BCD + ABC'D + ABCD' + ABCD
 \end{aligned}$$

$$\begin{aligned}
 Z = & A'B'C'D' + A'B'CD + A'BC'D + A'BCD' + AB'C'D + AB'CD' + AB'CD + ABC'D' + ABCD
 \end{aligned}$$



### Faculty of Engineering

.....  $Y = (A + B + C + D')(A + B + C' + D)$  .....

.....  $(A + B + C' + D')(A + B' + C + D)$  .....

.....  $(A + B' + C + D')(A + B' + C' + D)$  .....

.....  $(A' + B + C + D)(A' + B + C + D')$  .....

.....  $(A' + B + C' + D)(A' + B + C' + D')$  .....

.....  $(A' + B' + C + D)$  .....

.....  $Z = (A + B + C + D')(A + B + C' + D)$  .....

.....  $(A + B' + C + D)(A + B' + C' + D)$  .....

.....  $(A' + B + C + D)(A' + B' + C + D')$  .....

.....  $(A' + B' + C' + D)$  .....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....





Q2

A half adder is a circuit that adds two bits to give a sum and a carry. Give the truth table for a half adder, and design the circuit using only two gates. Then design a circuit which will find the 2's complement of a 4-bit binary number. Use four half adders and any additional gates. (*Hint: Recall that one way to find the 2's complement of a binary number is to complement all bits, and then add 1.*)

Sol  
2

XY	Sum	Cout
0 0	0	0
0 1	1	0
1 0	1	0
1 1	0	1

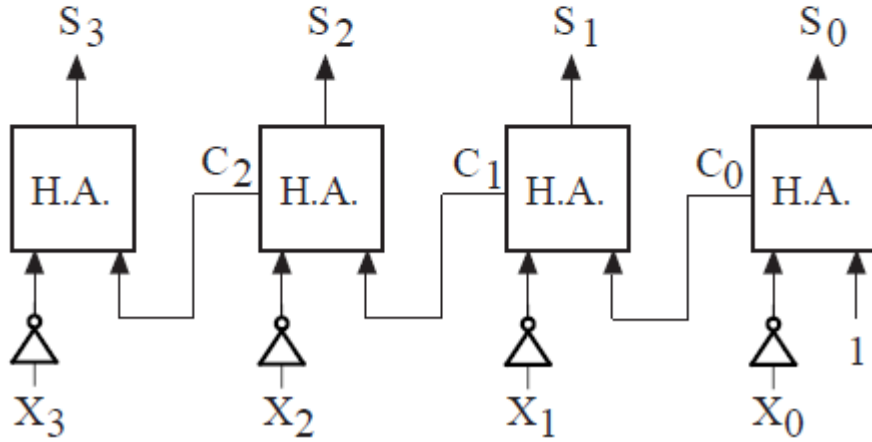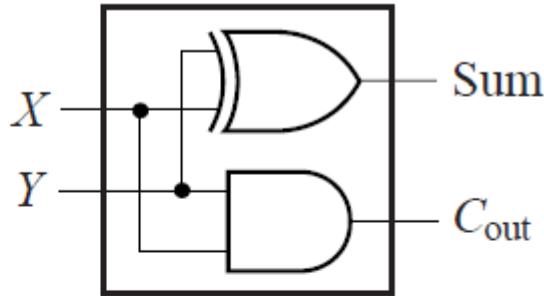



Faculty of Engineering

Q3	<p>(a) If <math>m_1</math> and <math>m_2</math> are minterms of <math>n</math> variables, prove that <math>m_1 - m_2 = m_1 \oplus m_2</math>.</p> <p>(b) Prove that any switching function can be written as the exclusive-OR sum of products where each product does not contain a complemented literal. [Hint: Start with the function written as a sum of minterms and use Part (a).]</p>
Sol 3	<p>... (a) <math>m_1 + m_2 = m_1(m_2' + m_2) + (m_1' + m_1)m_2</math> .....</p> <p>... <math>= m_1m_2' + m_1m_2 + m_1'm_2</math> .....</p> <p>... But <math>m_1m_2 = 0</math>, so <math>m_1 + m_2 = m_1m_2' + m_1'm_2</math> .....</p> <p>... <math>= m_1 \oplus m_2</math>.</p> <p>... (b) Using part (a), any function can be written as .....</p> <p>... the exclusive-or sum of its minterms. However, if .....</p> <p>... a product contains a complemented literal, it can .....</p> <p>... be written as the exclusive-or sum of two products .....</p> <p>... without a complemented literal by using .....</p> <p>... <math>x'p = (x \oplus 1)p = xp \oplus p</math>.</p> <p>... By repeated application of the preceding .....</p> <p>... relationship, all complemented literals can be .....</p> <p>... removed from the products. ....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p>