

# Logic Design – Tutorial

## 06

#	Student ID	Student Name	Grade (10)
-			



Q1

Work parts (a) through (d) with the given truth table.

A	B	C	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>	F <sub>4</sub>
0	0	0	1	1	0	1
0	0	1	X	0	0	0
0	1	0	0	1	X	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	X	0	1	0
1	1	0	0	X	X	X
1	1	1	1	X	1	X

- (a) Find the simplest expression for  $F_1$ , and specify the values for the don't-cares that lead to this expression.
- (b) Repeat for  $F_2$ .
- (c) Repeat for  $F_3$ .
- (d) Repeat for  $F_4$ .

Sol 1

If don't cares are changed to (1, 1), respectively,

$$F_1 = A'B'C' + ABC + A'B'C + AB'C \\ = A'B' + AC$$

If don't cares are changed to (1, 0), respectively

$$F_2 = A'B'C' + A'BC' + AB'C' + ABC' = C'$$

If don't cares are changed to (1, 1), respectively

$$F_3 = (A + B + C)(A + B + C') = A + B$$

If don't cares are changed to (0, 1), respectively

$$F_4 = A'B'C' + A'BC + AB'C' + ABC \\ = B'C' + BC$$



Faculty of Engineering

Q2

A combinational circuit has four inputs ( $A, B, C, D$ ) and three outputs ( $X, Y, Z$ ).  $XYZ$  represents a binary number whose value equals the number of 1's at the input.

For example if  $ABCD = 1011$ ,  $XYZ = 011$ .

(a) Find the minterm expansions for  $X, Y$ , and  $Z$ .

(b) Find the maxterm expansions for  $Y$  and  $Z$ .

Sol 2

$ABCD$	1's	$XYZ$
0000	0	000
0001	1	001
0010	1	001
0011	2	010
0100	1	001
0101	2	010
0110	2	010
0111	3	011
1000	1	001
1001	2	010
1010	2	010
1011	3	011
1100	2	010
1101	3	011
1110	3	011
1111	4	100

$$X = ABCD$$

$$Y = A'B'CD + A'BC'D + A'BCD' + A'B'CD' + AB'C'D + AB'CD' + AB'CD + ABC'D' + ABC'D + ABCD'$$

$$Z = A'B'C'D + A'B'CD' + A'BC'D' + A'BCD + AB'C'D' + AB'CD + ABC'D + ABCD'$$



$$Y = (A + B + C + D) (A + B + C + D')$$

$$(A + B + C' + D) (A + B' + C + D)$$

$$(A' + B + C + D) (A' + B' + C' + D')$$

$$Z = (A + B + C + D) (A + B' + C + D')$$

$$(A + B' + C' + D) (A' + B + C + D')$$

$$(A' + B + C' + D) (A' + B' + C + D)$$

$$(A' + B' + C' + D')$$


Q3

Design a circuit which will add a 4-bit binary number to a 5-bit binary number. Use five full adders. Assume negative numbers are represented in 2's complement. (Hint: How do you make a 4-bit binary number into a 5-bit binary number, without making a negative number positive or a positive number negative? Try writing

down the representation for -3 as a 3-bit 2's complement number, a 4-bit 2's complement number, and a 5-bit 2's complement number. Recall that one way to find the 2's complement of a binary number is to complement *all* bits to the left of the first 1.)

Sol 3

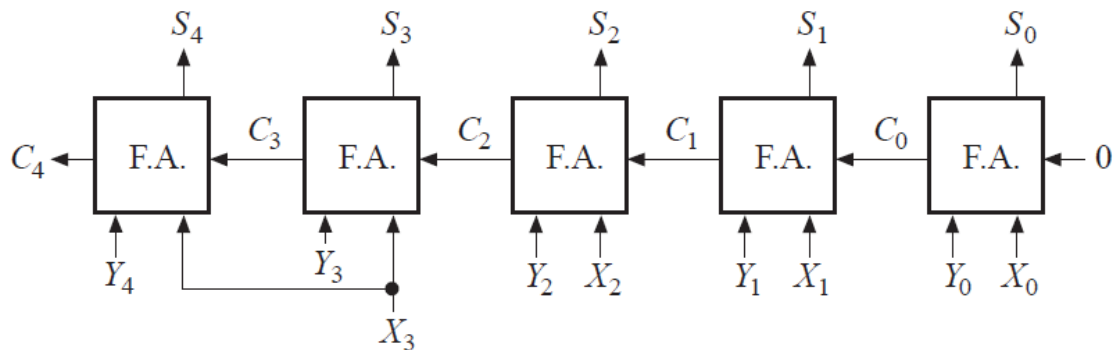Notice that the sign bit  $X_3$  of the 4-bit number is extended to the leftmost full adder as well.





Q4

- Write the switching function  $f(x, y) = x + y$  as a sum of minterms and as a product of maxterms.
- Consider the Boolean algebra of four elements  $\{0, 1, a, b\}$  specified by the following operation tables and the Boolean function  $f(x, y) = ax + by$  where  $a$  and  $b$  are two of the elements in the Boolean algebra. Write  $f(x, y)$  in a sum-of-minterms form.
- Write the Boolean function of part (b) in a product-of-maxterms form.
- Give a table of combinations for the Boolean function of Part (b). (*Note:* The table of combinations has 16 rows, not just 4.)
- Which four rows of the table of combinations completely specify the function of Part (b)? Verify your answer.

	'		+	0	1	a	b		•	0	1	a	b
0	1	0	0	0	1	a	b	0	0	0	0	0	0
1	0	1	1	1	1	1	1	1	1	0	1	a	b
a	b	a	a	a	1	a	1	a	a	0	a	a	0
b	a	b	b	b	1	1	b	b	0	b	0	b	b



Sol 4

(a)

$$f = x(y+y') + y(x+x') = xy + xy' + x'y$$

(sum-of-minterms)

$$f = x + y \text{ already in product-of-maxterms form}$$

(b)

$$\begin{aligned} f &= ax + by = ax(y+y') + by(x+x') \\ &= axy + axy' + bxy + bx'y = (a+b)xy + axy' + bx'y \\ &= xy + axy' + bx'y \end{aligned}$$

(c)

$$\begin{aligned} f' &= (a'+x')(b'+y') = (b+x')(a+y') \\ &= ab + ax' + by' + x'y' = ax'(y+y') + by'(x+x') + x'y' \\ &= ax'y + ax'y' + by'x + by'x' + x'y' \\ &= ax'y + by'x + x'y'(a+b+1) = ax'y + by'x + x'y' \text{ so} \end{aligned}$$

$$\begin{aligned} f &= (a'+x+y')(b'+x'+y)(x+y) \\ &= (b+x+y')(a+x'+y)(x+y) \end{aligned}$$

Alternatively,

$$\begin{aligned} f &= ax + by = (a+by)(x+by) = (a+b)(a+y)(x+b)(x+y) \\ &= (a+xx'+y)(b+yy'+x)(x+y) \\ &= (a+x+y)(a+x'+y)(b+x+y)(b+x+y')(x+y) \\ &= [(a+x+y)(b+x+y)(x+y)](a+x'+y)(b+x+y') \\ &= (ab+xx'+y)(a+x'+y)(b+x+y') \\ &= (x+y)(a+x'+y)(b+x+y') \end{aligned}$$



Faculty of Engineering

(d)		(e)	
$xy$	$f$	$xy$	$f$
00	0	a0	a
01	b	a1	1
0a	0	aa	a
0b	b	ab	1
10	a	b0	0
11	1	b1	b
1a	a	ba	0
1b	1	bb	b

f(x,y) is completely specified by the coefficients of the minterms in the sum of minterms expression. These coefficients are determined by the value of the function for  $xy = 00, 01, 10$  and  $11$ .