

Logic Design I – Laboratory 01 (Not ,AND, & OR gate) Gates (7804, 7408, & 7432)

#	Student ID	Student Name	Grade (10)	Instructor signature
1				
2				

Delivery Date	
---------------	--

Objective


- To get familiar with ED100 logic design evaluation and testing kit.
- To test and verify the behavior of not gate.

Theory Overview

The basic logic gates are the building blocks of more complex logic circuits.

These logic gates perform the basic Boolean functions, such as Inversion.

Fig. below shows the circuit symbol of not gate, the small circle on the output of the circuit symbols designates the logic complement.

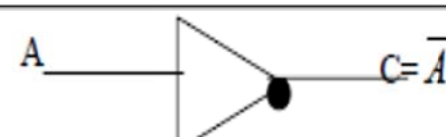GATE	SYMBOL	INPUTS		OUTPUT
		A	B	C
NOT IC 7404		1	-	0
		0	-	1

Digital IC gates are classified by family to which they belong.

Each logic family has its own basic electronic circuit upon which more complex digital circuits and functions are developed. The following logic families are the most frequently used;

TTL _Transistor-transistor logic

ECL _Emitter-coupled logic

MOS _Metal-oxide semiconductor


CMOS _Complementary metal-oxide semiconductor.

TTL and ECL are based upon bipolar transistors. TTL has a well-established popularity among logic families. ECL is used only in systems requiring high-speed operation. MOS and CMOS, are based on field effect transistors. They are widely used in large scale integrated circuits because of their high component density and relatively low power consumption. CMOS logic consumes far less power than MOS logic.


There are various commercial integrated circuit chips available. TTL ICs are usually distinguished by numerical designation as the 5400 and 7400 series.

Procedure

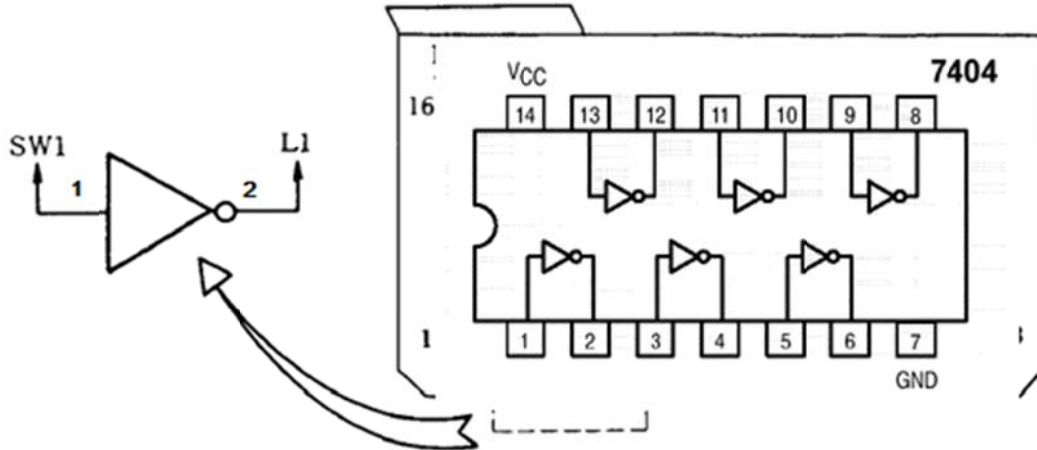1. Insert a NOT gate [TTL 7404 #4-T] into the logic lab breadboard
2. Construct the circuit as shown in Fig




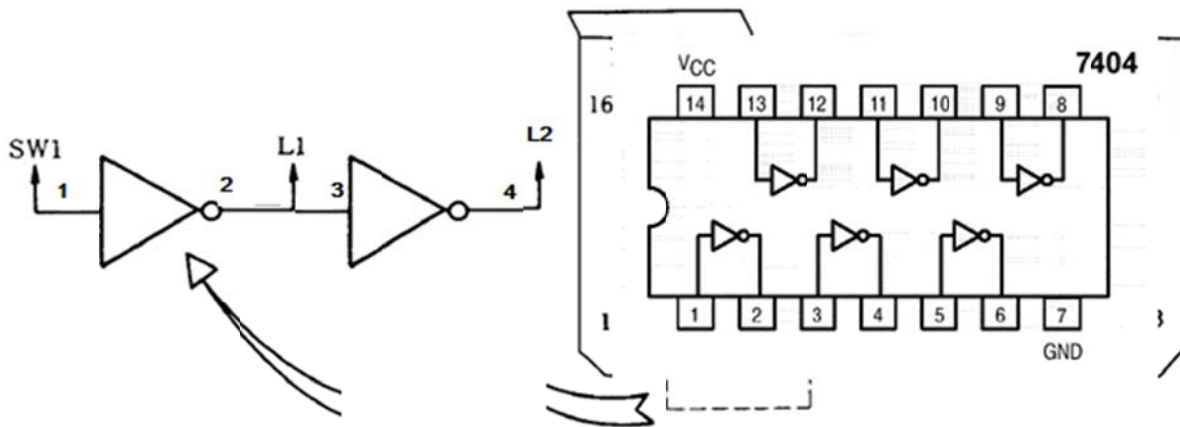3. Set data switch SW1. Record the level of the output L1
4. Connect the output of first not gate as input to the next not gate, connect output to L2, as shown in figure



5. Set data switch SW1. Record the level of the output L1, L2

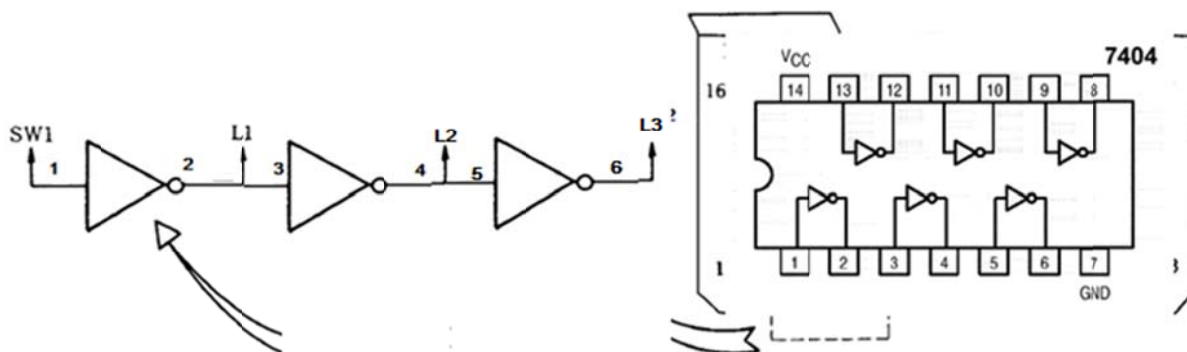6. Connect the output of 2nd not gate as input to the next not gate, connect output to L3, as shown in figure



5. Set data switch SW1. Record the level of the output L1, L2, L3

Results and data analysis

Single not gate

Input (SW1)	Output (L1)
1	
0	

Two cascaded not gate

Input (SW1)	Output (L1)	Output (L2)
1		
0		

Three cascaded not gate

Input (SW1)	Output (L1)	Output (L2)	Output (L3)
1			
0			

Questions and Conclusions

1. What is the minimum number of gates needed to build a repeater or interface to a new circuit stage (detect the input signal and generate new clean signal)?

.....

.....

.....

.....

.....

.....

2. In the two cascaded not gates, use voltmeter to measure the input voltage value and the final output voltage level? Is the output voltage level is the same as input voltage? Justify your answer?

Input (volt)	Final Output (volt)

.....

.....

.....

.....

.....


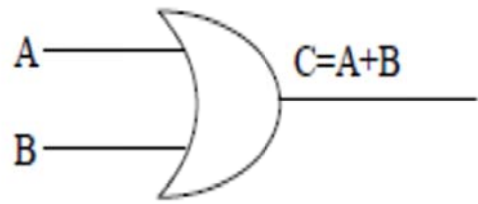
.....

Objective

To find the basic AND & OR gates concept and study on multiple inputs and propagation delay.

Theory Overview



The basic logic gates are the building blocks of more complex logic circuits. These logic gates perform the basic Boolean functions, such as AND, OR gates, Fig. below shows the circuit symbol, Boolean function, and truth table.

GATE	SYMBOL	INPUTS		OUTPUT
		A	B	C
AND IC 7408		0	0	0
		0	1	0
		1	0	0
		1	1	1
OR IC 7432		0	0	0
		0	1	1
		1	0	1
		1	1	1


AND gate

Procedure

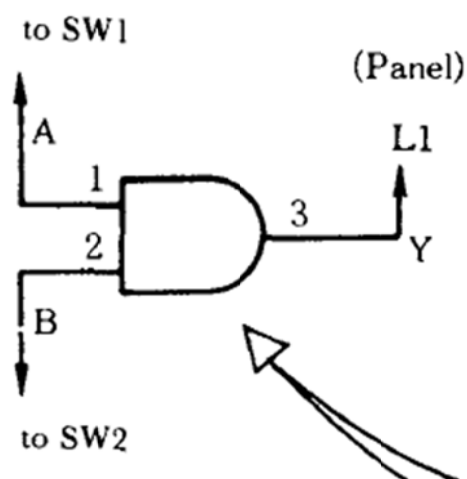 
1. Insert a AND gate [TTL 7408 #4-T] into the logic lab breadboard Construct the circuit as shown in Fig



 2. Set data switches (SW1, SW2) as shown in Table 1 and check the outputs (L1)
3. Construct the two level 3-input AND gate using 2-input AND gates



 4. The circuit can be represented symbolically as



5. Set data switches (SW1, SW2, SW3) as shown in Table 2 and check the outputs (L1, L2)

Results and data analysis

Table 01

Input1 (SW1)	Input2 (SW2)	Output (L1)



Table 02

Input1 (SW1)	Input2 (SW2)	Input3 (SW3)	Output1 (L1)	Output2 (L2)

OR gate


Procedure

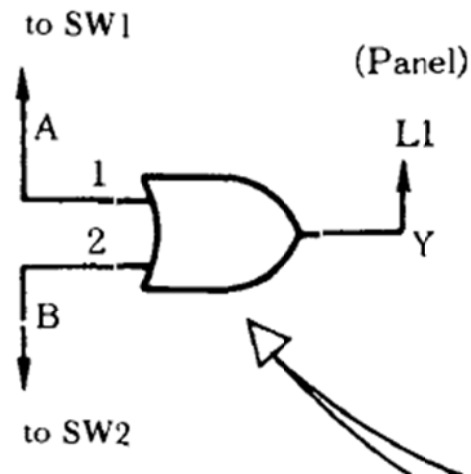 1. Insert a AND gate [TTL 7432 #4-T] into the logic lab breadboard Construct the circuit as shown in Fig




2. Set data switches (SW1, SW2) as shown in Table 3 and check the outputs (L1)

 3. Construct the two level 3-input AND gate using 2-input AND gates



 4. The circuit can be represented symbolically as



5. Set data switches (SW1, SW2, SW3) as shown in Table 2 and check the outputs (L4)

Results and data analysis

Table 03

Input1 (SW1)	Input2 (SW2)	Output (L1)

Table 04

Input1 (SW1)	Input2 (SW2)	Input3 (SW3)	Output1 (L1)	Output2 (L2)



كلية الهندسة

Faculty of Engineering



جامعة الأهرام الكندية
AHRAM CANADIAN UNIVERSITY