



Lecture (05)

Boolean Algebra 3

By:

Dr. Ahmed ElShafee

Dr. Ahmed ElShafee, ACU : Spring 2017, Logic Design I

Multiplying Out and Factoring Expressions (POS& SOP)

- Multiplying out

- $X(Y + Z) = XY + XZ$

- $(X + Y)(X + Z) = X + YZ$

$$\begin{aligned} (X + Y)(X + Z) &= XX + XZ + YX + YZ \\ &= X + XZ + XY + YZ \\ &= X + XY + YZ = X + YZ \end{aligned}$$

Operations with 0 and 1:

1. $X + 0 = X$
2. $X + 1 = 1$

- 1D. $X \cdot 1 = X$
- 2D. $X \cdot 0 = 0$

Idempotent laws:

3. $X + X = X$

- 3D. $X \cdot X = X$

Involution law:

4. $(X')' = X$

Laws of complementarity:

5. $X + X' = 1$

- 5D. $X \cdot X' = 0$

Commutative laws:

6. $X + Y = Y + X$

- 6D. $XY = YX$

Associative laws:

7. $(X + Y) + Z = X + (Y + Z)$
 $= X + Y + Z$

- 7D. $(XY)Z = X(YZ) = XYZ$

Distributive laws:

8. $X(Y + Z) = XY + XZ$

- 8D. $X + YZ = (X + Y)(X + Z)$

DeMorgan's laws:

9. $(X + Y)' = X'Y'$

- 9D. $(XY)' = X' + Y'$

absorption

$$x + xy = x$$

$$(b) \quad x(x + y) = x$$

- $(X + Y)(X' + Z) = XZ + X'Y$

$$= XX' + XZ + YX' + YZ$$

$$= 0 + XZ + X'Y + YZ$$

$$= XZ + X'Y + (X + X')YZ$$

$$= XZ + X'Y + XYZ + X'YZ$$

$$= XZ(1 + Y) + X'Y(1 + Z)$$

$$= XZ + X'Y$$

Operations with 0 and 1:

1. $X + 0 = X$

2. $X + 1 = 1$

1D. $X \cdot 1 = X$

2D. $X \cdot 0 = 0$

Idempotent laws:

3. $X + X = X$

3D. $X \cdot X = X$

Involution law:

4. $(X')' = X$

Laws of complementarity:

5. $X + X' = 1$

5D. $X \cdot X' = 0$

Commutative laws:

6. $X + Y = Y + X$

6D. $XY = YX$

Associative laws:

7. $(X + Y) + Z = X + (Y + Z)$
 $= X + Y + Z$

7D. $(XY)Z = X(YZ) = XYZ$

Distributive laws:

8. $X(Y + Z) = XY + XZ$

8D. $X + YZ = (X + Y)(X + Z)$

DeMorgan's laws:

9. $(X + Y)' = X'Y'$

9D. $(XY)' = X' + Y'$

absorption

$x + xy = x$

(b) $x(x + y) = x$

- **Factoring (rules from multiplying out)**

- $XY + XZ = X(Y + Z)$

- $X + YZ = (X + Y)(X + Z)$

- $XZ + X'Y = (X + Y)(X' + Z)$

Example 01

Multiplying out (POS => SOP)

$$(A+B+C')(A+B+D)(A+B+E)(A+D'+E)(A'+C)$$

o

Dr. Ahmed ElShafee, ACU : Spring 2017, Logic Design I

$$X + YZ = (X + Y)(X + Z)$$

$$XZ + X'Y = (X + Y)(X' + Z)$$

$$(A+B+C')(A+B+D)(A+B+E)(A+D'+E)(A'+C)$$

$$\underbrace{(A+B+C')}_{A+B \rightarrow X, C' \rightarrow Y, E \rightarrow Z; 1^{st} \text{ law}} \underbrace{(A+B+D)}_{A \rightarrow X, D'+E \rightarrow Y, C \rightarrow Z; 1^{st} \text{ law}} \underbrace{(A+B+E)}_{A+B \rightarrow X, C'D \rightarrow Y, E \rightarrow Y; 1^{st} \text{ law}} \underbrace{(A+D'+E)}_{A \rightarrow X, D'+E \rightarrow Y, C \rightarrow Z; 1^{st} \text{ law}} \underbrace{(A'+C)}$$

$$= (A+B+C'D)(A+B+E)[AC+A'(D'+E)]$$

$A+B \rightarrow X, C'D \rightarrow Y, E \rightarrow Y; 1^{st} \text{ law}$
Distributive law

$$= (A+B+C'DE)(AC+A'D'+A'E)$$

Distributive law

$$= AAC + \cancel{AA'D'} + \cancel{AA'E} + ABC + A'BD' + A'BE +$$

$$\cancel{ACC'DE} + \cancel{A'C'DD'E} + A'C'DEE$$

$$= AC + \cancel{ABC} + A'BD' + A'BE + A'C'DE$$

7

Dr. Ahmed ElShafee, ACU : Spring 2017, Logic Design I

Example 02

Factoring (SOP => POS)

$$AC + A'BD' + A'BE + A'C'DE$$

Y

Dr. Ahmed ElShafee, ACU : Spring 2017, Logic Design I

$$X + YZ = (X + Y)(X + Z)$$

$$XZ + X'Y = (X + Y)(X' + Z)$$

$$AC + A'BD' + A'BE + A'C'DE$$

A' common factor

$$= \underbrace{AC}_{XZ} + \underbrace{A'(BD' + BE + C'DE)}_{X'Y}$$

A → X, (BD' + BE + C'DE) → Y, C → Z; 2nd law

$$= (A + BD' + BE + C'DE)(A' + C)$$

$$= \underbrace{[A + C'DE + B(D' + E)]}_{XY} (A' + C)$$

A + C'DE → X, (B) → Y, (D' + E) → Z; 1st law

$$= (A + B + C'DE)(A + C'DE + D' + E)(A' + C)$$

$$= (A + B + C')(A + B + D)(A + B + E)(A + D' + E + C')(A + D' + E + D)(A + D' + E + E)(A' + C)$$


$$= (A + B + C')(A + B + D)(A + B + E)(A + D' + E)(A' + C)$$

Exclusive-OR

Exclusive-OR: $0 \oplus 0 = 0$ $0 \oplus 1 = 1$
 $1 \oplus 0 = 1$ $1 \oplus 1 = 0$

Truth table and gate for $X \oplus Y$

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

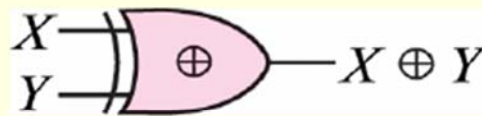

$X \oplus Y = 1$ if and only if $X=1$ or $Y=1$ and X and Y are not both 1.

9

Dr. Ahmed ElShafee, ACU : Spring 2017, Logic Design I

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- $X \oplus Y = X'Y + XY'$
- Theorems apply to *exclusive OR*:

$$X \oplus 0 = X$$

$$X \oplus 1 = X'$$

$$X \oplus X = 0$$

$$X \oplus X' = 1$$

$$X \oplus Y = Y \oplus X \text{ (commutative law)}$$

$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z \text{ (associative law)}$$

$$X(Y \oplus Z) = XY \oplus XZ \text{ (distributive law)}$$

$$(X \oplus Y)' = X \oplus Y' = X' \oplus Y = XY + X'Y' \text{ D'emorgans}$$

- Proof of the distributive law

$$X(Y \oplus Z) = XY \oplus XZ$$

Proof:

$$\begin{aligned} XY \oplus XZ &= XY(XZ)' + (XY)'XZ = XY(X' + Z') + (X' + Y')XZ \\ &= XYZ' + XY'Z \\ &= X(YZ' + Y'Z) = X(Y \oplus Z) \end{aligned}$$

Equivalence


- The equivalence operation(\equiv) is defined by

$$(0 \equiv 0) = 1 \quad (0 \equiv 1) = 0$$

$$(1 \equiv 0) = 0 \quad (1 \equiv 1) = 1$$

- The truth table for $X \equiv Y$ is

X	Y	$X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

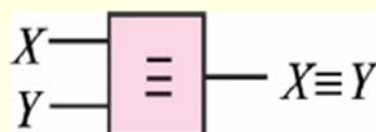

- ◆ $(X \equiv Y) = 1$ if and only if $X = Y$.


- $(X \equiv Y) = XY + X'Y'$

Equivalence is the **complement** of *exclusive-OR*:

$$(X \oplus Y)' = (X'Y + XY')' = (X + Y')(X' + Y)$$

$$= XY + X'Y' = (X \equiv Y)$$

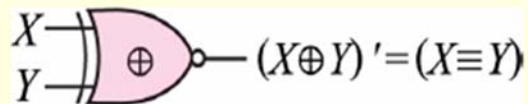- Alternate symbol for the equivalence gate



The equivalence gate is also called an **exclusive-NOR** gate.

Example 03

- Find SOP $A' \oplus B \oplus C$:

$$\begin{aligned}
 \bullet \quad A' \oplus B \oplus C &= [A'B' + (A')'B] \oplus C \\
 &= (A'B' + AB)C' + (A'B' + AB)'C \\
 &= (A'B' + AB)C' + (A'B + AB')C \\
 &= A'B'C' + ABC' + A'BC + AB'C
 \end{aligned}$$

Xor
comple
ment -
.equiv

Conversion of Sentences to Boolean Equation

- The *three main steps* in designing a **single output combinational switching circuit** are:
 1. Find a switching function which specifies the desired behavior of the circuit.
 2. Find a simplified algebraic expression for the function.
 3. Realize the simplified function using available logic elements.

Example 08

- Translate sentences into Boolean equation
- *“Mary watches TV if it is Monday night and she has finished her homework.”*

-
- *“Mary watches TV if it is Monday night and she has finished her homework.”*
 - Define two-valued variables:
 - **F=1** if *“Mary watches TV”* is true; otherwise, **F=0**.
 - **A=1** if *“it is Monday night”* is true; otherwise **A=0**.
 - **B=1** if *“she has finished her homework”* is true; otherwise **B=0**.
 - **F=A.B**, **F** is true if **A** and **B** are both true.

Example 09

An alarm circuit is to be designed which operates as follows:

The alarm will ring if and only if the alarm switch is on and the door is not closed or it is after 6 P.M. and the window is not closed.

١٩


Dr. Ahmed ElShafee, ACU : Spring 2017, Logic Design I

An alarm circuit is to be designed which operates as follows:

The alarm will ring if and only if the alarm switch is on and the door is not closed or it is after 6 P.M. and the window is not closed.

$$Z = AB' + CD'$$

$$Z = A(B' + CD')$$

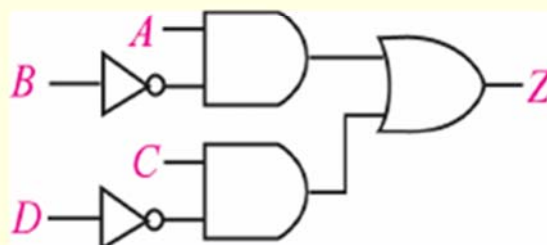

٢٠


Example 10

Design a switching circuit with three inputs A , B , and C and one output f . The input A, B , and C represent the *first*, *second*, and *third* bits, respectively, for a binary number N . $f=1$ if $N \geq 011_2$ and $f=0$ if $N < 011_2$.

٢١

Dr. Ahmed ElShafee, ACU : Spring 2017, Logic Design I

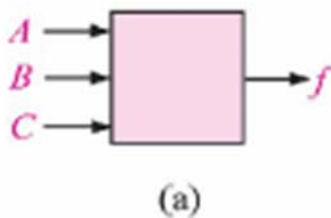- N . $f=1$ if $N \geq 011_2$ and $f=0$ if $N < 011_2$.



A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

(b)

٢٢

Dr. Ahmed ElShafee, ACU : Spring 2017, Logic Design I


<i>A</i>	<i>B</i>	<i>C</i>	<i>f</i>	<i>f'</i>
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Derive an algebraic expression for f from the truth table by using the combinations of values of $A, B,$ and C for which $f=1$.

$$f = A'BC + AB'C' + AB'C + ABC' + ABC$$

$$= A'BC + AB' + AB = A'BC + A = A + BC$$

The circuit is

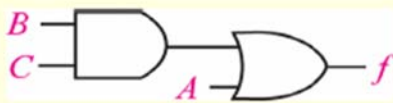

First write f' as a sum of products, and then complement the result. f' is 1 for input combinations $ABC=000, 001, 010,$ so

$$f' = A'B'C' + A'B'C + A'BC'$$

$$f = (f')' = (A'B'C' + A'B'C + A'BC')'$$

$$= (A + B + C)(A + B + C')(A + B' + C)$$

(Three 3 - input OR gates and one 3 - input AND gate)

$$= (A + B)(A + B' + C) \quad \text{[Two OR gates and one AND gate]}$$

$$= A + BC$$



Thanks,..
See you next week (ISA),...

Dr. Ahmed ElShafee, ACU : Spring 2017, Logic Design I