



# Lecture (07)

## AC photocell, 0-9 BCD counter




By:

Dr. Ahmed ElShafee


Dr. Ahmed ElShafee, ACU : Spring 2017, Practical App EE

II

### photo cell

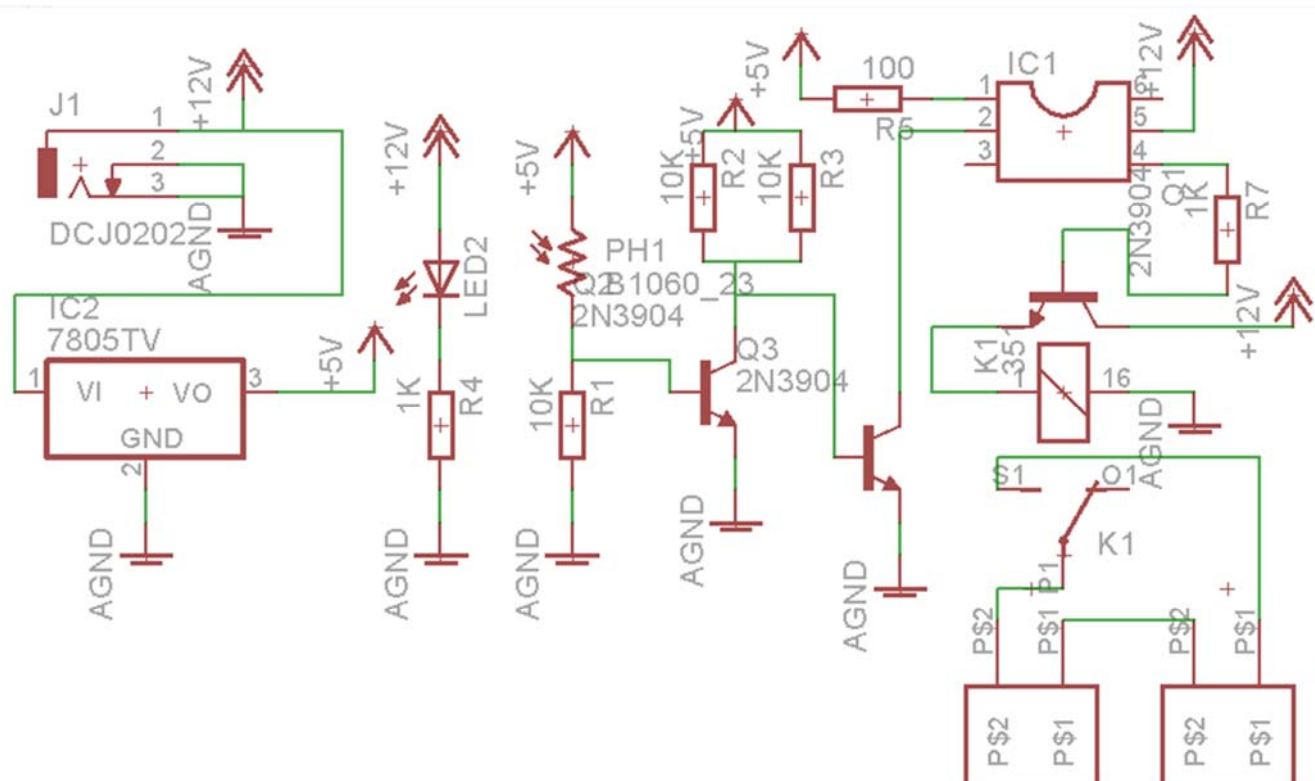

# 0-9 BCD counter

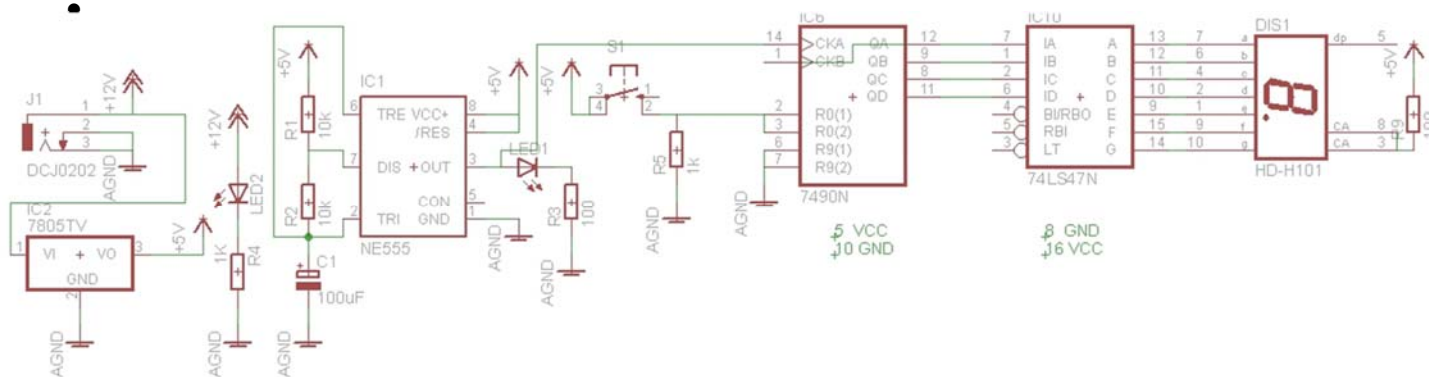

٣

Dr. Ahmed ElShafee, ACU : Spring 2017, Practical App EE II

Thanks,..

See you next week (ISA),...

Dr. Ahmed ElShafee, ACU : Spring 2017, Practical App EE II