



Lecture (03.01)
**Digital DC lamp
dimmer (design)**
**PCB design with eagle
(astable)**




By:


Dr. Ahmed ElShafee

Dr. Ahmed ElShafee, ACU : Spring 2017, Practical App EE
IV

Digital DC lamp dimmer (5 switches)

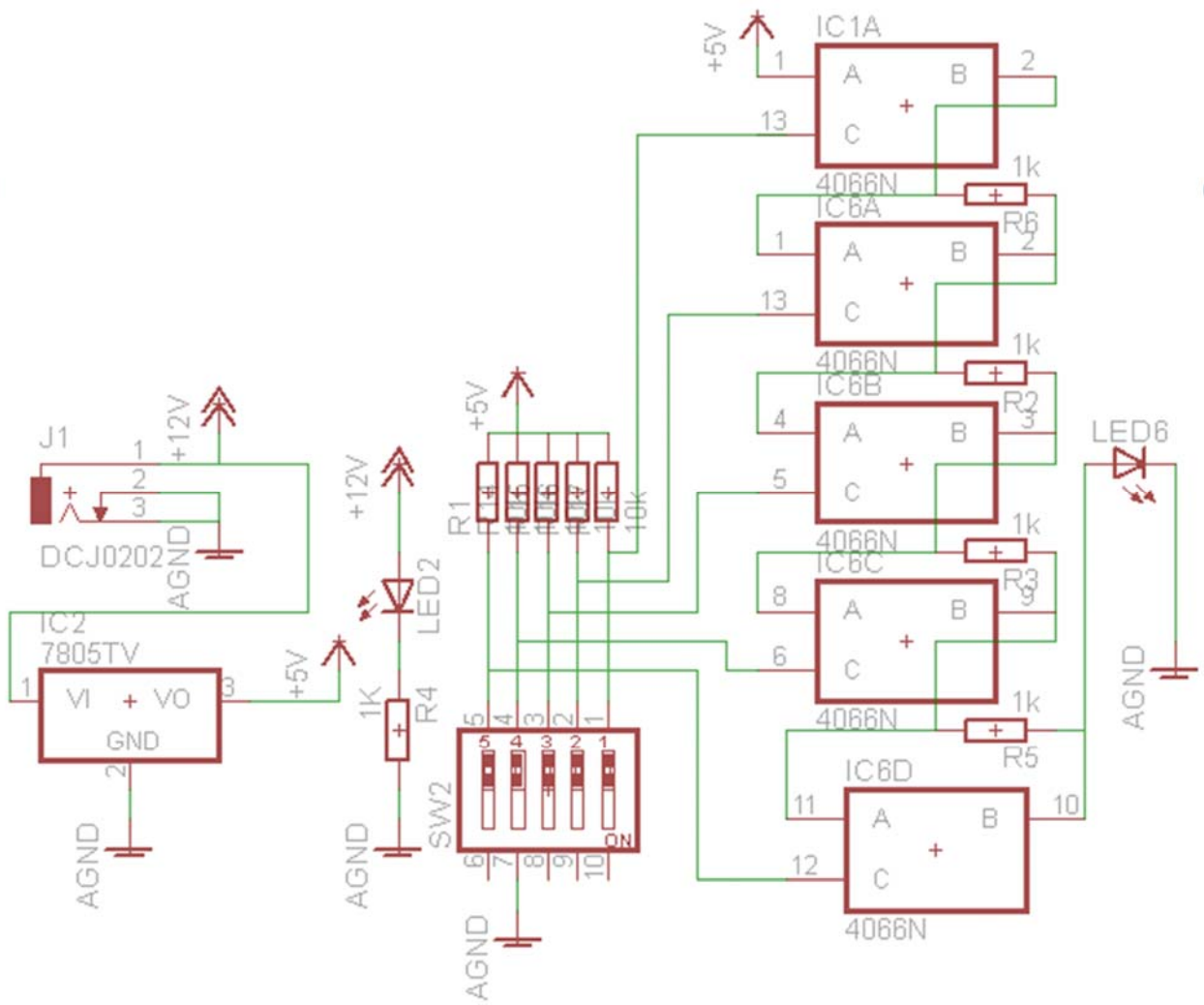

AStable PCB

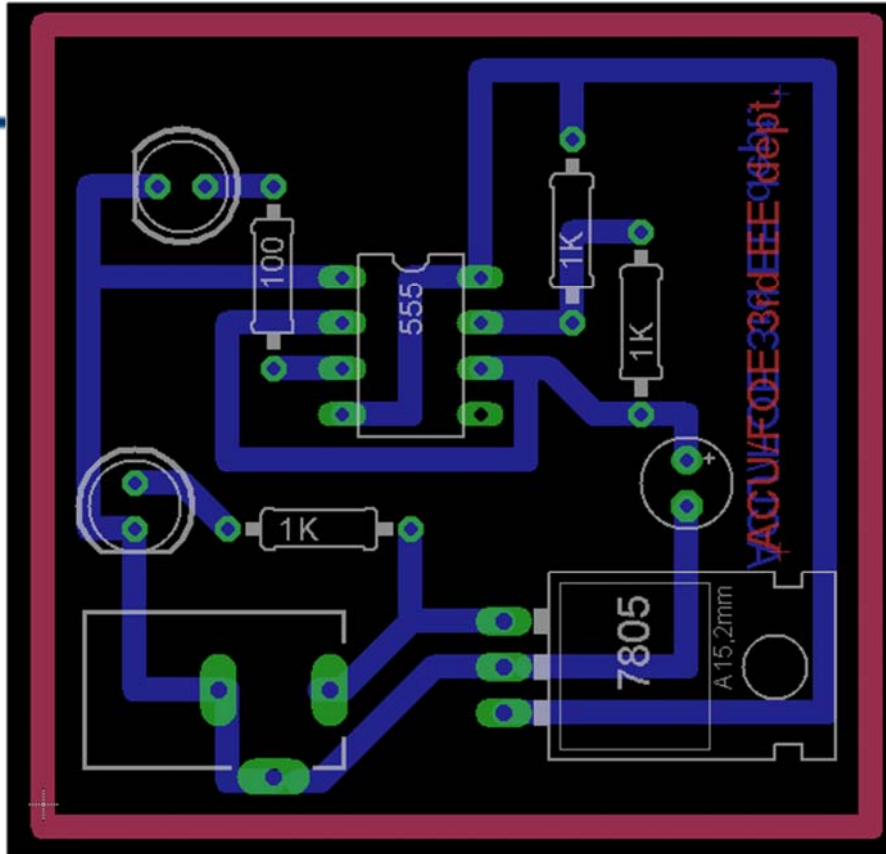

Dr. Ahmed ElShafee, ACU : Spring 2017, Practical App EE IV

Thanks,..
See you next week (ISA),...

Dr. Ahmed ElShafee, ACU : Spring 2017, Practical App EE IV