



# Lecture (01) Multi-Level Gate Circuits



By:

**Dr. Ahmed ElShafee**

Dr. Ahmed ElShafee, ACU : Spring 2018, CSE303 Logic design II

## Multi-Level Gate Circuits

- In this lecture, we will use the following terminology:
  1. *AND-OR circuit* means a two-level circuit composed of a level of AND gates followed by an OR gate at the output.
  - **Sum-of-products(SOP):  $AB'+ACD+ABC'$  .....**
  2. *OR-AND circuit* means a two-level circuit composed of a level of OR gates followed by an AND gate at the output.
  - **Product-of-sums(POS):  $(A+B')(A+C+D)(A+B+C')$  .....**
  3. *OR-AND-OR circuit* means a three-level circuit composed of a level of OR gates followed by a level of AND gates followed by an OR gate at the output.
  4. Circuit of AND and OR gates implies no particular ordering of the gates; the output gate may be either AND or OR.

- What's the concerned issues from a logic designers:

1. Number of gates


2. Gate inputs

3. Level of a circuit


- a. Cascaded circuit will increase the **gate-delay**
- b. and also the cost.
- c. gate-delay will slow down the operation of a digital system
 
## Tree Diagrams

- Each node on a tree diagram represents a gate, and the number of gate inputs is written beside each node.



$$Z = (AB + C)(D + E + FG) + H$$

 


4 level, 6 gates, 13 gate inputs

Dr. Ahmed ElShafee, ACU : Spring 2018, CSE303 Logic design II

$$Z = (AB + C)(D + E + FG) + H$$
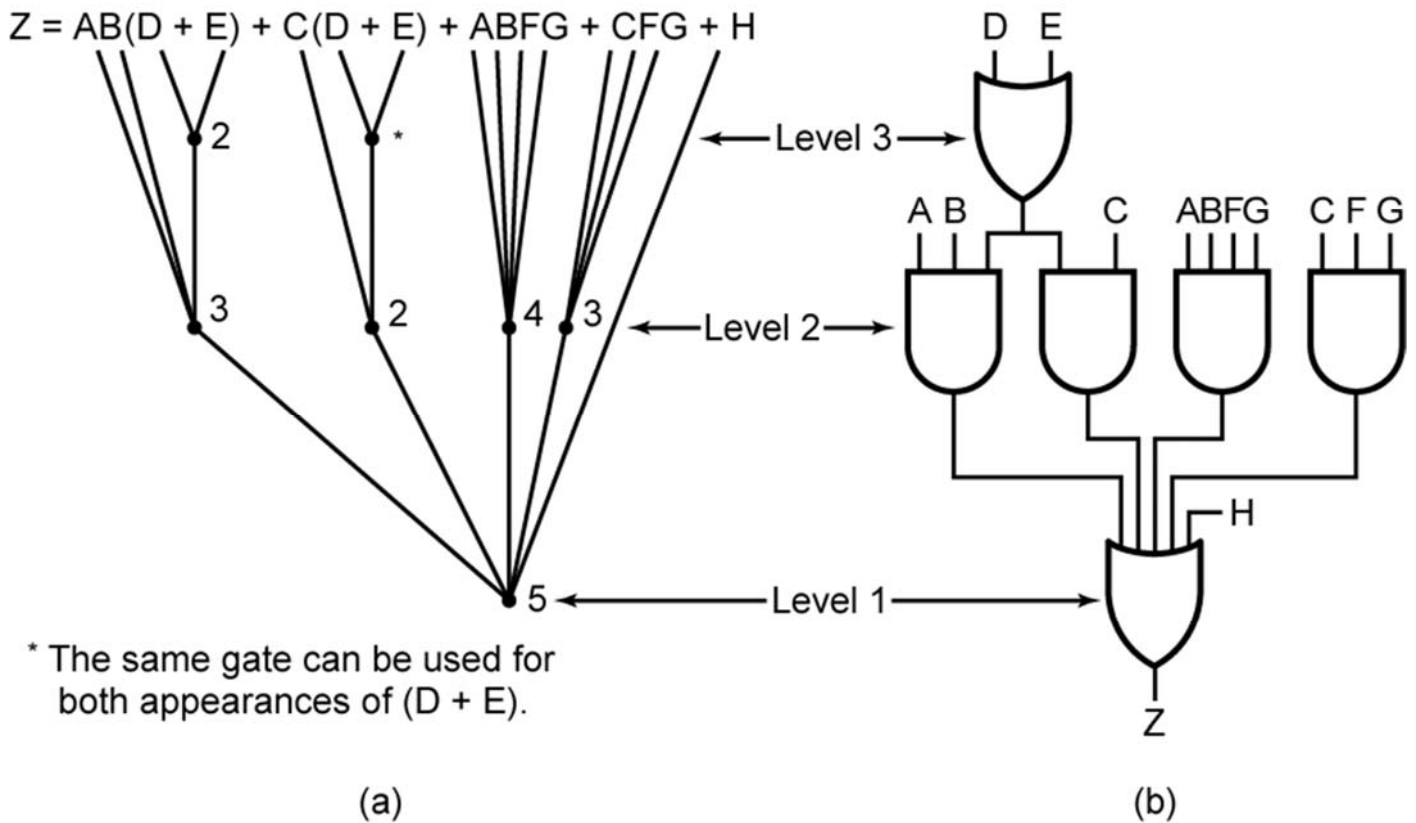
$$Z = AB(D + E) + C(D + E) + ABFG + CFG + H$$



\* The same gate can be used for both appearances of (D + E).

3 level, 6 gates, 19 gate inputs

# Example

Find a circuit of AND and OR gates to realize

$$f(a, b, c, d) = \sum m(1, 5, 6, 10, 13, 14)$$

Consider solutions with two levels of gates and three levels of gates. Try to **minimize the number of gates** and **the total number of gate inputs**. Assume that all variables and their complements are available as inputs.

Y

Dr. Ahmed ElShafee, ACU : Spring 2018, CSE303 Logic design II

OR gate at the output

$$f(a, b, c, d) = \sum m(1, 5, 6, 10, 13, 14)$$

- First, simplify  $f$  by using a **Karnaugh map**.

	ab			
cd	00	01	11	10
00	0	0	0	0
01	1	1	1	0
11	0	0	0	0
10	0	1	1	1

$$f = a'c'd + bc'd + bcd' + acd'$$


A

Dr. Ahmed ElShafee, ACU :

$$f = a'c'd + bc'd + bcd' + acd'$$

•

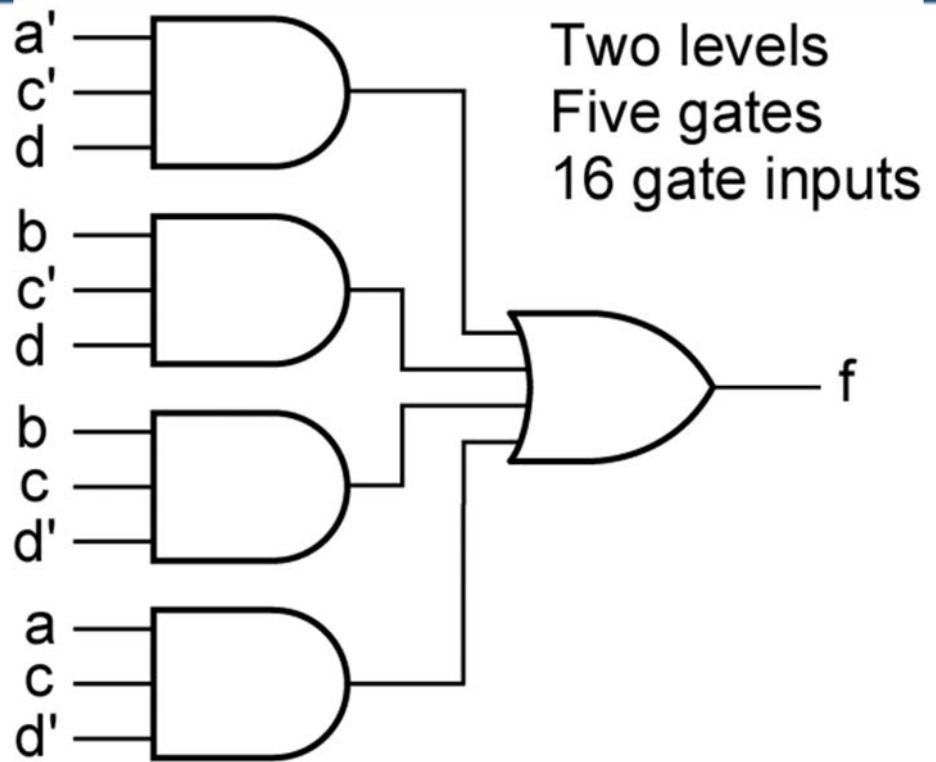This leads directly to a two-level AND-OR gate circuit.




9

$$f = a'c'd + bc'd + bcd' + acd'$$

Factoring yields

$$f = c'd(a' + b) + cd(a + b)$$

•

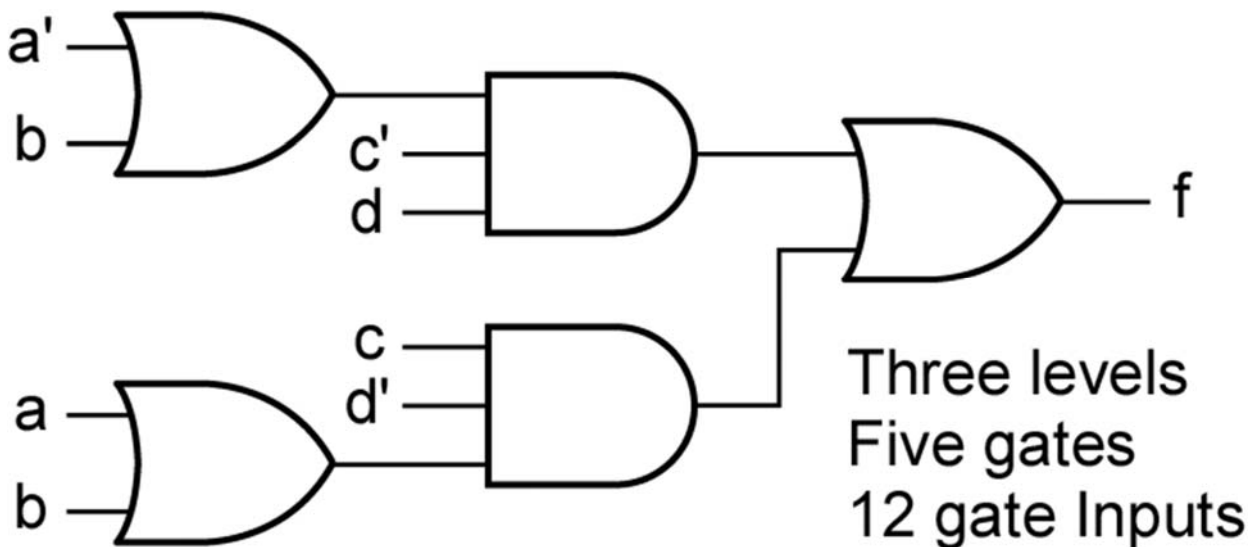

10

## AND gate at the output

- Both of these solutions have an **OR gate at the output**. A solution with an **AND gate at the output** might have fewer gates or gate inputs. A two-level OR-AND circuit corresponds to a product-of-sums expression for the function. This can be obtained from the 0's on the Karnaugh map as follows:


$$f = (c + d)(a' + b + c)(c' + d')(a + b + c)$$

leads directly to a two-level OR-AND circuit

		ab			
		00	01	11	10
cd	00	0	0	0	0
	01	1	1	1	0
	11	0	0	0	0
	10	0	1	1	1

11

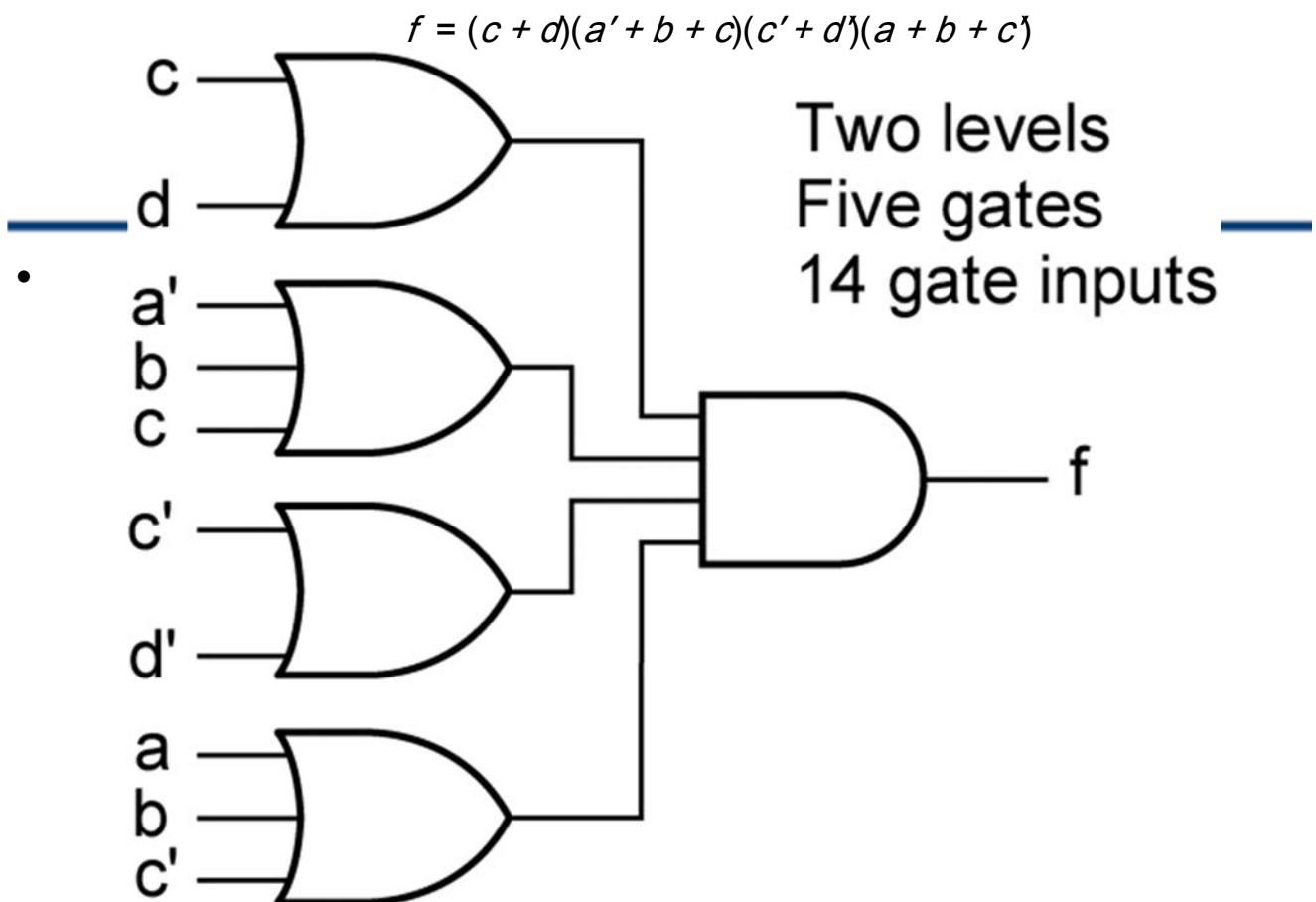Dr. Ahmed ElShafee, ACU : Spring 2018, CS



12

Dr. Ahmed ElShafee, ACU : Spring 2018, CSE303 Logic design II

$$f = (c + d)(a' + b + c)(c' + d')(a + b + c)$$

To get a three-level circuit with an AND gate output, we partially multiply out Equation using  $(X + Y)(X + Z) = X + YZ$ .

$$f = (c + d)(a' + b + c)(c' + d')(a + b + c)$$


$$f = [c + d(a' + b)][c' + d(a + b)]$$

Equation would **require four levels of gates to realize**; however, if we multiply out  $d'(a + b)$  and  $d(a' + b)$ , we get


$$f = (c + a'd + bd)(c' + ad' + bd')$$

which leads directly to a **three-level AND-OR-AND circuit**.


$$f = (c + a'd + bd)(c' + ad' + bd')$$

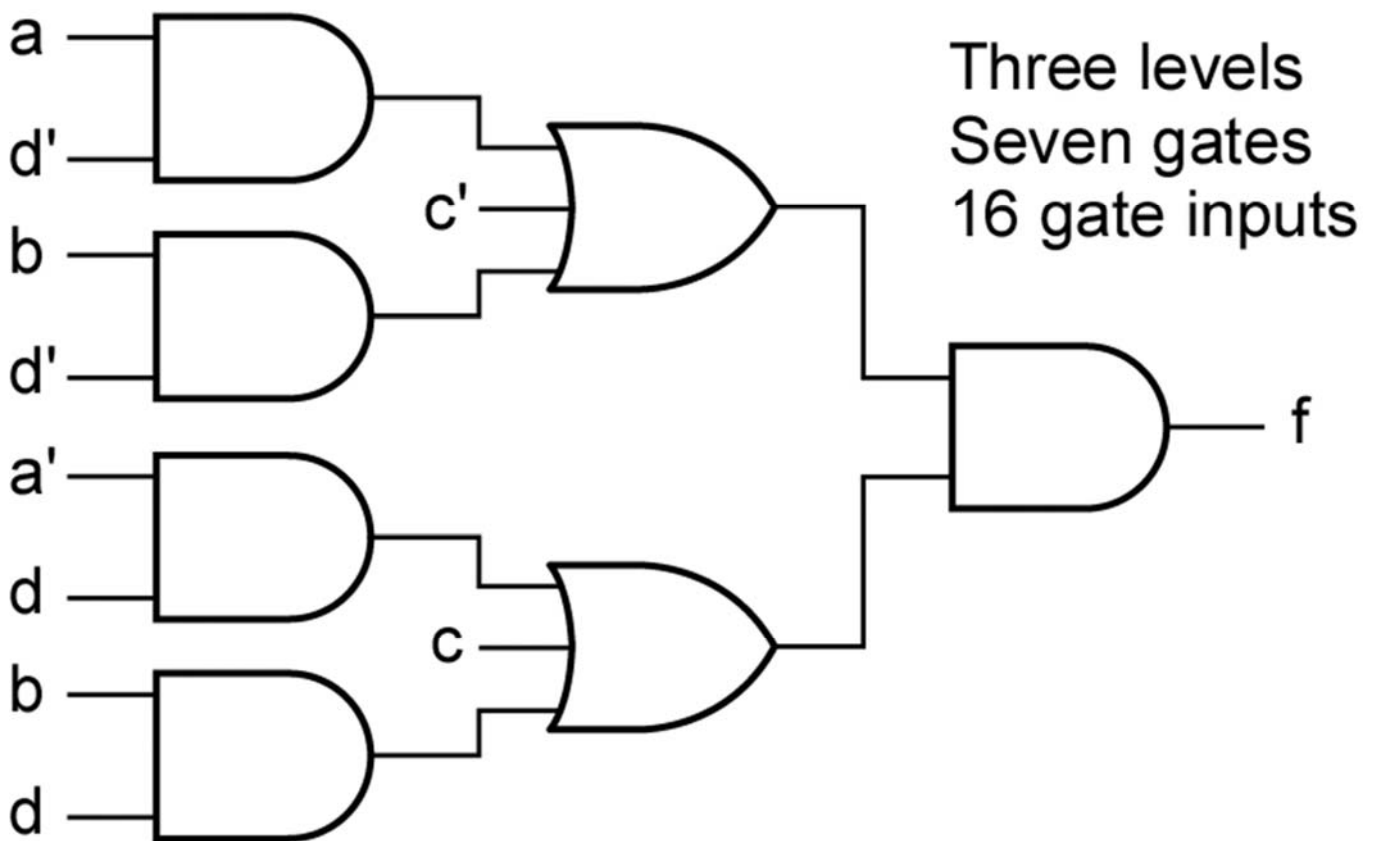


$$f = a'c'd + bc'd + bcd' + acd'$$

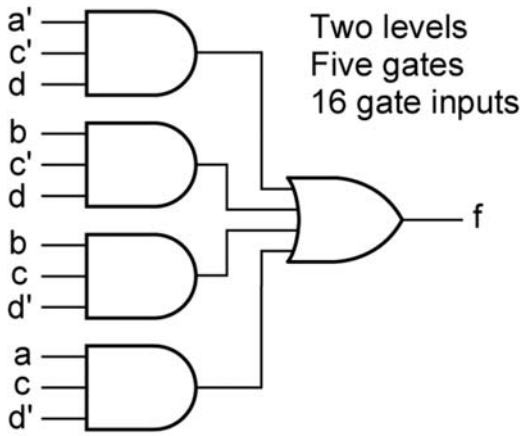


$$f = c'd(a' + b) + cd(a + b)$$

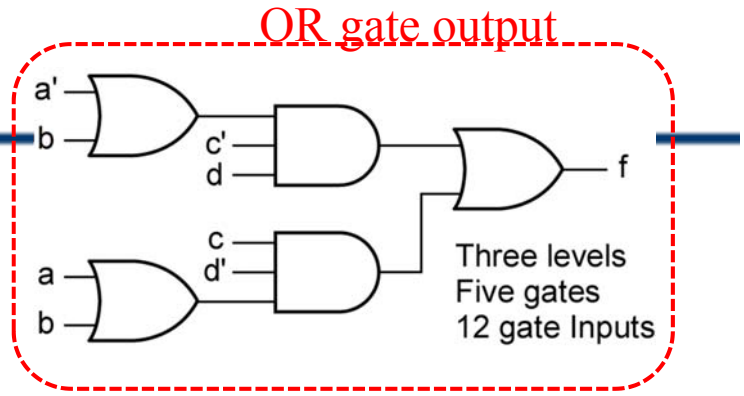
 
$$f = (c + d)(a' + b + c)(c' + d')(a + b + c)$$





$$f = (c + a'd + bd)(c' + ad' + bd')$$

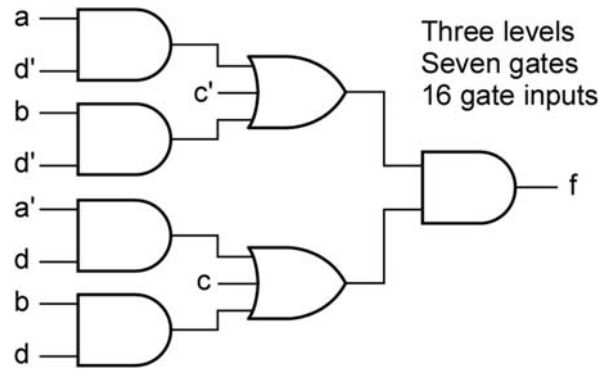

ACU : Spring 2018, CSE303 Logic design II

  ' For this particular example, the best two-level solution had an AND gate at the output, and the best three-level solution had an OR gate at the output. **In general, to be sure of obtaining a minimum solution, one must find both the circuit with the AND-gate output and the one with the OR-gate output.**







Thanks,..

Dr. Ahmed ElShafee, ACU : Spring 2018, CSE303 Logic  
design II