

CSE303 Logic Design II – Tutorial 02


#	Student ID	Student Name	Grade (10)
-			

Q1

7.22 A combinational switching circuit has four inputs and one output as shown. $F = 0$ iff three or four of the inputs are 1.

(a) Write the maxterm expansion for F .

(b) Using AND and OR gates, find a minimum three-level circuit to realize F (5 gates, 12 inputs).


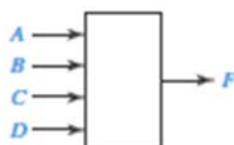


Sol 1

(a) F is 0 if any 3 (or 4) of the inputs are 1 so

$$F = (A + B' + C' + D')(A' + B' + C + D) \\ (A' + B' + C' + D)(A' + B' + C + D) \\ (A' + B + C' + D) \\ = (A' + B' + C')(A' + B' + D)(A' + C' + D) \\ (B' + C' + D)$$

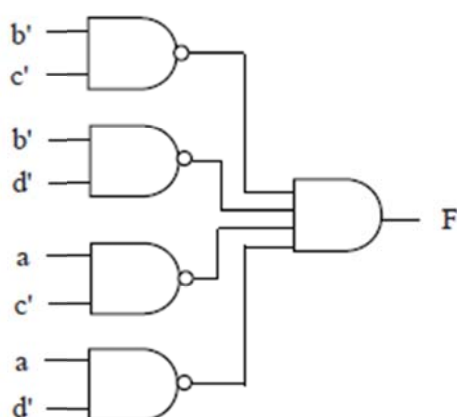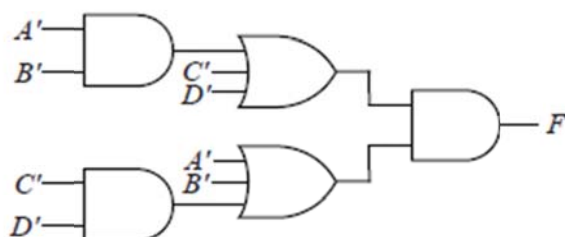(b) $F = (A' + B' + C'D')(A'B' + C' + D)$ or
 $F = (A' + C' + B'D)(A'C' + B' + D)$



Q2


7.35 Realize the following functions, using only two-input NAND gates. Repeat using only two-input NOR gates.

(a) $F = A'BC' + BD + AC + B'CD'$

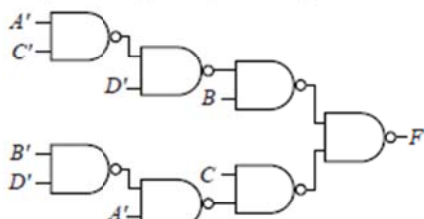(b) $F = A'CD + AB'C'D + ABD' + BC$

Sol 2

$F = A'BC' + BD + AC + B'CD'$
 $= B(D + A'C) + C(A + B'D)$




CD \ AB	00	01	11	10
00	0	1	0	0
01	0	1	1	0
11	0	1	1	1
10	1	0	1	1

Many NOR solutions exist. Here is one.


$F = (B + C)(A' + C + D)(A + B + D')(A + B' + C' + D)$
 $= (B + C)[A + (B + D')(B' + C' + D)](A' + C + D)$
 $= (B + C)[A(C + D) + A'(B + D')(B' + C' + D)]$
 $= (B + C)[A(C + D) + A'(B(C' + D) + B'D')]$

CD \ AB	00	01	11	10
00	0	1	0	0
01	0	1	1	0
11	0	1	1	1
10	1	0	1	1

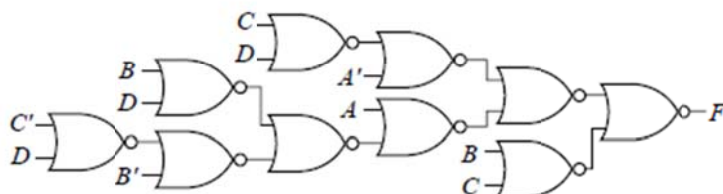


CD \ AB	00	01	11	10
00	0	0	1	0
01	0	0	0	1
11	1	1	1	0
10	0	1	1	0

$F = A'CD + BC + AB'C'D + ABD'$

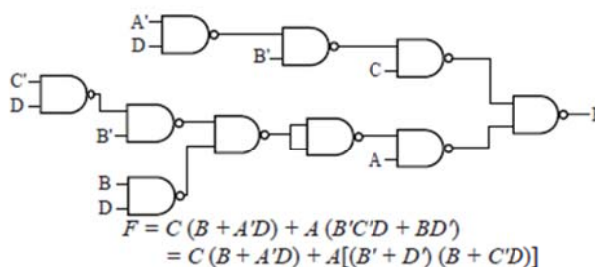


CD \ AB	00	01	11	10
00	0	0	1	0
01	0	0	0	1
11	1	1	1	0
10	0	1	1	0

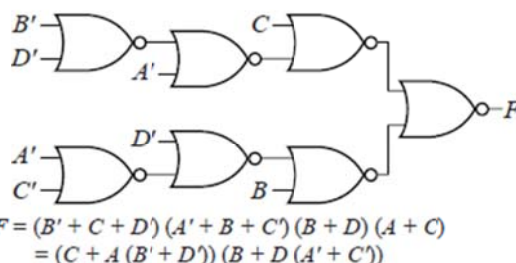$F = (A + C)(B + D)(A' + B + C')(B' + C + D)$




Q3

- 7.24 (a) Use gate equivalences to convert the circuit into a four-level circuit containing only NAND gates and a minimum number of inverters. (Assume the inputs are available only in uncomplemented form.)
 (b) Derive a minimum SOP expression for f .
 (c) By manipulating the expression for f , find a three-level circuit containing only five NAND gates and inverters.

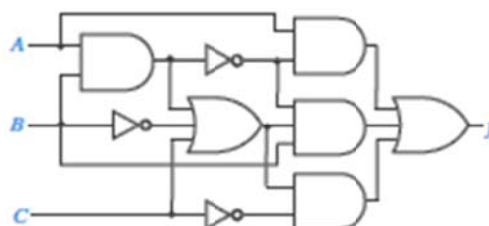

Sol 3

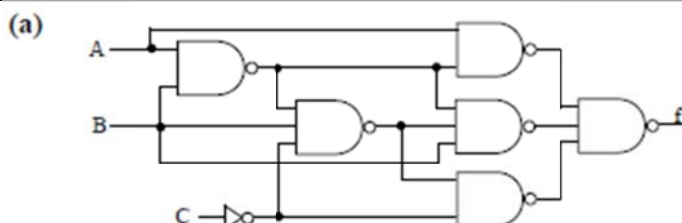

(b)
$$f = A(AB)' + (AB)[AB + B' + C]B + [AB + B' + C]C'$$

$$= AB' + (A' + B')[AB + BC] + AC' + B'C'$$

$$= AB' + A'BC + AC' + B'C'$$

(c)
$$f = A(B' + C') + A'BC + B'C'$$

