




Lecture (03)

Dr. Ahmed ElShafee

Dr. Ahmed ElShafee, ACU Summer 2016, Practical App. CS II


Connecting led

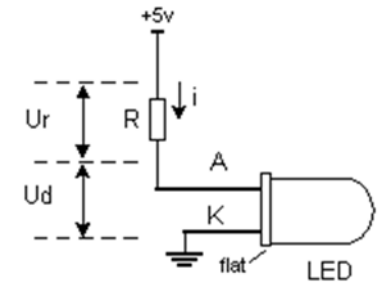- Two types based on its diameter, which is usually 3 or 5 mm
- working current which is usually about 10mA
- current-limiting resistor must be the correct value so that the LED is not damaged or burn out (overheated).
- The voltage drop will range from 1.2v to 1.6v depending on the color of the LED.




Dr. Ahmed ElShafee, ACU
Spring 2014, Practical
Applications CS II

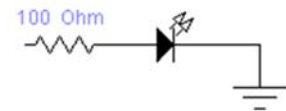- LEDs are connected to a microcontroller in two ways.
- One is to switch them on with logic zero, and other to switch them on with logic one.
- The first is called NEGATIVE logic and the other is called POSITIVE logic.
- The optimum value for limiting resistor is 330Ω, 220 Ω or 100Ω




Active high led indicator

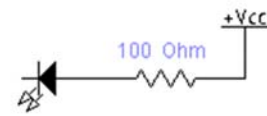


Active Low led indicator

Dr. Ahmed ElShafee, ACU
Spring 2014, Practical
Applications CS II

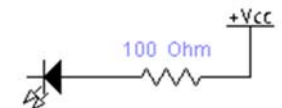- Calculating limiting resistor value
- optimum LED forward voltage is 1.6V (data sheet)
 $V_f=1.6V$
- The total voltage applied to both LED and limiting resistor is 5V
- Then the voltage drop over limiting resistor is
 $V_r = V_{cc} - V_f = 5 - 1.6 = 3.4$ volt
- Optimal led current is 25mA (data sheet)
 $I = 25$ mA
 $R = V_r/I = 3.4/(25*10^{-3}) = 136$ ohm




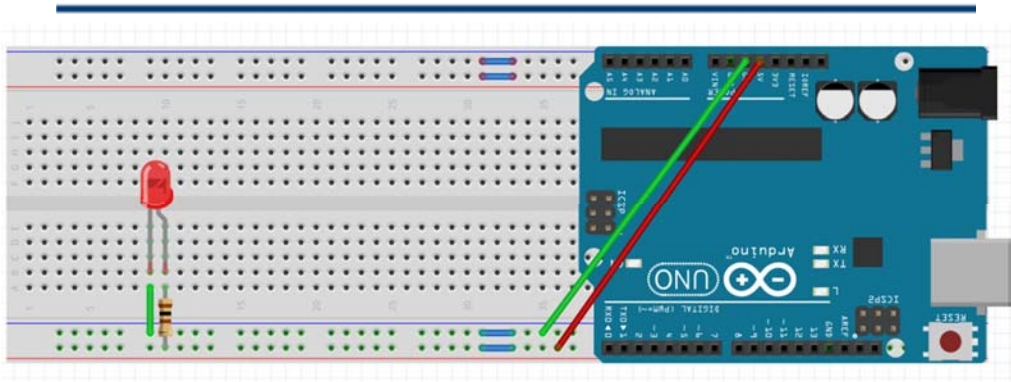Dr. Ahmed ElShafee, ACU
Spring 2014, Practical
Applications CS II



Dr. Ahmed EIShafee, ACU Summer 2016, Practical App. CS II

Resistor color code

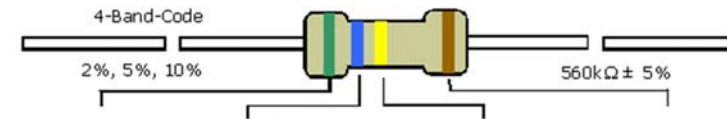

COLOR	1st BAND	2nd BAND	3rd BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1Ω	
Brown	1	1	1	10Ω	± 1% (F)
Red	2	2	2	100Ω	± 2% (G)
Orange	3	3	3	1KΩ	
Yellow	4	4	4	10KΩ	
Green	5	5	5	100KΩ	± 0.5% (D)
Blue	6	6	6	1MΩ	± 0.25% (C)
Violet	7	7	7	10MΩ	± 0.10% (B)
Grey	8	8	8		± 0.05%
White	9	9	9		
Gold				0.1	± 5% (J)
Silver				0.01	± 10% (K)

• 100 Ω



• 220 Ω



• 330 Ω



• 1 K Ω



• 10 k Ω



• 100 k Ω




Dr. Ahmed EIShafee, ACU Spring 2014, Practical Applications CS II


Connecting Press

- Buttons that are used here are also called "press-buttons".
- A pull-up resistor is needed to avoid producing short circuit between Vcc, and Gnd
- There are two possible connections as shown
 - Active high
 - Active low
- The average current consumed by resistor
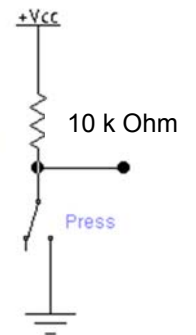
$$I_r = V_{cc} / R = 5 / (10 \cdot 1000) = 0.5 \text{ mA}$$




Active high input press

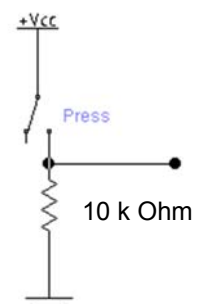

Active Low input press

Dr. Ahmed EIShafee, ACU Spring 2014, Practical Applications CS II

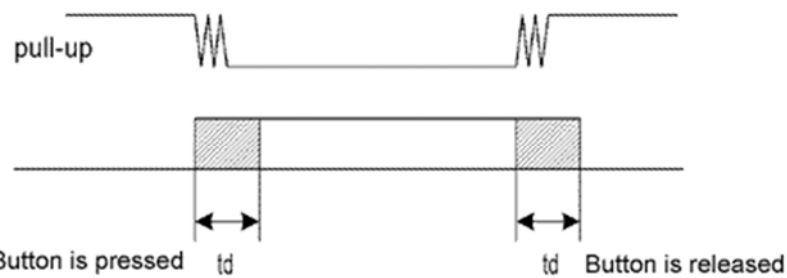
- there is a short time period when vibration (oscillation) can occur as a result of unevenness of mechanical contacts, or as a result of the different speed in pushing a button (this depends on person who pushes the button).
- this phenomena is called SWITCH (CONTACT) DEBOUNCE.



Dr. /
Spring
App


- If this is overlooked when program is written, an error can occur, or the program can produce more than one output pulse for a single button push.
- to avoid this, we can introduce a small delay when we detect the closing of a contact.
- This will ensure that the push of a button is interpreted as a single pulse.

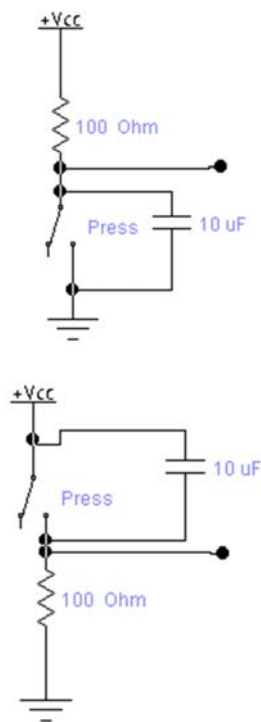- The problem can be partially solved by adding a capacitor across the button, but a well-designed program is a much-better answer.
- The program can be adjusted until false detection is completely eliminated.




Dr. Ahmed ElShafee, ACU
Spring 2014, Practical
Applications CS II

11

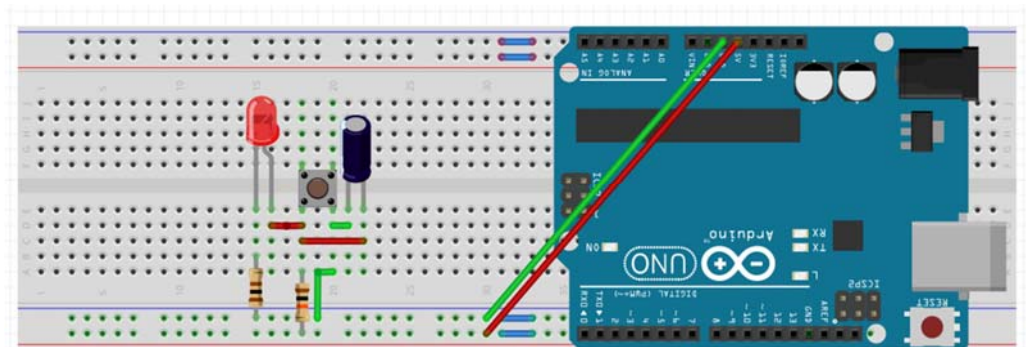

Dr. Ahmed ElShafee, ACU
Spring 2014, Practical
Applications CS II


12

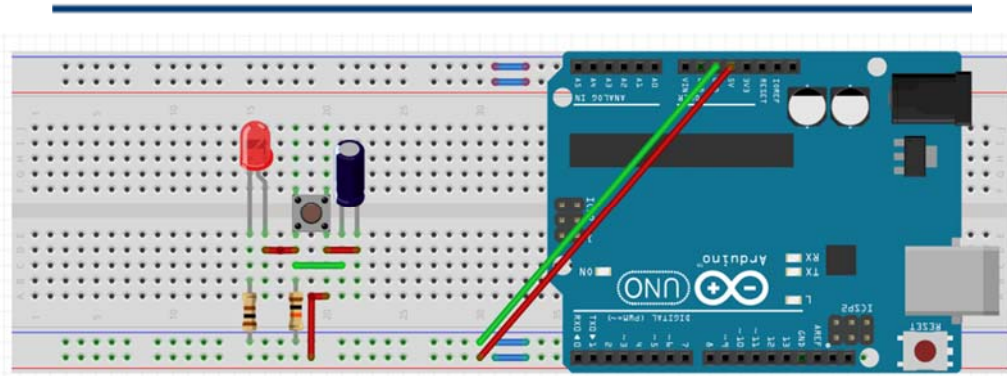

Dr. Ahmed ElShafee, ACU
Spring 2014, Practical
Applications CS II

12

Led Flasher

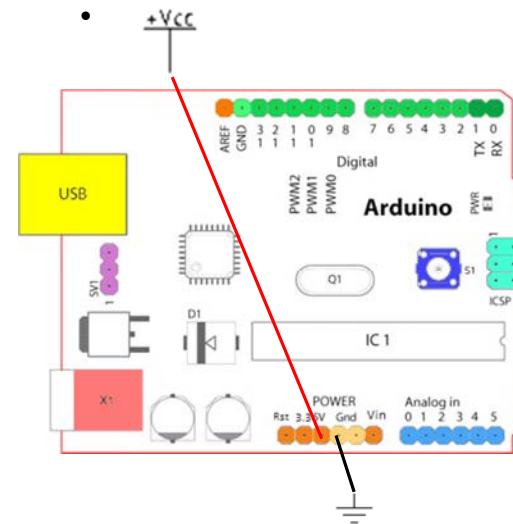

Dr. Ahmed ElShafee, ACU Summer 2016, Practical App. CS II

13

```


LedFlasher | Arduino 1.5.2
File Edit Sketch Tools Help
LedFlasher$
#define LED 13

void setup()
{
  pinMode(LED, OUTPUT);
}


void loop()
{
  digitalWrite(LED, HIGH);
  delay(100);
  digitalWrite(LED, LOW);
  delay(100);
}
  
```

Dr. Ahmed ElShafee, ACU Summer 2016, Practical App. CS II

10

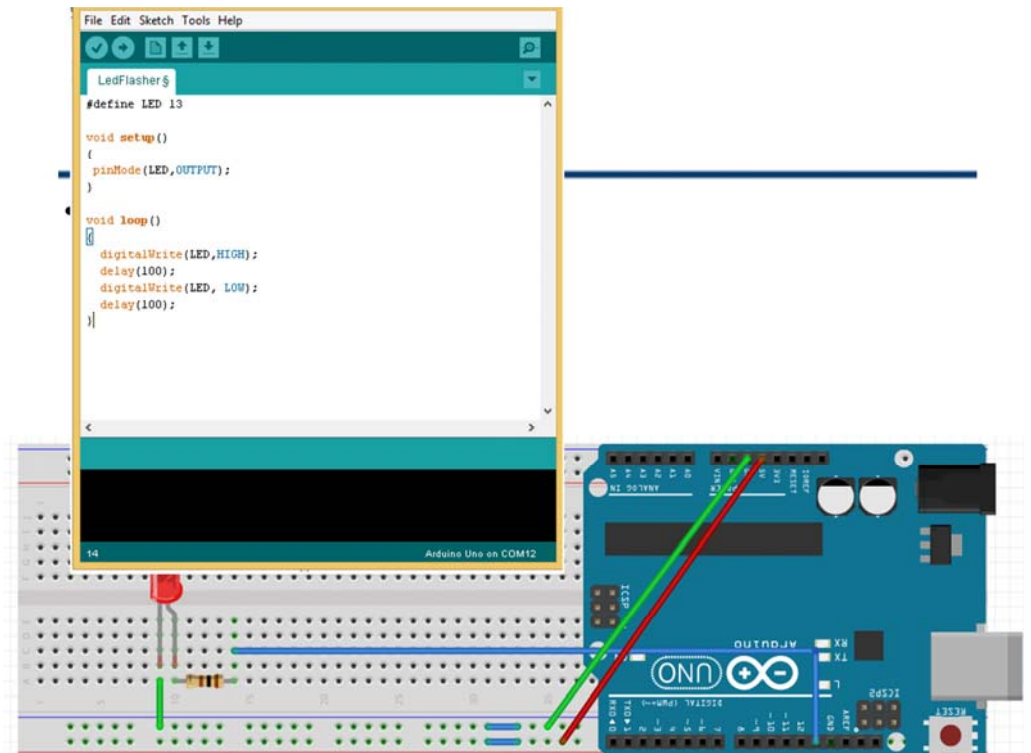

PressControlledFlasher

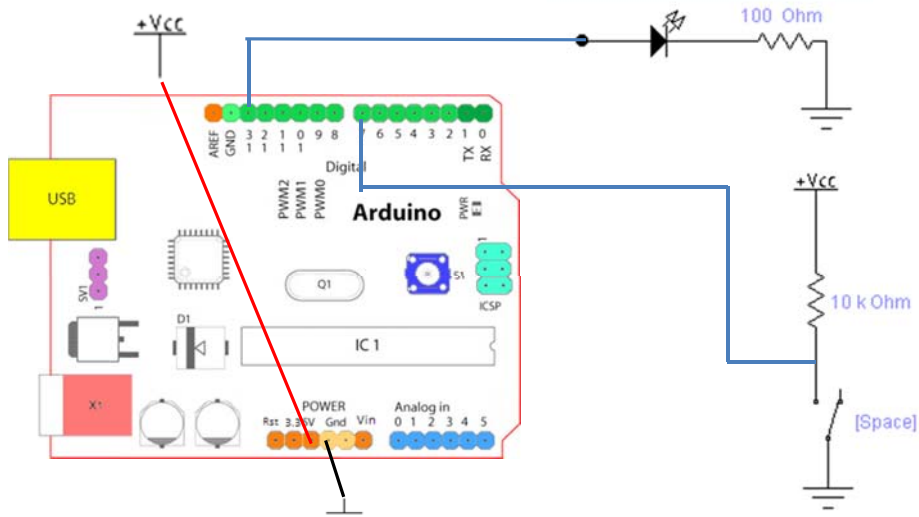

17

Dr. Ahmed ElShafee, ACU Summer 2016, Practical App. CS II

```


PressControlledFlasher | Arduino 1.5.2
File Edit Sketch Tools Help
PressControlledFlasher
#define LED 13
#define BUTTON 7
int Button_status=0;
int Led_status=0;

void setup()
{
  pinMode(LED, OUTPUT);
  pinMode(BUTTON, INPUT);
}

void loop()
{
  Button_status=digitalRead(BUTTON);
  if(Button_status==LOW)
  {
    delay(1000);
    if(Led_status==LOW)
      Led_status=HIGH;
    else
      Led_status=LOW;
  }
  else
    Led_status=LOW;
  digitalWrite(LED,Led_status);
}
Done Saving
Arduino Uno on COM12
  
```


18

4 Leds In Action 1

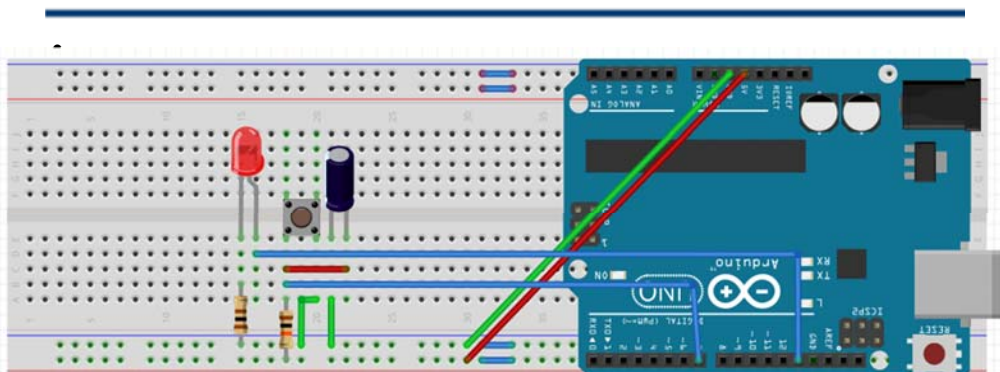

19

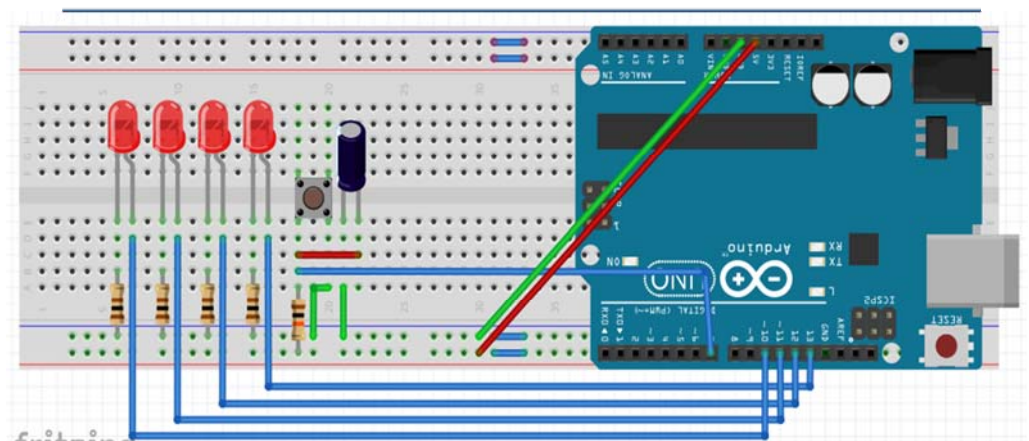Dr. Ahmed ElShafee, ACU Summer 2016, Practical App. CS II



20

Dr. Ahmed ElShafee, ACU Summer 2016, Practical App. CS II

```

#define Led4 13
#define Led3 12
#define Led2 11
#define Led1 10
#define button 7
int led4_status = 0;
int led3_status = 0;
int led2_status = 0;
int led1_status = 0;
int status = 0;
int direction = 1;
void setup()
{
  pinMode(Led1, OUTPUT);
  pinMode(Led2, OUTPUT);
  pinMode(Led3, OUTPUT);
  pinMode(Led4, OUTPUT);
  pinMode(button, INPUT);
}

void loop()
{
  if(digitalRead(button)==LOW)
  {
    if(status == 0)
    {
      led1_status = LOW;
      led2_status = LOW;
      led3_status = LOW;
      led4_status = LOW;
    }
    else if(status == 1)
    {
      led1_status = HIGH;
      led2_status = LOW;
      led3_status = LOW;
      led4_status = LOW;
    }
  }
}

```

```

else if(status == 2)
{
  led1_status = HIGH;
  led2_status = HIGH;
  led3_status = LOW;
  led4_status = LOW;
}

else if(status == 3)
{
  led1_status = HIGH;
  led2_status = HIGH;
  led3_status = HIGH;
  led4_status = LOW;
}

else if(status == 4)
{
  led1_status = HIGH;
  led2_status = HIGH;
  led3_status = HIGH;
  led4_status = HIGH;
}

digitalWrite(Led1, led1_status);
digitalWrite(Led2, led2_status);
digitalWrite(Led3, led3_status);
digitalWrite(Led4, led4_status);
delay(100);
if(status == 4)direction = -1;
if(status == 0)direction = 1;
status = (status + direction);
}
else
{
  status=0;
  direction = 1;
}
}
}

```

Thanks,
See you next Week, isA