

Electronic Circuits – Assignment

06

Special Purpose Diodes

II

#	Student ID	Student Name	Grade (10)
-			

Delivery Date	
---------------	--

١. يتم تسليم التمرين محلولا في خلال أسبوع من تاريخ التمرين، و يتم حذف درجتين من التمرين عن كل أسبوع تأخير
٢. يتم التسليم لمعيد المقرر مباشرة
٣. تتم أجابه التمرين في نفس ورق الأسئلة



كلية الهندسة

Faculty of Engineering



FACULTY OF ENGINEERING
AHRAM CANADIAN UNIVERSITY

T & F



جامعة الأهرام الكندية
AHRAM CANADIAN UNIVERSITY

#	Question	
1	The LED is based on the process of electroluminescence.	
2	OLED stands for operational light-emitting diode.	
3	The reverse current of a photodiode increases as the incident light increases.	

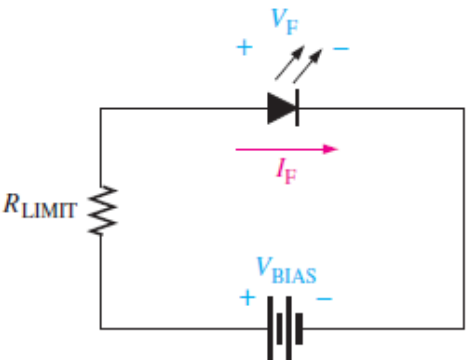
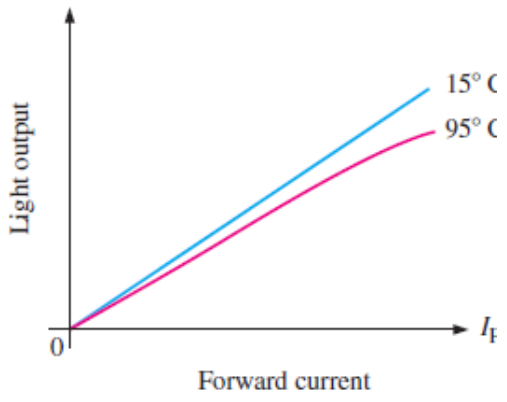
#	Question
1	<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;">  <p>(a) Forward-biased operation</p> </div> <div style="text-align: center;">  <p>(b) General light output versus forward current for two temperatures</p> </div> </div> <p>If the bias voltage in Figure 3–30 is reversed, the light output of the LED will</p> <p>(a) increase (b) decrease (c) not change</p> <p>(b)</p>
2	<p>A varactor diode exhibits</p> <p>(a) a variable capacitance that depends on reverse voltage</p> <p>(b) a variable resistance that depends on reverse voltage</p> <p>(c) a variable capacitance that depends on forward current</p> <p>(d) a constant capacitance over a range of reverse voltages</p>
3	<p>Compared to a visible red LED, an infrared LED</p> <p>(a) produces light with shorter wavelengths (b) produces light of all wavelengths</p> <p>(c) produces only one color of light (d) produces light with longer wavelengths</p>
4	<p>An OLED differs from a conventional LED in that it</p> <p>(a) requires no bias voltage</p> <p>(b) has layers of organic material in the place of a <i>pn</i> junction</p> <p>(c) can be implemented using an inkjet printing process</p> <p>(d) both (b) and (c)</p>



5	The internal resistance of a photodiode (a) increases with light intensity when reverse-biased (b) decreases with light intensity when reverse-biased (c) increases with light intensity when forward-biased (d) decreases with light intensity when forward-biased	
	A diode that has a negative resistance characteristic is the (a) Schottky diode (b) tunnel diode (c) laser diode (d) hot-carrier diode	



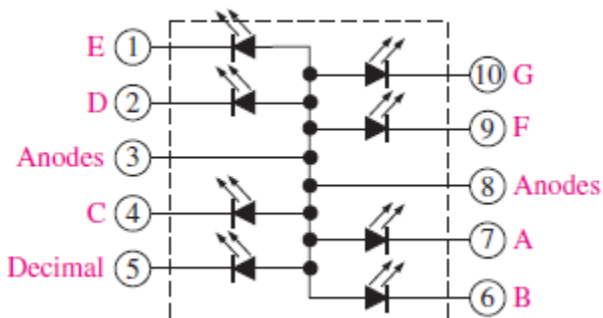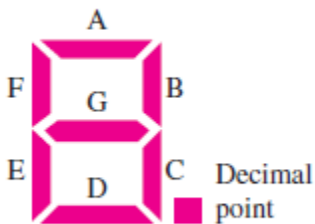Determine how to connect the seven-segment display in Figure 3-74 to display “5.” The maximum continuous forward current for each LED is 30 mA and a +5 V dc source is to be used.



.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

